

रोल नं./Roll No.

पाठ्यक्रम नाम/Course Name

शाखा/प्रभाग/Branch/Div.

शिक्षण बैच/Tutorial Batch

अनुभाग/Section

पाठ्यक्रम सं./Course No.

तिथि/Date




EE618 [ZELE]

2018 - 2019


MIDSEM
SOLUTIONS

Q.1.

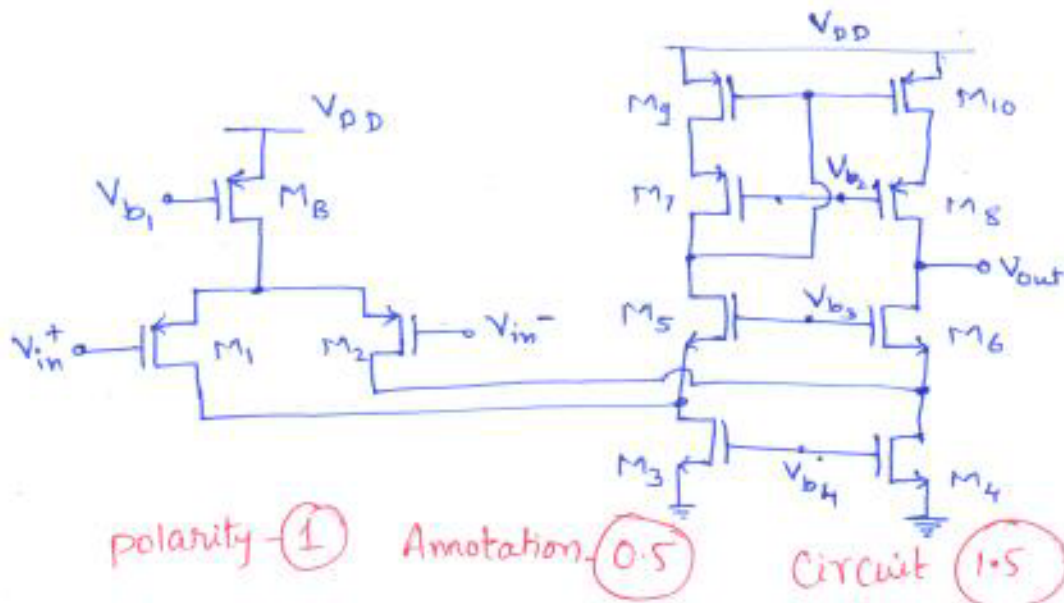

No credits if Schematic is wrong.

Biassing circuit \therefore

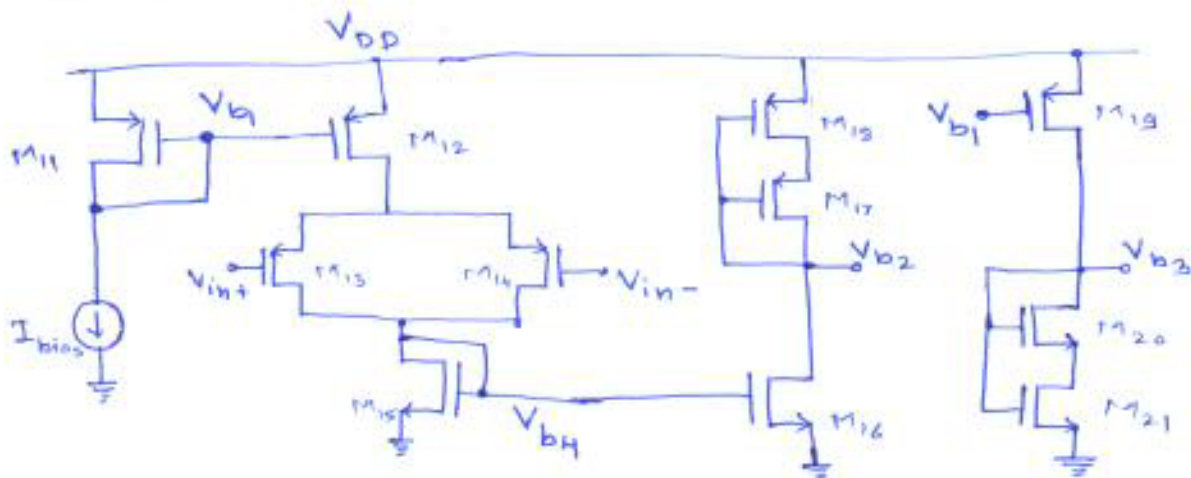


Here, M_{18} and M_{21} sizes are decided to provide a voltage drop of $\approx V_{dsat}$.

$V_{b1}, V_{b2}, V_{b3}, V_{b4} - 4 \times (0.5)$

QUESTION 2

At Node A

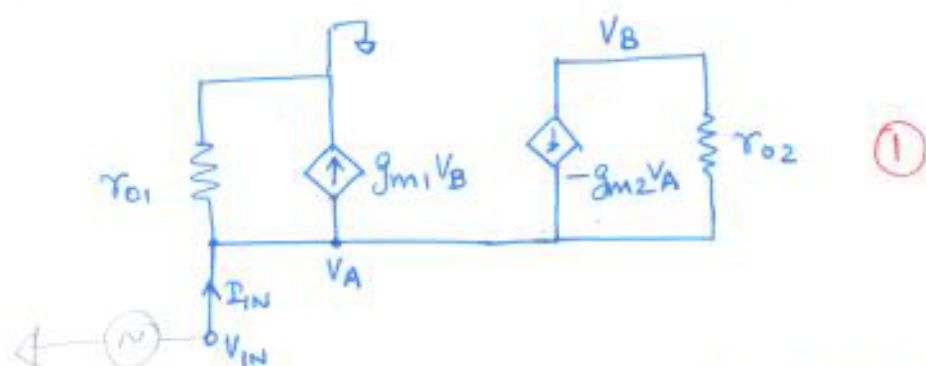


$$V_A = V_{IN}$$

(1/2) KCL at Node B $\Rightarrow (V_B - V_{IN}) = g_{m2} V_A r_{O2}$
 $\Rightarrow \boxed{V_B = (1 + g_{m2} r_{O2}) V_{IN}} \quad \text{--- (1)}$

(1/2) KCL at Node A $\Rightarrow I_{IN} = g_{m1} V_B + \frac{V_{IN}}{r_{O1}}$
 $= g_{m1} (1 + g_{m2} r_{O2}) V_{IN} + \frac{V_{IN}}{r_{O1}}$

(1) $\Rightarrow \underline{\underline{Z_{IN,A} = \frac{r_{O1}}{1 + g_{m1} r_{O1} (1 + g_{m2} r_{O2})}}} \approx \frac{1}{g_{m1} (g_{m2} r_{O2})} \quad (\text{Approximated } g_m r_O \gg 1)$

At Node B

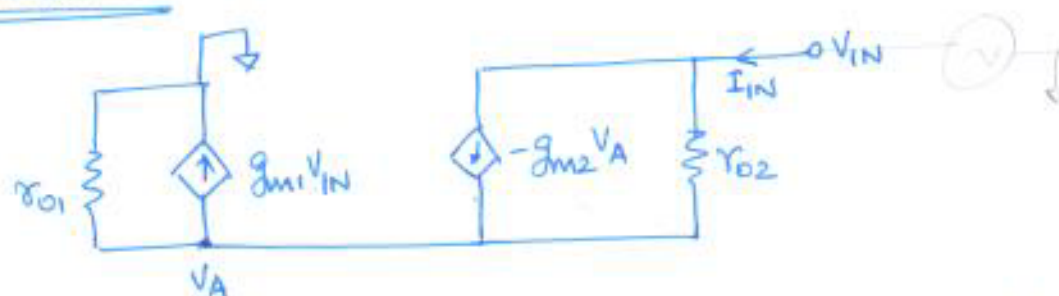

KCL at Input Node: $I_{IN} = -g_{m2} V_A + \frac{V_{IN} - V_A}{r_{O2}} \quad \text{--- (2)}$

KCL at Node A: $I_{IN} = g_{m1} V_{IN} + \frac{V_A}{r_{O1}} \quad \text{--- (3)}$

PROCEDURE/REASONING

(0.5)

Using ② and ③ to eliminate V_A ,

$$\frac{V_A}{r_{o1}} + \frac{V_A}{r_{o2}} + g_{m2} V_A = \frac{V_{IN}}{r_{o2}} - g_{m1} V_{IN}$$

$$\Rightarrow \frac{V_A}{r_{o1}} [r_{o2} + r_{o1} + g_{m2} r_{o1} r_{o2}] = V_{IN} [1 - g_{m1} r_{o2}]$$

$$\Rightarrow \frac{V_A}{r_{o1}} = V_{IN} \left[\frac{1 - g_{m1} r_{o2}}{r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}} \right]$$

Substituting in ③

$$I_{IN} = g_{m1} V_{IN} + V_{IN} \left[\frac{1 - g_{m1} r_{o2}}{r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}} \right]$$

⑤.5 $\Rightarrow \frac{V_{IN}}{I_{IN}} = Z_{IN,B} = \frac{r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}}{1 + g_{m1} r_{o1} + g_{m1} g_{m2} r_{o1} r_{o2}} \approx \frac{1}{g_{m1}}$
(Assuming $g_m r_o \gg 1$)

Rewriting $Z_{IN,B} = \frac{r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}}{1 + g_{m1} r_{o1} (g_{m2} r_{o2} + 1)}$

COROLLARY:

Approximately, I_{IN} from mode B will flow through M2 and M1.

* V_A changes to allow I_{IN} through M2


* Hence I_{IN} is directly controlled by M1 — g_{m1}

$\Rightarrow Z_{IN} = 1/g_{m1}$ ⑤.5

Q. 3.

a) OPAMP polarity:


①

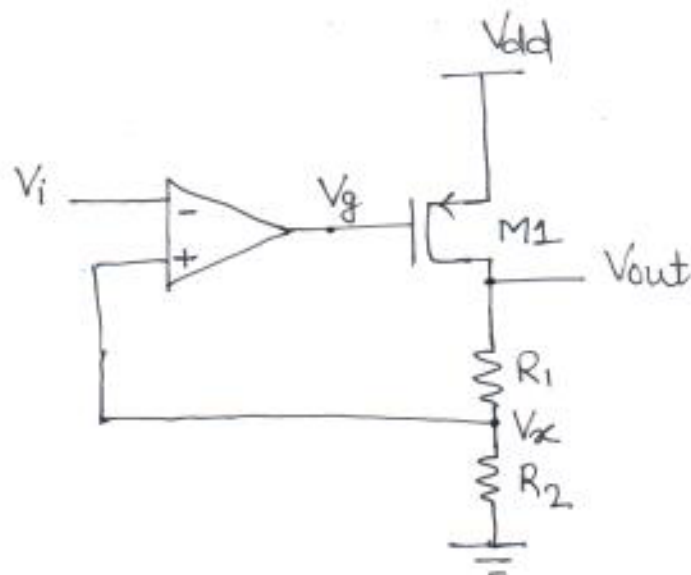

As V_i increases, V_g decreases and hence V_{out} and V_x increases (Due to the gate to drain inversion of M_1). Hence negative feedback is established.

b) Transfer function:

Small signal model:

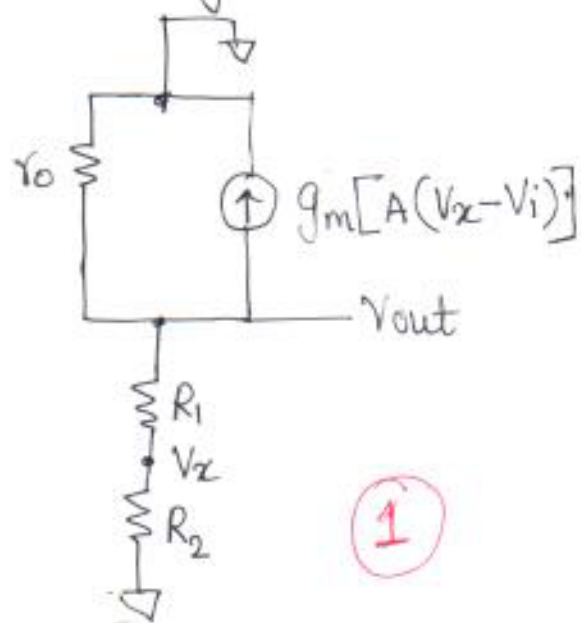

$$V_x = V_{out} \left(\frac{R_2}{R_1 + R_2} \right) \quad \text{--- ①}$$

Applying KCL at V_{out} node,

$$\frac{V_{out}}{r_o} + g_m A (V_x - V_i) + \frac{V_{out}}{R_1 + R_2} = 0 \quad \text{--- ②}$$


0.25

from ① & ②, we get,

$$V_{out} \left[\frac{1}{r_o} + \frac{g_m A R_2}{R_1 + R_2} + \frac{1}{R_1 + R_2} \right] = g_m A V_i$$

$$\Rightarrow \frac{V_{out}}{V_i} = \frac{A \cdot (g_m r_o) (R_1 + R_2)}{R_1 + R_2 + A (g_m r_o) R_2 + r_o} \quad (0.5)$$

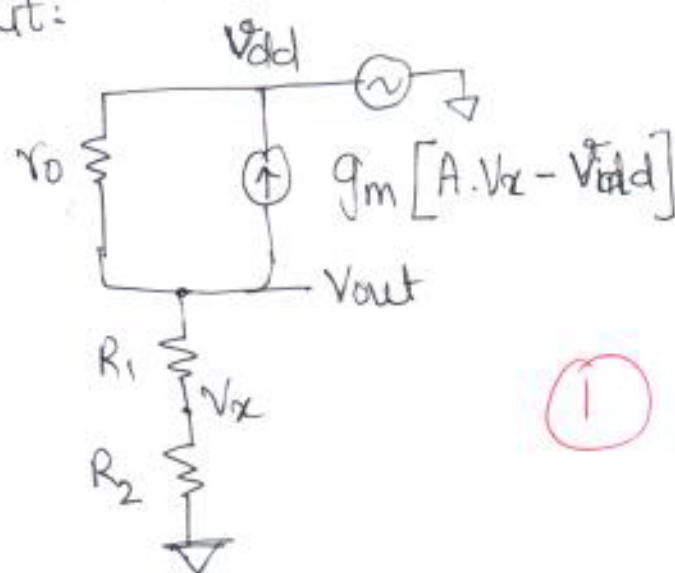c) V_{dd} to V_{out} transfer function:
small signal circuit:



$$V_x = V_{out} \cdot \frac{R_2}{R_1 + R_2} \quad \text{--- ①} \quad (0.25)$$

by KCL @ V_{out} node gives,

$$\frac{V_{out} - V_{dd}}{r_o} + g_m [A V_x - V_{dd}] + \frac{V_{out}}{R_1 + R_2} = 0 \quad \text{--- ②} \quad (0.25)$$

from ① & ②, we get

$$\frac{V_{out}}{V_{dd}} = \frac{(1 + g_m r_o) (R_1 + R_2)}{A (g_m r_o) R_2 + R_1 + R_2 + r_o} \quad (0.5)$$

d) $A \rightarrow \infty$ & $g_m r_o \rightarrow \infty$

for part b)

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{\frac{R_1 + R_2}{A g_m r_o} + R_2 + \frac{r_o}{A g_m r_o}} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_2} \text{ as } A g_m r_o \rightarrow \infty$$

①

for part c)

$$\frac{V_{out}}{V_{dd}} \approx \frac{(g_m r_o)(R_1 + R_2)}{A(g_m r_o)R_2 + R_1 + R_2 + r_o} = \frac{R_1 + R_2}{A R_2 + \frac{R_1 + R_2}{g_m r_o} + \frac{1}{g_m}}$$

$= 0$ as A & $r_o \rightarrow \infty$.

①

Q.4

$$a) I_5 = 10 \times I_B = 100 \mu A$$

①

$$b) I_7 = 50 \times I_B = 500 \mu A$$

①

$$c) \text{ power dissipation} = (I_B + I_5 + I_7) V_{DD}$$

$$= 610 \mu A \times 1.8 V$$

①

$$P_{\text{diss}} = 1.098 \text{ mW}$$

$$d) \underline{V_B}$$

$$V_B = V_{DD} - V_{SG3}; \quad V_{SG3} = |V_{TH3}| + \sqrt{\frac{2I_{D3}}{\mu_p C_{ox} (W/L)_3}}$$

0.5

$$V_{SG3} = 0.4 + \sqrt{\frac{2 \times 50 \times 10^{-6}}{62 \times 10^{-6} \times 32}}$$

$$V_B = 1.8 V - 0.6245 V$$

$$V_B = 1.17549 V$$

0.5

$$e) \underline{(W/L)_6} \Rightarrow \text{for no systematic offset, } V_{dsat3} = V_{dsat4} = V_{dsat6}$$

$$\Rightarrow V_{dsat3} = V_{dsat6}$$

①

$$\sqrt{\frac{2I_{D3}}{\mu_p C_{ox} (W/L)_3}} = \sqrt{\frac{2I_{D6}}{\mu_p C_{ox} (W/L)_6}} \quad \frac{1}{4} \quad I_{D3} = \frac{I_5}{2}$$

$$I_{D6} = I_7$$

$$(W/L)_3 = \frac{I_5}{2 \cdot I_7} (W/L)_6 \Rightarrow \left(\frac{W}{L}\right)_6 = \frac{32 \times 500}{50}$$

$$(W/L)_6 = 320 \Rightarrow \boxed{W_6 = 320 \mu m}$$

4(2)

1

f.)

DC Gain:

$$A_{V_{tot}} = A_{V_1} \cdot A_{V_2} = \frac{g_{m1}}{(g_{ds2} + g_{ds4})} \cdot \frac{g_{m6}}{(g_{ds6} + g_{ds7})}$$

1

$\therefore g_{ds} = \lambda \cdot I_D \quad \& \quad \lambda_1 L_1 = \lambda_2 L_2$ for any two different lengths,

$$\lambda_n = 0.48 V^{-1} \quad \lambda_p = 0.328 V^{-1} \quad \text{for } L = 0.18 \mu m$$

$$\Rightarrow (0.48)(0.18) = \lambda_n \text{ for } L = 1 \mu m \Rightarrow \boxed{\lambda_n = 0.0864 V^{-1}}$$

1

$$\lambda_p = (0.18)(0.328) V^{-1} \text{ for } L = 1 \mu m \Rightarrow \boxed{\lambda_p = 0.05904 V^{-1}}$$

$$A_{V_1} = \frac{g_{m1}}{g_{ds4} + g_{ds2}} = \frac{\sqrt{2 \cdot (I_5/2) \cdot K_n \cdot (W/L)_1}}{\left(\frac{I_5}{2}\right) (\lambda_n + \lambda_p)} = \sqrt{\frac{2 \mu_n C_{ox} (W/L)_1}{(I_5/2) (\lambda_n + \lambda_p)^2}}$$

$$= \sqrt{\frac{2 \times 263 \times 16}{50} \cdot \frac{1}{(0.0864 + 0.05904)}}$$

0.5

$$\boxed{A_{V_1} = 89.2039}$$

$$A_{V_2} = \frac{g_{m6}}{g_{ds6} + g_{ds7}} = \sqrt{\frac{2 \mu_p C_{ox} (W/L)_6}{I_6 (\lambda_n + \lambda_p)^2}}$$

$$= \sqrt{\frac{2 \times 62 \times 320}{500} \cdot \frac{1}{(0.0864 + 0.05904)}} = 61.25$$

$$\boxed{A_{V_2} = 61.25}$$

0.5

$$\text{DC Gain} = A_{v1} \cdot A_{v2} = 89.2039 \times 61.25$$

$$\boxed{\text{DC Gain} = 5463.877 = 74.75 \text{ dB}}$$

①

g.)

V_{ICMR}(max)

$$= V_{B1} + V_{thn1}$$

$$V_{ICMR}(\text{max}) = V_{DD} - |V_{SAs}| + V_{thn1}$$

$$= V_{DD} - |V_{thp}| - V_{dsat3} + V_{thn}$$

$$= V_{DD} - |V_{thp}| + V_{thn} - \sqrt{\frac{2(I_{S/2})}{\mu_n C_{ox} (W/L)_3}}$$

$$= 1.8 - 0.4 + 0.48 - \sqrt{\frac{2 \times 50}{62 \times 32}}$$

$$\boxed{V_{ICMR}(\text{max}) = 1.6555 \text{ V}}$$

①

h.)

V_{ICMR}(min)

$$V_{ICMR}(\text{min}) = V_{GS1} + V_{dsat5}$$

$$= V_{thn} + V_{dsat1} + V_{dsat5}$$

$$= V_{thn} + \sqrt{\frac{2(I_{S/2})}{\mu_n C_{ox} (W/L)_1}} + \sqrt{\frac{2 \cdot I_5}{\mu_n C_{ox} (W/L)_5}}$$

$$= 0.48 + \sqrt{\frac{2 \times 50}{263 \times 16}} + \sqrt{\frac{2 \times 100}{263 \times 15}}$$

$$= 0.159$$

$$= 0.225$$

$$\boxed{V_{ICMR}(\text{min}) = 0.8593 \text{ V}}$$

①

2) Location of 'zero'

H (4)

Due to the feedforward path through R_z and C_c between first and second stages, the OTA transfer function consists a zero

at f_z (Zero-frequency) $V_{out} = 0$

$$-g_{m6} V_A + \frac{V_A s C_c}{1 + s R_z C_c} = 0 \quad \text{--- (1)}$$

$$g_{m6} = \frac{s C_c}{1 + s R_z C_c}$$


$$s C_c (1 - g_{m6} R_z) = g_{m6}$$

$$s_z = \frac{g_{m6}}{(1 - g_{m6} R_z) C_c}$$

$$s_z = \frac{1}{\left(\frac{1}{g_{m6}} - R_z\right) C_c}$$

$$f_{zero} = \frac{1}{2\pi C_c \left(\frac{1}{g_{m6}} - R_z\right)} \text{ Hz}$$

(1)

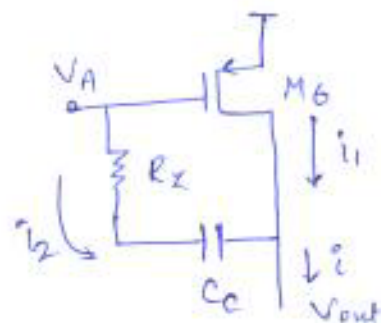

j) R_z value to achieve the best Phase margin.

to achieve the best phase margin the zero has to be placed at the non-dominant pole location.

$$\Rightarrow P_2 = -\frac{g_{m6}}{C_L}$$

$$\Rightarrow R_z = \frac{1}{g_{m6}} \left(1 + \frac{C_L}{C_c} \right) \quad (1)$$

$$g_{m6} = \sqrt{2 K_p \cdot (W/L)_6 \cdot I_7} \quad K_p = \mu_p C_{ox}$$

$$= \sqrt{2 \times 62 \times 500 \times 320 \text{ nS}}$$

$$g_{m6} = 4.4542 \text{ mS}$$

$$R_z = \frac{1}{4.4542 \times 10^{-3}} \left(1 + \frac{4 \text{ pF}}{1 \text{ pF}} \right)$$

$$\boxed{R_z = 1.122536 \text{ k}\Omega} \quad (1)$$

k) Unity gain frequency:

$$f_{UGF} = \frac{g_{m1}}{2\pi C_c} \quad (1)$$

$$g_{m1} = \sqrt{2 \cdot \mu_n C_{ox} \cdot (W/L)_1 \cdot \frac{I_{SS}}{2}} = 0.648 \text{ mS}$$

$$= \frac{648.69 \times 10^{-6}}{2\pi \times 1 \times 10^{-12}} = \boxed{103.24 \text{ MHz}} \quad (1)$$

4.6

l) Slewrate (limited by input differential pair)

$$\frac{dV_{out}}{dt} = \frac{I_{SS}}{C_c} = \frac{100 \mu A}{1 pF} = 100 V/\mu s$$

m) Input referred noise

$$\overline{V_{mes}^2} = 2 \left[\overline{V_{n1}^2} + \overline{V_{n2}^2} \left(\frac{g_{m3}}{g_{m1}} \right)^2 \right]$$

$$= 2 \left[4KT \frac{1}{g_{m1}} + 4KT \frac{1}{g_{m3}} \left(\frac{g_{m3}}{g_{m1}} \right)^2 \right]; \gamma = 2/3$$

Noise of the second stage can be neglected due to high gain

$$= \frac{16KT}{3} \cdot \frac{1}{g_{m1}} \left[1 + \frac{g_{m3}}{g_{m1}} \right]$$

$k = 1.38 \times 10^{-23} \text{ J/K}$
 $T = 300^\circ K$

$$g_{m1} = 648.69 \mu S$$

$$g_{m3} = \sqrt{2(\mu_p C_{ox}) \left(\frac{W}{L} \right)_3 \cdot \frac{1.5}{2}}$$

$$g_{m3} = \sqrt{62 \times 100 \times 32} = 445.42 \mu S$$

$$\overline{V_{n,in}^2} = \frac{16 \times 1.38 \times 10^{-23} \times 300}{3 \times 0.6487 \times 10^{-3}} \left[1 + \frac{445.42}{648.69} \right]$$

$$\overline{V_{n,in}^2} = 5.74088 \times 10^{-17} \text{ V}^2/\text{Hz}$$

$$\overline{V_{n,in}^2} = 57.408 \left(\frac{1 \text{ V}}{\sqrt{\text{Hz}}} \right)^2$$

$$\overline{V_{n,in}} = 7.57 \text{ mV}/\sqrt{\text{Hz}}$$