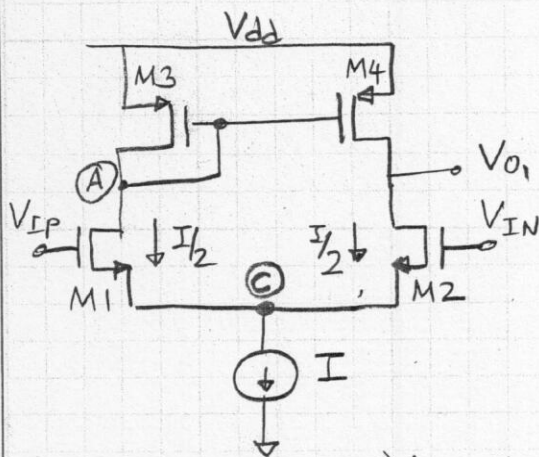


OTA Topologies

(— Allistot)

Single Stage OTA

Common-mode

$$V_{IP} = V_{IN} = V_{CM} \left(\frac{V_{DD}}{2} \right)$$


ASSUME

Feedback sets $V_{SD3} = V_{SD4}$

$$V_{SD3} = V_{SD4} = |V_{TP}| + \sqrt{\frac{2(I/2)}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p}}$$

$$V_{O1} = V_{DD} - |V_{TP}| - |V_{DSATp}|$$

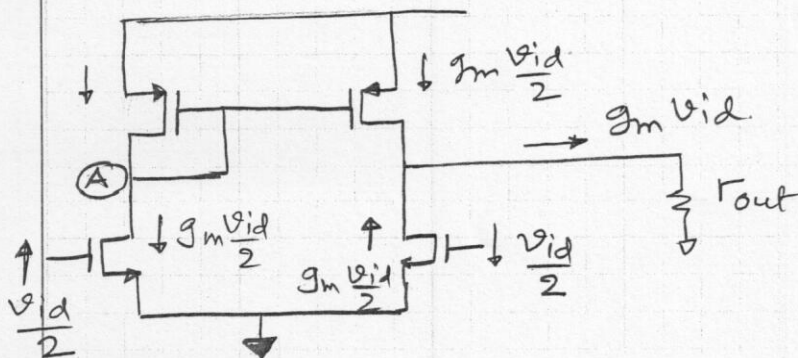Ac analysis - Node C - virtual ground node for differential signal.



Small signal o/p resistance
 $= \frac{1}{(g_{ds2} + g_{ds4})}$


$$V_{O1} = \frac{g_m v_{id}}{g_{ds2} + g_{ds4}}$$

$$A_v = \frac{g_m}{g_{ds2} + g_{ds4}} \quad \frac{25-100}{}$$

$$g_{outA} = g_{m3} + g_{ds3} + g_{ds1} \approx g_{m3} \text{ - low imp. wide Bandwidth node -}$$

Limited gain (one stage only)
 D2SE included.

Two Stage OTA

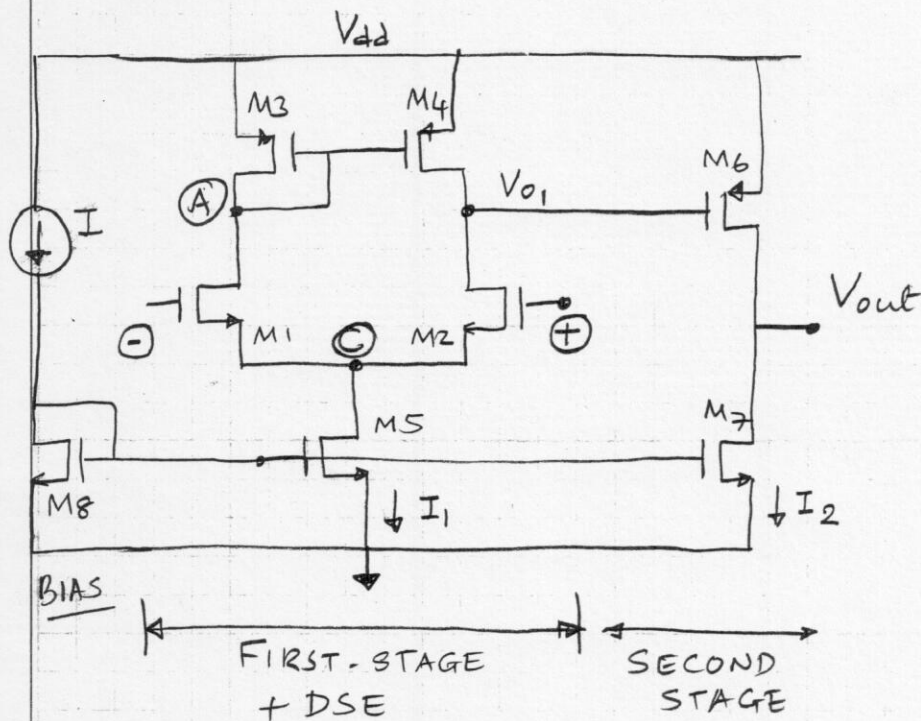

BIASING — To avoid systematic offsets

$$(DC) \quad V_A = V_{O1} \quad \left\{ \begin{array}{l} \text{Else} \\ V_{OS} = \frac{V_{O1} - V_A}{A} \leftarrow \text{FIRST STAGE GAIN} \end{array} \right.$$

$$V_A = V_{dd} - V_{SG3} = V_{O1} = V_{dd} - V_{SG6}$$

$$V_{SG3} = V_{SG6} \Rightarrow \text{Same } V_{dsat}$$

$$|V_{T3}| + \sqrt{\frac{2(I_1/2)}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} = |V_{T6}| + \sqrt{\frac{2(I_2)}{\mu_p C_{ox} \left(\frac{W}{L}\right)_6}}$$

Assuming $V_{T3} = V_{T6}$ (process matching)

$$\left(\frac{W}{L}\right)_6 = 2 \left(\frac{I_2}{I_1}\right) \cdot \left(\frac{W}{L}\right)_3$$

Good design practice

also use unit cell
design — keep W same

M3, M4, M6 — same L

M1, M2 same W & L.

M8, M5, M7 — same L.

$$V_{o1} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} v_{i2} \quad \& \quad V_{out} = \frac{g_{m6}}{g_{ds6} + g_{ds7}} V_{o1}$$

$$\text{Total gain} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} \cdot \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$

Each high impedance node
contributes a low freq pole
in frequency response

Each pole $\rightarrow 90^\circ$ phase shift

Two poles $\rightarrow 180^\circ$ phase shift \rightarrow the feedback

— Limit Two gain stages, for stability.

— Need for frequency compensation

Motivation to Study Feedback & Stability

\rightarrow Then comeback & figure out
frequency compensation of opamps.

Feedback & Stability

1927, Harold Black (Bell labs) - -ve feedback.

Advantages


1. Gain desensitization
2. Terminal Impedance Modification

| | |
|-----------|-------------|
| Shunt FB | ↓ impedance |
| Series FB | ↑ impedance |
3. Bandwidth Modification. (increase in BW)
4. Nonlinearity reduction.

Disadvantages

1. Gain Reduction
2. Potential Instability.

Negative feedback example

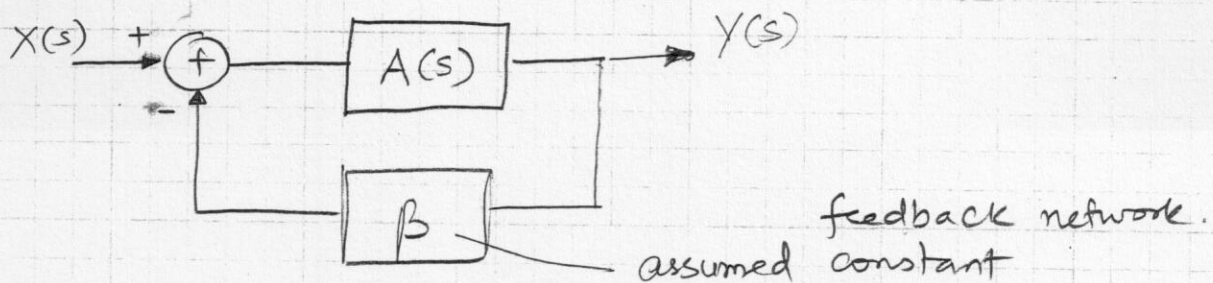

$$\frac{Y(s)}{X(s)} = \frac{A(s)}{1 + \beta A(s)}$$

Closed loop gain.

$$T = \text{loop gain} = \beta A(s).$$

Closed loop gain goes to ∞

When $\beta A(s) = -1$


$$|\beta A(s)| = 1$$

$$\angle \beta A(s) = -180^\circ$$

Barkhausen's criteria for

oscillation.

Consider Two-pole frequency response.

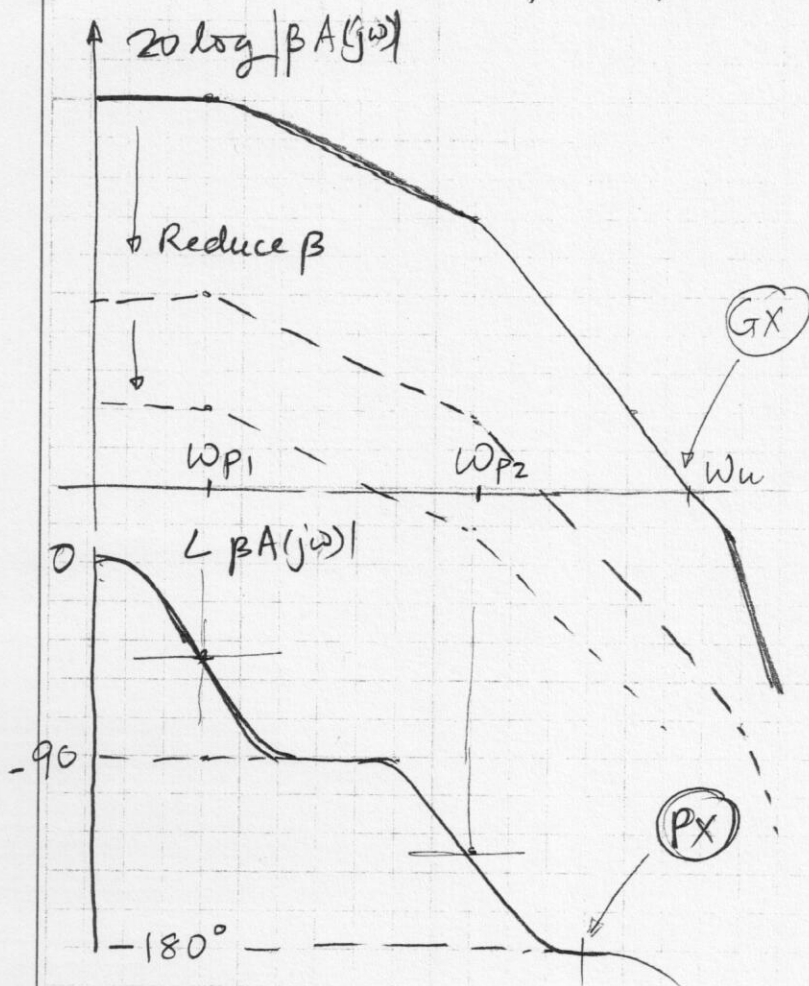

Gain Crossover freq. ω_u

- Loop gain unity


Phase Crossover freq. ω_u

- Loop phase shift 180°

For stability

ω_u must occur before ω_u

Measure of Stability

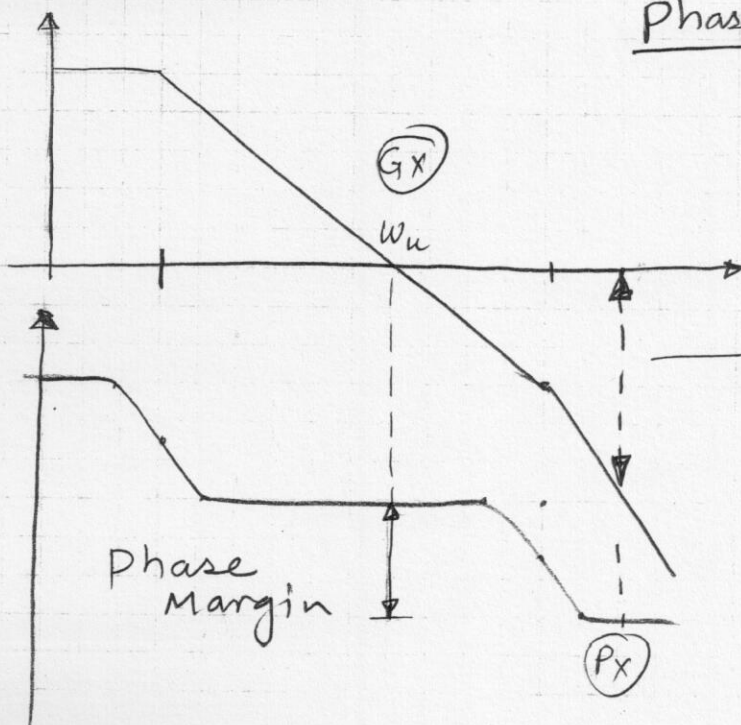

Phase Margin PM

$$= 180^\circ - \angle T(\omega_u)$$

$$= 60^\circ \text{ (max. flat gain)}$$

$$= 70^\circ \text{ (fast settling)}$$


Gain Margin GM

$$GM = -20 \log |T(\omega_{-180})|$$


$$= 12 \text{ dB (typ.)}$$

Pole location of closed Loop System

$$\frac{Y(s)}{X(s)}$$



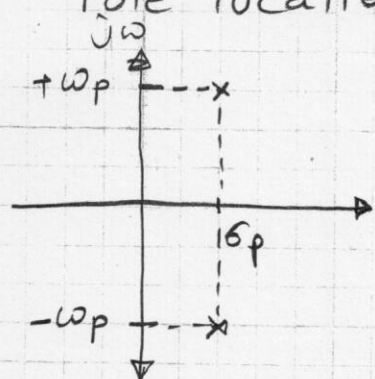


Freq domain

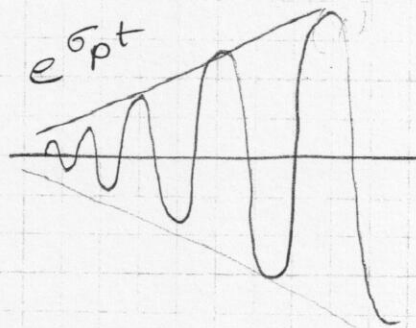


Time domain

Not
T(s)
Loop Gain

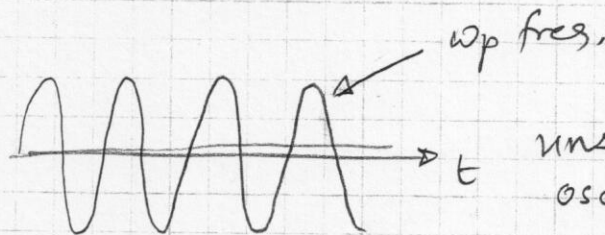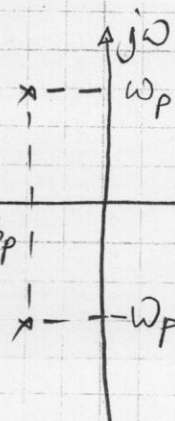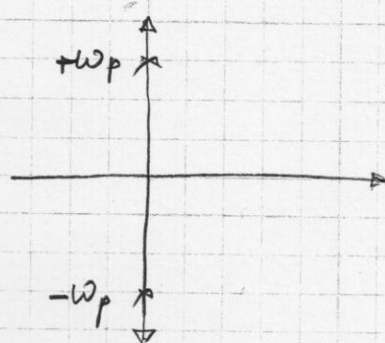

unstable
oscillating

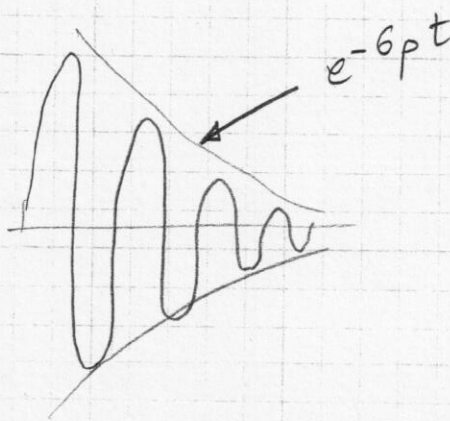

(stable)

Example One pole amplifier

$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)}$$

β constant


$$\text{Loop Gain } T(s) = \frac{\beta A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)}$$

Closed loop gain

$$\frac{Y(s)}{X(s)} = \frac{\frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)}}{1 + \frac{A_0 \beta}{\left(1 + \frac{s}{\omega_{p1}}\right)}} = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}} + A_0 \beta\right)}$$

$$\frac{Y(s)}{X(s)} = \frac{A_0 / (1 + A_0 \beta)}{1 + \frac{s}{\omega_{p1} (1 + A_0 \beta)}}$$

← used for Root locus.

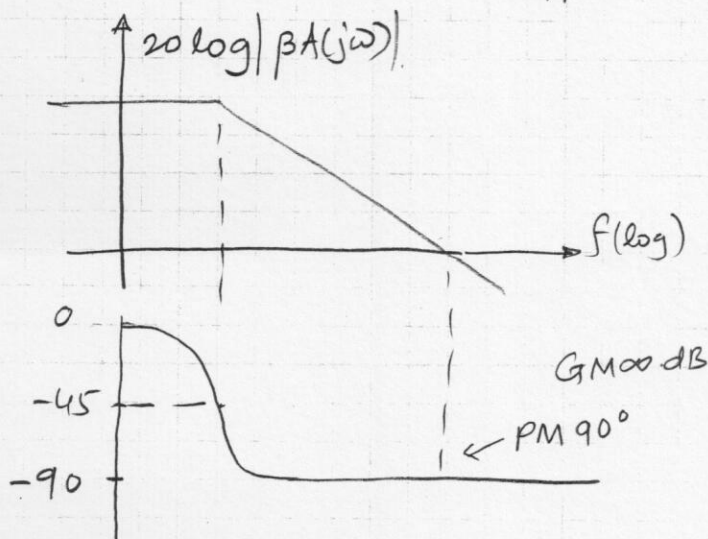

Unconditionally Stable

