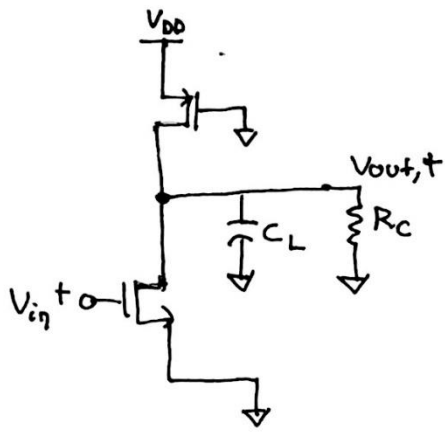



Q-1 Hand Calculations

- Node V_{sc} will be ac ground due to differential operation.
- Drain node of M_7 will also be at ac-ground.

1) Half Circuit:




SMALL SIGNAL CKT

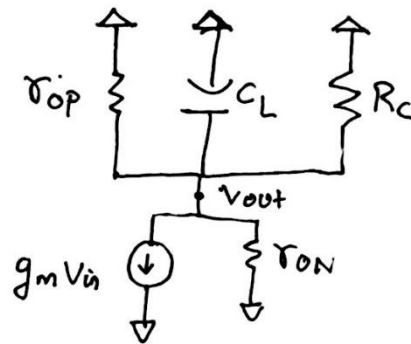

$$2) \text{ Gain} = g_{m_n} \cdot [r_{ON} \parallel r_{OP} \parallel R_C]$$

$$3) \text{ Bandwidth} \equiv \frac{g_{out}}{C_L} = \frac{1/r_{ON} \parallel r_{OP} \parallel R_C}{2\pi \cdot C_L}$$

4)

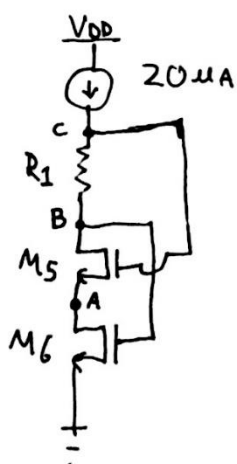i) Taking $V_{dsat, M6} = 200 \text{ mV}$ ii) Taking $V_{dsat, M5} = 150 \text{ mV}$

(Since $V_{dsat, M5} = V_{dsat, M3}$, lower $V_{dsat, M5}$ will result in higher value of g_{m3}).

iii) Now

$$V_C = V_A + V_{TN} + V_{dsat, M5}$$

$$V_B = V_{TN} + V_{dsat, M6}$$

Since $R_1 = \frac{V_C - V_B}{20 \mu A}$, value of R_1 depends on V_A .

For M_6 to remain in saturation, $V_A > V_{dsat, M6}$

Taking $V_A = 0.45 \text{ V}$

iii) iv) Name $R = 0.4V / 20\mu A = \underline{20k\Omega}$

v) Name using the equation: $\left(\frac{W}{L}\right) = \frac{I_D}{V_{sat}^2} \cdot \frac{2}{k_n}$

$W_5 = 1.2\mu m$; $W_6 = 1.9\mu m$

Since finger width = $0.5\mu m \Rightarrow W_5$ is taken $1\mu m$
 W_6 is taken $2\mu m$

vi) Since $\frac{I_{d,M7}}{I_{d,M6}} = \frac{W_{M7}}{W_{M6}}$, W_{M7} will decide tail current.

Since Bandwidth $\propto I_{M7}$, we use B/W expression to find W_{M7} .

$$B/W = \frac{1}{(r_{on} || r_{op} || R_c) \cdot C_L \cdot 2\pi} \approx \frac{1}{(r_{on} || r_{op}) \cdot C_L \cdot 2\pi} > 40MHz.$$

[We can ignore $R_c = 500k\Omega$ as $r_{on} \& r_{op} \ll R_c$ (500k Ω) typically]

$$\Rightarrow \frac{I_{d,M7}}{2} \cdot \frac{(1_n + 1_p)}{2\pi \cdot C_L} > 40 \times 10^6$$

$\Rightarrow I_{d,M7} > 420\mu A \Rightarrow$ Taking $I_{d,M7} = 400\mu A$

[Power Dissipation $\approx (0.4) \times 1.8mW = 0.7mW < 1.2mW$]

$$\therefore \frac{W_7}{W_6} = \frac{400\mu A}{20\mu A} = \underline{20} \Rightarrow \underline{W_7 = 40\mu m}$$

5) Replacing the values in gain expression:

$$\text{Gain} \approx g_{m3} \cdot [r_{op} || r_{on}] = \frac{2 \cdot (I_7) / V_{sat7}}{I}$$

$$= \frac{2 \times I_{d3} / V_{sat3}}{I_{d3} [1_n + 1_p]} = \frac{2}{(0.15V) [0.36V^{-1}]} = 37$$

$= 31dB$ $>$ (20dB specification)

The only specification to be satisfied are $V_{out, DC}$ voltage should lie b/w 0.9 - 1.1V &

V_{out} Voltage Headroom $> 0.4V$

→ $V_{out, headroom}$ is the max. output swing possible while keeping all transistors in sat.

$$\begin{aligned} \Rightarrow V_{out, headroom} &= V_{out, max} - V_{out, min} > 0.4V \\ &= (V_{DD} - V_{dsat,1}) - (V_{dsat,3} + V_{source, M3}) \\ &= 1.8 - V_{dsat,1} - (0.45 + 0.15) = 1.2 - V_{dsat,1} > 0.4V \\ \Rightarrow \underline{V_{dsat,1} < 0.6V} &\Rightarrow \underline{V_{dsat} \text{ of } M1 < 0.6V.} \end{aligned}$$

$$\begin{aligned} \rightarrow \text{Now } V_{out, CM} \text{ or DC value of } V_{out, P} &= V_x \\ &= V_{DD} - V_{SG, M1} = V_{DD} - V_{dsat,1} - V_{tp} \\ &= 1.3 - V_{dsat,1} \text{ should be } > 0.9 \text{ \& } < 1.1V \\ \text{Choosing } V_{out, CM} &= 1V \Rightarrow \underline{V_{dsat,1} = 0.3V.} \end{aligned}$$

Using Eqⁿ $\left(\frac{W}{L}\right) = \frac{I_d}{V_{sat}^2} \times \frac{2}{k_n}$, $W_{M1} = \underline{8\mu m}$.

Now, $\frac{W_{M3}}{W_{M5}} = \frac{I_{M3}}{I_{M5}} = \frac{200\mu A}{20\mu A} = 10 \Rightarrow \underline{W_{M3} = 10\mu m}$

Calculated Values


Parameter	Value
W1	8 μm
W2	8 μm
W3	10 μm
W4	10 μm
W5	1 μm
W6	2 μm
W7	40 μm
R1	20 $k\Omega$

Simulation Based Questions:


To obtain $V_{out,p}$ as 1 V, $W1$ and $W2$ were increased to 15 μm

To get a $V_{dsat,M6} = 200\text{ mV}$, $W6$ was reduced to 1.5 μm . Accordingly, $W7$ was reduced to 30 μm

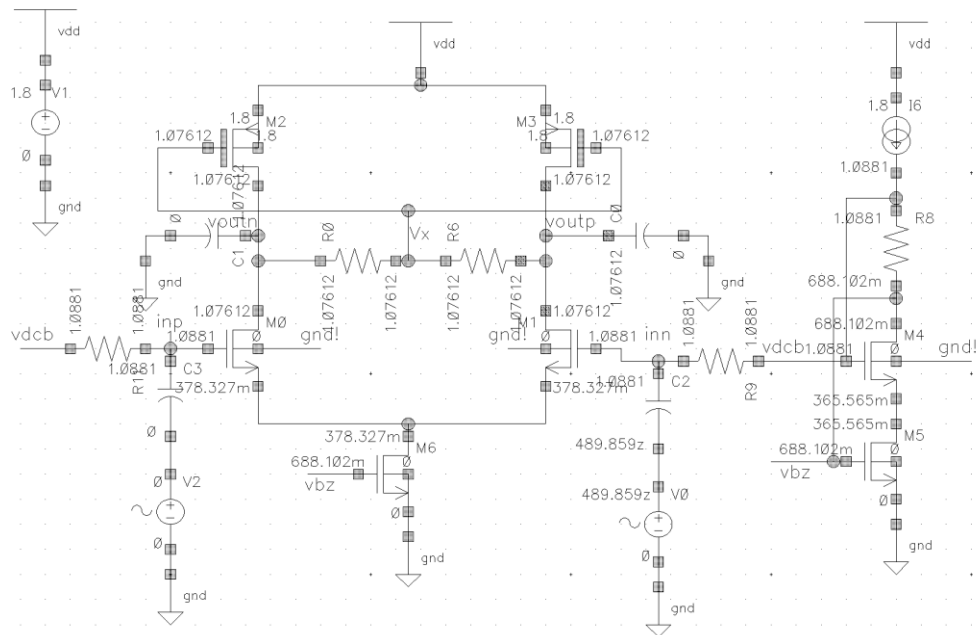1. Schematic with annotated Node Voltages:




2. Transistor Sizing:

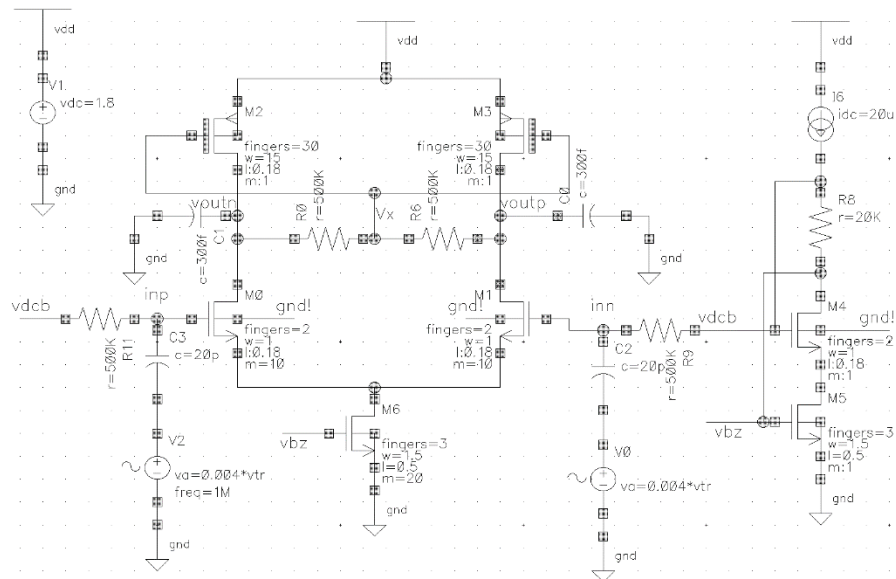


Transistor Sizing:

	Vdsat (V)	W (μm)	Multipliers	No of fingers
M1	0.224	15 μm	1	30
M2	0.224	15 μm	1	30
M3	0.142	1 μm	10	2
M4	0.142	1 μm	10	2
M5	0.154	1 μm	1	2
M6	0.217	1.5 μm	1	3
M7	0.217	1.5 μm	20	3
R1 value:	20 $\text{k}\Omega$			

3. DC Operating Points:

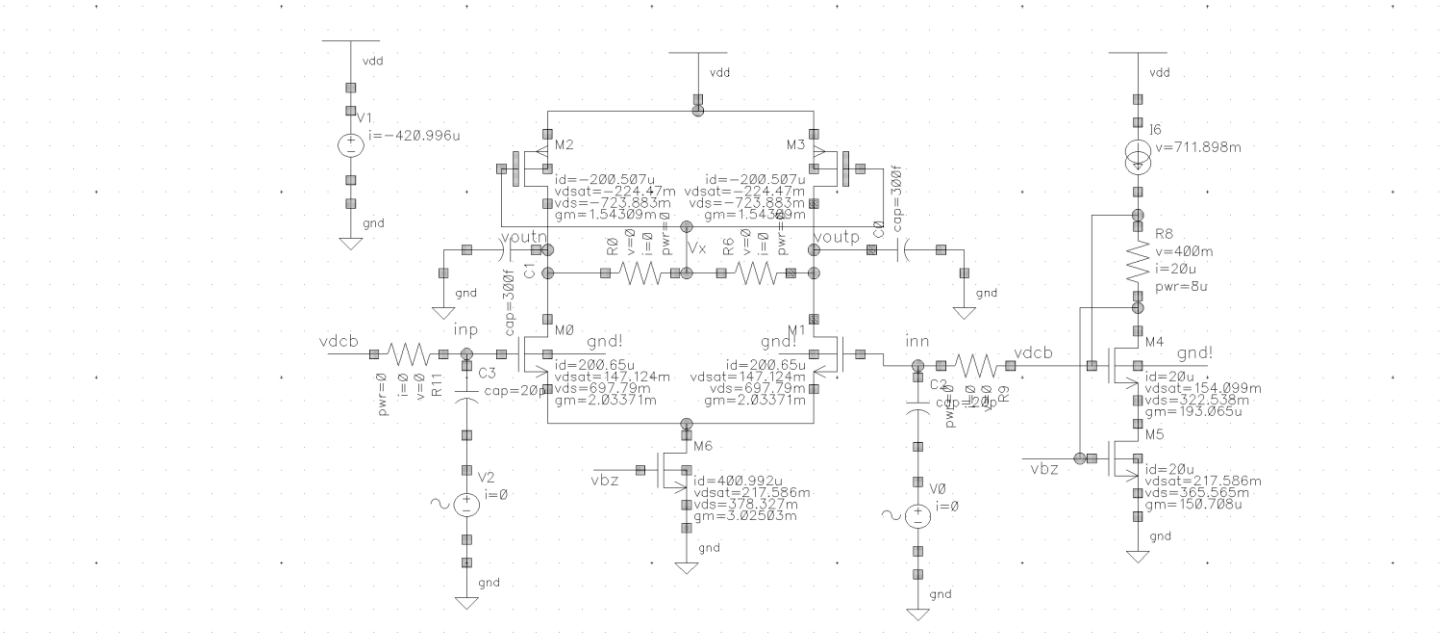


4. AC Plot:

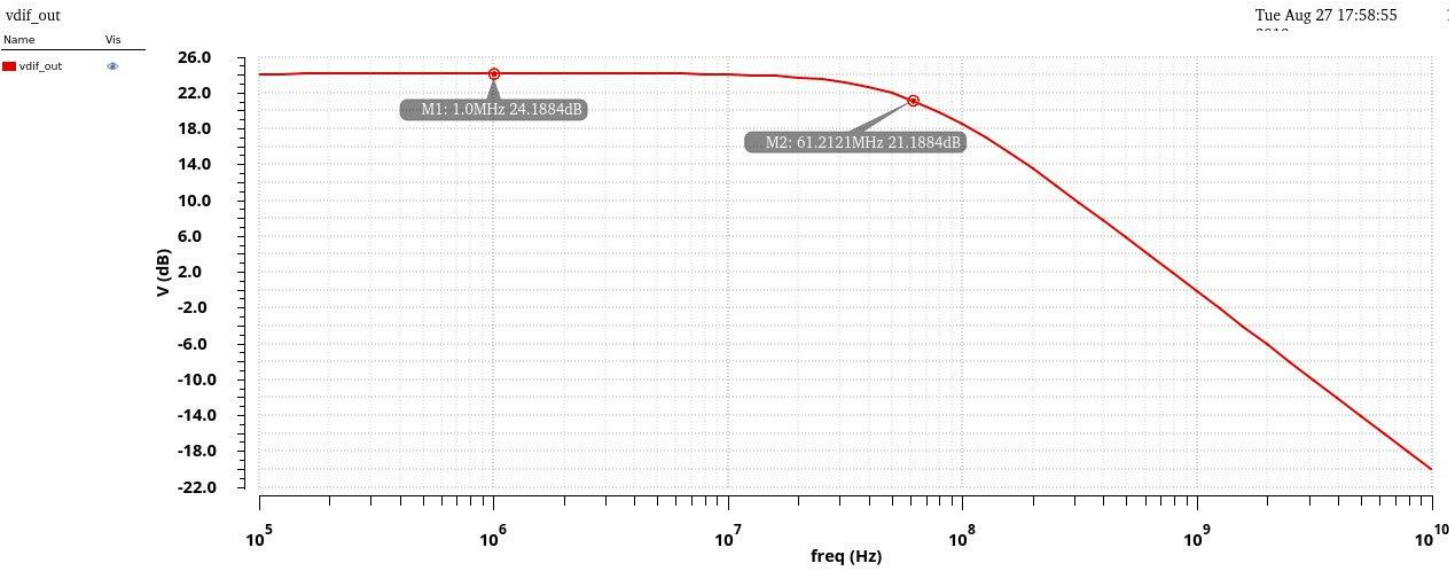

DC Gain: 24.2 dB


3dB Bandwidth: 61.2 MHz

5. Transient Pot:

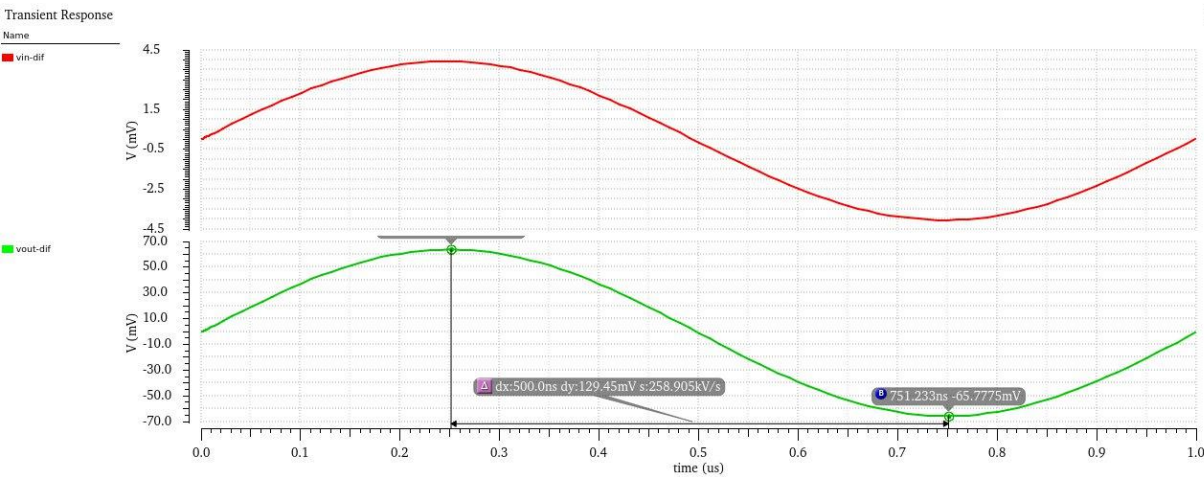

Vout pk-pk = 127.45 mV

Voutp and Vx:

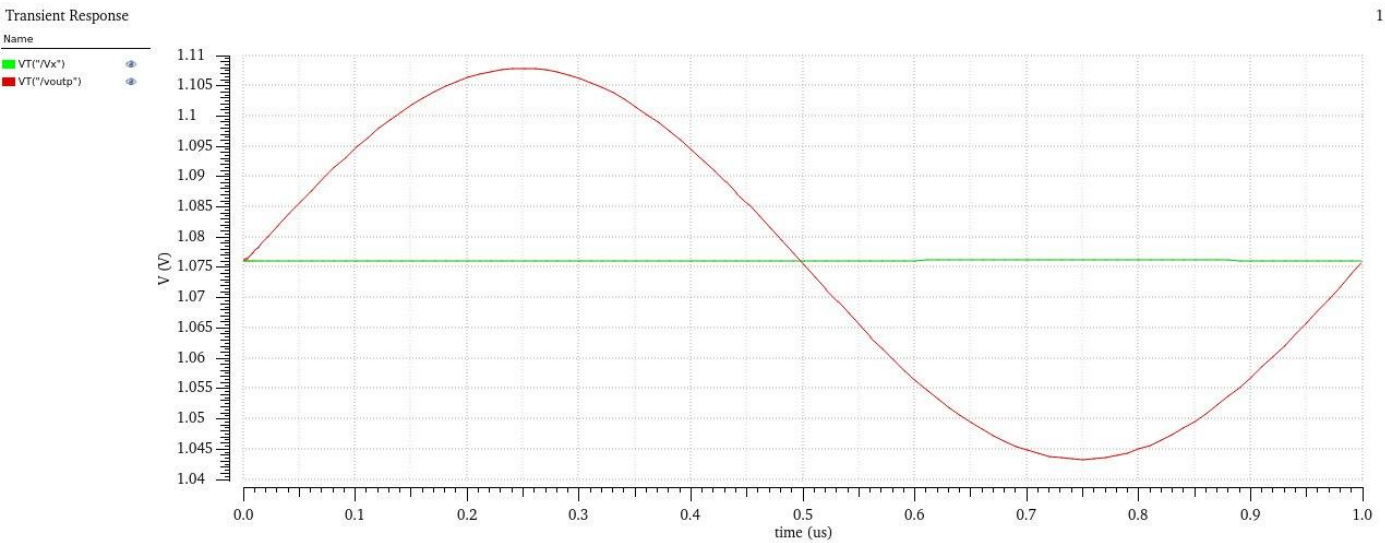

This shows Vx is at ac ground.

Parameter	Value Obtained	Specification
DC Power Consumption	0.76 mW	< 1.2 mW
Vout+ DC voltage	1 V	0.9 – 1.1 V
Differential Gain	24.2 dB	>20 dB
Vout Bandwidth	61 MHz	>40 MHz