
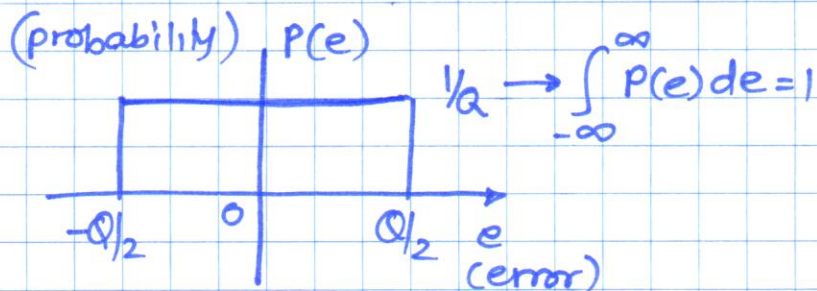
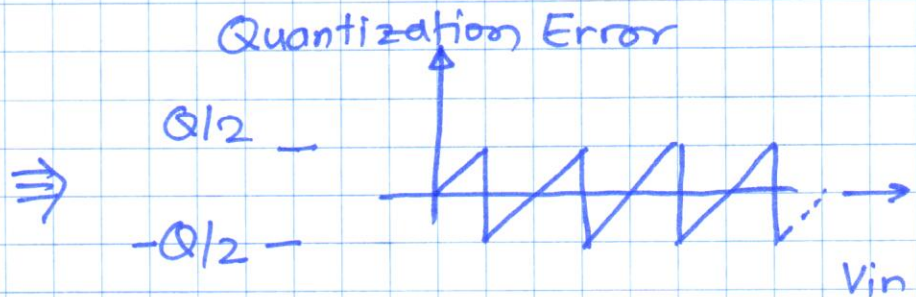



18 OCT 2019

SNR - QUANTIZATION NOISE DERIVATION.

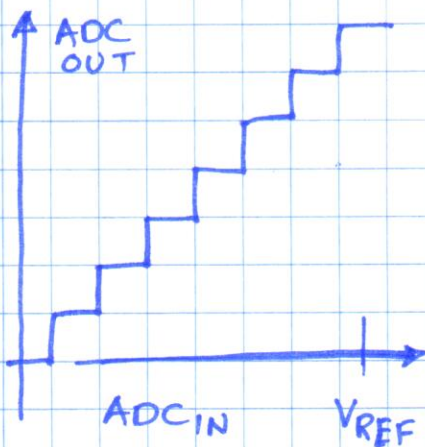

$$\sigma^2 = \text{Quantization Noise power} = \int_{-Q/2}^{Q/2} e^2 \cdot P(e) de$$
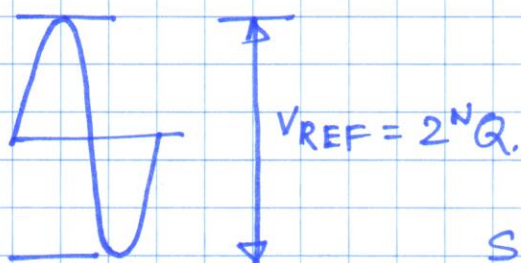
$$= \frac{1}{Q} \int_{-Q/2}^{Q/2} e^2 de = \frac{1}{Q} \left[\frac{e^3}{3} \right]_{-Q/2}^{Q/2} = \frac{Q^2}{12} = \overline{V_n^2} = V_{n, \text{rms}}^2$$



$$V_{\text{sig, rms}} = \frac{2^N Q}{\sqrt{2} \cdot 2}$$

$$\text{SNR} = 20 \log \left(\frac{V_{\text{sig, rms}}}{V_{n, \text{rms}}} \right)$$

$$= 20 \log \left(\frac{2^N Q}{2\sqrt{2}}, \frac{\sqrt{12}}{Q} \right)$$

$$\text{SNR} = 20 \log 2^N + 20 \log \left(\frac{\sqrt{3}}{2} \right) = 6.02 N + 1.76$$


Filter Approximations				
	Butterw	Chebyshev	Elliptic Cauer	Bessel
Passband	* * *	* * * *	* * * *	* *
Stopband Atten	* * *	* * * *	* * * * *	* *
Group Delay	* * *	* *	*	* * * *

Filter Design Process



1. Choose Filter Approx based on desired filter Characteristics
2. For Normalized f_{stopband} , use filter curves to determine order of filter.
3. Use filter tables to find out component values.

Signal flow Graph Technique SFG


Basics

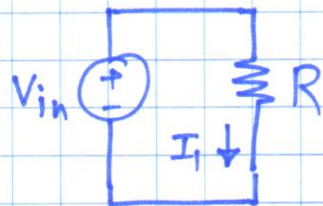



$$V_{in} = I_1 R$$

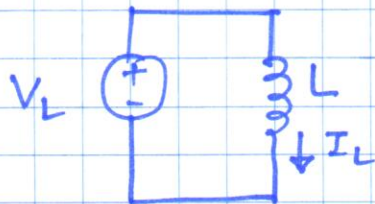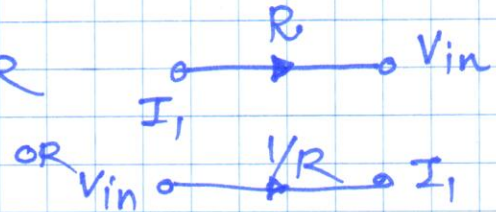


$$I_L = \frac{V_L}{sL}$$

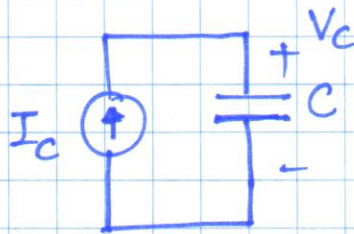


$$V_C = \frac{1}{sC} I_C$$

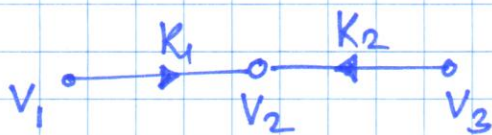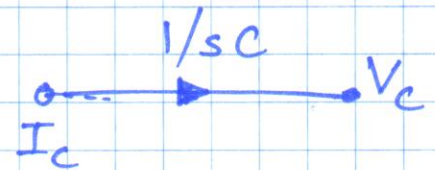

$$\Rightarrow V_2 = K_1 V_1 + K_2 V_3$$

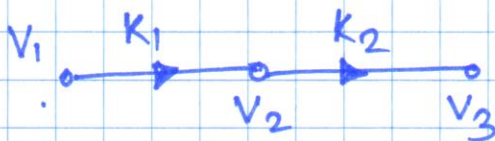

$$\Rightarrow V_3 = K_1 K_2 V_1$$

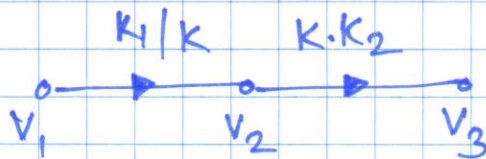


$$\Rightarrow V_3 = \frac{K_1}{K} \cdot K K_2 V_1$$

$$= K_1 K_2 V_1 \text{ equivalent}$$

Signal Flow Graph Technique simulates voltage-current relationship in passive network.


Example : One pole RC Lowpass filter

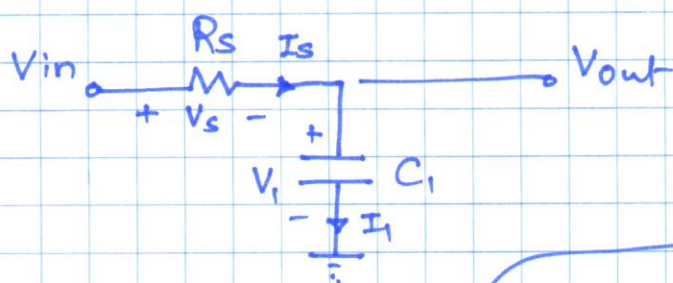

Equations for this ckt

$$\begin{cases} V_s = (V_{in} - V_i) \\ V_{out} = V_i \\ V_i = \frac{1}{sC_1} I_i \quad (\text{Integrator}) \\ I_s = I_i \\ I_s = \frac{V_s}{R_s} \end{cases}$$

Modeling in SFG Technique

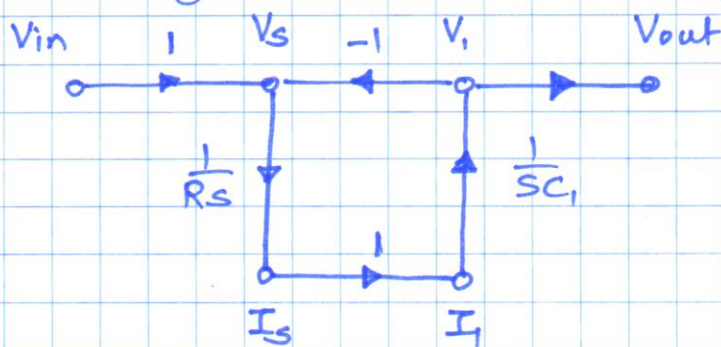


* Move $\frac{1}{R_s}$ around loop

* scaling resistance R

$$V_s' = R I_s$$


$$V_i' = R I_i$$

Choosing $R = 1$
(convenience)

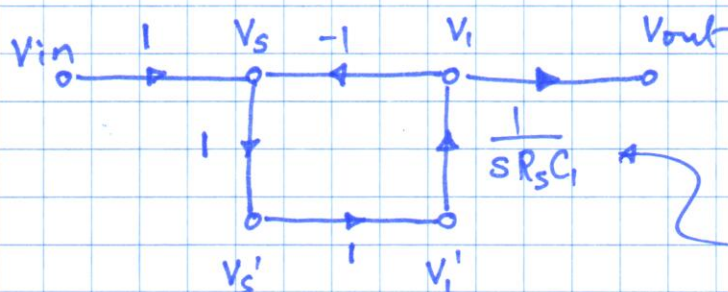


Integrator



Implementing Integrator

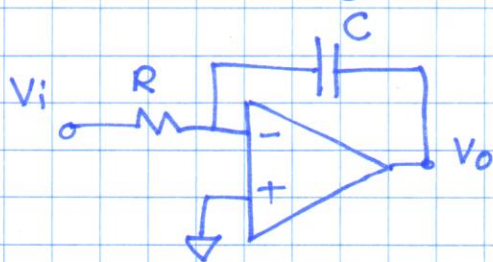

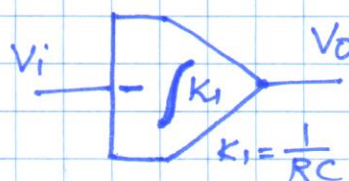
$$\frac{V_i}{R} = \frac{-V_o}{1/sC} \Rightarrow V_o = -\frac{V_i}{sRC}$$



Note: i/p &
o/p both
voltages.

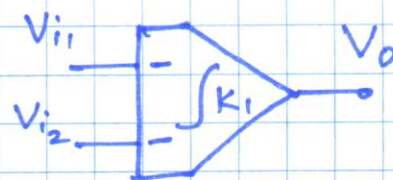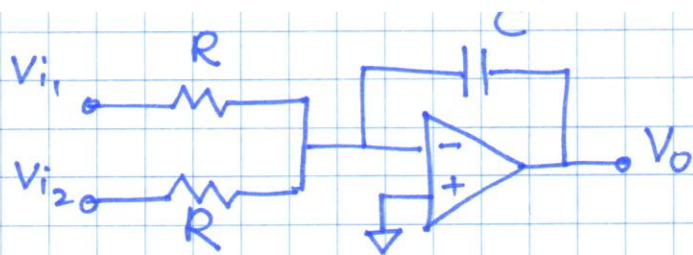


Pushing this in SFG

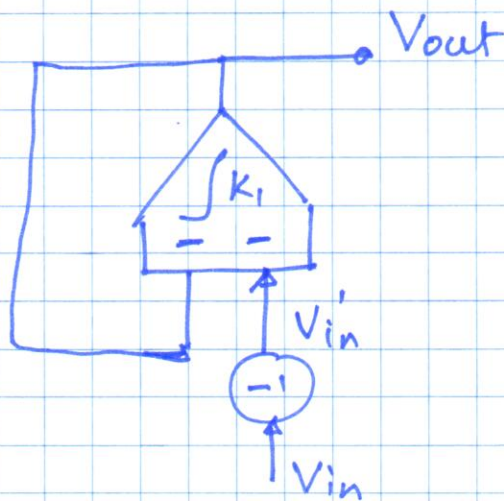

$$K_i = \frac{1}{R_s C_i}$$


★

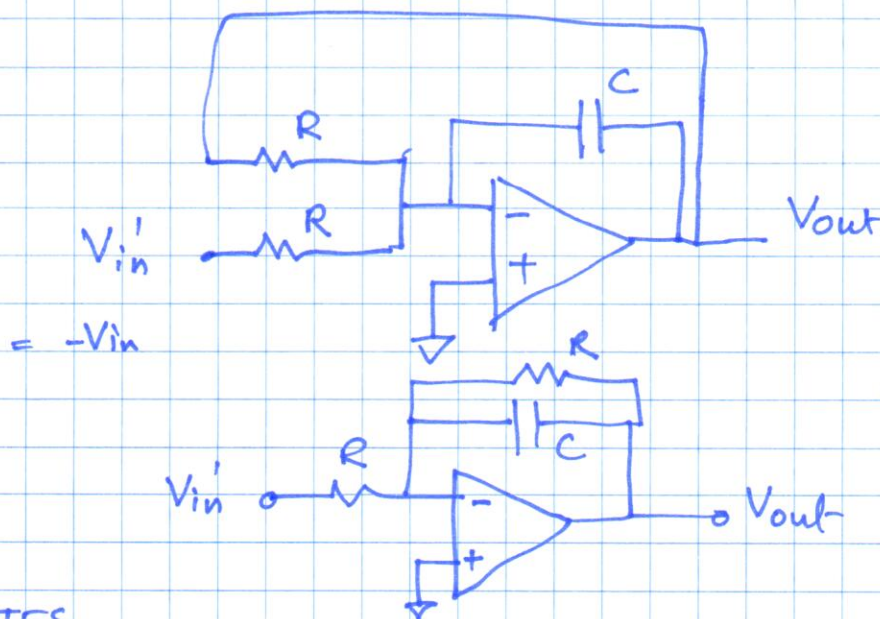


$$\frac{V_{out}}{V_{in}} = \frac{-1}{1 + RCs}$$

NOTES

- ★ Active RC (or OPAMP RC) integrator has inverting i/p only.
- ★ Other integrators we will study have both +/- i/p.
- ★ Active RC integrator can be used in fully differential configuration with both + & -ve i/p.
→ Will study fully differential circuits later.

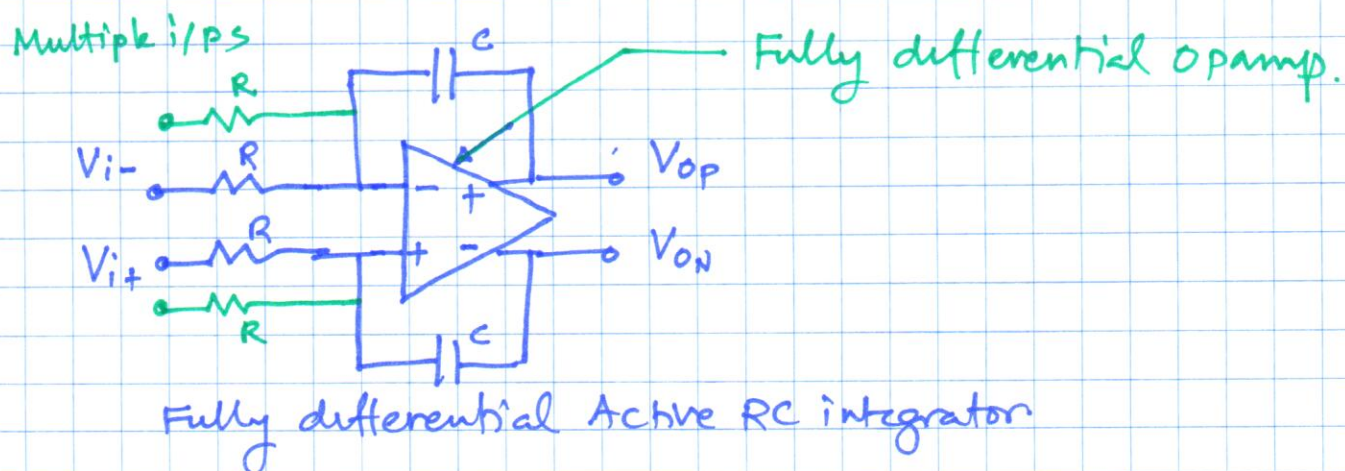


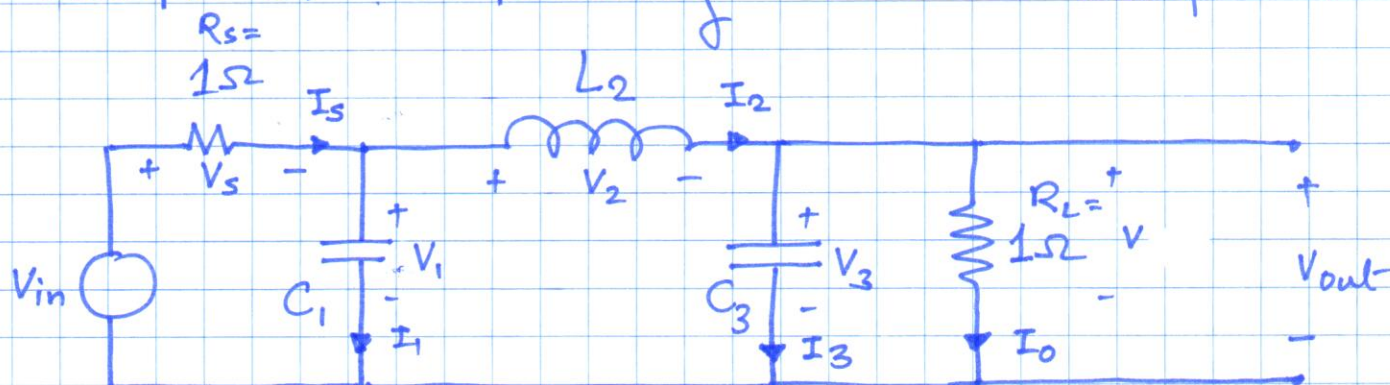Example 2. Implementing Third Order Chebyshev filter




SFG. Steps

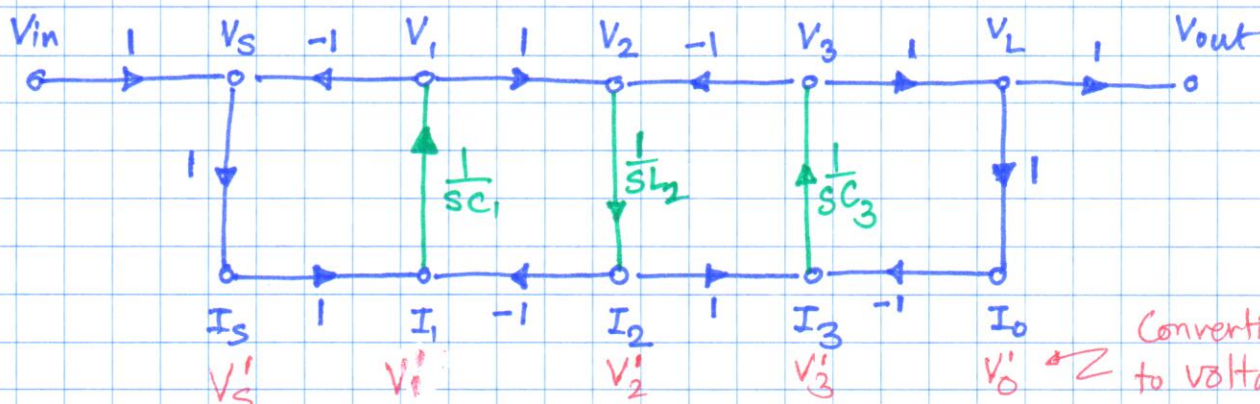1. Label all branch currents & voltages.
2. Draw voltage as "node" on top & current as "node" on bottom.
3. Represent Integrator relationships first
4. Complete SFG with Rest of KVL & KCL equations.



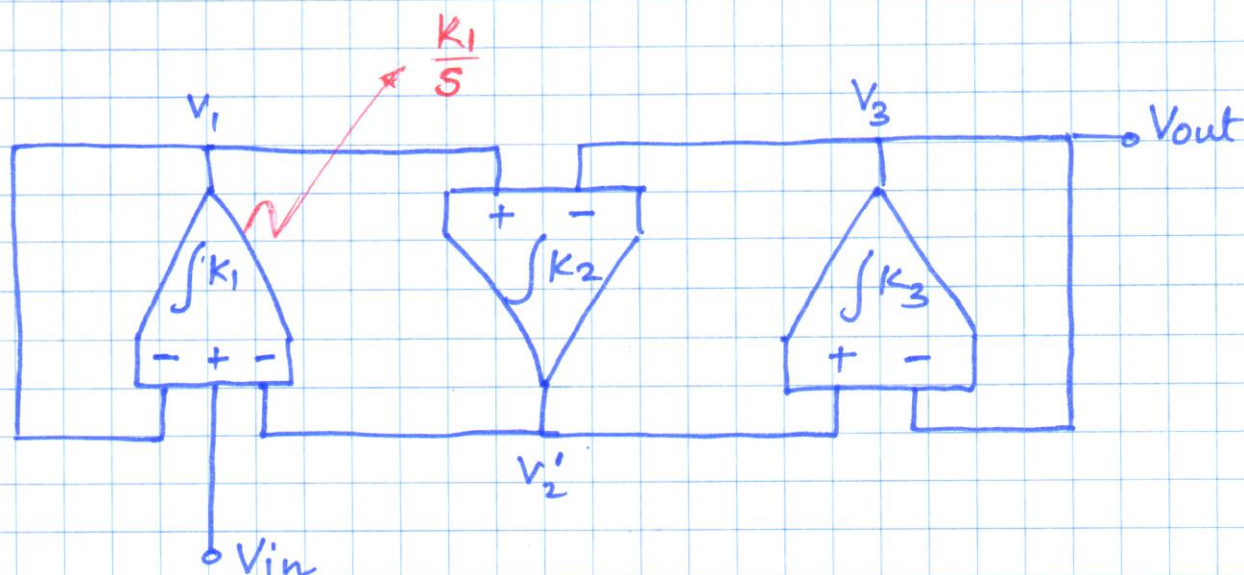Converting
to voltages
with scaling
 $R=1$




$$K_1 = \frac{1}{C_1}$$

$$K_2 = \frac{1}{L_2}$$

$$K_3 = \frac{1}{C_3}$$

For Chebyshev filter example

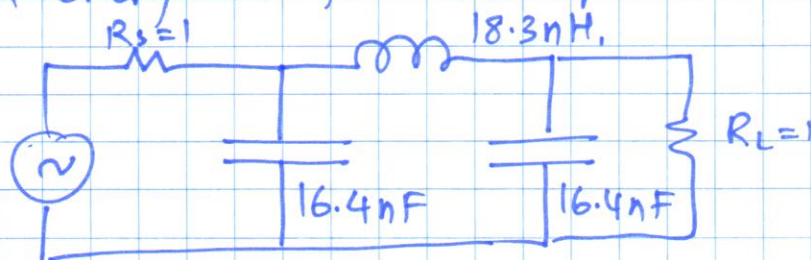

Implementing each integrator with fully diff. active RC integrator.

$$K_3 = K_1 = \frac{1}{16.4 \text{ n}} = \frac{1}{R_1 C_1} \Rightarrow$$

Choosing $C_1 = 1 \text{ pF}$
 $R_1 = 16.4 \text{ k}\Omega$


$$K_2 = \frac{1}{18.3 \text{ n}} = \frac{1}{R_2 C_2} \Rightarrow$$

Choosing $C_2 = 1 \text{ pF}$
 $R_2 = 18.3 \text{ k}\Omega$



Values compact
 realizable on chip.

Few comments on filter implementation.

1. Doubly-Terminated Ladder filter

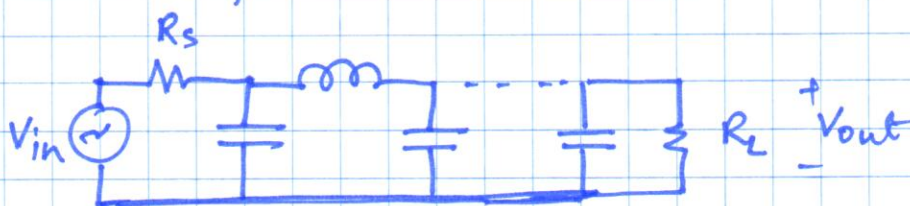


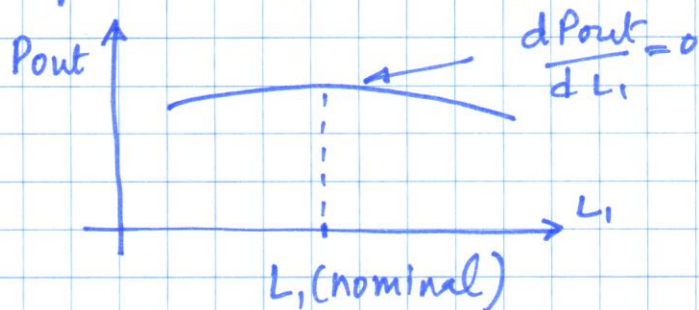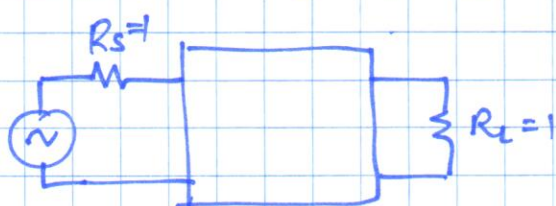Low sensitivity
due to component variation.



→ Component variation insensitivity in passband.

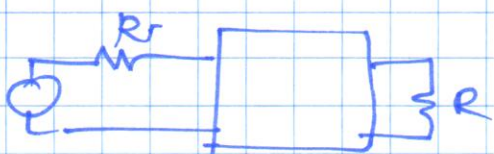2. Attenuation of 6dB due to double-termination



→ Can be corrected by adding gain @ i/p.

Next Lecture:

- Various ways of implementing Integrators.
- Trade-offs.