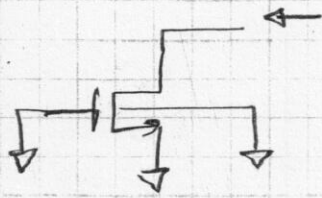


9AUG2019

## Small Signal Mos terminal impedances

①




$$g = g_{ds}$$

$$C = C_{gd} + C_{db}$$

↓ ← ac ground


High impedance

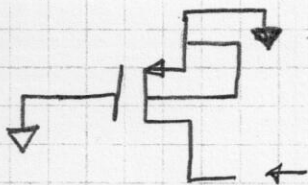Dc proper biasing to keep transistor in sat.




Looking into drain

②

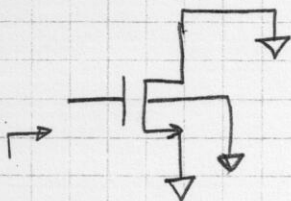

$$g = 0$$


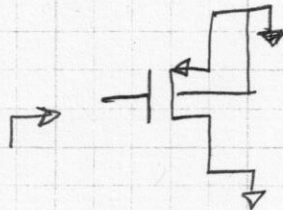


Looking into Gate

$$C = C_{gs} + C_{gd}$$

— High Impedance

③

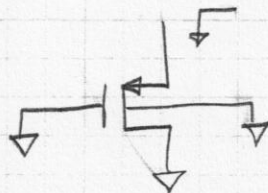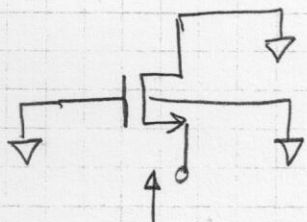



Looking into Source.

$$g = g_m + g_{mbs} + g_{ds}$$

$$C = C_{gs} + C_{sb}$$

Low impedance.



④

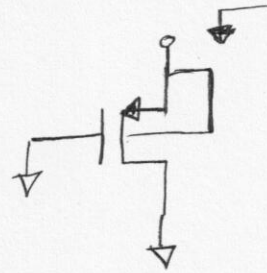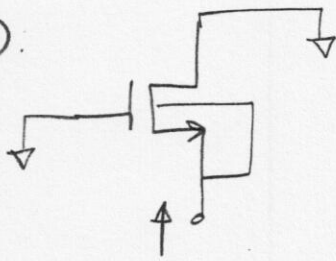

Looking into  
source  
(self biased  
well)



$$g = g_m + g_{ds}$$

$$C = C_{gs} + C_{gb} + C_{db} + C_{well}$$

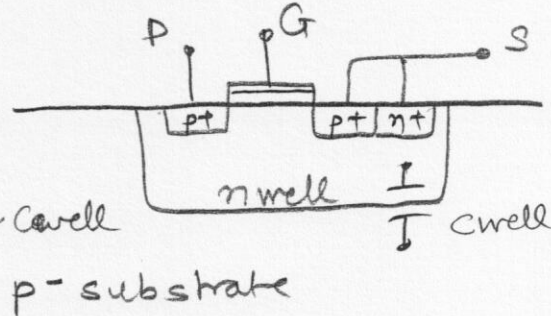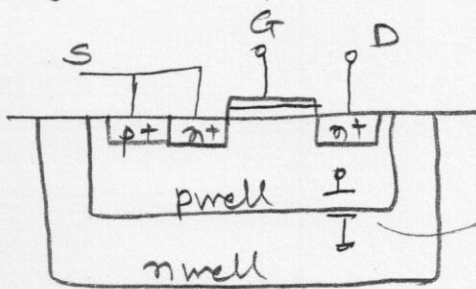C<sub>well</sub>

p-substrate

⑤

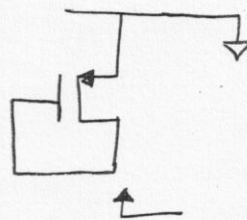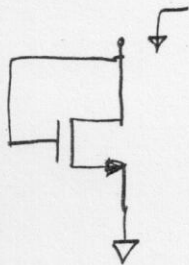



$$g = g_m + g_{ds}$$

$$C = C_{gs} + C_{db}$$


called diode connected device.

## Amplifiers

### 1. Common-Source amplifier

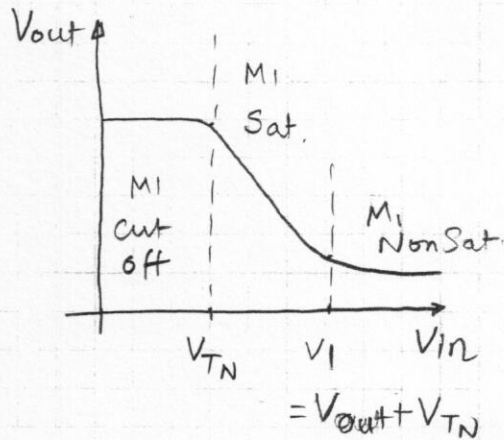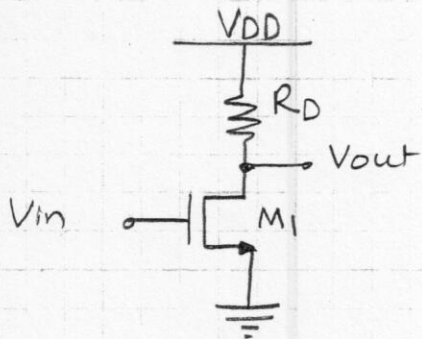

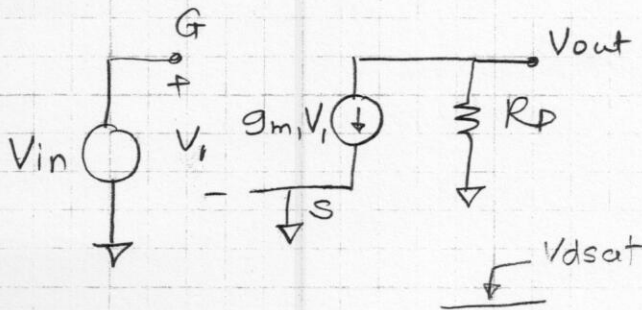Small Signal Model in Sat. region (ignoring  $r_o$ )



$$V_{out} = -g_m R_D V_{in}$$

$A_v$  voltage gain

$$g_m = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TN})$$

$$= \frac{2 I_D}{(V_{GS} - V_{TN})}$$

$$= \sqrt{2 \mu_n C_{ox} \left( \frac{W}{L} \right) I_D}$$

Small Signal  
Quantity

$I_D, V_{GS}$  = Bias  
values


key observation  
If i/p signal is large  
( $V_{GS} - V_{TN}$ ) & hence  $g_m$   
& hence gain of the  
circuit changes a lot.

Gain varies with signal  
swing.

⇒ Distortion



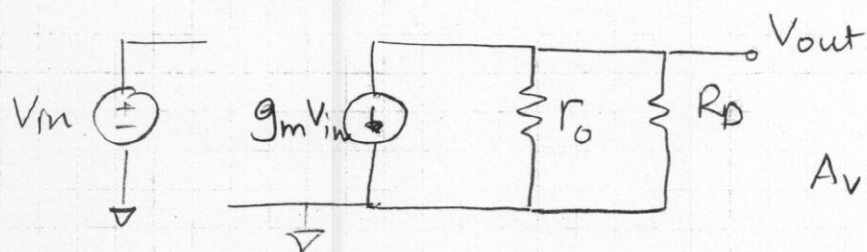Including channel length modulation ( $r_o$ ) effect -




$$A_v = \frac{V_{out}}{V_{in}} = -g_m \frac{r_o R_D}{r_o + R_D}$$

$$A_v = -g_m \cdot \underbrace{(r_o \parallel R_D)}_{\text{Effective output impedance}} = - \frac{g_m(\text{driver})}{g_{out\uparrow} + g_{out\downarrow}}$$

↑  
Driver  
 $g_m$

CS Amp with diode load

①

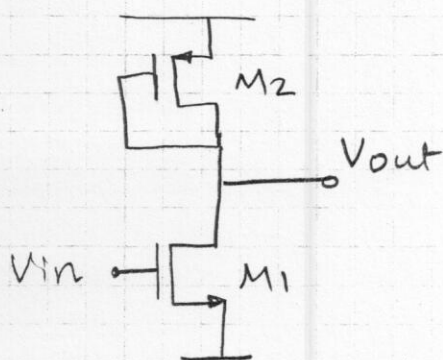

By inspection

$$A_v = - \frac{g_m(\text{driver})}{g_{out\uparrow} + g_{out\downarrow}}$$

$$A_v = - \frac{g_{m1}}{g_{m2} + g_{ds2} + g_{ds1}}$$

$$\approx - \frac{g_{m1}}{g_{m2}} = - \frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_N I_D}}{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_P I_D}}$$


$$\approx - \frac{\mu_n \left(\frac{W}{L}\right)_N}{\mu_p \left(\frac{W}{L}\right)_P}$$

→ Low voltage gain  $\sim 2-6$

→ Low o/p swing  $V_{omin} = V_{DSAT1} \quad (0.25V)$

$$V_{Omax} = V_{DD} - |V_{GS_P}| = V_{DD} - (V_{TP}) - V_{DSAT2}$$

$1.2V - 0.6 - 0.25V = 0.35V$

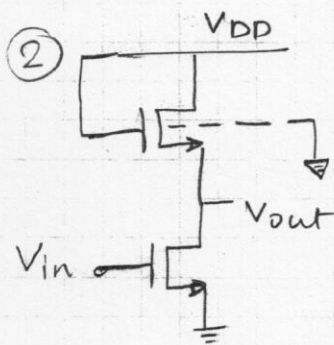



$$A_v = \frac{-g_m(\text{driver})}{g_{out\uparrow} + g_{out\downarrow}}$$

$$A_v = \frac{-g_{m1}}{g_{m2} + g_{mbs2} + \underbrace{g_{ds2} + g_{ds1}}_{\text{ignore}}}$$

$$A_v = - \frac{g_{m1}}{g_{m2} + g_{mbs2}} = - \frac{\sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot \frac{1}{1+\eta}}{\underbrace{1}_{\text{body effect } 0.25 \cdot g_{m2}}}$$

Low gain & Low swing.

C-S Amplifier with current source load.

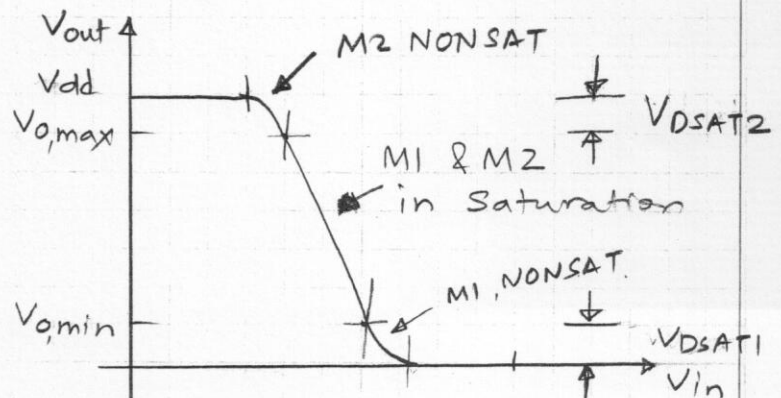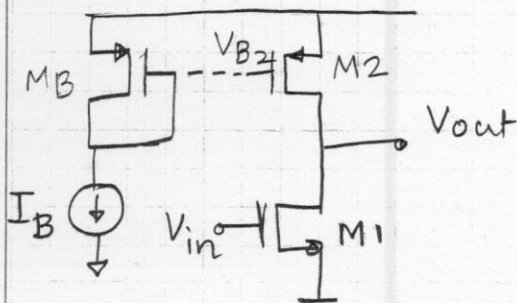

$$\left(\frac{W}{L}\right)_B = \left(\frac{W}{L}\right)_2 \Rightarrow I_1 = I_2 = I_B$$


$$V_{B2} = V_{DD} - (|V_{Tp}| + V_{DSAT2})$$

$$V_{B1} = V_{TN} + V_{DSAT1}$$

$$V_{DSAT1} = \sqrt{\frac{2 I_B}{\mu_n C_{ox} (W/L)_1}}$$

$$V_{DSAT2} = \sqrt{\frac{2 I_B}{\mu_p C_{ox} (W/L)_2}}$$

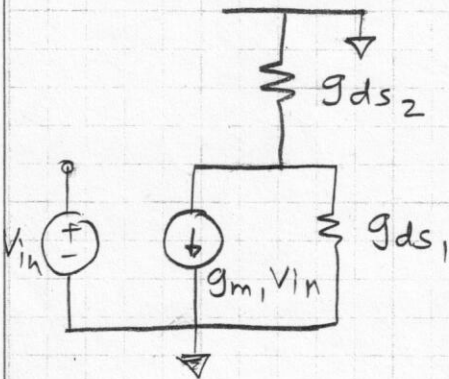When Both  $M1$  &  $M2$  are in saturation  
— small signal analysis



$$A_v = - \frac{g_{m1}}{g_{ds1} + g_{ds2}}$$

$$= - \frac{2I_B / (V_{GS} - V_T)_N}{\lambda_N I_B + \lambda_P I_B}$$


$$= - \frac{2}{V_{DSAT1} (\lambda_N + \lambda_P)}$$



Insight To increase gain, reduce  $V_{DSAT1}$  & increase channel length to reduce  $\lambda_N, \lambda_P$

★ Can you keep on reducing  $V_{DSAT}$  & ↑ gain?
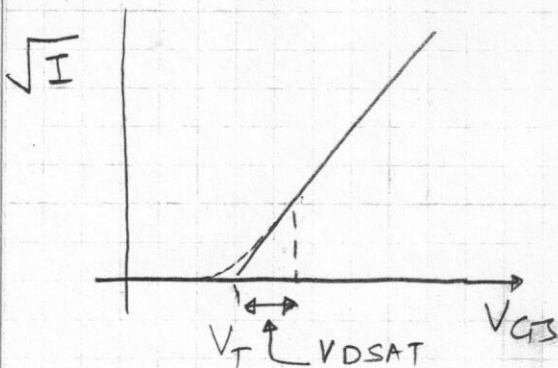
$$V_{DSAT1} = V_{GS} - V_T = \sqrt{\frac{2I}{\mu C_{ox} \left(\frac{W}{L}\right)}} \left\{ \begin{array}{l} \text{for given } I \\ \text{as you } \uparrow W/L \\ V_{DSAT} \downarrow \end{array} \right.$$



$$I = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

As you keep on reducing  $V_{DSAT} = (V_{GS} - V_T)$ ,





$V_{GS}$  very close to  $V_T$

→ sub-threshold operation

To allow for i/p signal swing & to keep out of sub-thresh region  $V_{DSAT} > 150 \text{ mV}$  (gen. design)



## CS Amp with Active Load

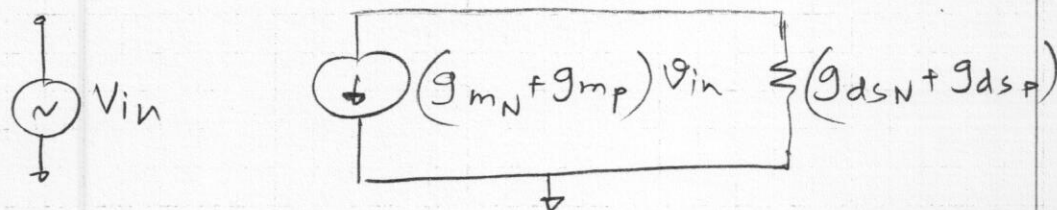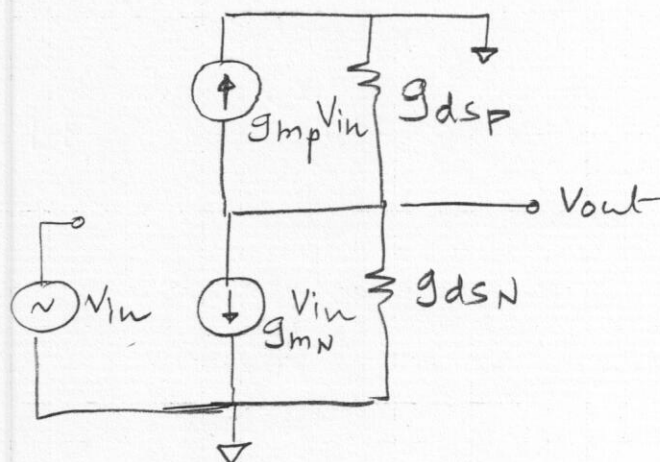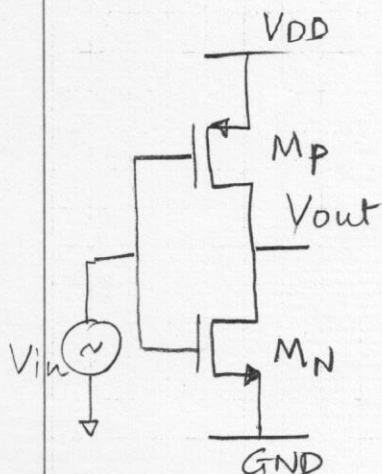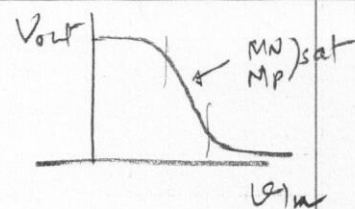

$$A_v = - \frac{(g_{mn} + g_{mp})}{(g_{dsn} + g_{dsp})}$$

Num. Example:



$$\text{gain } A_v \geq 100$$

$$V_{out\min} = 250\text{mV}$$


$$V_{out\max} = V_{dd} - 250\text{mV}$$

$$C_L = 1\text{pF} : f_u = 100\text{MHz}$$

unity gain frequency

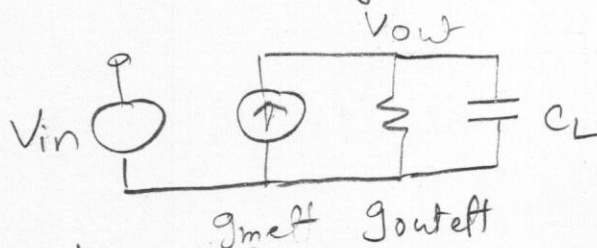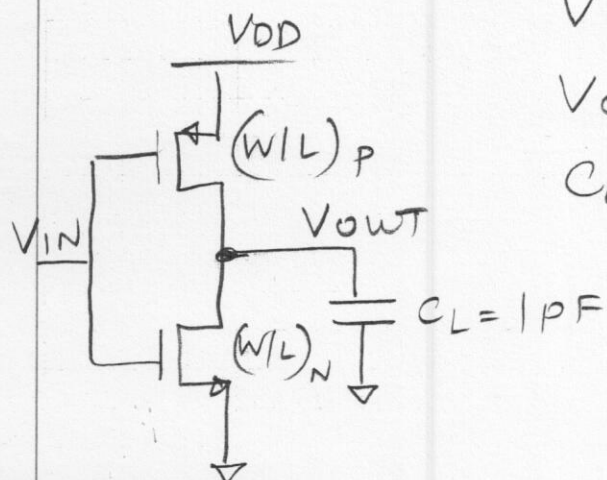

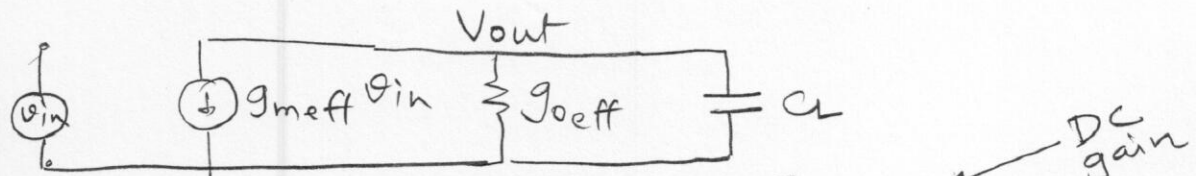
ignoring transistor internal caps. ( $\ll 1\text{pF}$ )



$$V_{out} = \frac{-g_{meff} v_{in}}{(g_{oeff} + s C_L)} = \frac{-\frac{g_{meff}}{g_{oeff}}}{\left(1 + \frac{s}{g_{oeff}/C_L}\right)}$$

DC gain

$\omega_p =$

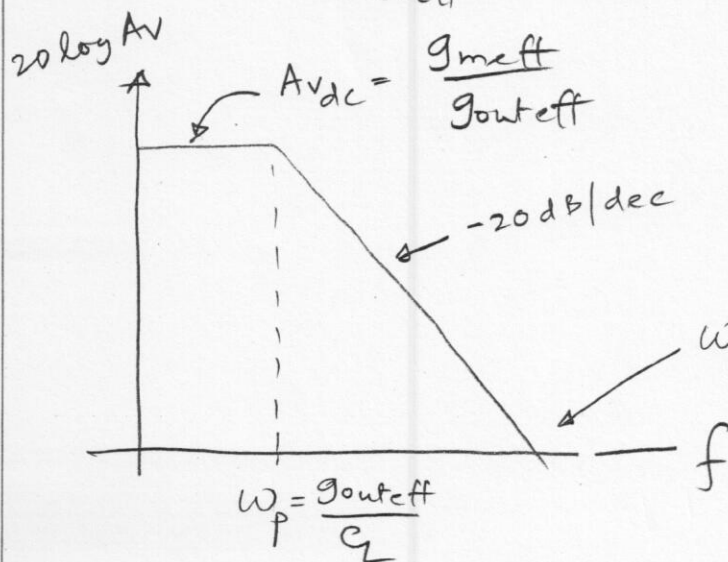

$$\omega_u = \frac{g_{meff}}{C_L} \quad |A_v| = 1$$

$$f_u = \frac{\omega_u}{2\pi} = \frac{1}{2\pi} \cdot \frac{g_{meff}}{C_L} = 100 \text{ MHz}$$

$$g_{meff} = 2\pi C_L \times 100 \text{ MHz} = 2 \times \pi \times 1 \times 10^{-12} \times 10^8 \text{ S}$$

$$= 628 \mu\text{S} \quad \text{--- (1)}$$

Symmetric O/p voltage swing  $V_{DSATN} = V_{DSATP} = 250 \text{ mV}$

$$\sqrt{\frac{2I}{K_N \left(\frac{W}{L}\right)_N}} = \sqrt{\frac{2I}{K_P \left(\frac{W}{L}\right)_P}} \Rightarrow \left(\frac{W}{L}\right)_P = \frac{K_N}{K_P} \left(\frac{W}{L}\right)_N$$

$$K_N = \mu_N C_{ox} = 136.5 \mu\text{A/V}^2$$

$$K_P = \mu_P C_{ox} = 39 \mu\text{A/V}^2$$

$$\left(\frac{W}{L}\right)_P = \frac{136.5}{39} \left(\frac{W}{L}\right)_N = 3.5 \left(\frac{W}{L}\right)_N \quad \text{--- (2)}$$

$$g_{m,n} = g_{m,p} = \frac{2I}{V_{DSAT}}$$



$$g_{meff} = g_{mN} + g_{mP} \Rightarrow g_{mN} = g_{mP} = 314 \mu S$$

$$\frac{2I}{V_{DSAT}} = 314 \mu S \Rightarrow I = \frac{314 \mu S \times 250 mV}{2} = 39.25 \mu A \quad (3)$$

To maximize voltage gain

$$A_v = \frac{g_{mN} + g_{mP}}{g_{dsN} + g_{dsP}} \Rightarrow g_{dsN} = g_{dsP}$$

$$g_{dsN} = \lambda_N I = \frac{0.05}{L_n \text{ (in } \mu m)} I$$

$$g_{dsP} = \lambda_P I = \frac{0.1}{L_p \text{ (in } \mu m)} I$$

$$\Rightarrow L_p = 2 L_n \quad (\text{Channel Length})$$

$$A_v = \frac{628 \mu S}{2 \cdot g_{ds}} = 100 \Rightarrow g_{dsN,P} = 3.14 \mu S$$

$$\frac{0.05 \times I}{L_n} = 3.14 \mu S \Rightarrow L_n = \frac{0.05 \times 39.25 \mu A}{3.14 \mu S}$$

(in  $\mu$ )

$$L_n = 0.625 \mu m$$

$$L_p = 2 \cdot L_n = 1.25 \mu m$$

0.5  $\mu m$  Technology  $\rightarrow$  grid 0.25  $\mu m$

Round up L values to get on grid & make sure  $A_v > 100$

$$L_n = 0.75 \mu m \quad L_p = 1.5 \mu m$$

$$V_{DSATN} = \sqrt{\frac{2I}{K_N (W/L)_N}} < 0.25 V$$


$$\left(\frac{W}{L}\right)_N > \frac{2I}{K_N \cdot (0.25)^2} = \frac{2 \times 39.25 \mu A}{136.5 \mu A/V^2 \times (0.25)^2 V^2} = 9.2$$

$$W_N > 9.2 \times 0.75 \mu m = 6.9 \mu m$$


$$W_N = 7 \mu m$$

$$\left(\frac{W}{L}\right)_P = 3.5 \times \left(\frac{W}{L}\right)_N \Rightarrow W_P = 3.5 \times \frac{7}{0.75} \times 1.5$$

$$W_P = 49 \mu m$$

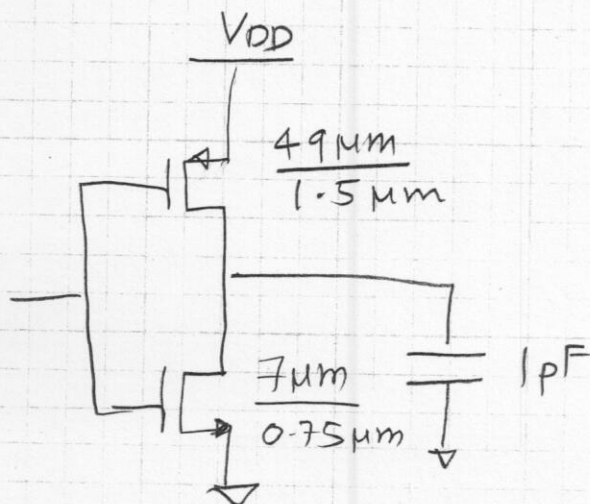



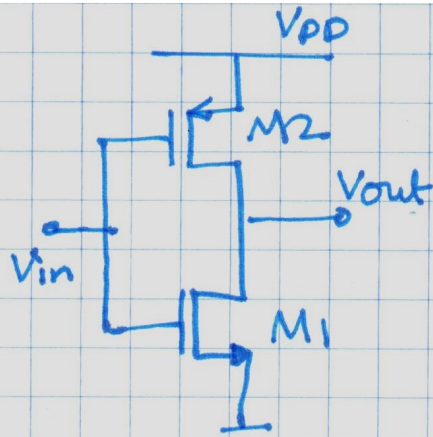

Represents AC behavior of circuit.

DC circuit - different

$$V_{DsatN} = V_{Dsatp} = 0.25V$$

$$\therefore V_{GSN} = V_{TN} + V_{Dsatn} = 0.5 + 0.25 = 0.75V$$


$$V_{SGp} = (V_{Tp}) + V_{Dsatp} = 0.6 + 0.25 = 0.85V$$

DC condition

$$V_{DD} = V_{SGp} + V_{GSN} = 0.85 + 0.75 = 1.6V$$

Satisfied only for  $V_{DD} = 1.6V$ .

Actual circuit implementation DC & AC.

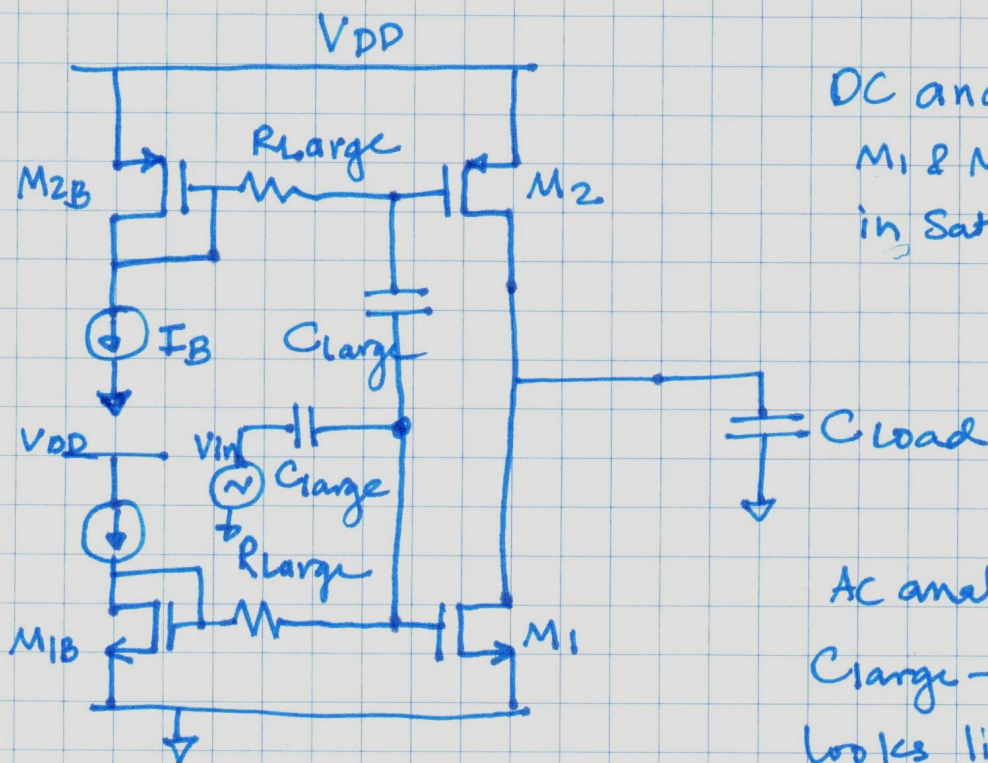

DC analysis

$M_1$  &  $M_2$  are biased in Sat with  $I_B$

AC analysis

Charge - short looks like inverter amplifier.