


11 OCT 2019

Since  $V_{REF} \approx 1.25V$   $V_{DD} > 1.25V$ .

What about  $V_{REF}$  for  $V_{DD} < 1V$ ?

### Reference

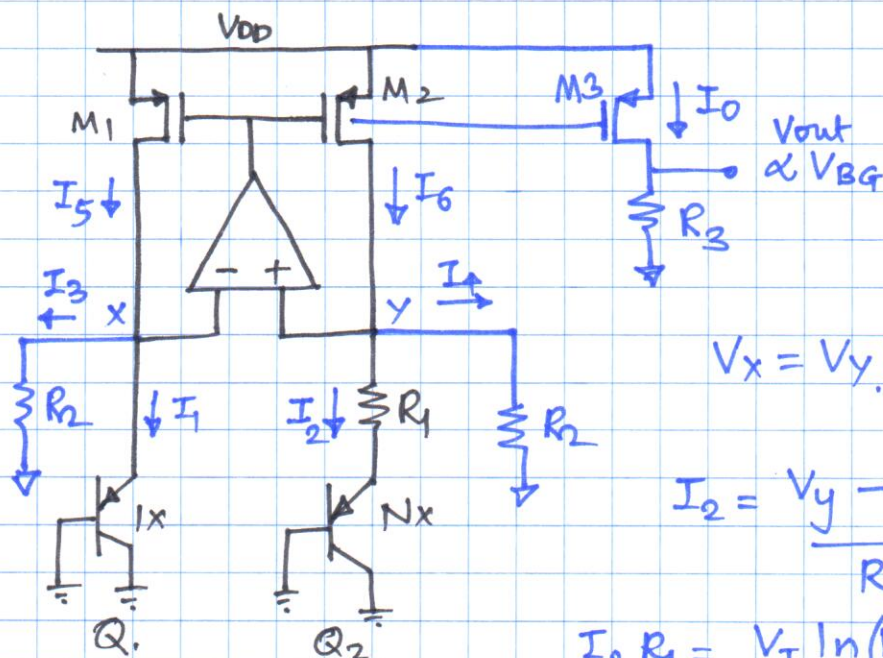H. Banba "CMOS BGAP REF with sub-1-V op"  
JSSC NOV 1997.



$V_x = V_y$  due to fbk (opamp)

$$I_2 = \frac{V_y - |V_{BE2}|}{R_1} = \frac{|V_{BE1}| - |V_{BE2}|}{R_1}$$

$$I_2 R_1 = V_T \ln(N) \quad \text{--- (1)}$$

Also  $I_3 = I_4 = \frac{V_{BE1}}{R_2}$

$$I_6 = I_2 + I_4 = \frac{V_T \ln N}{R_1} + \frac{|V_{BE1}|}{R_2} = \frac{1}{R_2} \left( |V_{BE1}| + \frac{V_T \ln N}{\left(\frac{R_2}{R_1}\right)} \right)$$

By choosing  $\frac{R_2}{R_1}$  term inside brackets =  $V_{BG}$

$$I_6 = \frac{V_{BG}}{R_2}$$

$$I_0 = \frac{V_{BG}}{R_2} \Rightarrow \boxed{V_{out} = \frac{R_3}{R_2} V_{BG}}$$

keep  $\frac{R_3}{R_2} < 1$  for  $V_{DD} < \underline{1V}$


Issue with Banba Bgap.

Nodes x & y DC voltage  $0.7V - 0.9V \sim$

→ Input diff pair of opamp - Native NMOS ( $V_T \approx -0.2V$ )

→ Leung / Mok solution

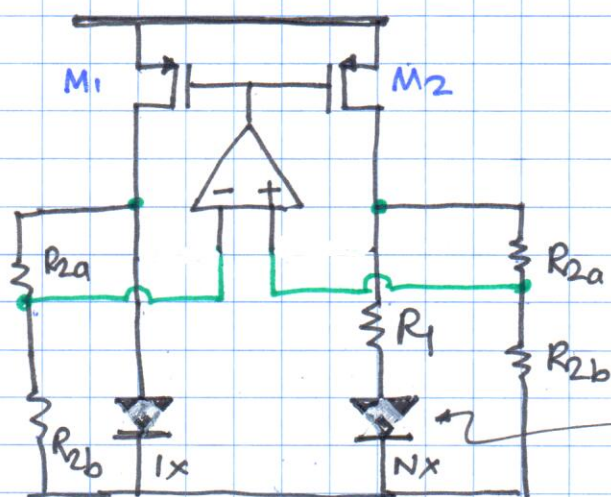IEEE JSSC Apr. 2002  
"A Sub-1-V 15-ppm/ $^{\circ}C$  CMOS Bgap..."



Lower common-mode i/p range of opamp using resistive divider.


$V_{BE}$  junction shown as diode

### \* Bandgap Startup Problem

- Undesired stable solution. - All currents zero.
- Can be observed when you ramp up power supply.
- Startup circuit detects this condition & pumps in juice to get to desired operation point.




## Startup Solution (one possible)

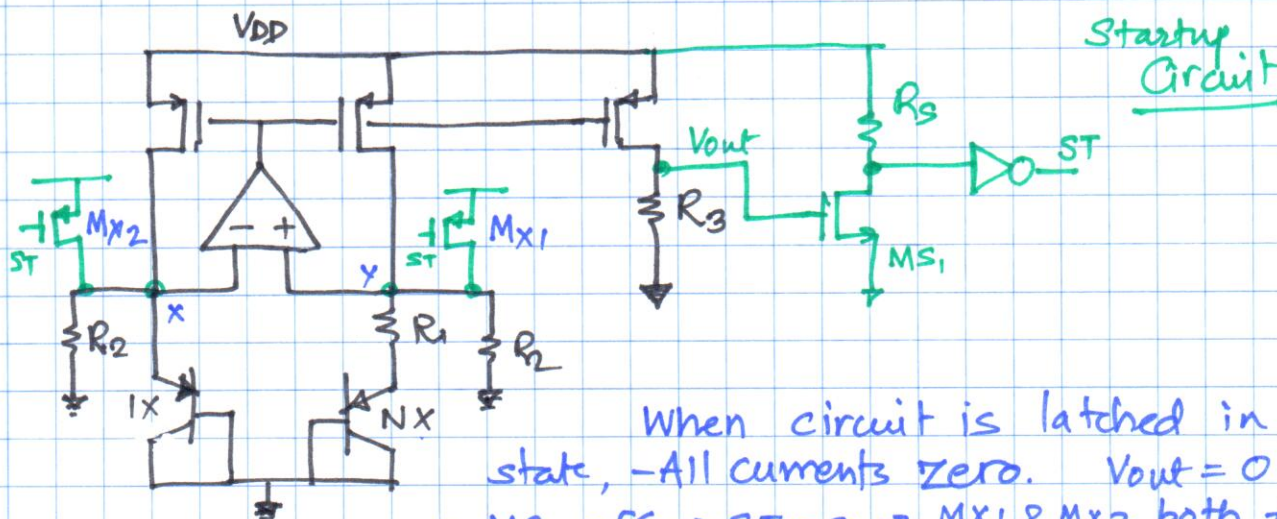


When circuit is latched in undesired state, - All currents zero.  $V_{out} = 0$   
 $\rightarrow MS_1$  off  $\rightarrow ST = 0 \rightarrow Mx1$  &  $Mx2$  both turn on  
 $\rightarrow$  Lift both Nodes  $x$  &  $y \rightarrow$  Opamp starts to work.

## \* PTAT Current source

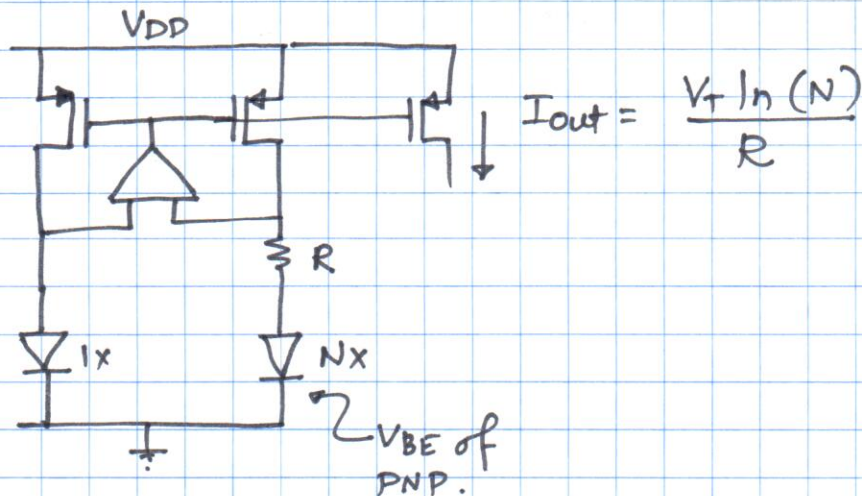
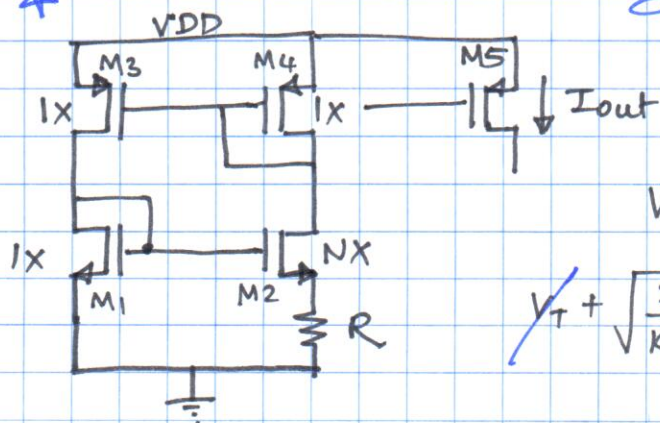
## \* Constant $G_m$ Biasing. $\rightarrow G_m \rightarrow$ PVT independent



$$V_{GS1} = V_{GS2} + IR$$

$$V_T + \sqrt{\frac{2I}{K_n(W/L)_1}} = V_T + \sqrt{\frac{2I}{K_n N(W/L)_1}} + IR$$

$$\Rightarrow I_{out} = I = \frac{2}{K_N \left(\frac{W}{L}\right)_1} \cdot \frac{1}{R^2} \cdot \left(1 - \frac{1}{\sqrt{N}}\right)^2$$

$$g_{m1} = \sqrt{2 \underbrace{\mu_n C_{ox}}_{K_N} \left(\frac{W}{L}\right)_1 I_1}$$

$$= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \times \frac{2}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1} \left(\frac{1}{R^2} \left(1 - \frac{1}{\sqrt{N}}\right)^2\right)}$$


$$= \frac{2}{R} \left(1 - \frac{1}{\sqrt{N}}\right)$$

on-chip or  
off chip

Scaler Ratio

→ can be tuned. digitally

### \* On-Chip Temperature Sensor

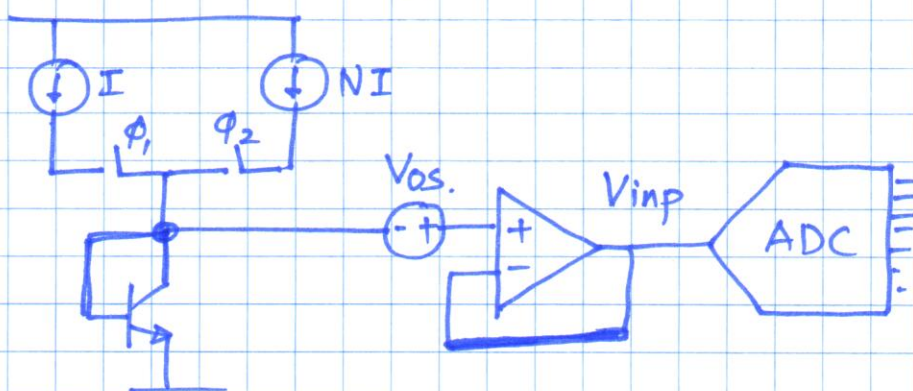

$$\text{In } \phi_1, V_{in} = V_{os} + V_T \ln\left(\frac{I}{I_s}\right)$$

$$\text{In } \phi_2, V_{in} = V_{os} + V_T \ln\left(\frac{NI}{I_s}\right)$$

A2D conversion

& Subtract digitally


Measure  $V_T \ln(N)$  ⇒ Give T in °K

Known Ratios


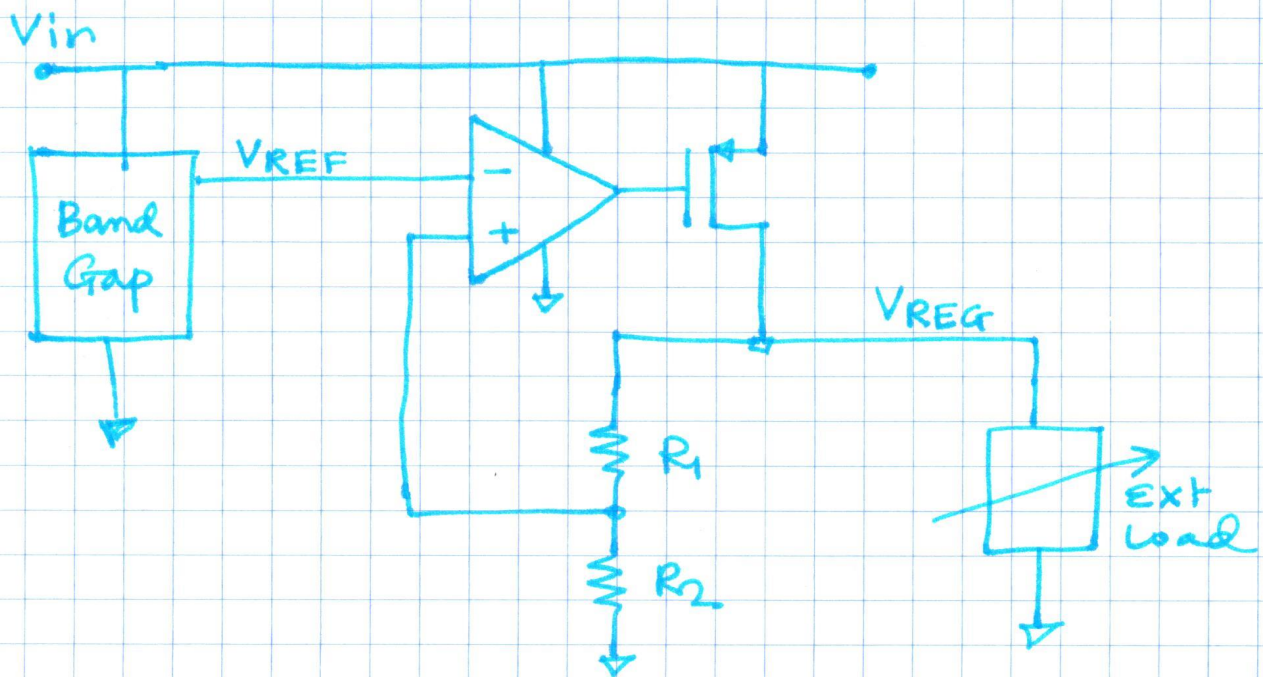
## Voltage Regulator

→ is a constant voltage source independent of load current and input voltage.



- $V_{REF}$  — from Bandgap Reference.  $\sim 1.2V$
- Error Amplifier — OTA
- Feedback Network
- Pass Transistor —  $V_{SG}$  increases as  $I_L$  increases.  
PMOS — large. — should be able to carry desired max load current.

$$V_{REG} = \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$