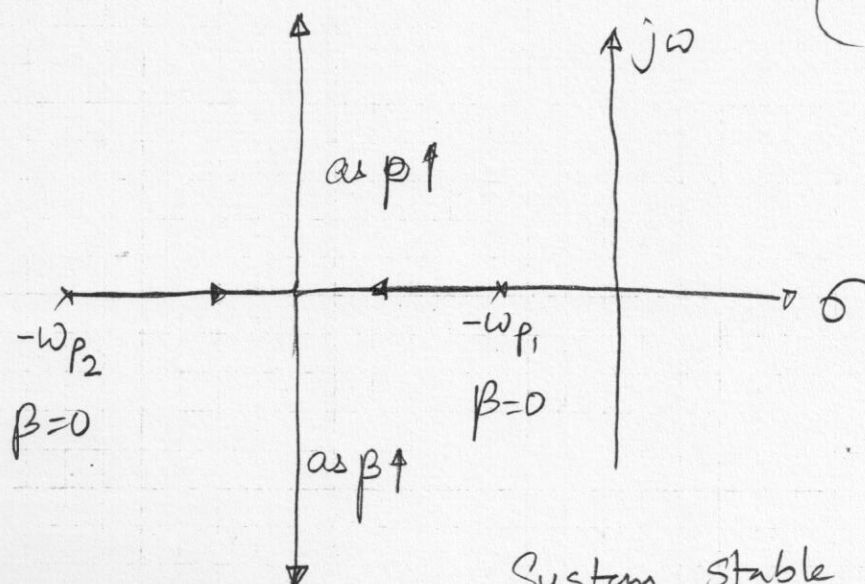


3 SEP 2019

Two pole system

$$A(s) = \frac{1}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$



System stable since both poles  
left half plane.

Note on Phase Margin

PM of  $45^\circ$   $|T(j\omega_u)| = 1$   $\angle T(j\omega_u) = -135^\circ$

Closed loop Gain


$$\frac{Y(s)}{X(s)} = \frac{A(j\omega_u)}{1 + T(j\omega_u)} = \frac{A(j\omega_u)}{1 + 1 \times \exp(-j135^\circ)}$$

$$= \frac{A(j\omega_u)}{0.29 - 0.71j}$$

$$\begin{cases} \angle \beta A(j\omega_u) = -135^\circ \\ |\beta A(j\omega_u)| = 1 \\ \Rightarrow |A(j\omega_u)| = 1/\beta \end{cases}$$

$$\left| \frac{Y(s)}{X(s)} \right| = \frac{1/\beta}{|0.29 - 0.71j|} = \frac{1.3}{\beta}$$




← peaking

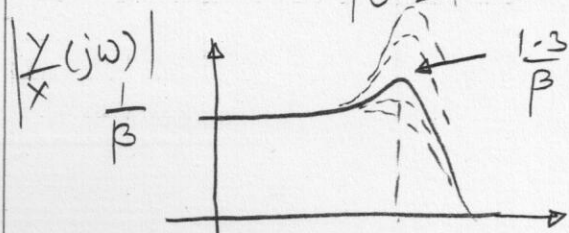

Peaking keeps increasing  
as PM ↓  
Oscillatory behavior.

Closed loop transient response

(Razavi pp. 419)

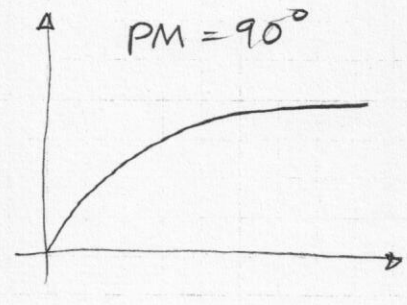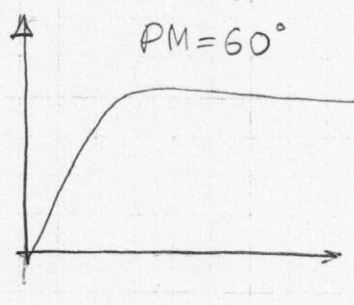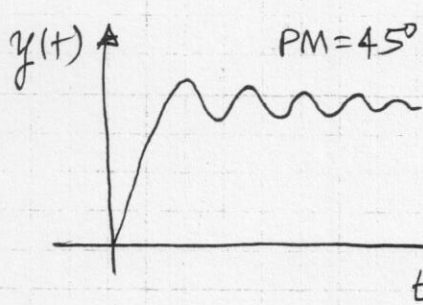



→ Valid only for small signal analysis.

## FREQUENCY COMPENSATION

$|BA(j\omega)| < 1$  way before  $\angle BA(j\omega) = -180^\circ$

How?

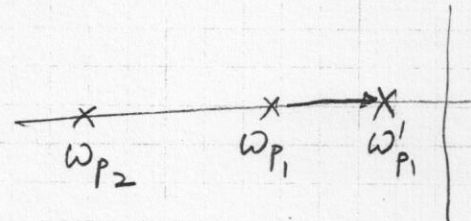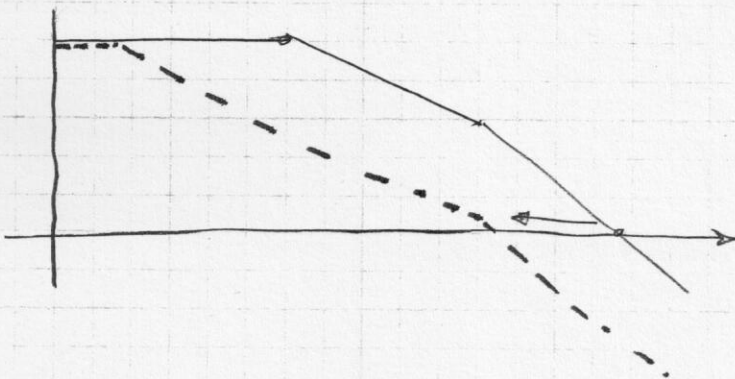- ① Drop gain vs frequency - get gain crossover pulled to low frequency.



→ low frequency gain maintained.

→ Bandwidth reduced a lot.

Example - Add tons of cap at  $\omega_{p1}$  node.

→ Not really good solution.




2. Minimize overall phase shift - push  $P_x$  out.

- Minimize number of poles in signal path
- # of stages limited - low gain / swing

Not great solution either.




Enter freq. compensation

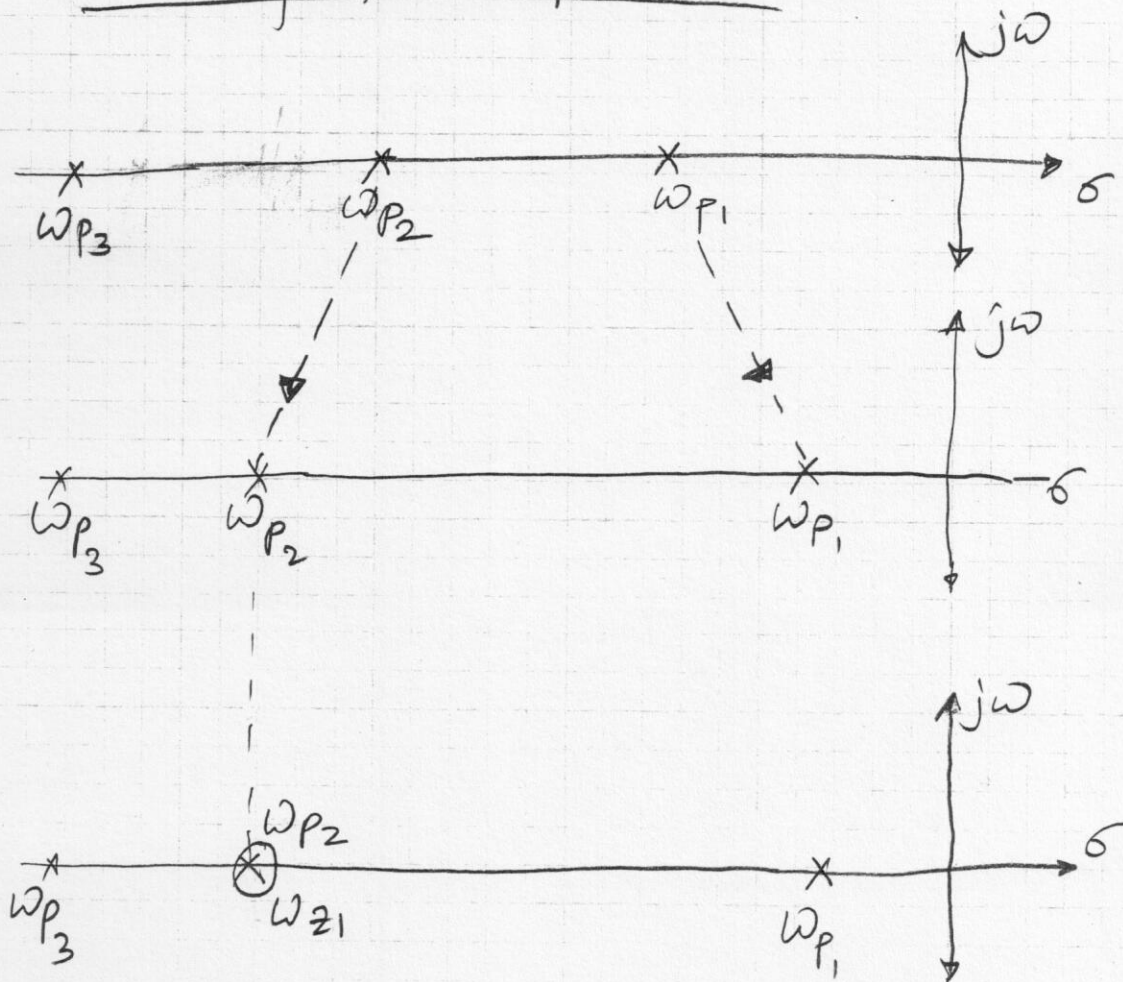

Make sure compensation trick  
holds true over PVT



## Back to Two Stage OTA

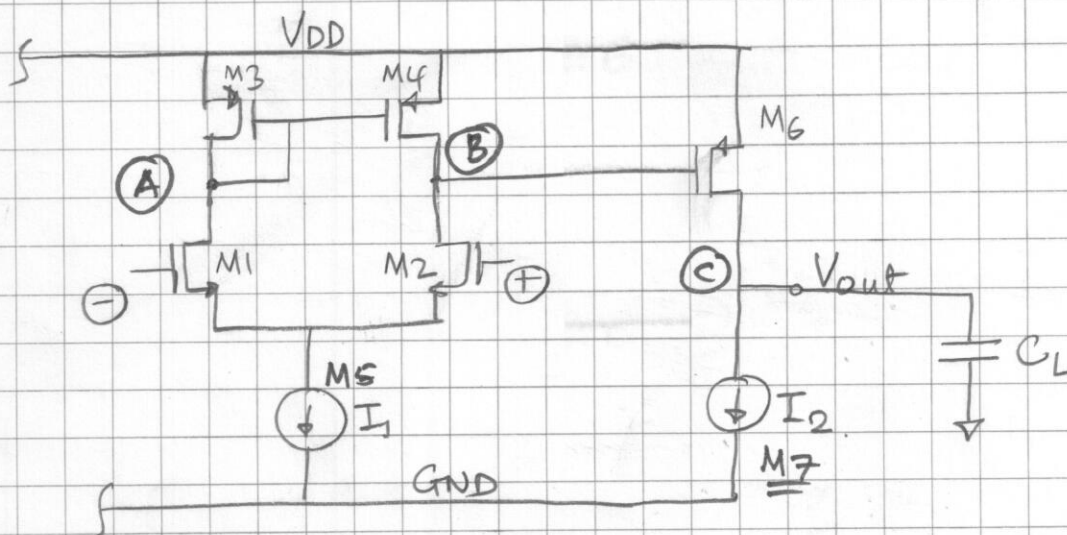

Signal path.  
Each node  $\rightarrow$  contributes pole  $\omega_{p_i} \approx \frac{g_i}{C_i}$


$$g_A = g_{ds1} + g_{m3} + g_{ds3} \approx g_{m3} \leftarrow \text{Low imp. node.}$$

$$g_B = g_{ds2} + g_{ds4}$$

$$g_C = g_{ds6} + g_{ds7}$$

High Impedance Nodes

Consider

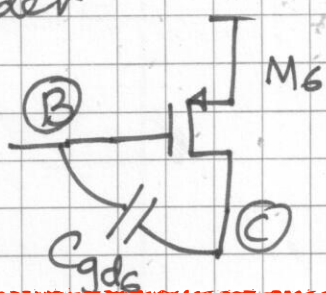

$C_{gd6}$  around inverting stage


$\rightarrow$  RHP zero  $\frac{g_{m6}}{C_{gd6}} \quad z_B$

$$\omega_A = \frac{g_{m3}}{2C_{gs3}}$$


Text

$$\omega_B = \frac{g_{ds2} + g_{ds4}}{C_{gs6}} ; \omega_C = \frac{g_{ds6} + g_{ds7}}{C_L}$$

$\uparrow j\omega$

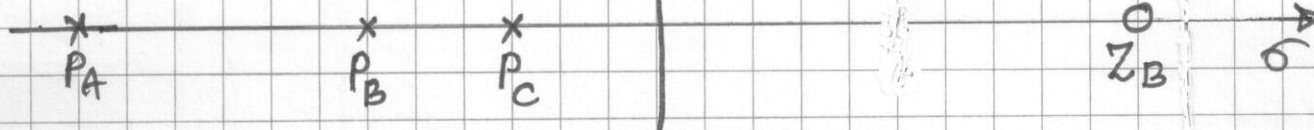

## Miller Compensation — Concept

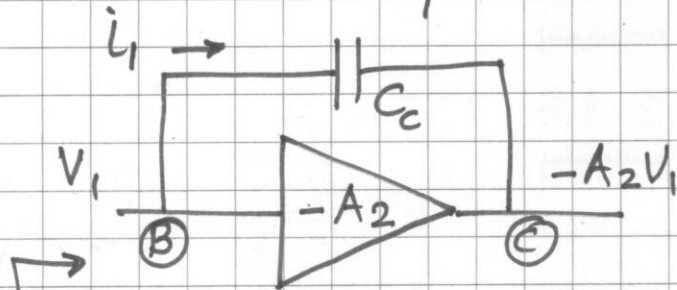


$$Z_{in} = \frac{V_i}{i_1} = \frac{V_i}{[V_i - (-A_2 V_i)] s C_c} = \frac{V_i}{V_i [1 + A_2] C_c s}$$

$$= \frac{1}{(1 + A_2) C_c s}$$

Capacitance multiplied by  $(1 + A_2)$  ← will move  $P_B$  a lot.  
large  $g_m r_o$

## Two Stage OTA

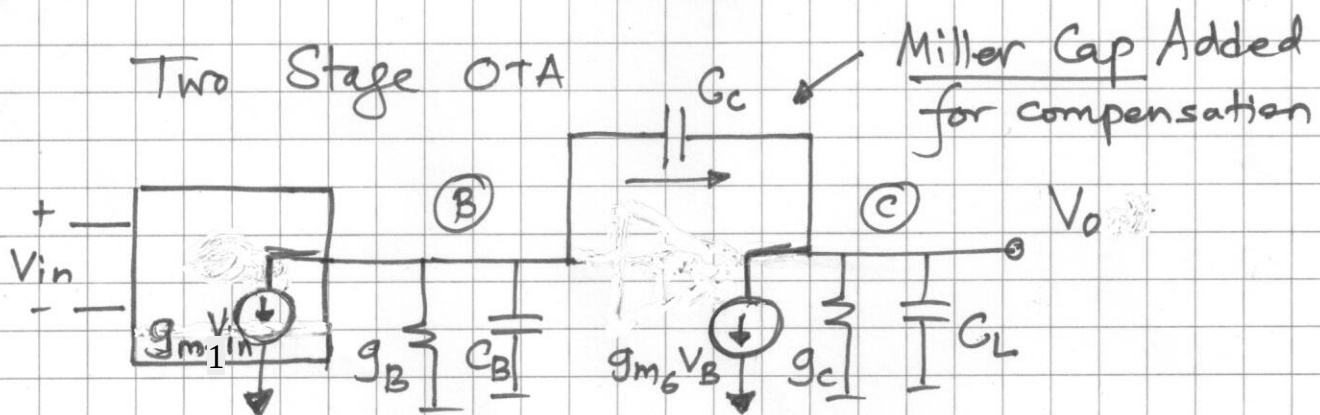

$$g_{m1} V_{in} + (g_B + s C_B) V_B + s C_c (V_B - V_o) = 0 \quad \text{--- (1)}$$

$$s C_c (V_B - V_o) = g_{m6} V_B + (g_c + s C_L) V_o \quad \text{--- (2)}$$

Need to Eliminate  $V_B$

$$\rightarrow V_B = \frac{[g_c + s (C_L + C_c)]}{(s C_c - g_{m6})} V_o \quad \text{--- (3)}$$

Substituting (3) in (1)

$$g_{m1} V_{in} + \left[ \frac{[g_B + s(C_B + C_c)][g_c + s(C_L + C_c)]}{[sC_c - g_{m6}]} - sC_c \right] V_o = 0$$

$$[sC_c - g_{m6}] g_{m1} V_{in} + \left( [g_B + s(C_B + C_c)][g_c + s(C_L + C_c)] - sC_c [sC_c - g_{m6}] \right) V_o = 0$$

Simplify  $\downarrow$

$$g_B g_c + s(C_B + C_c) g_c + s(C_L + C_c) g_B + sC_c g_{m6} + s^2(C_B C_L + C_c C_L + C_B C_c)$$

ignore  $g_c, g_B \ll g_{m6}$

$$(sC_c - g_{m6}) g_{m1} V_{in} + (g_B g_c + sC_c g_{m6} + s^2(C_B C_L + C_c C_L + C_B C_c)) V_o = 0$$

$$\frac{V_o}{V_{in}} = \underbrace{\left( \frac{g_{m1}}{g_B} \right) \left( \frac{g_{m6}}{g_c} \right)}_{\text{DC gain}} \underbrace{\left( 1 - \frac{sC_c}{g_{m6}} + s \frac{C_c}{g_B} \frac{g_{m6}}{g_c} + s^2 \frac{(C_B C_L + C_c C_L + C_B C_c)}{g_B \cdot g_c} \right)}_{\text{RHP zero}}$$

DOMINANT POLE APPROXIMATION.

Consider two poles  $P_D, P_{ND}$  such that

$$P_D \ll P_{ND}$$

Then  $\left( 1 + \frac{s}{P_D} \right) \left( 1 + \frac{s}{P_{ND}} \right) = 1 + \left( \frac{1}{P_D} + \frac{1}{P_{ND}} \right) s + \frac{s^2}{P_D P_{ND}}$

$$= 1 + \frac{s}{P_D} + \frac{s^2}{P_D P_{ND}}$$

compare



DOMINANT POLE  $P_D = \frac{g_B g_c}{C_c g_{m6}} = \frac{g_B / C_c}{(g_{m6} / g_c)}$

2nd stage gain, large #

NON-DOM POLE  $P_{ND} = \frac{g_B \cdot g_c}{(C_B C_L + \underline{C_c C_L} + C_B C_c)} \cdot \frac{C_c g_{m6}}{g_B \cdot g_c}$


$C_B$  small compared to  $C_L, C_c$

$\approx \frac{g_{m6} C_c}{C_L \cdot C_c}$

$\approx \frac{g_{m6}}{C_L} = \boxed{\frac{g_{m6}}{g_c}} \cdot \frac{g_c}{C_L}$

2nd stage gain large #

Zero Pole locations

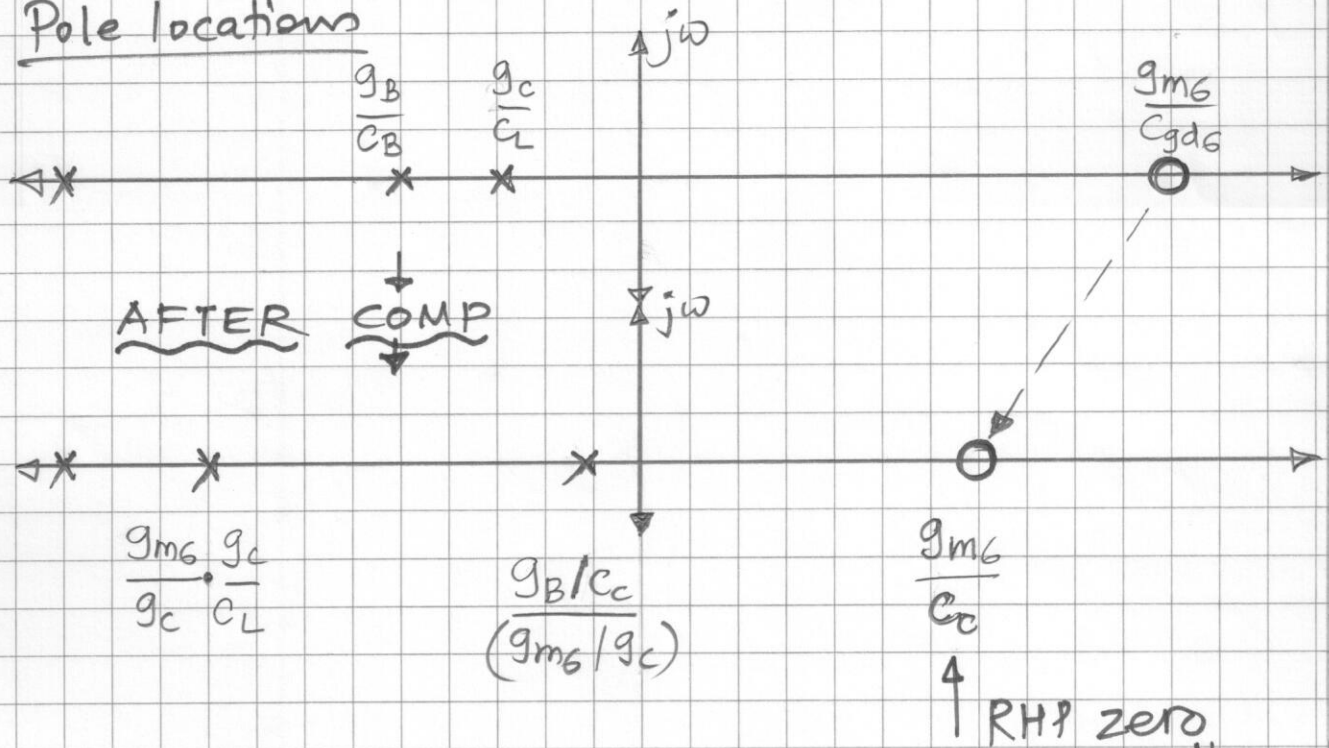

RHP zero — Phase gets worse while gain is lifted up.

$\frac{g_{m6}}{C_c} \leftarrow \text{large}$

Need to Take care of RHP zero!