

EE 618 (ZELE)

CMOS Aanalog VLSI Design : Tutorial-I

Note: Use the following wherever not specified explicitly,
 $V_{DD} = 3V$, $V_{Tn} = 0.7V$ and $V_{Tp} = -0.8V$. Neglect body effect. Assume low frequency small signal model whenever required.

1. For the CS Amplifier in Figure 1 with diode connected load, find the $v_{in,max}$ (in V).
Given $V_{DD} = 1.8V$, $gm_1 = gm_2$, $V_{IN} = V_{OUT} = 0.6V$, $V_{TN} = |V_{TP}| = 0.4V$.

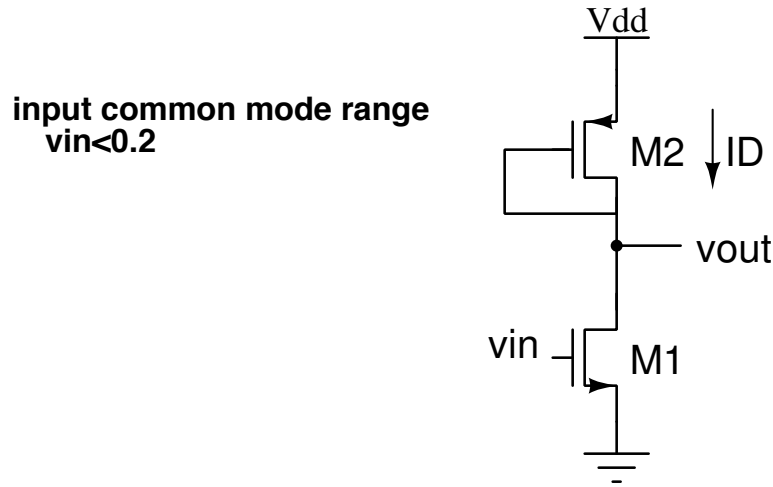


Figure 1

2. Given that M1 and M2 are in saturation, if the voltage at node Y is increased by a small value ΔV , then find the change in the voltage at node X.

 


Figure 2

3. Assuming all the transistors are in a saturation, find a small signal voltage gain for the following circuit:

 


Figure 4

4. Assuming all transistors are in a saturation, find a small signal voltage gain for the following circuits:

