

University of California  
Berkeley

College of Engineering  
Department of Electrical Engineering  
and Computer Science

Robert W. Brodersen  
EECS140


Fall, 2002

Analog Circuit Design

**More  
on Op Amps  
TELESCOPIC and FOLDED CASCODE**

## Telescopic - OP AMP

### Circuit 1 (Poor Bias Strategy)

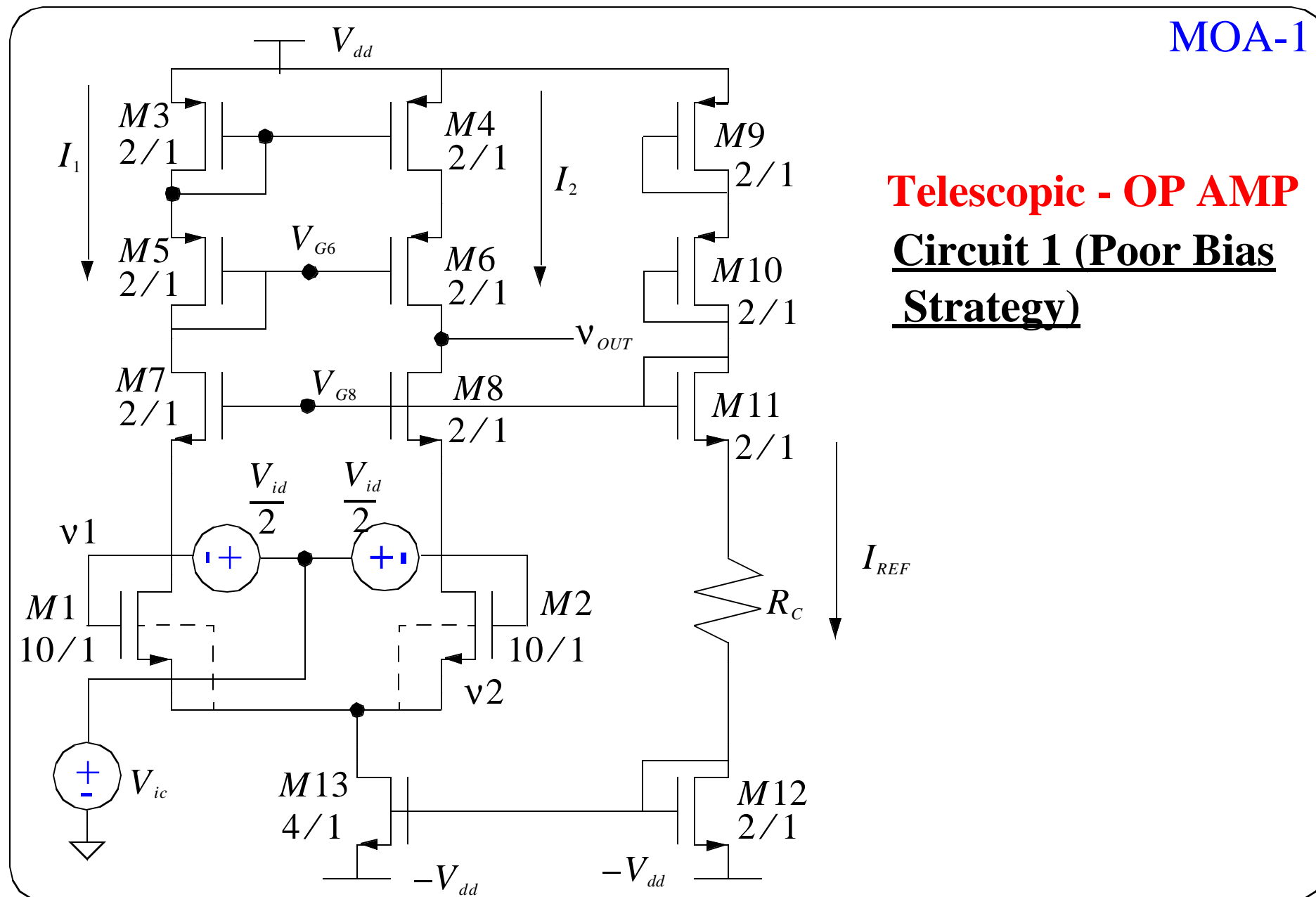

**Circuit 1 :****Telecopic OP AMP with “BAD” Bias of cascode :**

The currents are balanced so that all transistors have,

$$I_{DS} = I_{REF}$$

except for M13 which has,

$$I_{DS13} = 2 \cdot I_{REF}$$

Since,

$$I_1 = I_2 = I_{REF}$$

then,

$$V_{GS3} = V_{GS4} = V_{GS9} \quad (\text{all W/L's are equal also})$$

This also implies that,

$$V_{DS4} = V_{DS3}$$

similarly,

$$V_{DS5} = V_{DS6}$$

So if the input has,

$$V_{id} = 0$$

## MOA-3

then,

$$V_{OUT} = V_{DD} - 2 \cdot V_{To} - 2 \cdot V_{DSAT} = V_{G6} \quad (\text{if } \gamma = 0)$$

The gate of M8 is also at,

$$V_{DD} - 2 \cdot V_{To} - 2 \cdot V_{DSAT}$$

due to its connection to M11, so,

$$V_{OUT} = V_{G6} = V_{G8}$$

The swing in the positive direction will be,

$$V_{OUT,MAX}^+ = V_{G6} + V_T$$

But since,

$$V_{OUT} = V_{G6}$$

this means the swing is only  $1 V_T$  in the positive direction. In the negative direction,

$$V_{OUT,MIN}^- = V_{G8} - V_T$$

but since,

$$V_{OUT} = V_{G8}$$

the swing is only  $V_T$  again.

## MOA-4

Thus the total swing is only  $2V_T$  ... not too good.

In the positive direction we could use a high swing configuration as was described for the cascoded current source.

On the low side we can use a better circuit.

### Circuit 2 :

Telescopic with a cascode bias that gives a better swing in the negative direction.

Maximum voltage in the positive direction is given by M6 going linear when,


$$V_{OUT,MAX}^+ > V_{DD} - V_{GS3} - V_{DSAT6}$$

Negative swing is limited by M8 going linear,

$$V_{OUT,MIN}^- = V_A - V_{T8}$$

Set  $V_A$  so that M1 & M2 are at the edge of saturation
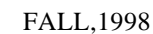
## Telescopic - OP AMP Circuit 2 (Better Bias)




# Telescopic Op Amp

MOA-6

Max swing positive :

$$V_{DD} - 2 \cdot \Delta V - V_T$$

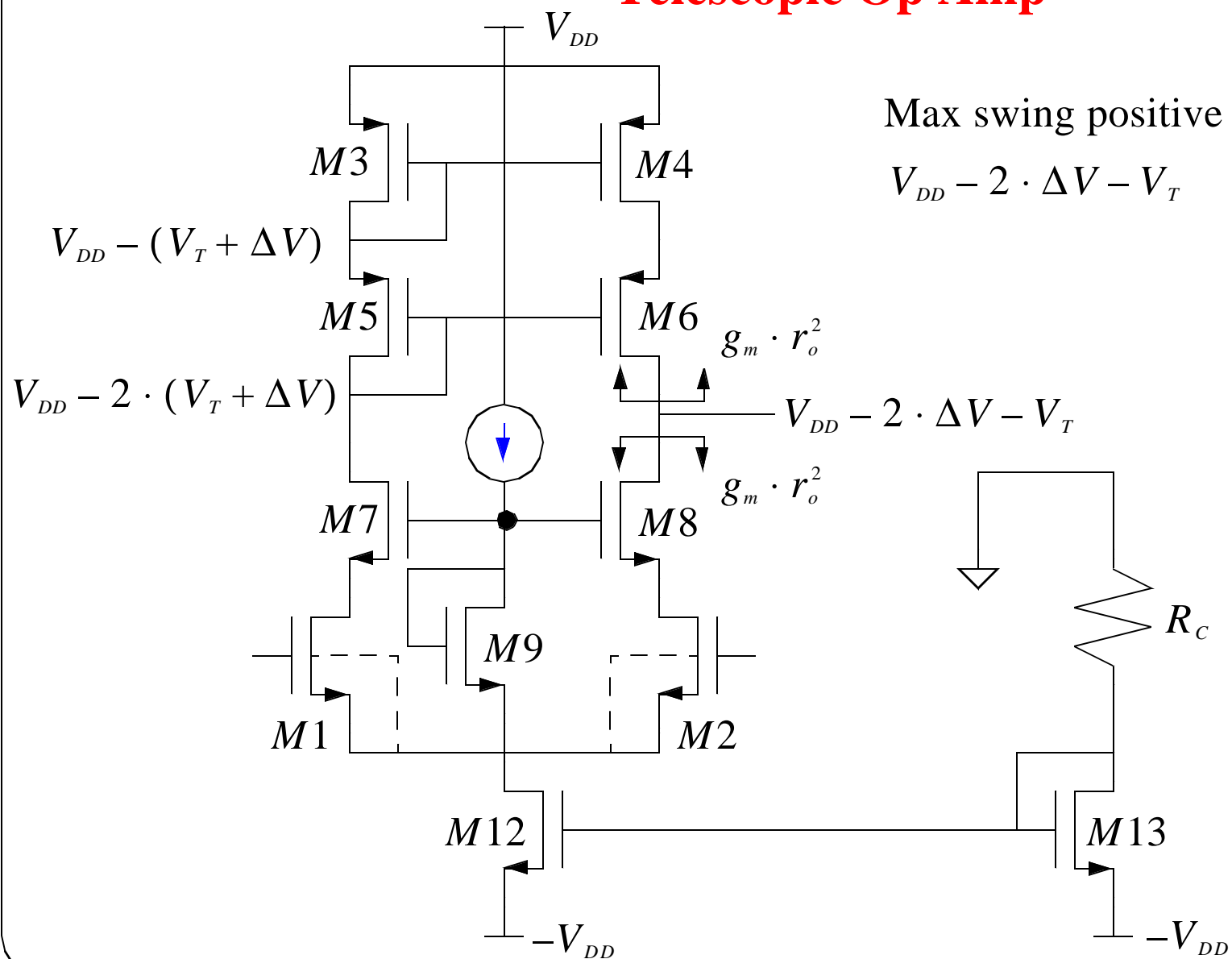

**Telescopic Op Amp (Cont.)**

MOA-7

$$V_A = V_S + V_{DSAT9} + V_{T9}$$

$$V_{DS2} = V_{DSAT2} \quad \text{for setting M2 at EOS}$$

$$\begin{aligned} V_{DS2} &= V_A - V_{T8} - V_{DSAT8} - V_S \\ &= V_S + V_{DSAT9} + V_{T9} - V_{T8} - V_{DSAT8} - V_S \end{aligned}$$

$$V_{DS2} = V_{DSAT9} - V_{DSAT8} = V_{DSAT2} \quad \text{for EOS}$$

$$V_{DSAT9} = V_{DSAT2} + V_{DSAT8}$$

$$\left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_7 \quad \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$



## MOA-8

This means that,

$$V_A = V_S + V_{DSAT2} + V_{T8} + V_{DSAT8}$$

Since this will set,

$$V_{DS2} = V_{DSAT2}$$

To calculate the  $(W/L)_9$  and  $I_B$  to do this we set,

$$V_{DS,9} = V_A - V_S = V_{DSAT2} + V_{T8} + V_{DSAT8}$$

since,

$$V_{DS,9} = V_{T9} + V_{DSAT9}$$

$$V_{DSAT9} = (V_{T8} - V_{T9}) + V_{DSAT2} + V_{DSAT8}$$

If we say,

$$V_{T8} \approx V_{T9}$$

then

$$\left( \frac{2 \cdot I_B}{k'_n \cdot \left( \frac{W}{L} \right)_9} \right)^{1/2} = \left( \frac{2 \cdot I_{DS2}}{k'_n} \right)^{1/2} \cdot \left( \frac{1}{\left( \frac{W}{L} \right)_8^{1/2}} + \frac{1}{\left( \frac{W}{L} \right)_2^{1/2}} \right)^2$$

so,

$$\left(\frac{W}{L}\right)_9 = \frac{I_B}{I_S} \cdot \left[ \left(\frac{W}{L}\right)_8^{-1/2} + \left(\frac{W}{L}\right)_2^{-1/2} \right]^2$$

if,

$$\left(\frac{W}{L}\right)_2 = 10 \quad \left(\frac{W}{L}\right)_8 = 2 \quad I_B = 0.79\mu A \quad I_S = 10.5\mu A$$

then,

$$\left(\frac{W}{L}\right)_9 \approx \frac{1}{15}$$

Gain and  $R_{out}$

$$GM = g_{m1} \quad (\text{cas coding has no effect on } g_m)$$

$$R_{OUT} = [(g_{m6} \cdot r_{o4}) \cdot r_{o6}] \parallel [(g_{m8} \cdot r_{o2}) \cdot r_{o8}]$$

$$A_{vd} = g_{m1} \cdot \left[ \frac{g_{m6} \cdot g_{m8} \cdot (r_{o4} \cdot r_{o6} \cdot r_{o2} \cdot r_{o8})}{g_{m6} \cdot r_{o4} \cdot r_{o6} + g_{m8} \cdot r_{o2} \cdot r_{o8}} \right]$$

## MOA-10

$$g_{m6} \cdot r_{o4} \cdot r_{o6} = \left( \frac{2 \cdot I_{DS}}{V_{DSAT6}} \right) \cdot \left( \frac{1}{\lambda_p \cdot I_{DS}} \right) \cdot \left( \frac{1}{\lambda_p \cdot I_{DS}} \right)$$

$$A_{vd} = \left( \frac{2 \cdot I_{DS}}{V_{DSAT1}} \right) \cdot \frac{2}{I_{DS}} \cdot \left( \frac{1}{V_{DSAT6} \cdot \lambda_p^2} \parallel \frac{1}{V_{DSAT8} \cdot \lambda_n^2} \right)$$

$$= \frac{4}{V_{DSAT1}} \cdot \left( \frac{1}{V_{DSAT6} \cdot \lambda_p^2 + V_{DSAT8} \cdot \lambda_n^2} \right)$$

To see the current dependence let,


$$g_m = g_{m1} = g_{m6}$$


and,

$$r_o = r_{o4} = r_{o6} = r_{o2} = r_{o8}$$

$$A_{vd} \approx g_m^2 \cdot r_o^2 \sim \frac{I_{DS}}{I_{DS}^2} \sim \frac{1}{I_{DS}}$$

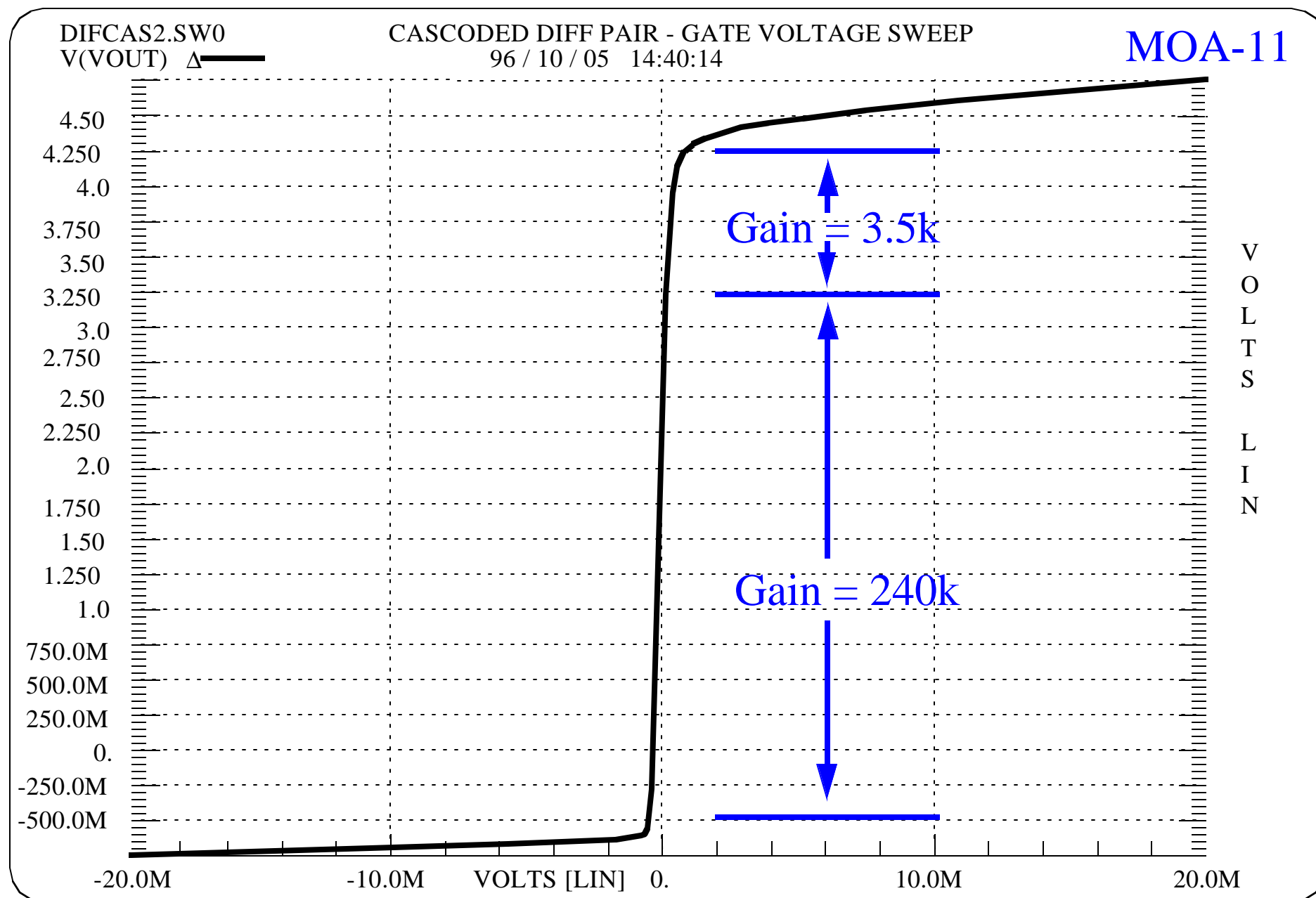Gain keeps increasing as we decrease the current.



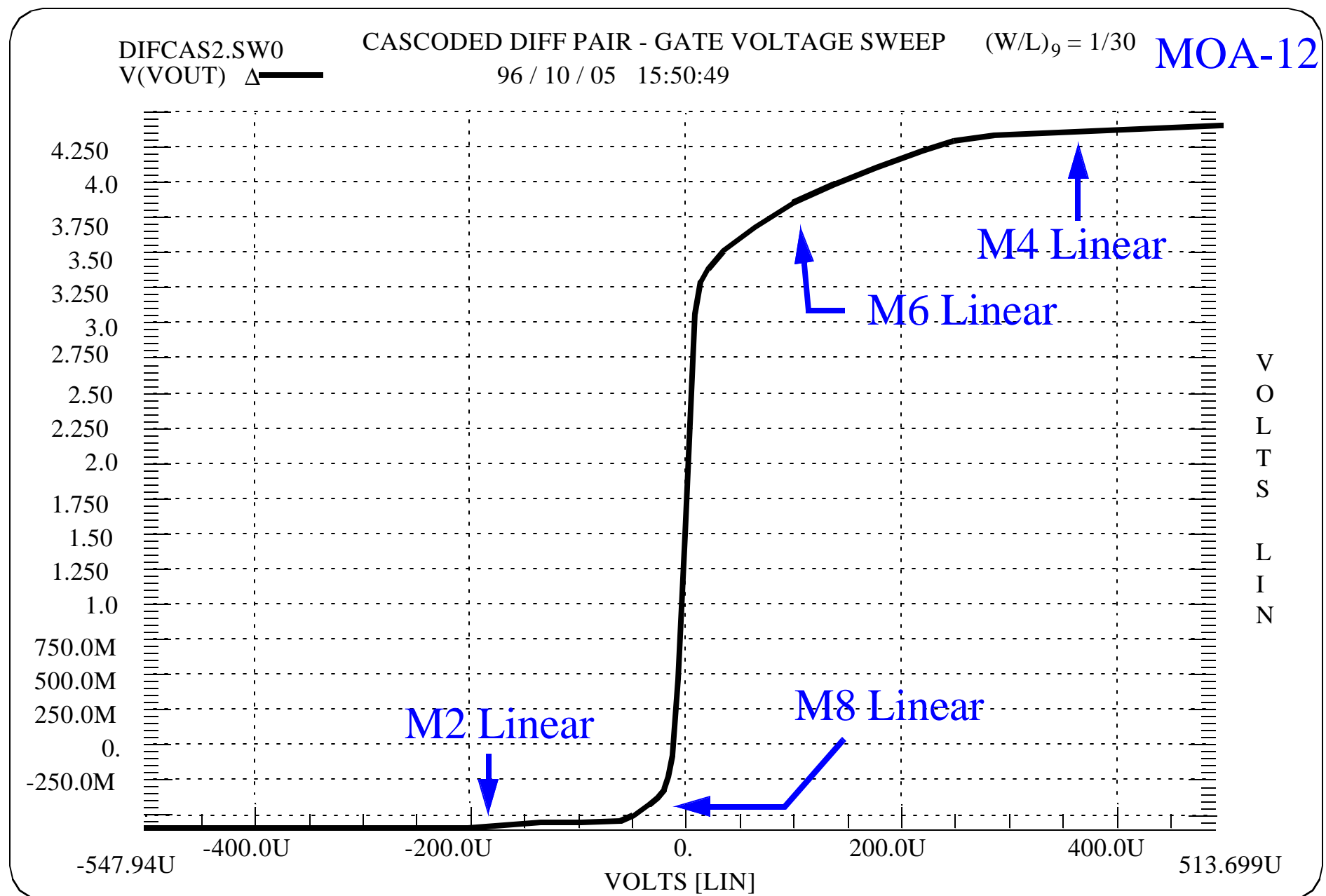

## MOA-13

```

*****
diff pair - gate voltage sweep
*****
* reading file: /bobtools/commercial/hspice/hspice.ini
*
.model nch nmos level = 1 tox = 170 vto = 0.7 kp = 90.0e-6 lambda = 0.01
+ gamma = 0.5 phi = 0.6 capop = 0 cgso=5.e-10 cgdo=5.e-10 cgbo=4.e-10 cj=1e-4
.model pch pmos level = 1 tox = 170 vto = -0.7 kp = 30.0e-6 lambda = 0.01
+ gamma = 0.5 phi = 0.6 capop = 0 cgso=3.e-11 cgdo=3.e-11 cgbo=4.e-10 cj=6e-4

.option nopage post=2 nomod

*name drain gate source bulk model
m1 d1 vi1 vs vs nch l=1u w=10u
m2 d2 vi2 vs vs nch l=1u w=10u
m3 d3 d3 vdd vdd pch l=1u w=2u
m4 d4 d3 vdd vdd pch l=1u w=2u
m5 d5 d5 d3 vdd pch l=1u w=2u
m6 vout d5 d4 vdd pch l=1u w=2u
m7 d5 d9 d1 vdd- nch l=1u w=2u
m8 vout d9 d2 vdd- nch l=30u w=2u
m12 d12 d12 vdd- vdd- nch l=1u w=2u
m13 vs d12 vdd- vdd- nch l=1u w=2u

rref 0 d12 180k
r9 d9 vdd 5x

vic vic 0 0
vid1 vi1 vic 0.0
evld2 vic vi2 vi1 vic 1
vdd vdd 0 5.0
vdd- vdd- 0 -5.0

*other half of the vid input


.dc vid1 -.02 .02 .00001
* sweep the input voltage
*.dc vid1 -5 5 .1
*.print dc v(out)
*.print dc i(m1)
* i is the ids of m1
* von=1v9 vdsat=1x9 gds=1x8
* plots gm=1x7 gmbs=1x9 gds=1x8
* initial operating point
*.print dc lv9(m1) lv10(m1) lx7(m1)
*.op
.tf v(vout,0) vid1
* makes it do the power calculation
*.measure tot_power avg power


.end

```

**Folded Cascode****Circuit 3 :**

MOA-14

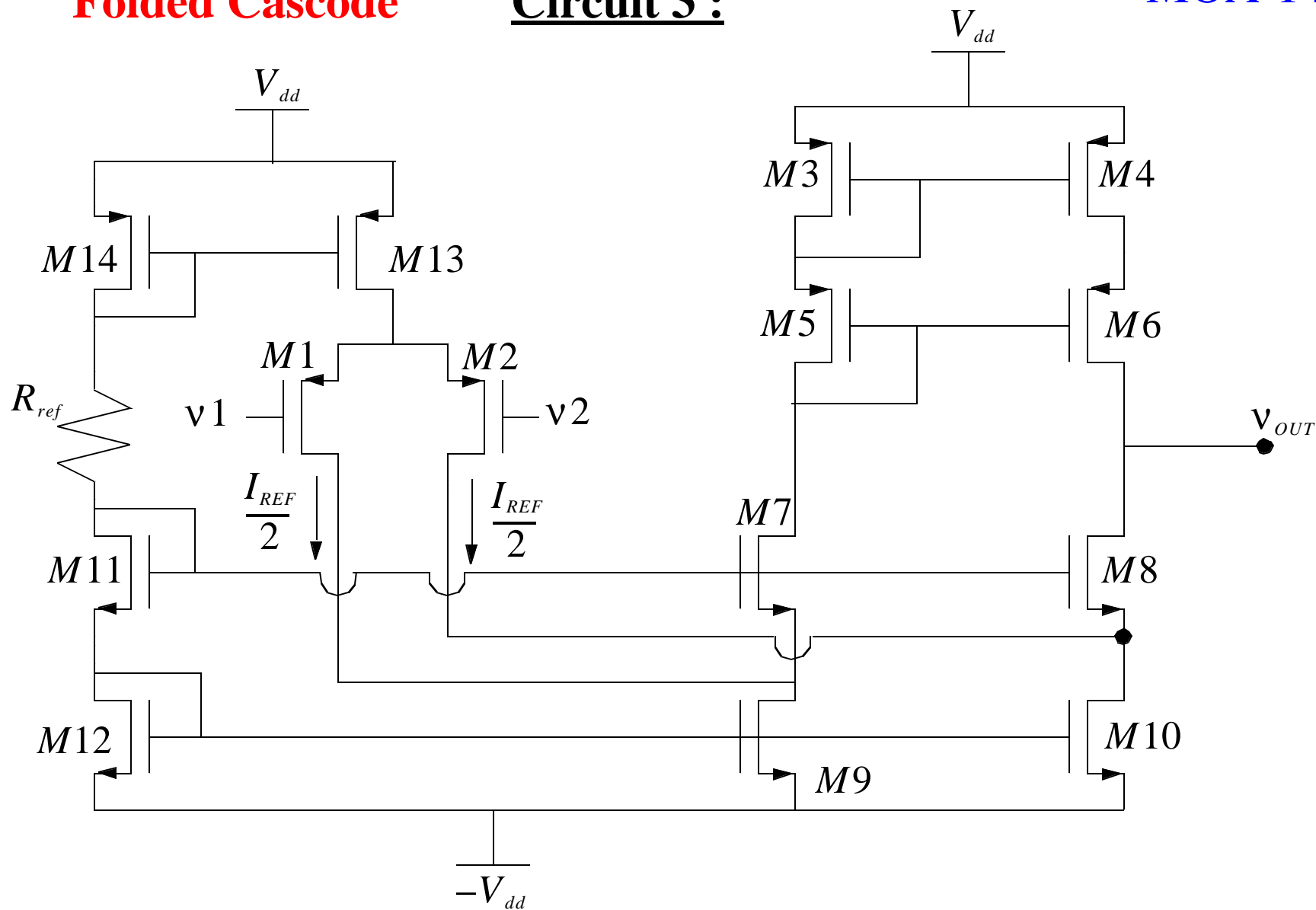

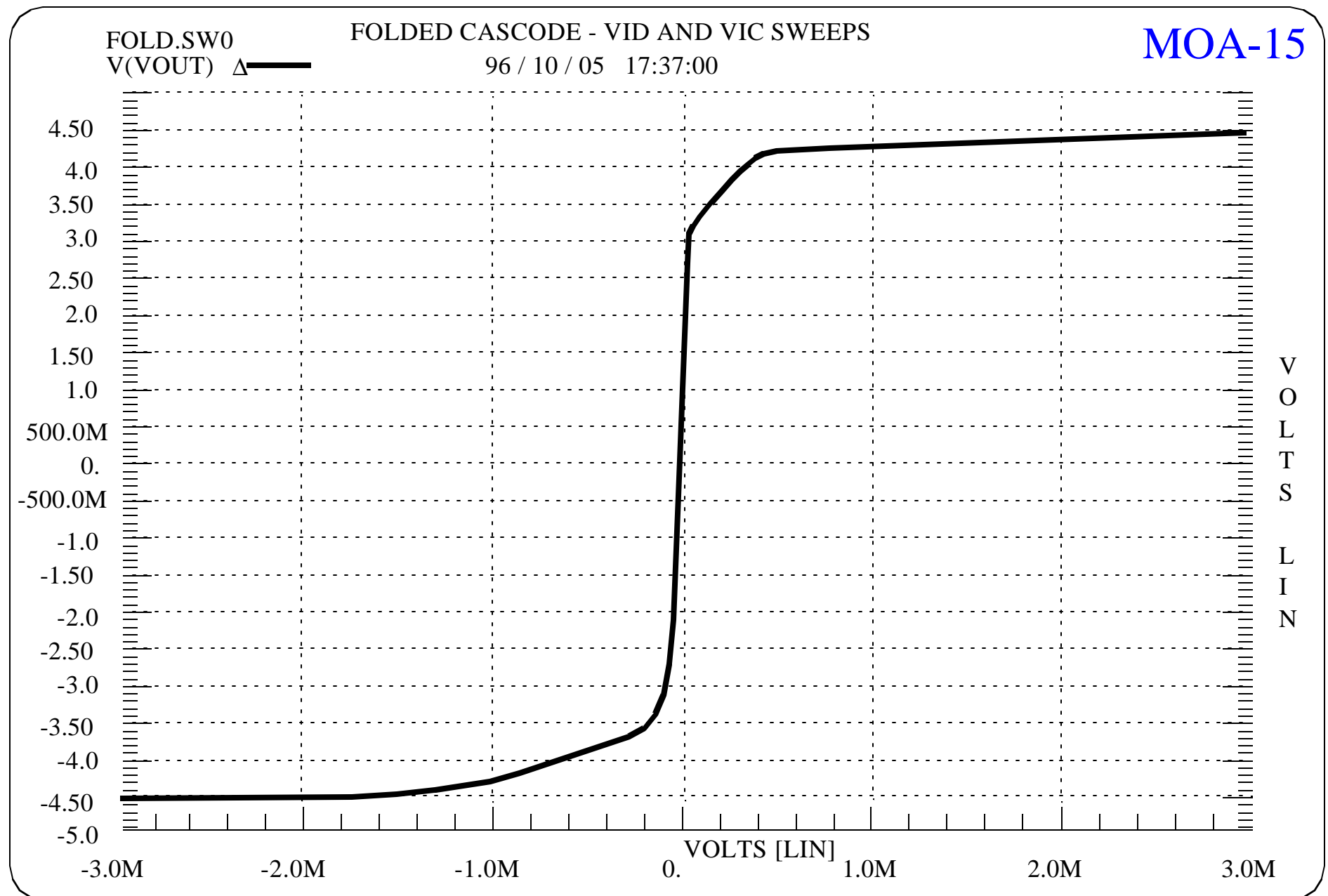



## MOA-16

```

*****
folded cascode - vid and vic sweeps
*****
* reading file: /bobtools/commercial/hspice/hspice.ini
*
.model nch nmos level = 1 tox = 170 vto = 0.7 kp = 90.0e-6 lambda = 0.01
+ gamma = 0.5 phi = 0.6 capop = 0 cgso=5.e-10 cgdo=5.e-10 cgbo=4.e-10 cj=1e-4

.model pch pmos level = 1 tox = 170 vto = -0.7 kp = 30.0e-6 lambda = 0.01
+ gamma = 0.5 phi = 0.6 capop = 0 cgso=3.e-11 cgdo=3.e-11 cgbo=4.e-10 cj=6e-4

.option nopage post=2 nomod

*name drain gate source bulk model
m1 d1 v1 vs vs pch l=1u w=10u
m2 d2 v12 vs vs pch l=1u w=10u
m3 d3 d3 vdd vdd pch l=1u w=2u
m4 d4 d3 vdd vdd pch l=1u w=2u
m5 d5 d5 d3 vdd pch l=1u w=2u
m6 vout d5 d4 vdd pch l=1u w=2u
m7 d5 d11 d1 vdd- nch l=1u w=2u
m8 vout d11 d2 vdd- nch l=1u w=2u
m9 d1 d12 vdd- vdd- nch l=1u w=2u
m10 d2 d12 vdd- vdd- nch l=1u w=2u
m11 d11 d11 d12 vdd- nch l=1u w=2u
m12 d12 d12 vdd- vdd- nch l=1u w=2u
m13 vs d14 vdd vdd pch l=1u w=2u
m14 d14 d14 vdd vdd pch l=1u w=2u
rref d11 d14 270k

vic vic 0 0
vid1 v1 vic 0.0
ev1d2 vic v12 v1 vic 1
vdd vdd 0 5.0
vdd- vdd- 0 -5.0

*other half of the vid input

.de vid1 -20m 20m .01m
*.dc vid1 -.2 .2 10m
*.print dc v(out)
*.print dc i(m1)
*
*.print dc 1v9(m1) 1v10(m1) 1x7(m1)
*.op
*.tf v(vout,0) vid1
*.measure tot_power avg power
*
.end


```

\*sweep the input voltage  
\*sweep the input voltage  
\* i is the ids of m1  
\* von=1v9 vdsat=1x9 gds=1x8  
\* plots gm=1x7 gmbs=1x9 gds=1x8  
\*initial operating point  
\*makes it do the power calculation

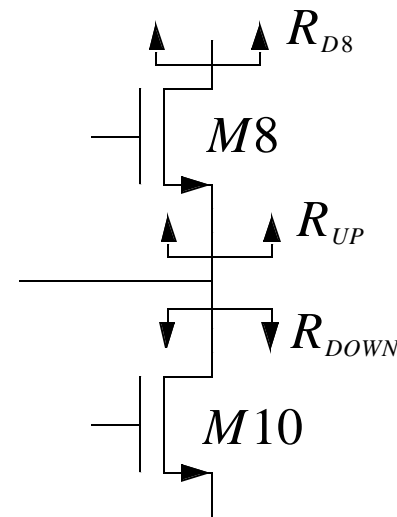**Folded Cascode (Cont.)****MOA-17**

Upper and lower cascodes could be biased for high swing thus max swing could be within  $2V_{DSAT}$  of each rail.

$$GM = gm \cdot \frac{R_{DOWN}}{R_{UP} + R_{DOWN}}$$



There is some current splitting at the point of the folding. However when calculating GM the output (drain of M8) is grounded so  $R_{UP}$  is about  $1/g_m$  with  $R_{DOWN}$  being  $r_o$ .

**Folded Cascode (Cont.)****MOA-18**


There is a loss in  $R_{out}$  as well since M10 must sink DC current from both M2 and M8, thus reducing its  $r_o$

|           | <i>CASCODE</i>  | <i>FOLDED CASCODE</i> |
|-----------|-----------------|-----------------------|
| $A_v$     | 336K            | 125K                  |
| $R_{OUT}$ | 2,446K $\Omega$ | 1,486K $\Omega$       |

same currents,  
same device size  
from examples

# High Swing Folded Cascode


MOA-19

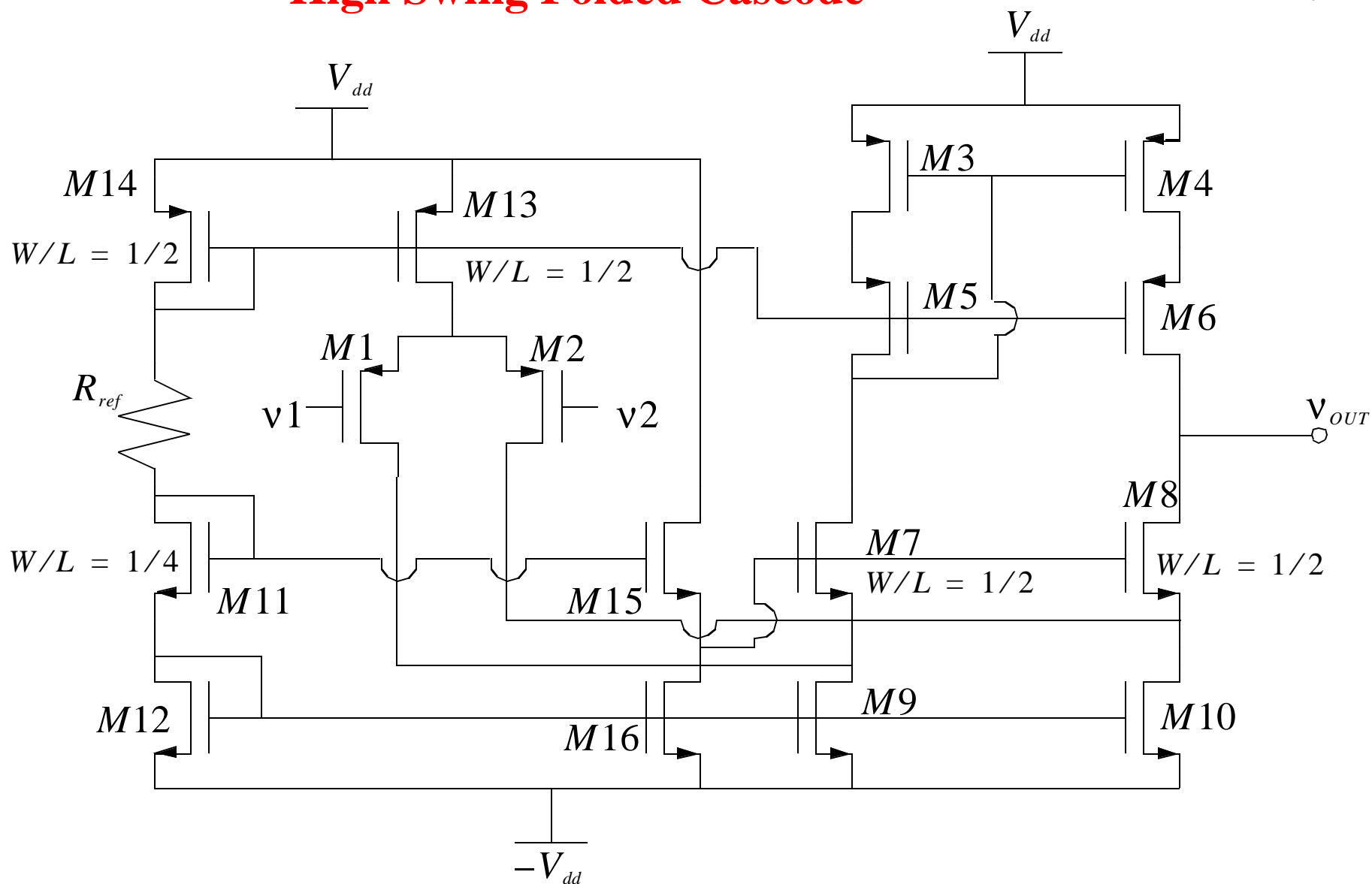

## MOA-20



MOA-21

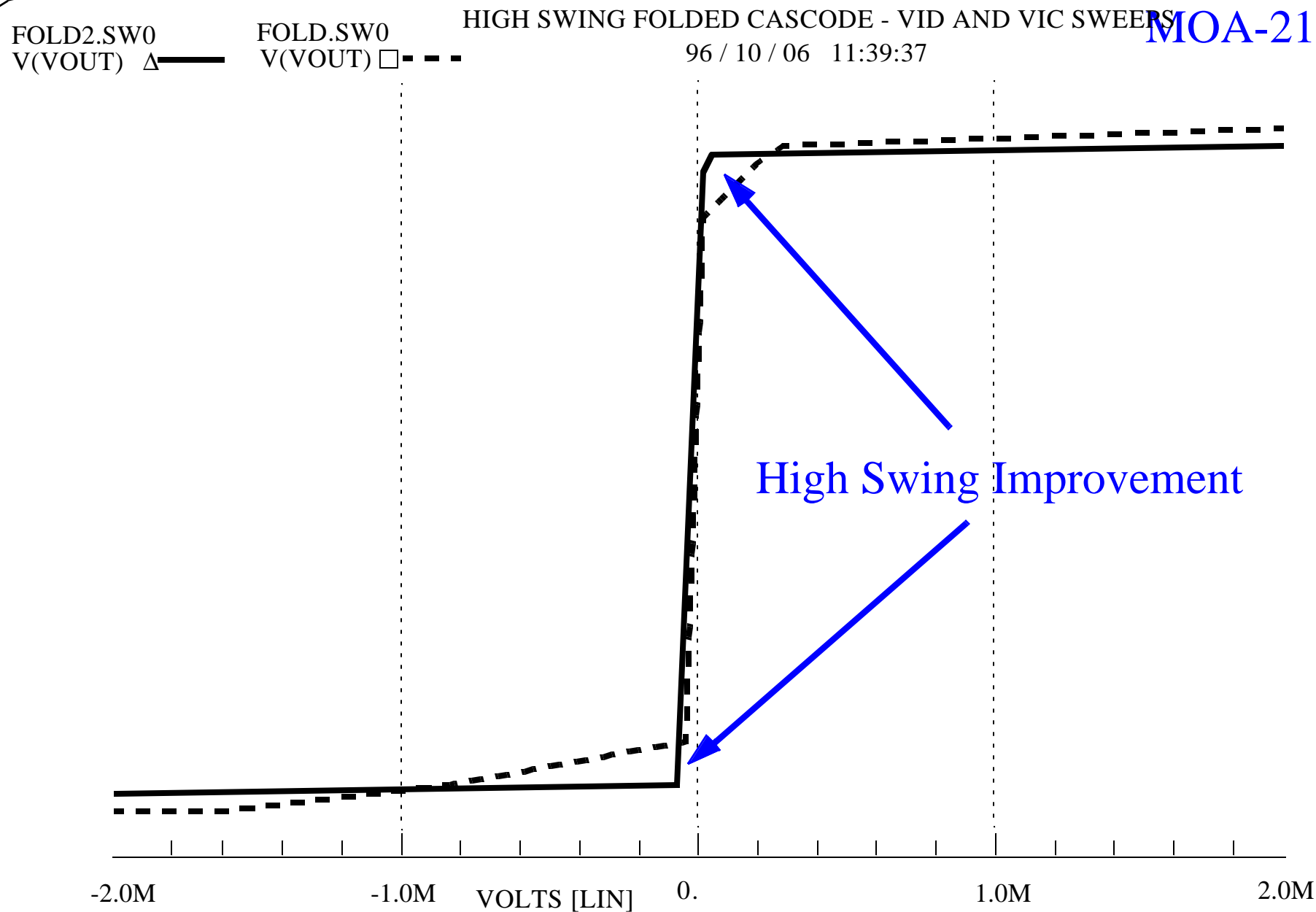

### Circuit 4 :

M15-M16 perform level shift to bias M9 and M10 at the edge of linear.

M7 and M8 have  $1/2$  sized W/L because the current is  $I_{ref}/2$ .

The connection to M5 from M14 sets the M3 at the edge of linear operation.

The W/L's are 1 unless otherwise shown. This is smaller than you would want to use, but this was done to show the ratioing that is required to place the output in high swing.

The Gain and Rout calculations are the same as for circuit 3 and are carried out as described by DP-21 to DP-23.

## High Swing Folded Cascode (Cont.)

MOA-23

$$R_{O,UP} = \frac{r_{o8} + R_D}{1 + (1 + \chi) \cdot r_{o8} \cdot g_{m8}}$$

$$R_D \rightarrow 0$$

$$R_{O,UP} = \frac{1}{\frac{1}{r_{o8}} + (1 + \chi) \cdot g_{m8}} \approx \frac{1}{(1 + \chi) \cdot g_{m8}}$$

$$R_D \approx g_m \cdot r_o^2 \quad \chi = 0$$

$$R_{O,UP} \approx \frac{g_{m6} \cdot r_{o4} \cdot r_{o6}}{r_{o8} \cdot g_{m8}} \approx r_o$$

$$R_{O,UP} = \frac{r_{o8} + g_{m6} \cdot r_{o4} \cdot r_{o6}}{1 + (1 + \chi) \cdot r_{o8} \cdot g_{m8}}$$

$$R_{OUT,S8} \approx \frac{r_o}{3}$$