
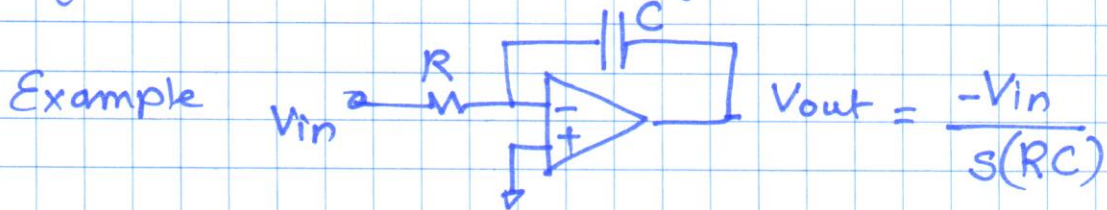


23 OCT 2019

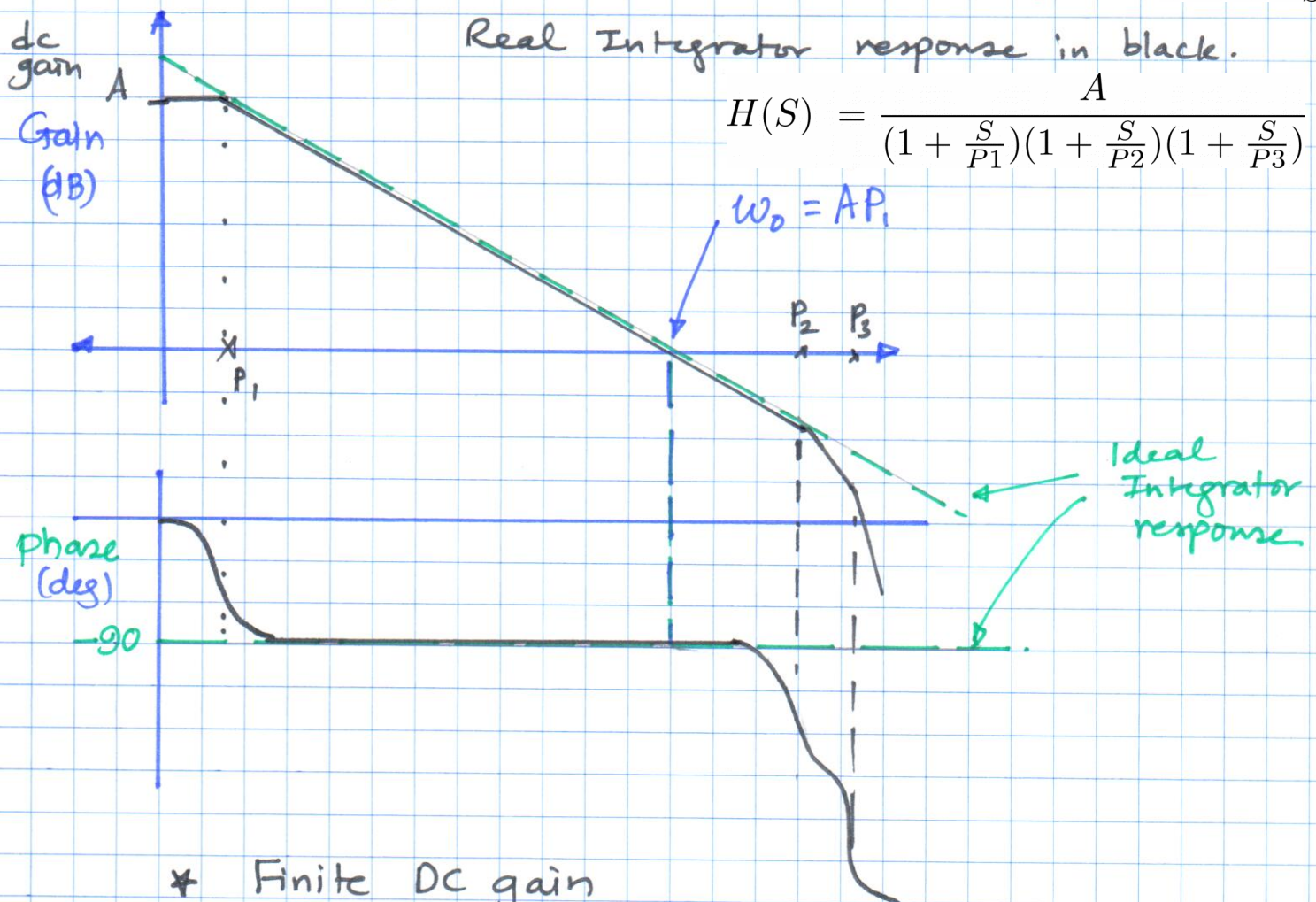\* Key Element in filter design (ladder)  $\rightarrow$  Integrator




Ideal Integrator Response shown in green.  $H(s) = \frac{\omega_0}{s}$



\* Finite DC gain

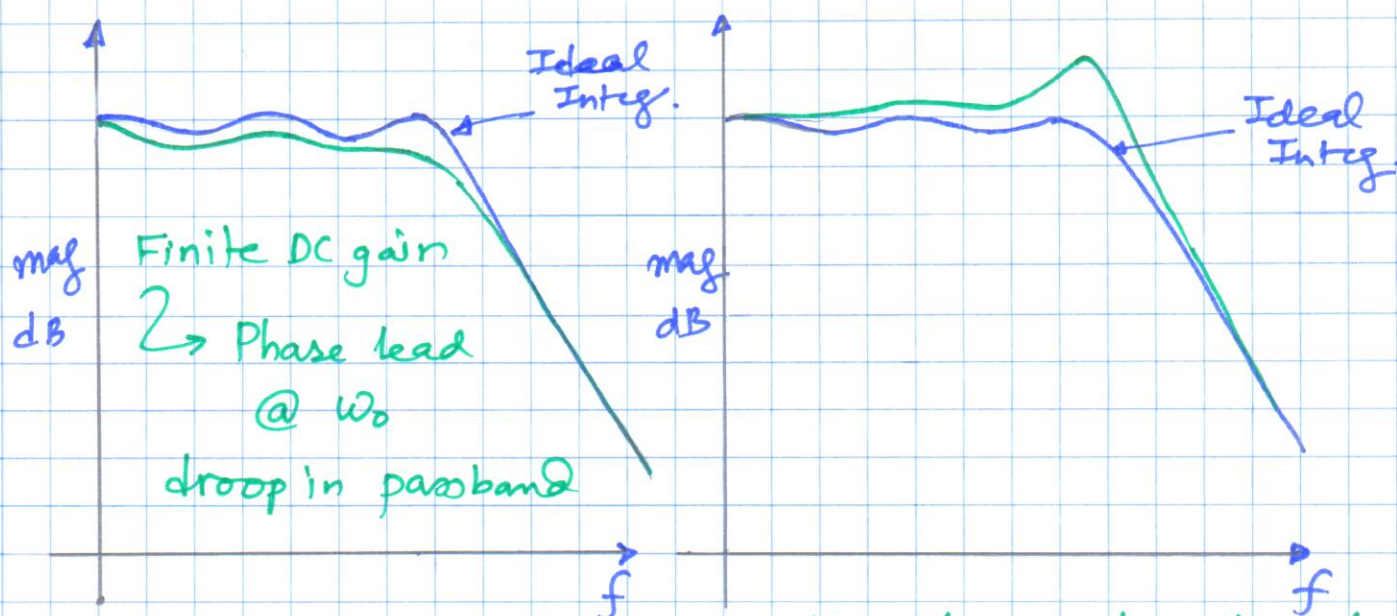\* Phase shift @ unity gain frequency due to Non-dominant poles  $P_2, P_3$  etc.



Non-dom poles close to integrator U.G.F  $\omega_0$ .

$\rightarrow$  phase lag @  $\omega_0$   
 $\rightarrow$  peaking - could be oscillatory.  $\rightarrow$  careful.


## Integrator Quality factor

$$\text{Ideal integrator} = \frac{K}{s} = \frac{1}{j\omega RC}$$

$$\text{Non Ideal Integrator} = \frac{1}{(\text{Real}) + j(\text{Imag})}$$

$$Q_{\text{integrator}}(\omega) = \frac{\text{Imaginary}}{\text{Real.}} \rightarrow \omega = 0 \quad Q = \infty \quad @ \omega_0$$


## Band pass filter example

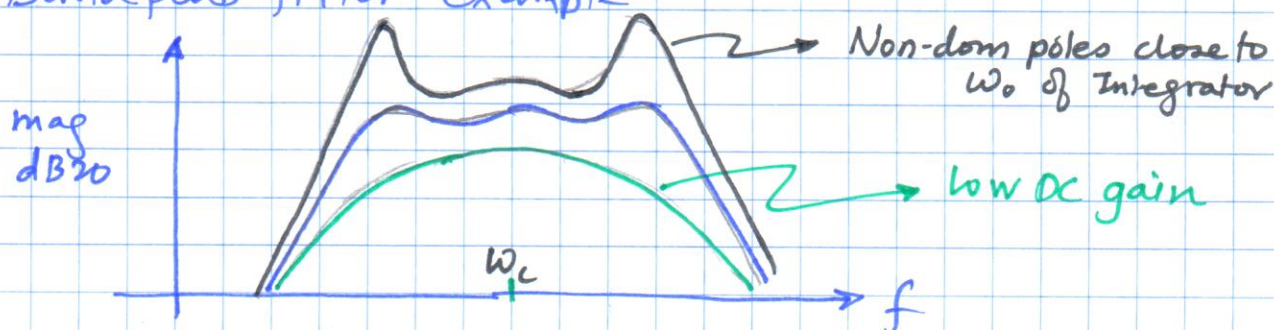



## Gm-C Filters

Gm - transconductance

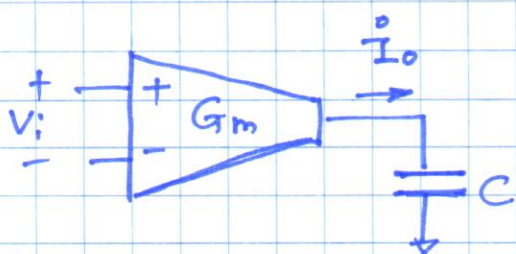


$$I_o = G_m V_i$$


$$V_o = \frac{I_o}{sC} = \frac{G_m V_i}{sC}$$

$$\frac{V_o}{V_i} = \frac{\omega_o}{\omega} \rightarrow \left( \frac{G_m}{C} \right)$$

Multi-input integrator/summer

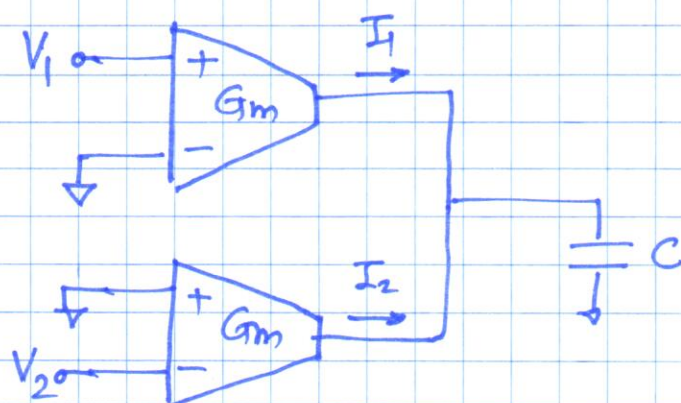

$$V_o = \frac{G_m}{sC} (V_1 - V_2)$$

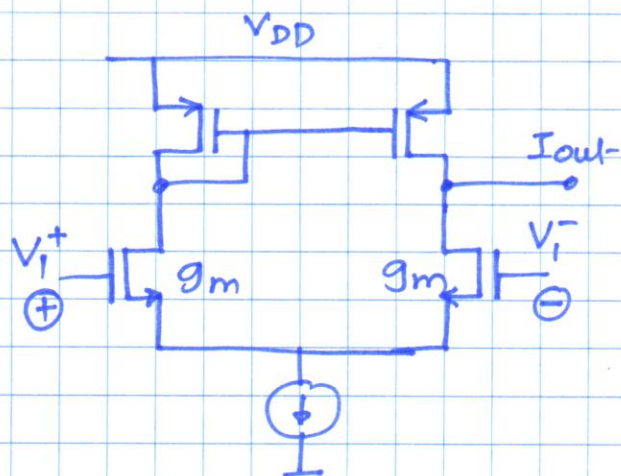




Gm.C filters

- + Simple circuit
- + Leads to high frequency performance
- Linearity.

↳ Can be improved by source degeneration

⚡ Tuning Required due to Gm variations.


# Fully-Differential Gm-C integrator

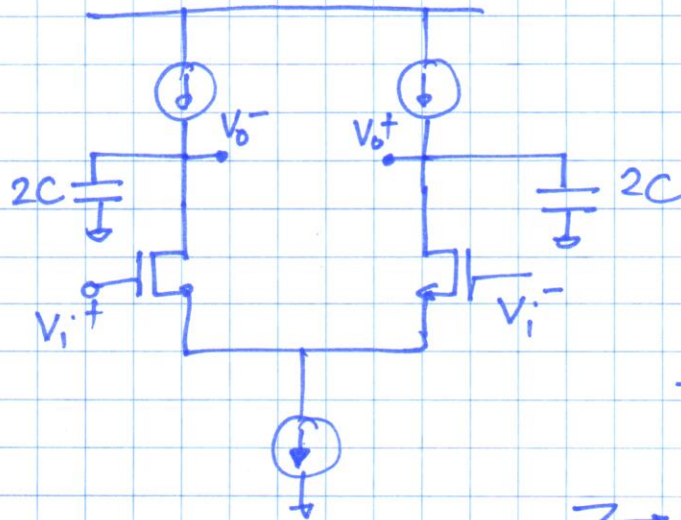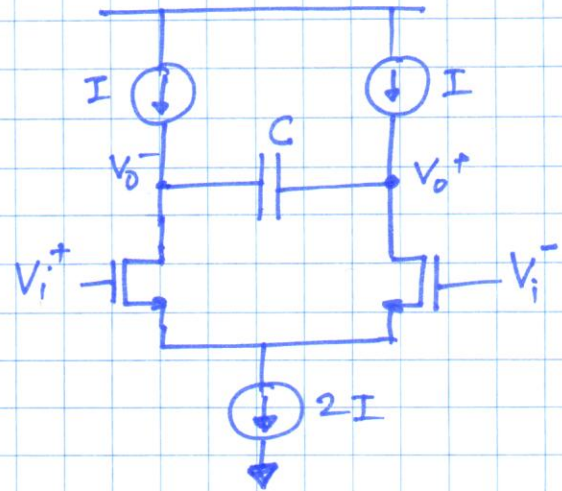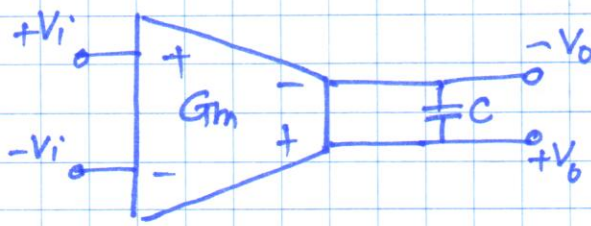


← Better since common-mode path also has capacitors.

→ Although larger size.

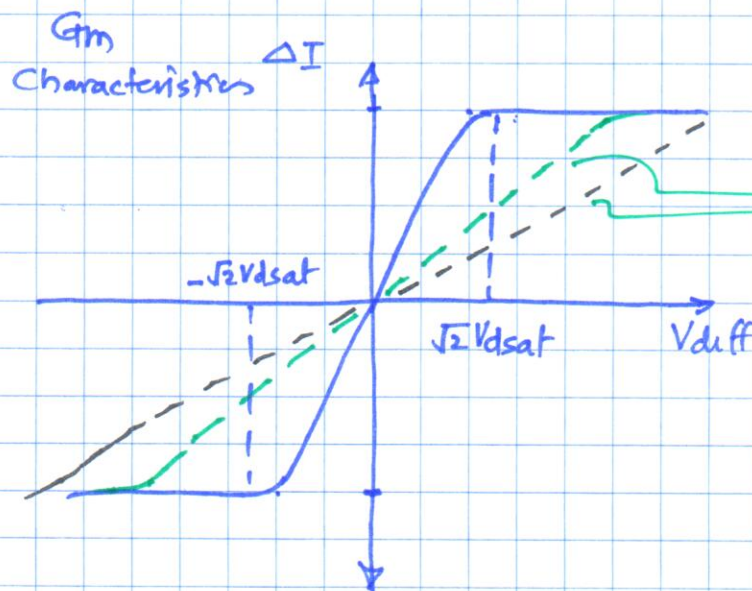
→ Reference H. Khorramabadi  
"High Freq. CMOS filters" JSSC DEC 84.



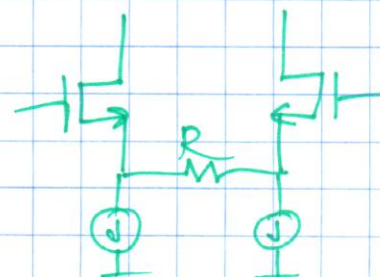Source degeneration  
to improve linearity  
of Gm cell.





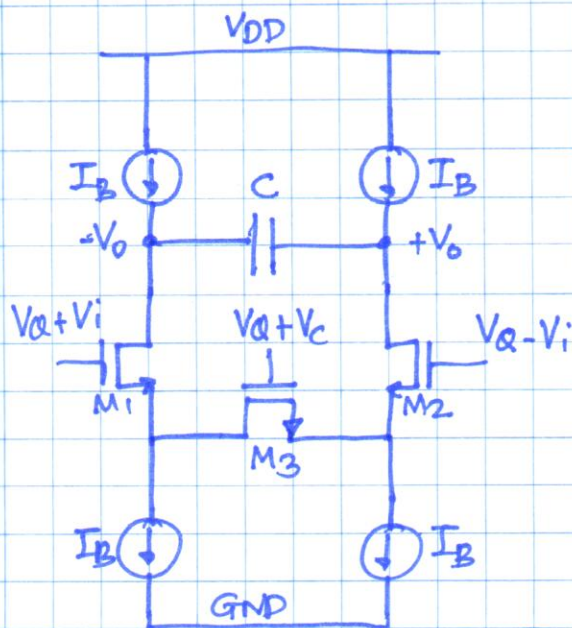


source degeneration using  
MOS Transistor M3 in Triode region

$V_c$  - used for tuning  $G_m$   
& filter corner frequency

→ J.M. Khoury JSSC Dec. 91

Another variation

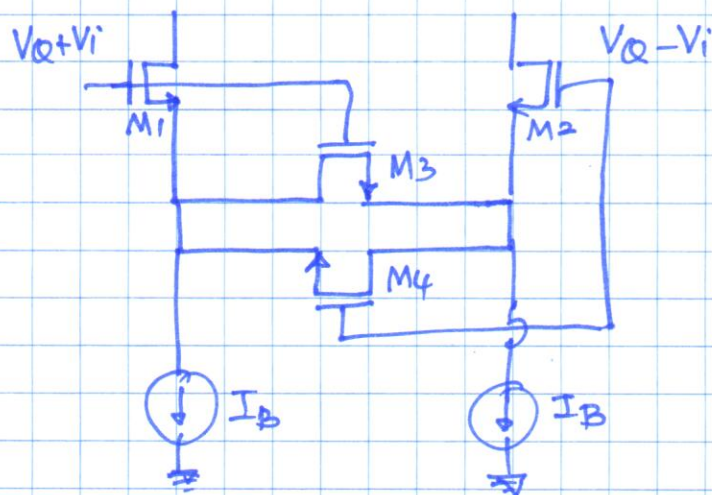

M3, M4 in triode region

They are biased from i/p signal.

Better distortion performance.

$$G_m = \frac{4K_1K_3}{(K_1 + 4K_3)} \sqrt{\frac{2I_B}{K_1\mu_n C_{ox}}}$$

$$K_1 = \left(\frac{W}{L}\right)_1 \quad K_3 = \left(\frac{W}{L}\right)_3$$

→ Reference F. KROMMENACHER.

A 4MHz CMOS. Cont. time filter with on-chip  
Automatic tuning. JSSC - JUNE 1988.

Key issue in design of High Frequency Gm-C filter


\* Parasitic caps. (top plate parasitics, interconnect caps  
Next stage loading.)

→ appear in parallel with integration cap. affecting frequency response accuracy.

→ can't be compensated & matched.

Goal - Parasitic Insensitive topology.

\* Gm-C OpAMP Filters

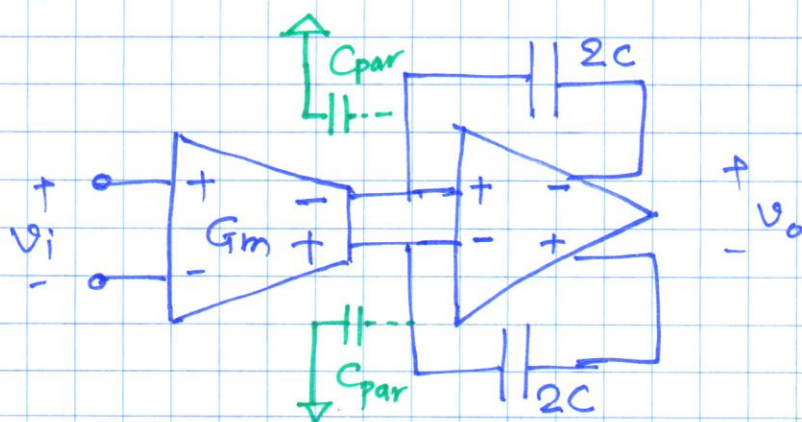

\* Parasitic caps @ o/p of Gm - connected to virtual gnd.

\* Gm o/p doesn't handle large swings

\* Higher Integrator gain

\* wideband OTA can be used instead of OPAMP.

Ref: 1. K.S.TAN & P.GRAY JSSC DEC 78


2. C. Laber & P. GRAY JSSC April 93

- Overall higher power


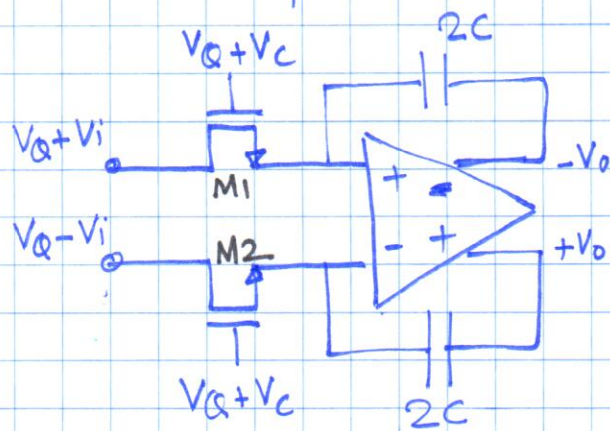
## MOSFET - C Filters

- Replace  $G_m$  transconductor with MOS in triode region.
- Lower power.



$M1$  &  $M2$  in triode region.

$$\omega_o = \frac{1}{RC} \quad \text{UGF of Integrator.}$$


$$R = \frac{1}{\mu C_{ox} \left( \frac{W}{L} \right) (V_c - V_T)}$$

- \* Fully-balanced operation - MOS even-order non-linearities are cancelled.
- \* Third order (odd) non-linearities - keep signal amplitude low

Ref: Fully Integrated Active RC filters in MOS tech"  
M. Banu, Y. Tsividis - JSSC Dec 1983.
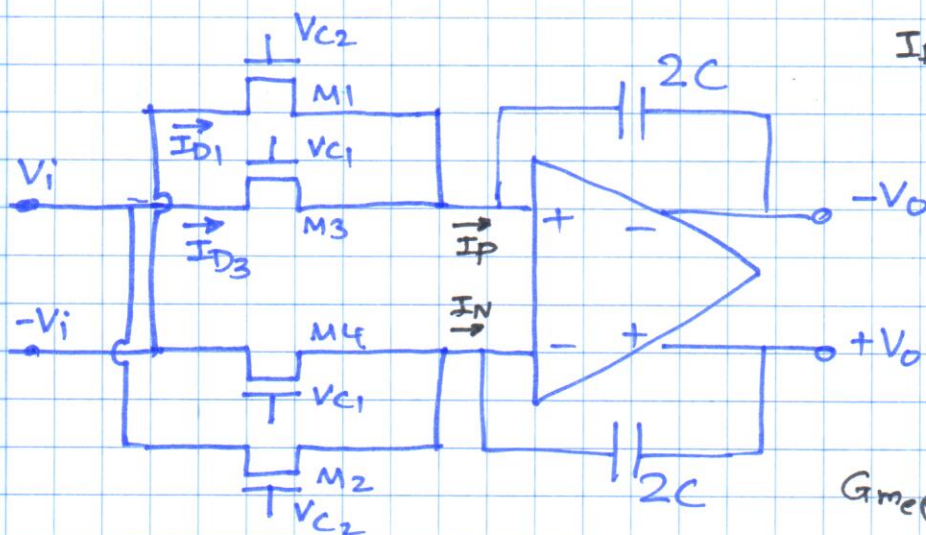
## Improving Linearity further

$$\text{TRIODE EQ. } I_D = K (V_{gs} - V_T - \frac{V_{ds}}{2}) V_{ds}$$



$$I_{D1} = K (V_{gs1} - V_T + \frac{V_i}{2}) V_i$$

$$I_{D3} = K (V_{gs3} - V_T - \frac{V_i}{2}) V_i$$

$$I_P = I_{D1} + I_{D3} = K V_i (V_{gs3} - V_{gs1} - V_i)$$

$$I_N = K V_i (V_{gs1} - V_{gs3} - V_i)$$

$$I_P - I_N = 2K V_i (V_{gs3} - V_{gs1})$$

$$G_{m,eff} = \frac{\partial (I_P - I_N)}{\partial (2V_i)} = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{c1} - V_{c2})$$

Ref: Z. Czornul  
M. Ismail

IEEE - Tran CAS JULY 1986.  
JSSC Feb 88.

Large Signal Linear behavior  
→ 50-70dB linearity.