

- RA = can access in any order without any loss of performance

Sequential = eg: shift registers
data rotated in a very long chains
don't require address decoding
→ helpful when we want to keep performing operation on a set of data periodically

- ROM: even though it's random access

Bridge = Flash memory

(can't write many times)

- also called 'write Rarely Read Often'

- Read takes long time

R/W M


Content Addressable Memory: check if any cell has the data

- Read Access time: time between giving read instruction and getting the data output

write Access time: time between giving write inst. and how long we need to keep the data unchanged to complete write

Cycle time: time b/w 2 successive read statements

(can be more than read access time)

 

MEMORY

Cycle time: worst case time b/w

Read-Read, W-W, R-W, W-R

- when we want large amt. of memory, using lot of D-flip flop is expensive in space (area) and time (control signals) and power (charge rail-to-rail)
- Rather we make analog ckt;
make sure we get a sufficient voltage change which can be subsequently amplified to a rail value.
→ noise may cause problem hence we use differential amplifier

Addressing

- address has to settle before issuing a \overline{RD} or \overline{WR} (we might otherwise destroy some other data)

- sometimes memory takes care of it internally

→ having multiple enable signals is inefficient

→ rather we arrange memory in a 2×2 array and get the row and column address

• RAS: Row Address Strobe

CAS: Column — " —

give RAS first then CAS


• Address line: Bit addressable

Word — " —

- $$- \overline{R1D} / \overline{W12}$$


use same add. to now send column
then CS
then $\overline{RD}/\overline{WR}$

- like programmable logic array

 

- the selected cell is pulled down to 0.
- may not be hauled to 0, can have a compar^{ator} at end \Rightarrow small transistors used


→ NAND memory

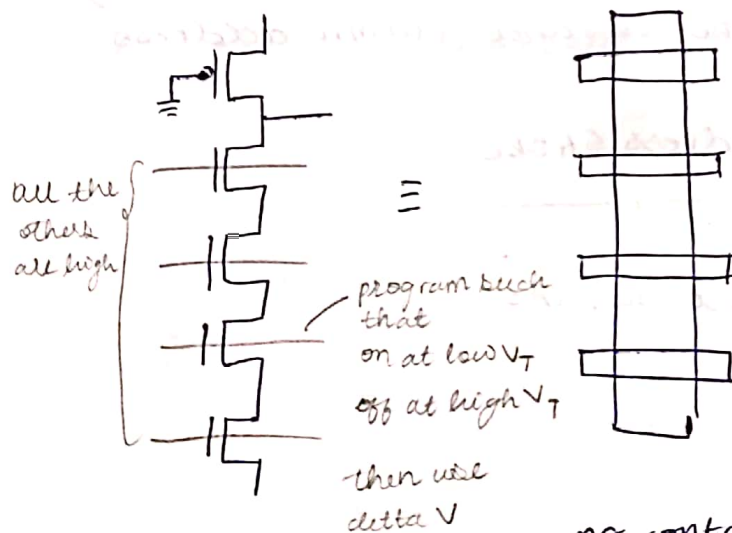

→ used for
thumb drives,
SSD

→ NAND has less density, but slower than NOR.

no contact window

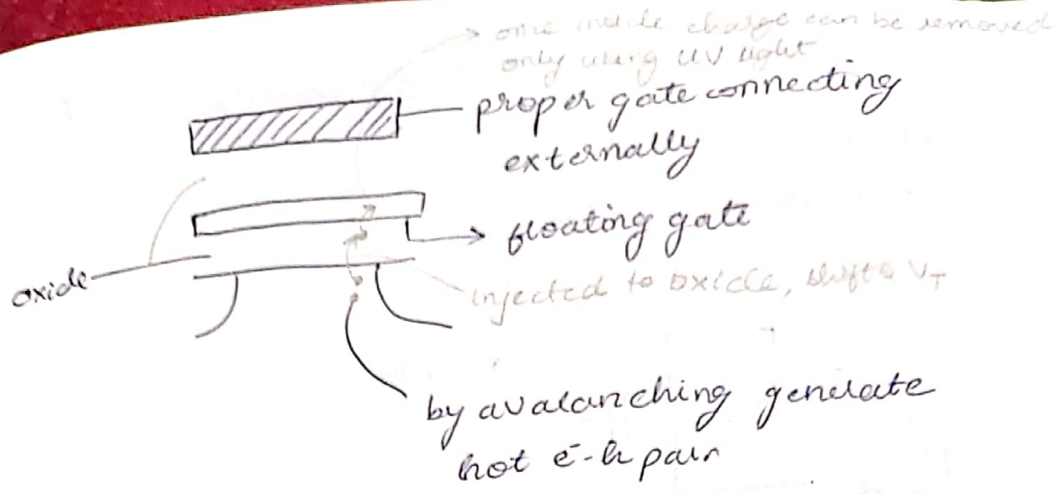


→ removal not perfect, damage producing
 hence can only programme a no. of times.

→ PROM


→ modern devices are small enough that tunnelling occurs and it can be erased electrically

→ EEPROM

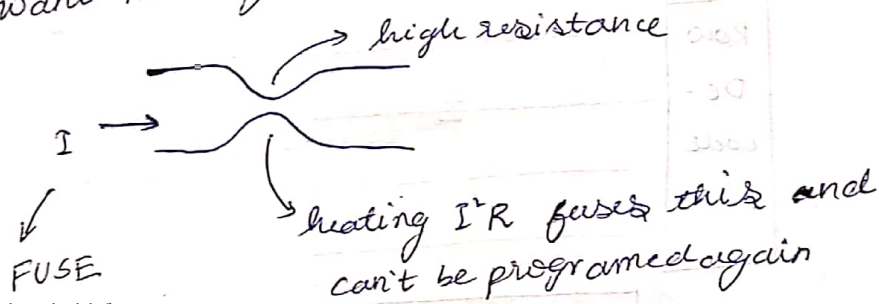
• want memory that can be programmed once




fuse something that can break the flow

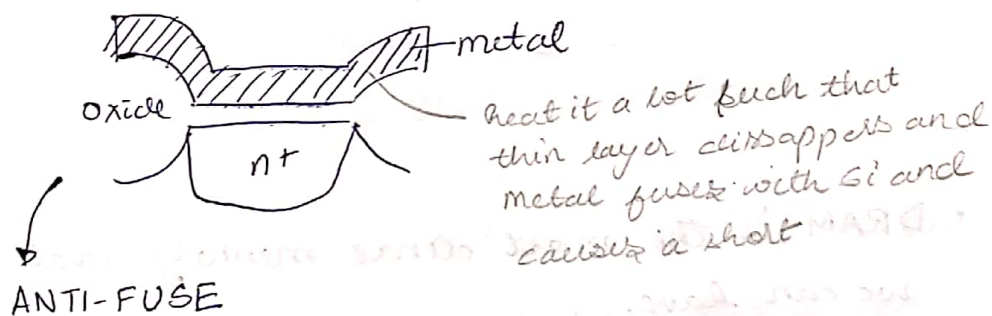

 - If we want to program frequently we have
 - static memory
 - dynamic memory




 - DRAM should be a separate chip than the rest of the ckt
- when we read we need to write back a 1



by capacitor sharing charge sharing occurs



24/10

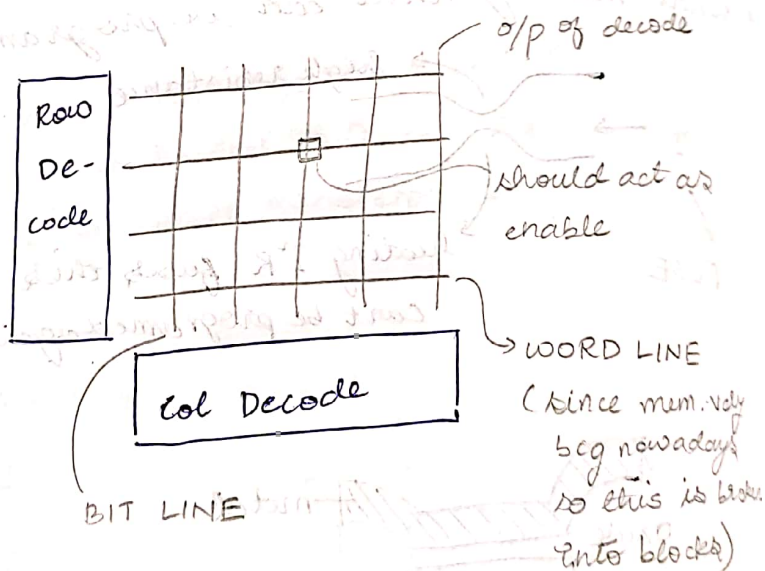

- DRAM is the most dense memory that we can have.
- Read in a DRAM is destructive, so after reading we must write it back
Thus, cycle time for reading and writing diff

- Since DRAM requires a trench cap. and auto control for reading, it is usually kept separate from the std. technology chip

• SRAM

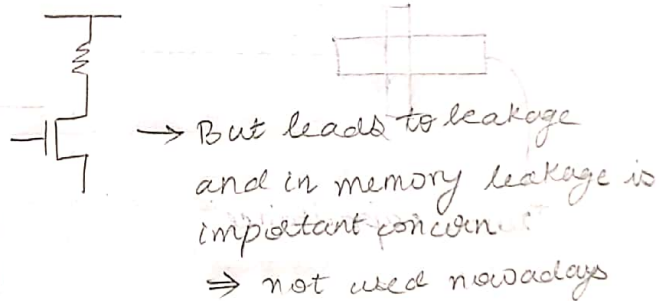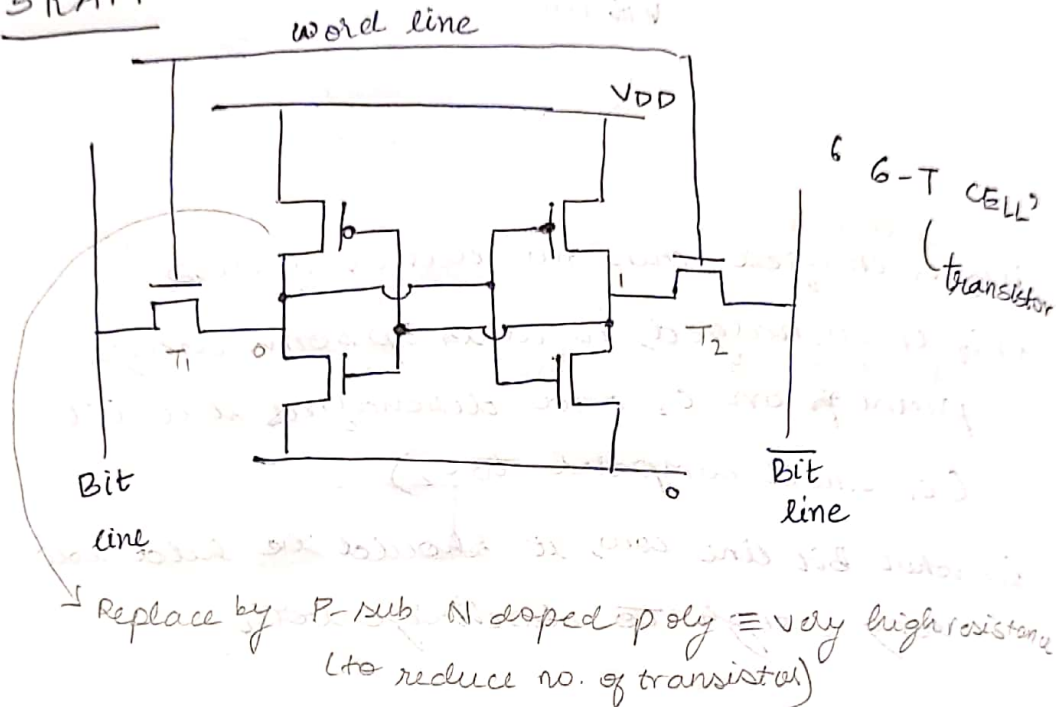


- If word line not connected, then this cell is isolated
- Column decoder decides the value of Bit & $\overline{\text{Bit}}$.
 $\overline{\text{Bit}}$ & Bit are taken high when not used word line high when selecting that row
- If column is 1, then Bit = 1, $\overline{\text{Bit}}$ = 0

T_1 & T_2 should be strong compared to the other transistors in case of write. However, the requirement is opposite in case of read. Thus, assigning their ratios is important

- i) Charge Bit & $\overline{\text{Bit}}$ to a high value then turn it off
- ii) Now, charge word line and turn it off
- iii) Suppose, T_1 sees a 1 so it tries to discharge the big capacitance of Bit line
- iv) the Bit and $\overline{\text{Bit}}$ lines sent to comparator
- v) when we turn the word line off, the cell becomes isolated and by positive feedback restore the value


when we turn a row on, the cell activated is being written into while the others (in that row) are being read.

while reading

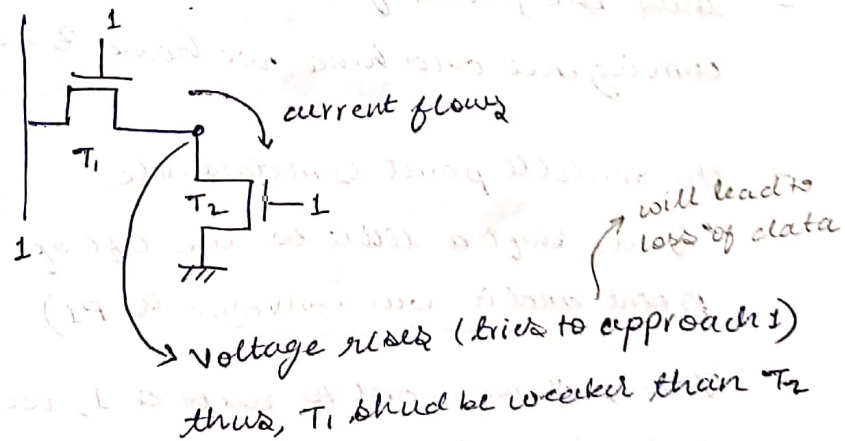



 doesn't go to 0 since connected to rail but it and would line




- if V_i connected to V_o , then on starting with V_i we end up in V'' . Thus, this goes on till we converge at a point
- Thus the points of intersection lead to convergence and hence we have 3 solutions
- the middle point is metastable
 (if we shift a little to the left of this point and it will converge to P_1)
- Thus, if we want to write a 1, we put our voltage to the right of P_2 . However, if it is too close to P_2 it will

take a lot of time to reach 1 so we put it close to P3

28/10

i) Precharge


(use p-mos, also use a shorting tran.)

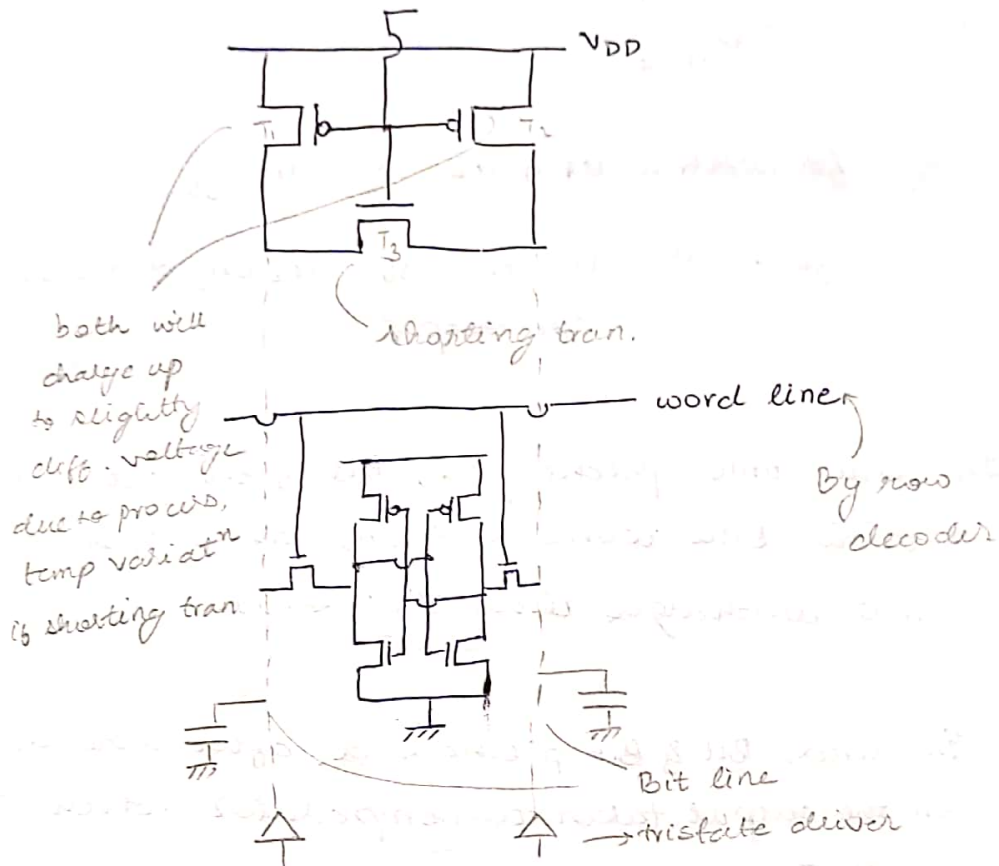

- all 3 pmos turned on, Bit lines turn on
- turn off T_1, T_2 first then T_3
- then turn word line on

If T_1, T_2 are pmos, then common mode range rises up to V_{DD} . So we use nmos instead (compact to use ³nmos) which doesn't charge fully up to V_{DD} .

 - Until decoding done can't do R/W
 - ⇒ speed of decoder imp.
 - ⇒ make decoder multi staged (by logical effort multi stage faster)
- typically comparators are 2 stages, act like a linear amplifier




for write, Tr_1 & Tr_2 on, Tr_3 off

for read, Tr_1, Tr_2 off, Tr_3 on, data becomes an output

In write, pmos precharged, Bit & \overline{Bit} get data & \overline{data} . Once word line on, which of bit & \overline{bit} is 0, discharges that transistor




In read, Bit & \overline{Bit} precharged, after word line on the output taken to comparator which sends it to Tr_3

Read conflict

 



If initially 0 & 1 were written and we want to read that.

 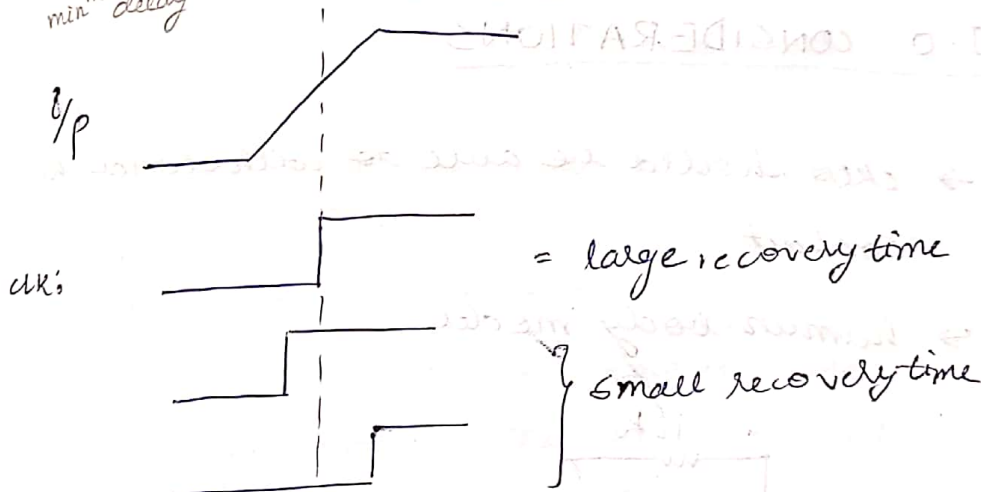 0/1/0. external ϕ transition can occur at any time w.r.t. clock, so it might change when clock changes. so while sampling, ext. ϕ might be close to metastable pt. \rightarrow it can take an unpredictable amt. of time to become stable.



\Rightarrow ext. clock will shift it $\delta(A)$ before the clock time

• Synchronizer

  

A might be metastable, but B would latch onto a value, instability vastly reduced.
by the time next clock comes


→ as clock period reduces, the problem of metastability becomes significant.

(if T small, then by the time next clock comes we won't move far enough from metastable point (V_m))

I-O CONSIDERATIONS

→ ckt should be able to withstand human contact

→ human body model

 

① ⇒ protection imp.

② voltage translation


- chips from diff. generations can be together
- voltage translation needed at input

- ③ signal conditioning
 - robust signal that removes noise
- ④ drive large capacitive loads
 - for bidirectional ports

voltage translation

 
(A) at input

- input swing higher than V_{DD}
 - ⇒ safety issue



- input lower than V_{DD}
 - problem with high, low is same
 - also, pmos is the one who can't drive with a small i_p
 - so we use CUSL (doesn't need to be driven by input)

 
anyways present in pad which are large, hence area not a big concern



low voltage inverter

[pseudo nmos can be used but it consumes static power]

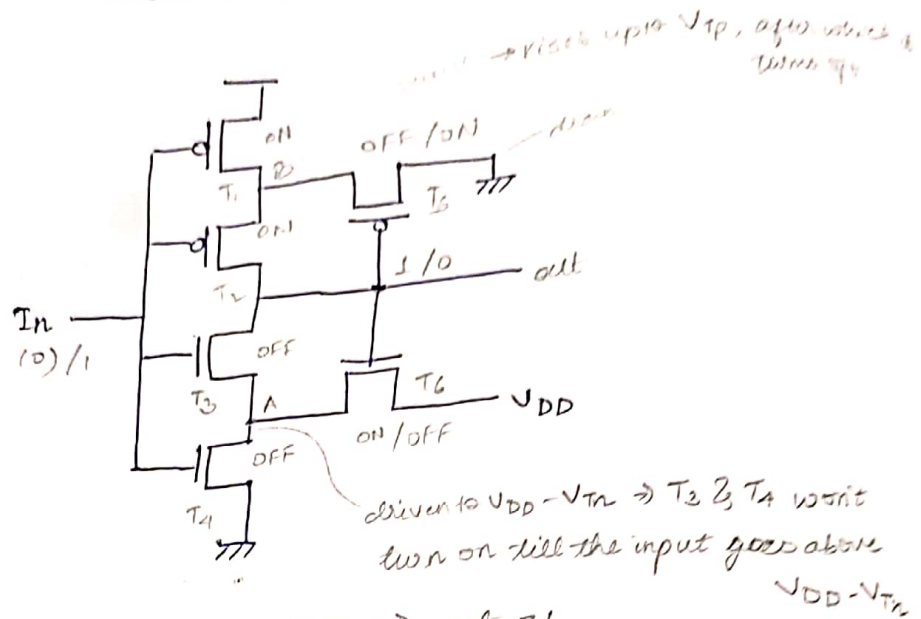⇒ high thresh. higher than average
and low thresh. lower than avg.



(1) Input 0 for long time ⇒ out = 1

When In reaches V_{tn} , T_1 turns on and tries to discharge A, but A is supplied by T_6 so, A is somewhat above gnd. so the In that turns on T_3 is somewhat above V_{tn}

T_4, T_6 form a potential divider


(2)

As T_5 turns on, B becomes V_{tp} , as T_1 turns on it tries to make B V_{DD} but due to T_5 it is a little below V_{DD}

⇒ T_2 requires an i/p lower than V_B by V_{tp} , hence the turning on voltage reduces.

• C element

→ used for asynchronous design

 

A	B	out
0	0	1
1	1	0
0	1	prev
1	0	prev

Tristate, neither of p or n mos are on as a whole so not connected to power
 \Rightarrow take value of capacitance

\rightarrow equal input \Rightarrow inverter

unequal inputs \Rightarrow latch

\Rightarrow called 'Event Logic'

\rightarrow need event on both inputs (not necessarily simultaneous)
 for the output to change

{std logic = level logic}



\rightarrow C element

(AND of events rather than AND of levels)


• Asynchronous transfer of data

\rightarrow request - acknowledge

talker
 \rightarrow put data on data bus, once data settles, it puts request



 the other side uses this as a clk and latch the data. Once latched it acknowledges and allows next data to be sent



\rightarrow since 4-transitions \Rightarrow '4-phase', request-ack

The 2nd edge on both transitions only restores the value, doesn't do any job.

so we use event logic

→ change of state now tells us whether whether
req or ack

⇒ less switching ⇒ less power consumed

→ however not used coz it is
event driven and hence we would need
to change the entire logic family.

• DFT (Design for testing)

- generation of test vectors that encompass
all possibilities

- approachability of nodes


if $S \rightarrow$ scalability

pack $\propto 45 \Rightarrow$ no. of pins reduced, hence
difficulty to test


(A) Border Scan

- test vectors put in series

- synchronous design

 

⇒ in test mode:

 

6f form a chain


put input in each ff and run for 1 clk
cycle, new values stored in ff's.

Now, put in test mode and view

the outputs of all subckts

→ as we take out one output at a time,

 put in one input vector for the next test



→ since test vector passes through all combinations, need to make sure none of them make any subckt invalid

→ never use asynchronous set-reset in such a struct.

→ In border scan can have upto 5 inputs

- Digital In
- Digital Out
- Test In
- Test Out
- Scan
- reset

(B) on-chip test units - req. memory

- test. vector generator (pseudo-random)

