

23/09 • Try with fork 2-3 & 3-4 and vary load for last que. of midsem

• ADDERS

- $\text{sum} = 1$ if A, B, C have odd 1's (full adder)
 \Rightarrow parity circuit
- $\text{cout} = 1$ if 2 or more inputs are 1

\therefore an adder is counting the number of ones hence sometimes called 'counter' (not the same as conventional counter)

• Faster Adder

- elemental adder faster
- how to arrange to minimize delay

• In addition, carry is on the critical path ^{optimize}
 (thus sum_n need not be made faster)

\Rightarrow sum derived from carry (C_{in}, C_{out})

\hookrightarrow inserting inverter is useful when we have heavy load to reduce delay


\rightarrow heavily loaded \Rightarrow more stage

lightly - " - \rightarrow less - " -

\hookrightarrow Pinv becomes large otherwise

3

 - Mirror symmetry : we can produce sum using same circuitry and complemented inputs
- only for sum & carry attributed to the xor function to use



however inverting in here using inverting would lead to additional delay

+ 31 inverters removed

⇒ this helps when capacitive loading not high

(otherwise inverter would've helped)

⇒ we can use the same configuration for PMOS as the NMOS in a CMOS structure

[For NOR larger transistor (PMOS) was in series, hence it is inferior to NAND]

→ But here both are same, hence faster


⇒ elemental adder is faster

$$\rightarrow f(\bar{x}_i) = \bar{f}(x_i)$$



→ ripple carry adder

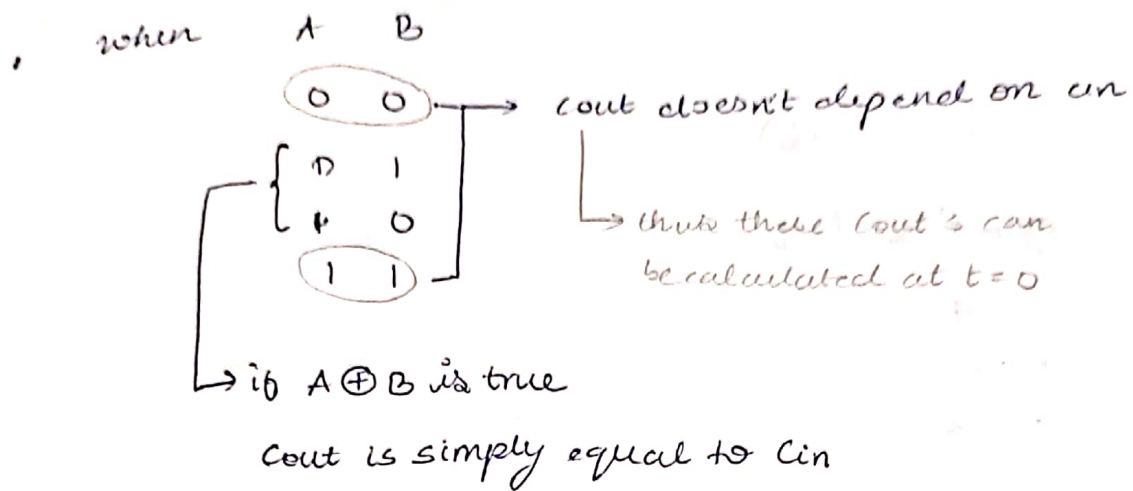- Adders that use grouping have bad results for small number of bits, however good for larger bits.



A	B	
0	0	= kill cond ⁿ (K)
0	1	} = pass cond ⁿ (P)
1	0	
1	1	= generate cond ⁿ (G)

- XOR difficult to implement; OR easier,
 1 1 is the only diff b/w them
 ⇒ need to make G dominate over P
- of K, P, G only one is true at a time
 ⇒ compute only 2

$$\Rightarrow C_{i+1} = G_i + P_i C_i$$

$$= G_i + P_i (G_{i-1} + P_{i-1} C_{i-1}) \Rightarrow \text{carry look Ahead}$$

24/09 • For 3 inputs

if no. of 1's in input = n

then no. of 1's in input complement = 3 - n

complement

Input

Sum: odd

carry: ≥ 2

$\Rightarrow 3-n = \text{even}$

$\Rightarrow 3-n \leq 2$

• for $ab+c (a+b)$

logical effort of

$$a = 4^{(12/3)}$$

$$b = 4^{(12/3)}$$

$$c = 2^{(6/3)}$$

• For K&G we have minimal delay
(don't have to wait for carry)


\rightarrow use a pass-gate

• Delay = $n d_i$

\rightarrow reducing elemental delay
through mirror gates

\rightarrow reduce it through grouping

 for eg: for 64 bits we break it into
groups of 4 bits



\rightarrow Worst case:

$$C_{i+1} = P_i + P_i C_i$$

all P_i 's are one (so will
need to wait)


\rightarrow but if all P_i 's are 1
then group for output

$$C_{out} = C_{in}$$

\rightarrow so we just AND all P_i 's
and put a switch, bypassing the

⇒ carry-bypass adder

 - These adders are the fastest adders (for very large number of bits)



if $C_i = G_i + P_i C_{i-1}$ → propagate at that stage

$$\begin{aligned} C_4 &= G_4 + P_4 C_3 \\ &= G_4 + P_4 (G_3 + P_3 C_2) \\ &= G_4 + P_4 G_3 + P_4 P_3 (G_2 + P_2 C_1) \\ &= G_4 + P_4 G_3 + P_4 P_3 G_2 + P_3 P_2 P_4 C_1 \end{aligned}$$

$$G_{gp} = G_4 + P_4 G_3 + P_4 P_3 G_2$$

$$P_{gp} = \prod P_i$$

$$\Rightarrow C_4 = G_{gp} + P_{gp} C_1$$

• Karnaugh = optimizing recursive relation

- Carry select adder

Make 2 adders
 $\left. \begin{array}{l} \text{— assumed carry} = 1 \\ \text{— assumed carry} = 0 \end{array} \right\} \text{select one using Mux based on output carry}$


- power consumptionⁿ ↑ but time reduced

- do it for all groups, not within the group (inside the group we can have any adder)


eg: for 128 bit adder all results are ready in 4 bit adder time

• Modula to eliminate delay:


- zero delay
- unit delay
- full delay

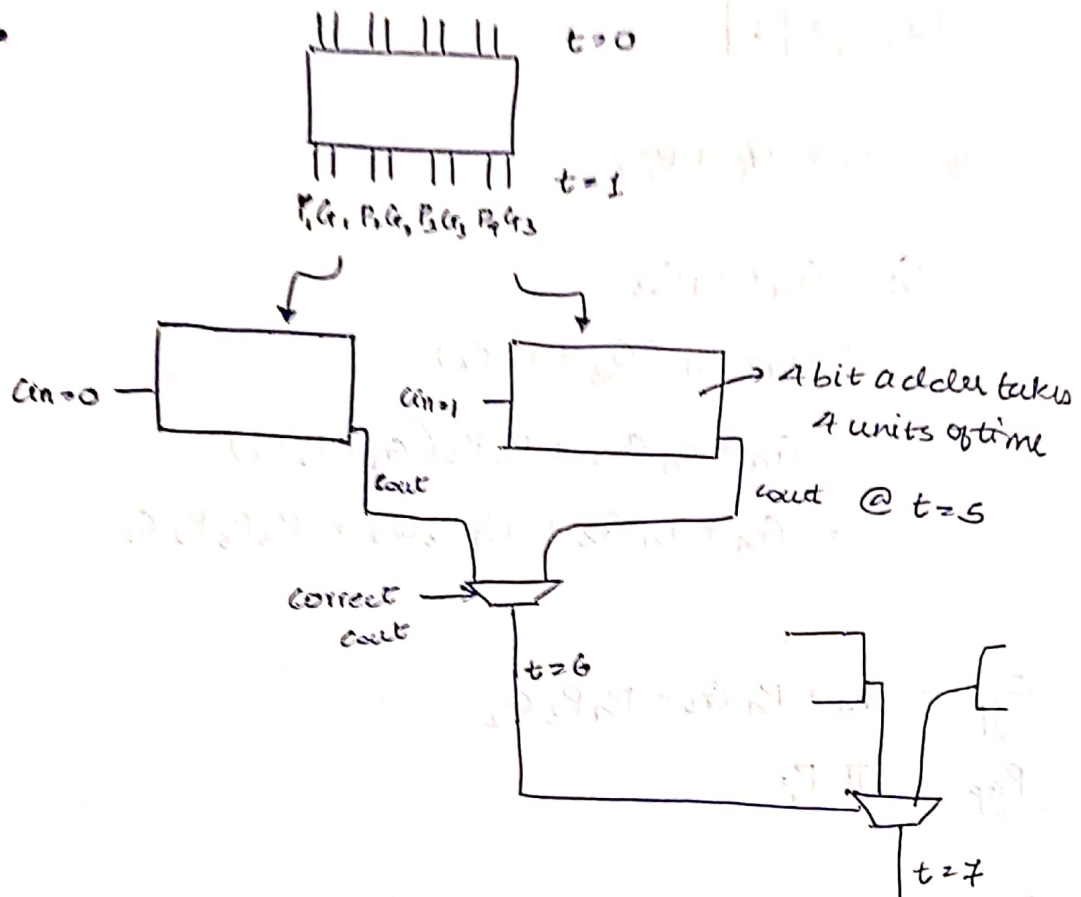

26/09

 

 total delay
 $\frac{n}{g}$ - max delay
 group delay




- $[P, G]$ takes 1 unit of time and 4 bit adder takes 4 units of time, so C_i arrives by $t=5$
- As complexity \uparrow , time taken \uparrow linearly
- To make t smaller, then need to \uparrow the length of an individual block

→ when tiling is $4 + 4 + 5 + 6 + 7 + \dots$ carry arrives at this time

$$\Rightarrow \frac{n(n+1)}{2}$$

time is square root of no. of bits.

 - If no. of bits \uparrow significantly then the time will be too much, so want to use a different architecture then.
 - so we use 'logarithmic Adder'



$$\text{Carry} = G + P \cdot C_{in} \quad (\text{I want } G \text{ to be dominant})$$

if $G = 1$, capacitance discharges to 0
when clk goes high

at A if

$P \& \bar{C} = 1$, then A will get 1

$P = 1, \bar{C} = 0$, A pulled down

- we can't make bigger chains through this.
we take it to limited stagger (3-4) buffer
it. $P \& G$ calculated using simple OR gate.
output is not propagating.

$$C_{out} = C_i + P_i C_{in}$$



Let's fix one convention on now

$$i = 0, \dots, n-1$$

$$C_{in} \rightarrow \boxed{i} \rightarrow C_i, \quad C_{i+1} = G_i + P_i C_i$$

The idea is to make
for ripping

and use groups

  

Let my 2 bit adder be basic adder

$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 (G_0 + P_0 C_0)$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

don't depend on carry depends on carry


→ Prefix adder or Logarithmic or Breadkirk

- It can be broken into some G_i & P_i .
 G can always be computed & P can also be precomputed. Any contiguous block of these adder's can be treated together and their combined G 's can be calculated.
- G is calculated same way as we had computed carry of single elemental adder.
- Since C is not available, it can't be calculated unlike G which is calculated as carry of single elemental adder.

For T circuit, we calculate c . G is calculated
in the same way as carry of single elemental
adder. So only for c_0 stage we need to do
this.

30/09

SERIAL ADDER

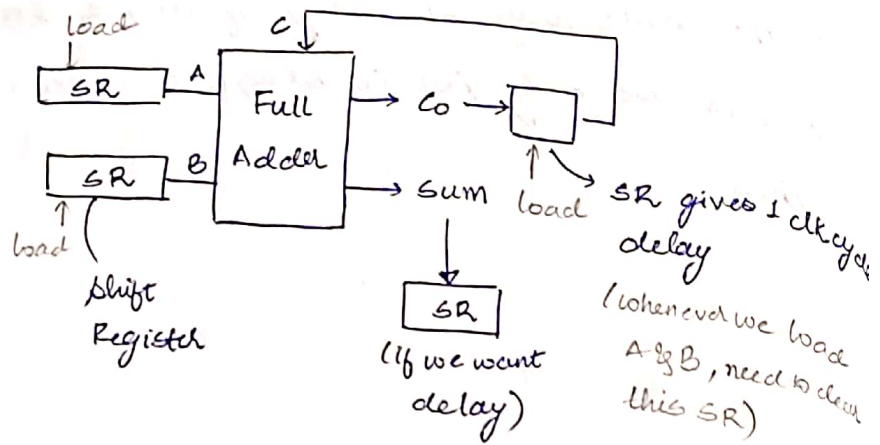

Ripple carry adder = n (addition time)
(time taken)

Serial adder = n (clk cycles (if clocks are matched period))

→ as good as ripple carry adder)

ASSGN


FO4 delay

Fanout 4 → do for 64 bit broadcast adder)

SHIFTER

- they do shift and rotate
- shift \times or \div by 2
- shift right — signed (replicate MSB)
— unsigned (insert 0)
- if we want to do 27 shifts, simple shift register takes 27 clks (while if remains same) → not desired
- so we have parallel shifter (used in Barrel Shifter)
→ ideally produces op in 1 clk cycle

 - essentially we need to compute the new position for a bit
- if amount of shift is const (say 5) we just wire the ip to that bit position (\Rightarrow no extra hardware needed)



- if B loaded with MSB of A then it becomes ^{right} Arithmetic shift (signed RS)
- if B loaded with replica of A then it becomes rotate
- if amount of shift variable, each output connected to a MUX. Then shifting done is $(N \times 1 \text{ MUX})$ 1 clk cycle

New position = Current position + shift

\rightarrow But for large no. of bits, the circuit would be very large \Rightarrow clock increases.

\rightarrow Need to reduce complexity from N to $\log N$

- $-n = 2^n - n$: in 2's complement representatⁿ

1

 : sign-magnitude representatⁿ

\rightarrow MUX if 8 bit processor

each bit has 8×1 MUX $\Rightarrow 8 \times 8$ complexity

for 32 bit : 32×32 complexity

• If we want to shift by 19 position


10011

161 : shift by 16
160 : no shift


helps
reduces complexity to begin

$\Delta \text{ dest.} = i \text{ or } i+16$


\Rightarrow 2 way MUX

 

MUX:

 


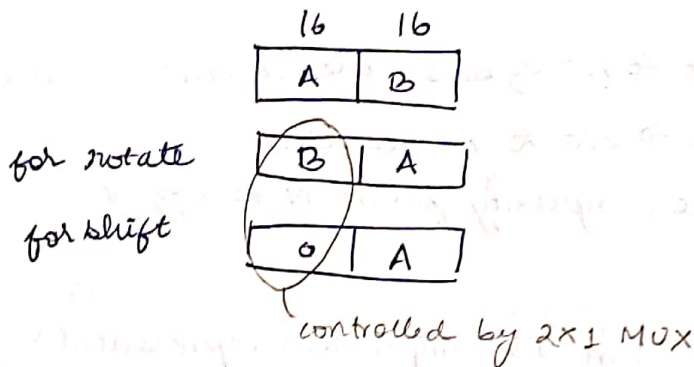• For a 32 bit ckt, shift or rotate by 16 requires only 1 2x1 mux



05/10

Making full adder from half adder

 


Multiplication:

conventional :

$$\begin{array}{r} \dots = \sum 2^i a_i \\ \dots = \sum 2^j b_j \\ \hline \text{Product} = \sum_{i=0}^n \sum_{j=0}^n a_i b_j 2^{i+j} \Big|_{i+j=k} \\ k = 0, \dots, n \end{array}$$

Shifting

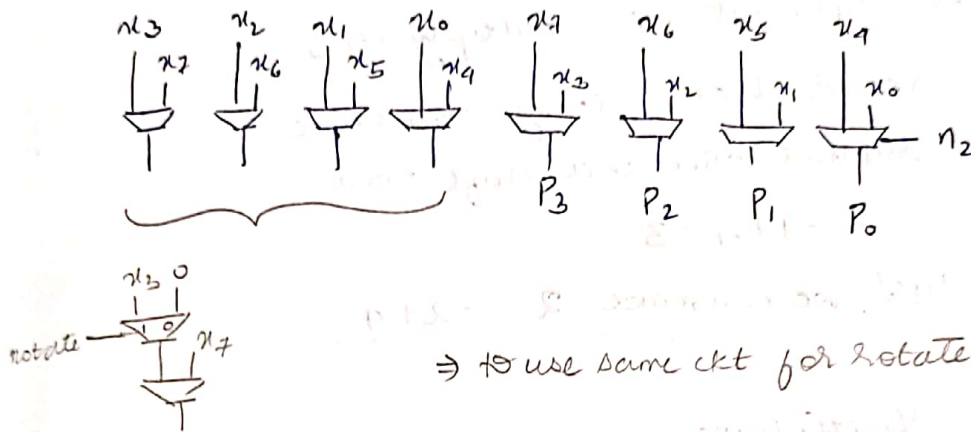

⇒ to use same ckt for rotate & shift

- combining left and right shift

→ keeping the same ckt, reverse the bit sequence being fed.

i.e. for left shifting, reverse the bits

Shift and Add Multiplier

Partial product : things to be added

- can add bit-by-bit or row-by-row

- in array multiplier: both sum & carry are in critical path (rippling down) (rippling left)

$2(n-1)$ = amount of rippling required

→ not good for large no. of bits

- To optimise we can reduce
 - number of stages of operation
 - time taken by operation

• $A = a_{n-1} \dots a_0$

⇒ combine 2 bits of B and multiply to get the rows we add finally

for $b_1 b_0 = 11$ i.e. multiply by 3

rather than adding 2 rows we subtract once and shift twice

⇒ $-1 + 4 = 3$

||ly, we can make $2 = -2 + 4$

03/10

• Multiplying 2 numbers:

- choose B such that it has fewer bits ⇒ fewer no. of additions

→ Group B into groups of 2 bits

Possibilities:

00	0
01	A
10	2A
11	3A

$3A = -A + 4A$

upon multiplying with A

done by the successive 2 bits of B


(Currently we are generating partial products

- we want them to be available parallelly)

2A can also be converted to

$-2A + 4A$

Partial Product Generator

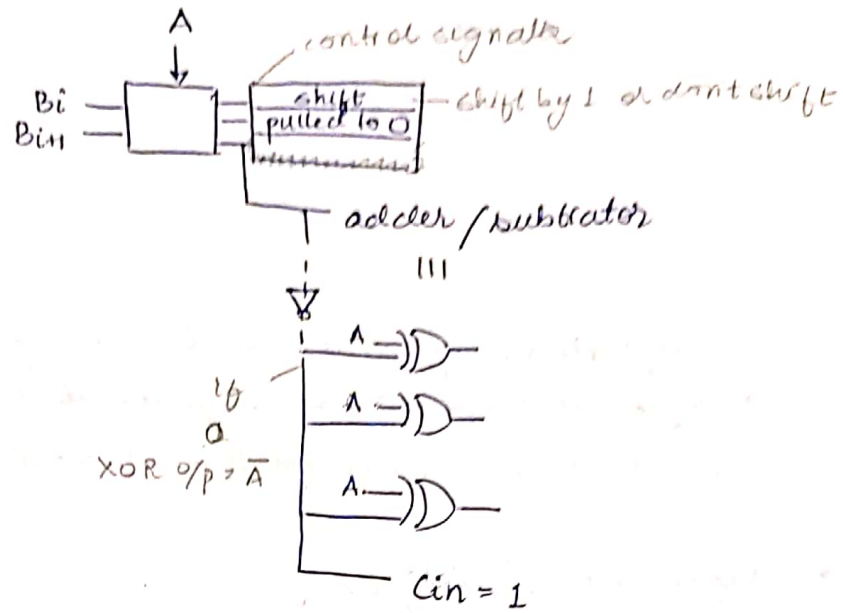

$$A = 1 + \bar{A} \Rightarrow \text{minus } A$$

For -2, shift by 1 then negative


- considering some in-between bits

00 00 00

we consider 3 bits the LSB of which tells us if we need to do +4A

- For the LSBs, add a zero at the end
- If groups get over, add zeros at the beginning

		Partial Product
00	0	0
	1	A
001	0	A
	1	2A
10	0	-2A (we want 2A, but MSB adds +4 so make it -2A)
	1	-A (we want 3A, but MSB adds 4A so make it -A)
11	0	-A
	1	0

 


- all negative quantities become full width and in final addition we require ~~it~~ twice as much size as normal multiplier adder

• Different Multipliers

- one feature of multiplier is multiple of adders
- carry (due to rippling) makes adders slow

Carry Save Adders (useful for large no. of bits)

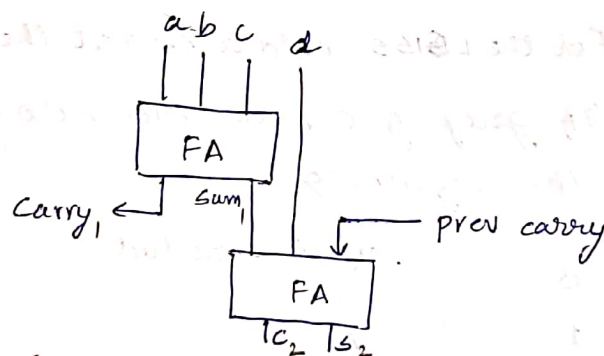- gives 2 numbers which must be added
- saving the carry for the end, so we don't ripple carry for the in-between steps



Carry has twice the weight

- one carry saved, other sent horizontally
- c_1, s_1 available in const. time i.e. at $t=1$
- prev. carry avail. at $t=1$, c_2, s_2 avail at $t=2$

However, these are avail. at const. time
doesn't depend on their position

ASSGN

$16 \times 16 = \text{multiplier} \Rightarrow 32\text{-bit adder}$

\hookrightarrow thus needs to
be faster

- carry save uses rectangular array whereas traditional adders are trapezoidal
- carry save not good for traditional addition

7/10 • Carry save adder \rightarrow addition doesn't
depend on c_{in}

\rightarrow store all carry in 1 register and
store all sum in 1 register

\rightarrow shift carry register by 1 place value

\rightarrow HA take 2/p and produce 20/p

however reduces to 1 wire at its place
value

FA : 3 \rightarrow 1 (at its place value)

- Wallace multiplier

\rightarrow reduce the no. of wires to only 2 at
each place value and put them in
2 registers

\hookrightarrow add these 2 registers using fast
adder


- HA uses (2,2) counter, FA is a (3,2) counter
carry save is a (4,2) counter

- Take the wires and make groups of 3

if it has

- 3 $\xrightarrow{\text{send}}$ to FA and send 1 to next bundle
- 1 \rightarrow do nothing; pass on to next stage
- 2 \rightarrow choice of using HA or passing it on

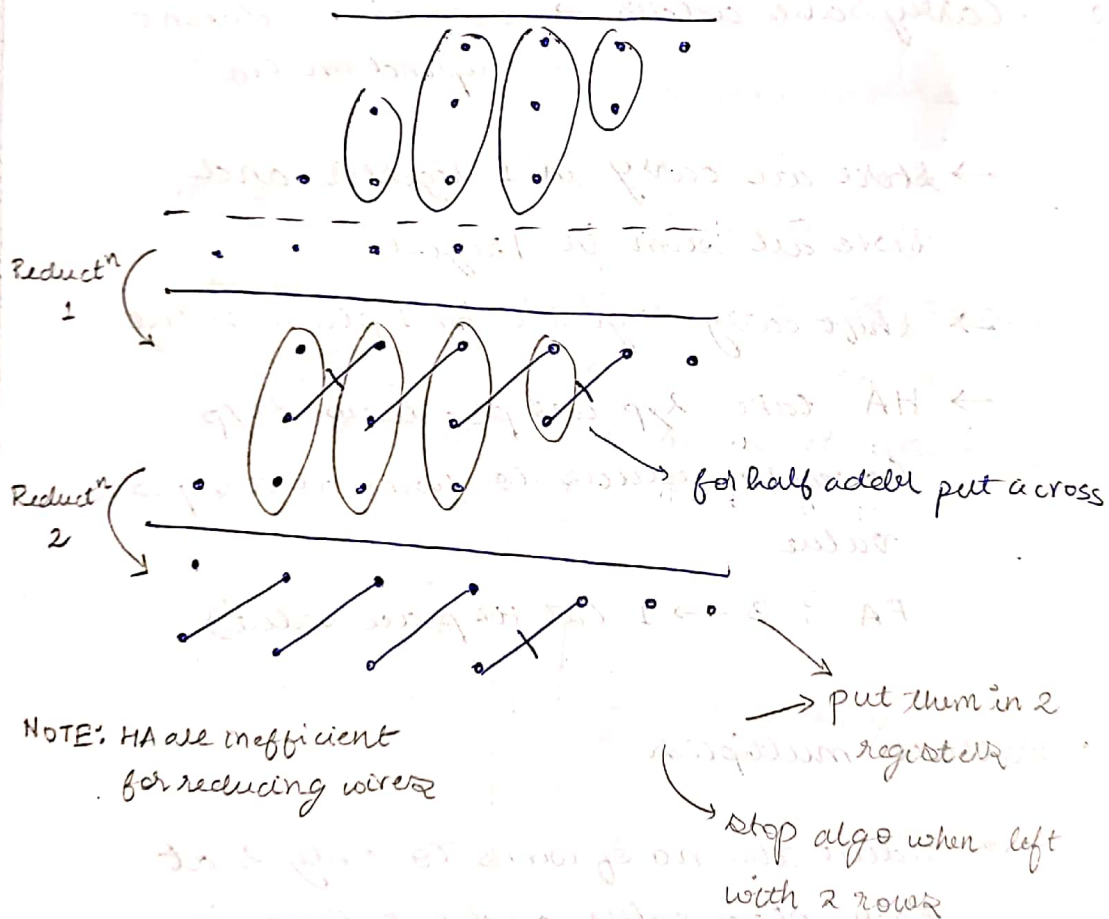\rightarrow Draw dotted line ^{as} along as one can make groups of 3



NOTE: HA are inefficient for reducing wires

• 8x8 multiplier Wallace

\rightarrow we don't put HA in rows of 2 coz they don't reduce the no. of wires, so using only HA we end up with too many bits at MSB

capacity = $\left\lfloor \frac{1.6 \times \text{successive no. of rows}}{2} \right\rfloor$
 (integer part)

→ fast adder becomes narrower(?)

• problem that we might get a 17th bit

→ comes up due to misinterpretation of Wallace algorithm

→ happens due to usage of more HA

(propagate selectⁿ of 2 bits so that we can use a FA later on)

→ if we are not exceeding the capacity of the next stage by passing the 2 wires then pass them through

(need to back calculate the capacity for each stage)

10/10

→ Get correct logic [structurally correct] [behaviorally

tick tock clock (present in library) synthesizable]
 (backannotation)

(delay needs to be added in library)

→ all gates should be inverting

→ Critical Path: when carry and sum both made

→ For AND = NOT + NAND : make your own cell

• 8x8 multiplier

$b_{15} b_{14} b_{13} b_{12} b_{11} b_{10} b_9 b_8 b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$
 1 2 3 4 5 6 7 8 7 6 5 4 3 2 1

no of wires

→ when we get 2 wires:

i) if all bits are to the left are 1 wire then pass it through

2) if on passing ^{it} through we exceed the capacity of the next layer then we use HA
 (go on till max^m no of wires are covered)

Capacity: 2, 3, 4, 6, 9

→ our capacity is 9 but we have 8. So we could've added an extra layer for accumulate after adding without increasing the time a lot

	1	2	3	4	5	6	7	8	7	6	5	4	3	2	1
b_6	b_{14}	b_3	b_{12}	b_{11}	b_{10}	b_9	b_2	b_7	b_6	b_5	b_1	b_3	b_2	b_1	b_0
	IP	2P	IF	IF	IF	2F	2F	2F	2F	2F	IF	IF	IF	IF	IP
				IP	2P		IP	2P	IP		2P	IP			

1	3	2	3	5	4	5	6	5	3	4	3	2	1	1	
IP	IF	2P	IF	IF	IF	IF	2F	IF	IF	IF	IF	IF	IF	IF	IP
				2P	IP	IF		2P		IP					

→ $1+2+2=5 > 4$ DO USE HA

2	1	3	2	4	4	4	3	4	2	3	2	1	1	1	
2P	IP	IF	2P	IF	IF	IF	IF	2F	2P	IF	IF	IF	IF	IF	
				IP	IP	IP		IP							

2	2	1	3	3	3	3	2	2	3	2	1	1	1	1	
2P	2P	IP	IF	IF	IF	IF	IF	IF	IF	IF	IF	IF	IF	IF	

capacity now is 2

2	1	1	1	1	
---	---	---	---	---	--

need to add only these wires now
 ⇒ add new bits to add 11 bits

DATA MULTIPLIER

- to reduce delay we minimize the no. of electronics used, rather pass through and no delay
- goal now is not wire reductⁿ rather reduce the stage delay
- FA has more delay than HA, so we aren't reluctant to use HA now

- Be wire reductⁿ capability of

FA = 2 (3 → 1 at same place)

HA = 1

- At every stage

even part managed by FA

odd part ——— by HA

(unnecessary bits by HA not generated)

if within the capacity of next layer pass through don't use FA)

→ capacity becomes capacity of current layer - no. of carries from previous stage

$b_{15} \ b_{14} \ b_{13} \ b_{12} \ b_{11} \ b_{10} \ b_9 \ b_8 \ b_7 \ b_6 \ b_5 \ b_4 \ b_3 \ b_2 \ b_1 \ b_0$

1 2 3 4 5 6 7 8 7 6 5 4 3 2 1
IP 2P 3P 4P 6P IF IF IF III 6P 5P 4P 3P 2P IP
3P III IH 5P
3P 3P

Slot available = $(6-1) = 5$
→ 3 need to be reduced
→ IH + IF

Slot available = 6
→ 1 needs to be reduced
→ III

1 2 3 4 6 6 6 6 6 6 5 4 3 2 1
IP IP IP IF 2F 2F 2F 2F 2F IF IH 4P 3P 2P IP
IH

TUTORIAL

10.107.90.71/72

EE671-16

P/W: EE671 → change P/W: PSSWD

→ login to cluster

→ 4 levels of metal → SCL process

15/10

Dada:

- use minimum no. of addlers
- of smallest size to reduce the no. of wires to the capacity

Disadv: since we don't pass through all the time, we don't get a narrow addler

→ the wires arriving late is passed through to reduce worst case delay

→ since multiplication is shift and add we add one more wire to the set of that we add also simultaneously

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1
								1H	GP	SP	4P	3P	2P	1P


-
- needs to be recirculating and buffer since they keep multiplying with A

17/20

$a_3 \ a_2 \ a_1 \ a_0 \rightarrow$ repeated multiple times
 $b_3 \ b_2 \ b_1 \ b_0$ and is 4 times faster compared to B

$$\begin{array}{ccccccc}
 & c_3 & & & & & \\
 & \swarrow & & \leftarrow c_2 & & \leftarrow c_1 & \\
 a_3 b_0 & & a_2 b_0 & & a_1 b_0 & & a_0 b_0 \\
 \downarrow c_6 & & \downarrow s_2 & & \downarrow s_4 & & \downarrow s_1 \\
 a_3 b_1 & & a_2 b_1 & & a_1 b_1 & & a_0 b_1 \\
 & & & & \downarrow s_5 & & \\
 a_2 b_3 & a_2 b_2 & a_2 b_1 & a_2 b_0 & & & \\
 & & & & \downarrow s_4 & & \downarrow s_0 \\
 a_3 b_3 & a_3 b_2 & a_3 b_1 & a_3 b_0 & a_2 b_0 & & \\
 \hline
 \end{array}$$

→

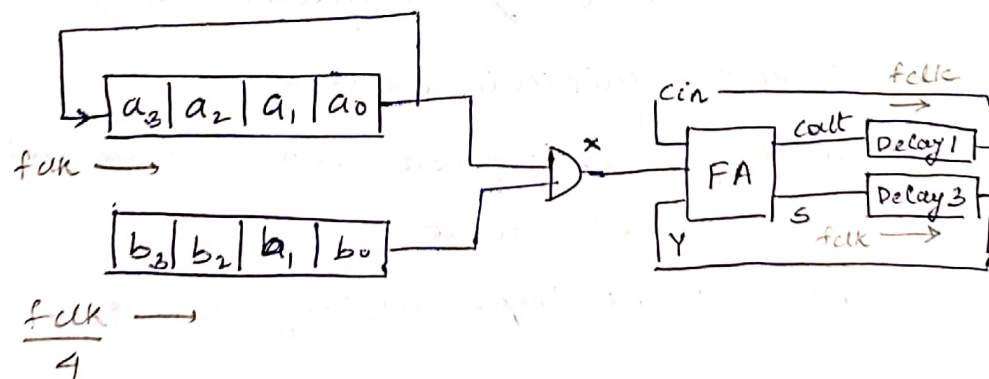

- Scanned by CamScanner

- We need to add a reset to the carry store since ~~the 1st row~~ doesn't need a carry.
- $a_0 b_0$ taken out 3 clks later
- However, $a_2 b_1$ is made by adding carry c_3 and carry c_6 , hence we need to add a mux whether to choose sum or carry to be sent again to the FA. The MUX takes carry at multiples of M . Also during these times, take out the sum
- The result arrives $M \times N$ clock cycles later

ROW-SERIAL MULTIPLIER

- The adder used for $a_0 b_0$ is used only once (if adder added only 1 place value terms). Hence, we keep shifting the place value terms a given adder adds
- Result available at $M+N$
- In the process, a given adder gets the same a_i throughout
Place value keeps increasing due to b_i
- Double precision multiplier (using control flow)

$$\begin{array}{rcl} \rightarrow & \begin{array}{l} P \text{ } Q \\ R \text{ } S \end{array} & \equiv \begin{array}{l} 2^n P + Q \\ 2^n R + S \end{array} \end{array}$$

$$\begin{array}{rcl} \rightarrow & -P = 2^n - P & \Rightarrow \begin{array}{l} -P \\ \times Q \end{array} \equiv \begin{array}{r} 2^n - P \\ Q \\ \hline 2^n Q - PQ \end{array} \end{array}$$