

EE 611

Course on Passive microwave circuits
Microwave integrated circuits

EE 611

5/1/19

- wave nature
- comparative wavelength
- parasitics (L, C present)


We can apply Maxwell's Law,
but that would be too complicated.

Elements which only be realized using distributed elements

- ① Circulators
- ② Couplers
- ③ Tee

Intermediate theory: Somewhat like Kirchoff's law with some part of Maxwell's law.

capacitance connected in shunt.

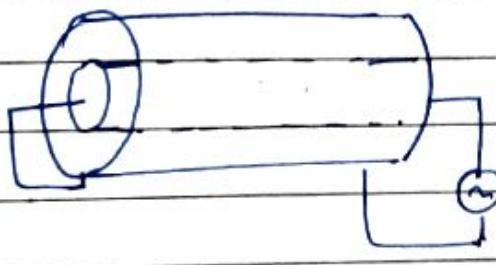

$$\begin{aligned} v_p &= \frac{\lambda}{T} = \frac{\omega}{B} \\ &= \frac{2\pi}{T} \cdot \frac{\lambda}{2\pi/B} \\ v_p &= \frac{c}{\sqrt{\epsilon_r/\mu_r}} \end{aligned}$$



Skin effect: depth of penetration of wave in conductor decreases with increase in the frequency.

$$\delta = \sqrt{\frac{2}{\omega \mu_r}} \rightarrow \text{for perfect conductor } \sigma \rightarrow \infty \Rightarrow \delta \rightarrow 0$$

$$L = \frac{\mu_r}{C \epsilon_r C^2}$$

Passive microwave devices:
 devices that do not produce power of their own. They have
 a gain either equal to or less than 1.
 eg: coupler, filters, attenuation.

EM theory with circuit theory.

S parameters will be used

in Distributed circuit theory, we'll be dealing with.


- ① Transmission lines
- ② open circuit stub
- ③ coupled lines
- ④ short circuit stub
- ⑤ tapered lines

Guided wave systems: (forms the basis of any transmission line)

- ① Two or more conductor systems

→ coaxial cable

→ Telegraph lines

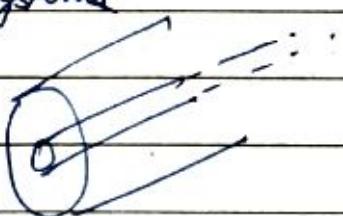

- ② Closed metallic wave guides consisting of hollow conductive pipes.

→ rectangular waveguides

→ cylindrical waveguides



- ③ Dielectric slabs enclosed by metallic sheets



pozar ch-2

- units important here]

→ go through solution of Maxwell's eqn again.

these derivations apply
for cartesian coordinate system.
Page

Maxwell's Laws:

$$\nabla \cdot \vec{D} = \rho$$

\vec{D} comes from Gauss's Law

$$\nabla \cdot \vec{B} = 0$$

\vec{E} comes from force/charge

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$$

$$\vec{D} = \epsilon \vec{E}$$

$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{B}}{\partial t}$$

$$\nabla \times \nabla \times \vec{E} = -\frac{\partial}{\partial t} (\nabla \times \vec{B})$$

$$\nabla^2 \vec{E} - \mu \epsilon \frac{\partial^2 \vec{E}}{\partial t^2} = 0$$

} assuming time dependence to be sinusoidal

$$\nabla^2 \vec{H} - \mu \epsilon \frac{\partial^2 \vec{H}}{\partial t^2} = 0$$

$$\rightarrow \vec{E}(x, y, z, t) = \text{Re}[\vec{E}(x, y, z) e^{j\omega t}]$$

$$\rightarrow \vec{H}(x, y, z, t) = \text{Re}[\vec{H}(x, y, z) e^{j\omega t}]$$

after eliminating time dependence

$$\nabla^2 \vec{E} + \mu \epsilon \omega^2 \vec{E} = 0, \quad \nabla^2 \vec{H} + \mu \epsilon \omega^2 \vec{H} = 0$$

$$\nabla^2 = \frac{\partial^2}{\partial x^2} + \frac{\partial^2}{\partial y^2} + \frac{\partial^2}{\partial z^2}$$

Helmholtz equation


Types of Solution for Helmholtz equations:

1. TEM waves, $E_z, H_z = 0$ → exists only when 2 or more

conductor wave guides

e.g. coaxial cable

→ micro strip line

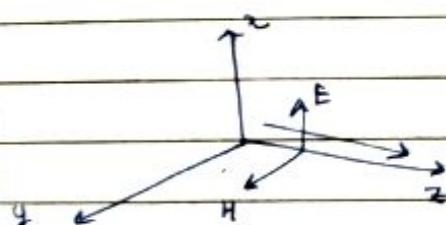


2. TE waves, $E_z = 0, H_z \neq 0$
 3. TM waves, $H_z = 0, E_z \neq 0$

can exist in 2 or more
as well as single conductor
wave guides

$\rightarrow E, B$ in coaxial cable,


→ 2 wire conductor,

→ Micro strip line,

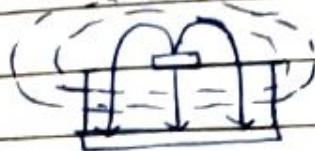

* Parallel plate waveguide:

① TEM wave solution

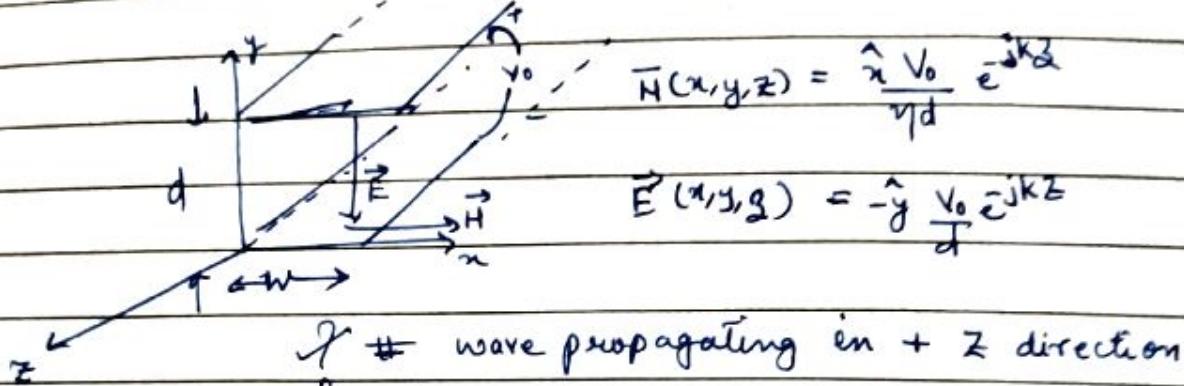

$$\vec{H}(x,y,z) = \hat{x} \frac{V_0}{\eta d} e^{-jkz}$$

$$\vec{E}(x,y,z) = -\hat{y} \frac{V_0}{d} e^{-jkz}$$

wave propagating in + z direction

$$\eta = \sqrt{\frac{\mu_0}{\epsilon_0}} = 377 \Omega \text{ (impedance offered by atm or vacuum)}$$

② TM wave

$$\vec{E}_z(x,y,z) = A_n \sin n\pi y \frac{e^{-jBz}}{d}$$

$$H_x(x,y,z) = \frac{j\omega \epsilon}{k_c} \frac{A_n}{d} \cos n\pi y \frac{e^{-jBz}}{d}, \quad n \text{ takes}$$

0 → solution as TM₀

$$E_y = \frac{-dB}{k_c} A_n \cos \left(\frac{n\pi y}{d} \right) \times e^{-jBz}$$

1
2

TM₁
TM₂

$$E_x = H_y = 0, k_c = \frac{n\pi}{d}$$

$$k = \frac{2\pi}{\lambda} \rightarrow p = \sqrt{k^2 - k_z^2} \rightarrow \text{tve only for certain values of } \omega.$$

if B imaginary, sinusoidal not attained, ⇒ evanescent modes

now, $k > k_c$

$$\rightarrow \omega \sqrt{\mu \epsilon} \geq k_c \quad \& \quad \frac{1}{\sqrt{\mu \epsilon}} = c$$

$$\frac{\omega}{c} > k_c$$

$$\frac{2\pi f}{c} > k_c$$

$$\Rightarrow f \geq \frac{c k_c}{2\pi}$$

(concept of cut-off freq. - watt exists for TM waves)


certain frequencies won't give solution

→ there exist a electro magnetic band gap.

→ Solve for TE mode

(assignment)

→ Rectangular waveguide

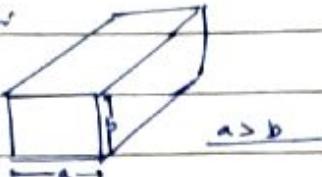

Solution for TE mode:

$$H_z(x, y, z) = A_{mn} \cos\left(\frac{m\pi x}{a}\right) \cos\left(\frac{n\pi y}{b}\right) e^{-jBz}$$

$$E_x = \frac{j\omega \mu_0 n \pi}{k_c^2 b} A_{mn} \cos\left(\frac{m\pi x}{a}\right) \sin\left(\frac{n\pi y}{b}\right) e^{-jBz}$$

$$k_c^2 \text{ given by } , k_c^2 = \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2$$

(∴ m, n two dimensions present)

modes will be like, TE₁₀, TE₁₁ etc.

mode with the lowest cut off frequency is called the dominant mode.

→ which of TE₁₀ or TM₁₀ is dominant (parallel)

→ in case of rect. w.g. TE₁₀ is dominant mode.


$$\beta = \sqrt{k^2 - k_c^2}, \quad k = \omega \sqrt{\mu \epsilon}$$

$$\begin{aligned} \beta &= \sqrt{\omega^2 \mu \epsilon - k_c^2} = \sqrt{\mu \epsilon} \sqrt{\omega^2 - \frac{k_c^2}{\mu \epsilon}} \\ &= \sqrt{\mu \epsilon} \sqrt{\omega^2 - (k\pi f_c)^2} = \sqrt{\mu \epsilon} \sqrt{\omega^2 - \omega_c^2} \end{aligned}$$

$$\beta = \sqrt{\mu \epsilon} \sqrt{\omega^2 - \omega_c^2}, \quad \beta \text{ being a measure of spatial frequency}$$

$$\beta = \frac{2\pi}{\lambda g}$$

quiz

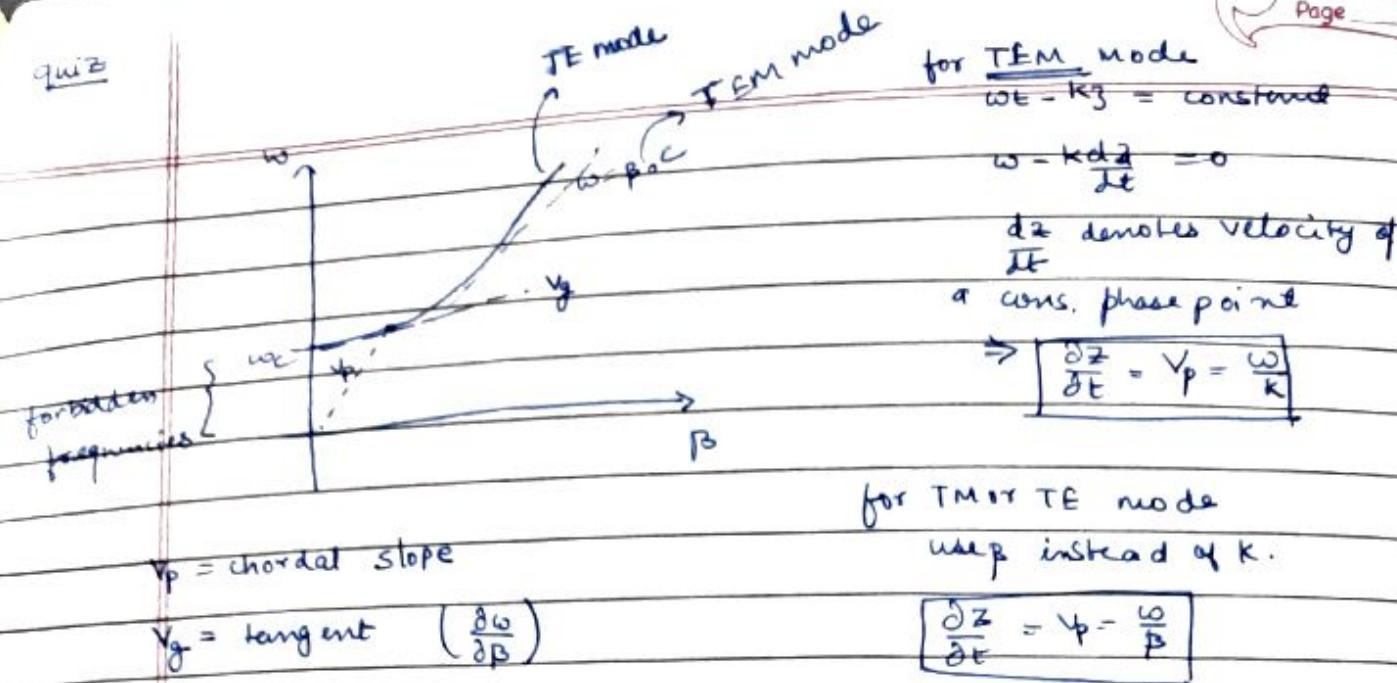

6/8/19

9/8/19

13/8/19

Tuesday Lecture 5

CLASSMATE


Date _____
Page _____

$$Z_{IN} = Z_0 \cdot \left(\frac{Z_L + Z_0 \tanh(\beta l)}{Z_0 + Z_L \tanh(\beta l)} \right)$$

$$\Gamma(l) = \frac{V^-(l)}{V^+(l)} = \frac{Z_L - Z_0}{Z_0 + Z_L}$$

Reflection coefficient

$$\Gamma(x) = \frac{V^-(x)}{V^+(x)}$$

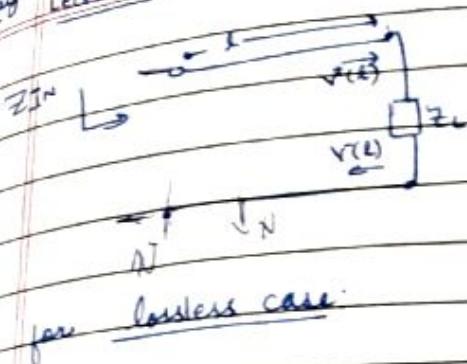

$$\gamma = jB, \alpha = 0$$

$$Z_{IN} = Z_0 \cdot \left(\frac{Z_L + Z_0 \tanh(j\beta l)}{Z_0 + Z_L \tanh(j\beta l)} \right) = Z_0 \cdot \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$

$$\rightarrow \beta l \rightarrow \beta l + \pi \quad (\because \tan(\beta l))$$

$$\rightarrow \frac{2\pi}{\lambda} l \rightarrow \frac{2\pi}{\lambda} l + \pi$$


$$\rightarrow \frac{2\pi}{\lambda} (l + \frac{\lambda}{2}) \rightarrow \text{(repeats after } \frac{\lambda}{2} \text{)} \quad \left. \begin{array}{l} \text{doesn't happen with lump} \\ \text{elements} \end{array} \right\}$$

$$\rightarrow \frac{2\pi f}{\nu_p} l \rightarrow \frac{2\pi f}{\nu_p} l + \pi$$

lossless being
transmission line periodic in
frequency, electrical length
as well as in length

* Special cases of lossless transmission line:


1. Shorted line, $Z_L = 0$, $Z_{IN} = jZ_0 \tan(\beta l)$

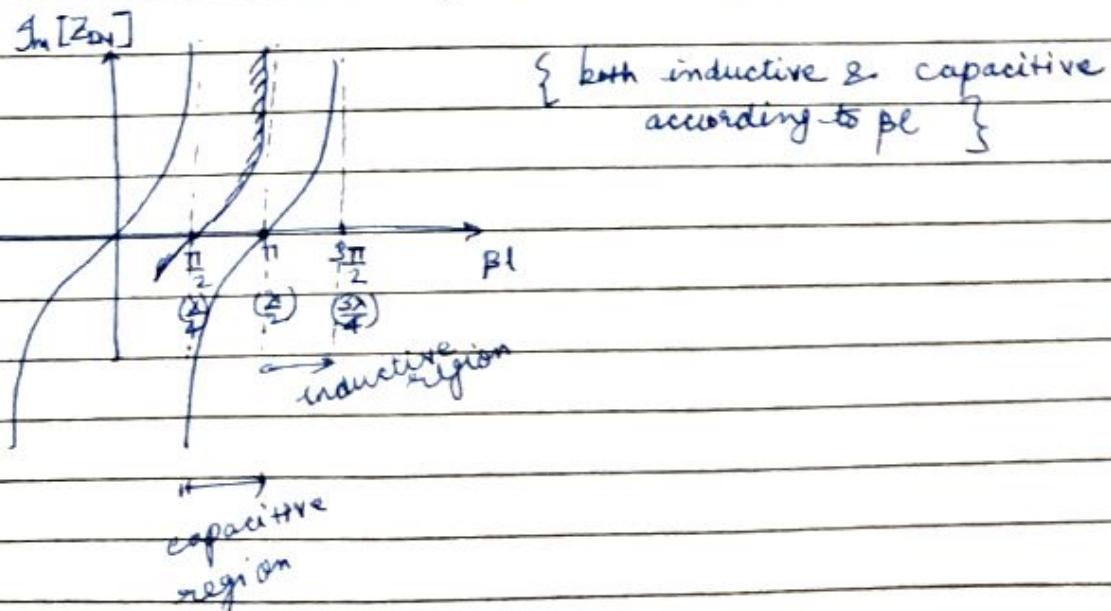 $\Im[Z_{IN}]$ 

T-line

② open, $Z_L = \infty$, $Z_{IN} = jZ_0 \tan \beta L$, $Z_{IN} = -jZ_0 \cot(\beta L)$

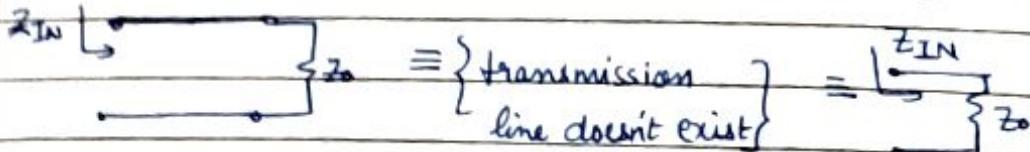③ Matched load line, $Z_L = Z_0$, $Z_{IN} = Z_0 \cdot \frac{(1 + j \tan \beta L)}{1 + j \cot \beta L} = Z_0$



④ Quarterwave transformer (T-line of length $\frac{\lambda}{4}$ for certain wavelength)

$\therefore \beta L = \frac{\lambda}{4}, \Rightarrow Z_{IN} = \frac{Z_0^2}{Z_L} = \frac{Z_0^2}{R_L}$

$\left\{ Z_{IN} \propto \frac{1}{R_L} \right\}$

Reflection coefficients:

$T(x) = \frac{Y^-(x)}{V_0^+(x)}$

$= \frac{V_0^- e^{j\gamma x}}{V_0^+ e^{-j\gamma x}} = \frac{V_0^- e^{+2j\gamma x}}{V_0^+}$

$T(d) = \frac{V_0^- e^{2j\gamma(d-d)}}{V_0^+}$

$= \frac{V_0^- e^{j\gamma t}}{V_0^+ e^{-j\gamma t}} e^{-2j\gamma d}$

now, $\gamma = \alpha + j\beta$


\because lossless, $\therefore \alpha = 0 \Rightarrow \gamma = j\beta$.

and if $\Gamma(x) = |\Gamma(x)| e^{j\phi_x}$

$\boxed{\Gamma(d) = \Gamma(0) e^{-2j\gamma d}}$


Reflection coefficient
at the load

$\boxed{\Gamma(d) = |\Gamma(0)| e^{j(\alpha t - 2\beta d)}}$

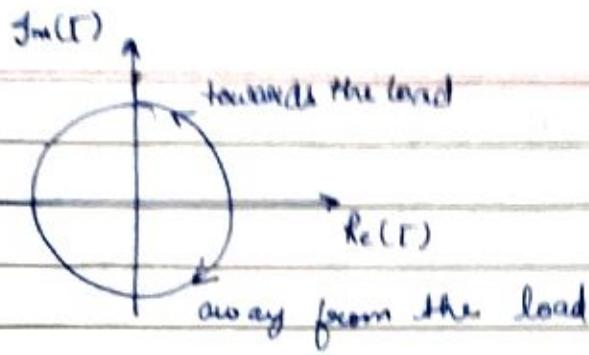

1/1
Final page
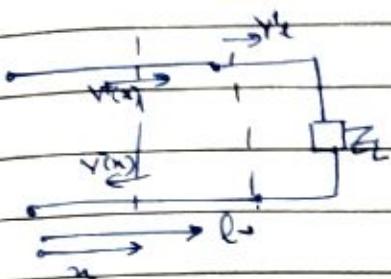
$$V(d) = V_L^+ e^{j\beta d} + V_L^- e^{-j\beta d}$$



$$Z(x) = \frac{V(x)}{I(x)} = \frac{V(u) + V(w)}{\frac{V(u) - V(w)}{Z_0}} = Z_0 \left[\frac{1 + \Gamma(x)}{1 - \Gamma(x)} \right]$$

$$\Gamma(x) = \frac{Z(x) - Z_0}{Z(x) + Z_0}, \text{ at } l, \Gamma(l) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$(\because Z(l) = Z_L)$$

Power delivered to load Z_L is

$$P_L = \frac{1}{2} \operatorname{Re} \{ V I^* \} = \frac{1}{2} \operatorname{Re} \left\{ (V_L^+ + V_L^-) \left(\frac{V_L^+ - V_L^-}{Z_0} \right)^* \right\}$$


$$P_L = \frac{1}{2} \left(\frac{|V_L^+|^2}{Z_0} - \frac{|V_L^-|^2}{Z_0} \right) = \underbrace{\frac{1}{2} \frac{|V_L|^2}{Z_0} (1 - |\Gamma(l)|^2)}_{P^+ (\text{power of the incident wave})} = P^+ (1 - |\Gamma(l)|^2)$$

$$\text{if } \Gamma(l) = 0 \Rightarrow P_L = P^+ \quad \{ \text{matched network} \}$$

* Smith Chart transforms Z to Γ , $\Gamma = \frac{Z - Z_0}{Z + Z_0}$ (Bilinear transformation)

$$\Gamma = \frac{\frac{Z}{Z_0} - 1}{\frac{Z}{Z_0} + 1} = \frac{z - 1}{z + 1}, \quad z = r + jx \quad \begin{matrix} \rightarrow \text{normalized resistance} \\ \rightarrow \text{normalized reactance} \end{matrix}$$

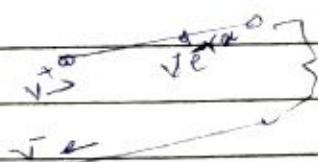→ by doing this all passive impedances on Right half plane of Z coordinates are mapped inside the unit circle.



ratio of voltage along a line is transmission line to line

(VSWR) Voltage standing wave ratio

$$\text{VSWR} = \frac{1 + |\Gamma(\omega)|}{1 - |\Gamma(\omega)|}, \quad \text{VSWR} < 2 \text{ is considered as a good design}$$

$$V(x) = V_0^+ e^{-jBx} + V_0^- e^{+jBx}$$

$$= V_0^+ e^{-jBx} (1 + |\Gamma| e^{j\alpha' + 2jBx})$$

$$|\Gamma(\omega)|_{\max} = V_0^+ (1 + |\Gamma|) \quad \alpha' + 2Bx = 2\pi$$

$$|\Gamma(\omega)|_{\min} = V_0^+ (1 - |\Gamma|) \quad \alpha' + 2Bx = \pi$$


16/8/19

Lectures

Broadband impedance matching

narrowband matching: matching for just a single frequency

What we defined matching earlier was $\Gamma=0$ but this is not easy to get, so we design a Γ_m , such that if $|\Gamma| \leq \Gamma_m$ then we say that circuit is matched.

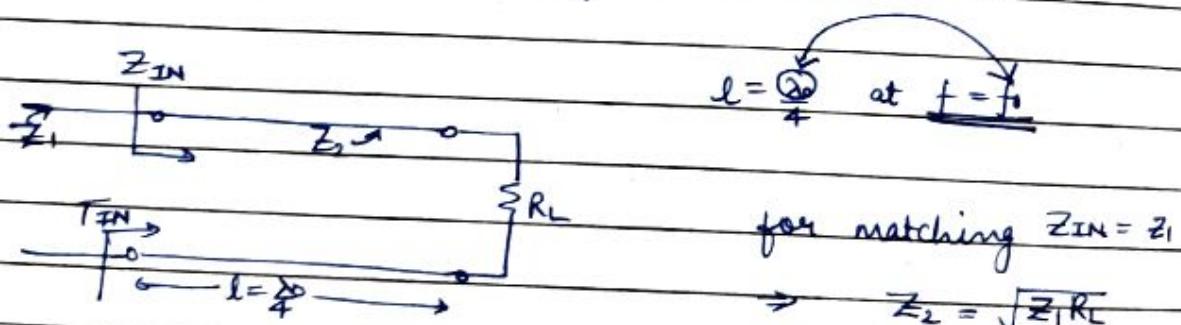

now above result holds only for certain frequency.

$$Z_{IN} = Z_2 \cdot \left(\frac{R_L + j Z_2 \tan \beta l}{Z_2 + j R_L \tan \beta l} \right), \quad \beta l = \frac{2\pi}{\lambda} \cdot \left(\frac{\lambda_0}{4} \right)$$

$$\text{at } \lambda = \lambda_0 \Rightarrow Z_2 = \sqrt{Z_1 R_L}$$

$$\text{at } \lambda \neq \lambda_0$$

$$\Gamma_{IN} = \frac{Z_{IN} - Z_1}{Z_{IN} + Z_1}$$

why not Z_2 ?
because Z_1 feed line.

$$\Gamma_{IN} = \frac{Z_2 R_L + j Z_2^2 \tan \beta l - Z_1 Z_2 - j Z_1 R_L \tan \beta l}{Z_2 R_L + j Z_2^2 \tan \beta l + Z_1 Z_2 + j Z_1 R_L \tan \beta l}$$

putting $Z_2 = \sqrt{Z_1 R_L}$

$$\Gamma_{IN} = \frac{R_L - Z_1}{R_L + Z_1 + j 2 \sqrt{Z_1 R_L} \tan \beta l}$$

$$|\Gamma_{IN}| = \frac{R_L - Z_1}{\sqrt{(R_L - Z_1)^2 + 4 R_L Z_1 + 4 R_L Z_1 \tan^2 \beta l}} = \frac{R_L - Z_1}{\sqrt{(R_L - Z_1)^2 + 4 R_L Z_1 \sec^2 \beta l}}$$

$$|\Gamma_{IN}| = \frac{1}{\sqrt{1 + \frac{4 R L Z_1 \sec^2 \beta l}{(R_L - Z_1)^2}}}, \quad \beta l = \frac{\pi f}{2} \frac{l}{\lambda_0}$$

at $f = 0$, $|\Gamma_{IN}| = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L$

assuming operation
near design frequency,
neglect. $\beta l \approx \pi / 2 \Rightarrow \sec^2 \beta l \gg 1$

at $f = f_0$, $|\Gamma_{IN}| = 0$.


$$\Rightarrow |\Gamma_{IN}| \approx \frac{|R_L - Z_1| \cos \beta l}{2 \sqrt{Z_1 R_L}}$$

$|\Gamma_{IN}|$ such that $R_L = \infty$

* $|\Gamma_D| = 1$

Γ_m

matching threshold

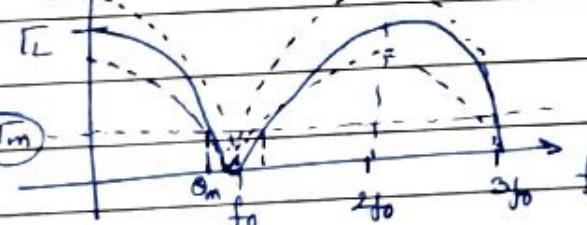

$\Delta\theta$ if axis on θ scale.

Bandwidth = $2\Delta\theta$

$$\Delta\theta = \frac{\pi}{2} - \theta_m$$

$$\Gamma_{IN}(\theta = \theta_m) = \Gamma_m$$

Fractional bandwidth = $\frac{2\Delta\theta}{\theta_0 (\frac{\pi}{2})}$

it is a measure
of quality of matching

$$= \frac{2(\frac{\pi}{2} - \theta_m)}{\theta_0} = \boxed{2 - \frac{4}{\pi} \theta_m}$$

$$\Gamma_{IN}(0) = \frac{1}{\sqrt{1 + \frac{4R_L Z_1}{(R_L - Z_1)} \sec^2 \theta}}$$

$$\Gamma_m = \left| \Gamma_{IN}(0) \right|_{\theta=0} = \sqrt{\frac{1}{1 + \frac{4R_L Z_1}{(R_L - Z_1)^2}} \sec^2 \theta_m} = \frac{|R_L - Z_1|}{\sqrt{(R_L - Z_1)^2 + 4R_L Z_1 \tan^2 \theta_m}}$$

$$(R_L - Z_1)^2 = \Gamma_m^2 \left((R_L - Z_1)^2 + 4R_L Z_1 \tan^2 \theta_m \right)$$


$$-4R_L Z_1 \sec^2 \theta_m = (R_L - Z_1)^2 \left[1 - \frac{1}{\Gamma_m^2} \right]$$

$$\sec^2 \theta_m = \frac{(R_L - Z_1)^2}{4R_L Z_1} \left[\frac{1}{\Gamma_m^2} - 1 \right]$$

$$\operatorname{Diss} \theta_m = \frac{2\sqrt{Z_1 R_L}}{|R_L - Z_1|} \cdot \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}}$$

θ_m can be found & so fractional b-w can be found.

Multi Section transformer:

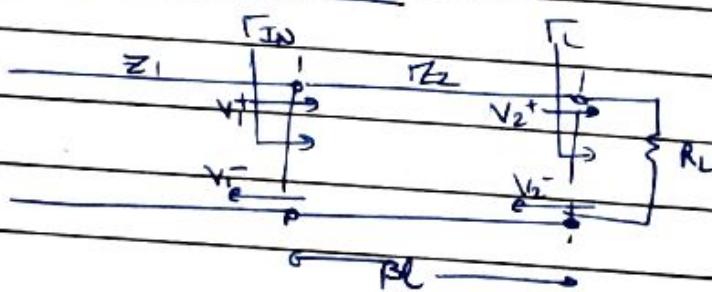

$$V_2 = V_2^+ + V_2^-$$

$$V_1 = V_1^+ + V_1^- = V_2^+ e^{j\beta l} + V_2^- e^{-j\beta l}$$

$$\Rightarrow V_1^+ \left[1 + V_1^- \right] = V_2^+ e^{j\beta l} \left(1 + \frac{V_2^-}{V_2^+} e^{-j\beta l} \right)$$

$$\Rightarrow V_1^+ \left[1 + \Gamma_{IN} \right] = V_2^+ e^{j\beta l} \left(1 + \Gamma_L e^{-j\beta l} \right)$$

$$I_1 = \frac{V_1^+ - V_1^-}{Z_1} = V_2^+ e^{j\beta l} - V_2^- e^{-j\beta l}$$

(Z₂) ?

$$\frac{V_1^+}{Z_1} \left(1 - \Gamma_{IN} \right) = \frac{V_2^+ e^{j\beta l}}{Z_2} \left(1 - \Gamma_L e^{-j2\beta l} \right)$$

$$\frac{1 - \Gamma_{IN}}{1 + \Gamma_{IN}} = \frac{Z_1}{Z_2} \left(\frac{1 - \Gamma_L e^{-j2\beta l}}{1 + \Gamma_L e^{-j2\beta l}} \right) \quad \text{--- (1)}$$

$$-\Gamma_{IN} = \frac{\frac{Z_1}{Z_2} \left(\frac{1 - \Gamma_L e^{-j2\beta l}}{1 + \Gamma_L e^{-j2\beta l}} \right) - 1}{\frac{Z_1}{Z_2} \left(\frac{1 - \Gamma_L e^{-j2\beta l}}{1 + \Gamma_L e^{-j2\beta l}} \right) + 1}$$

$$y = x + ny \\ y(xn) = 1 - n$$

$$\Gamma_{IN} = \frac{z_2 - z_1 + \Gamma_L e^{j2\beta l}(z_1 + z_2)}{z_1 + z_2 + (z_2 - z_1)\Gamma_L e^{-j2\beta l}}$$

$$\Gamma_{IN} = \frac{z_2 - z_1}{z_2 + z_1} + \Gamma_L e^{j2\beta l}, \quad \Gamma_{21} = \frac{z_2 - z_1}{z_2 + z_1}$$

$$+ \frac{z_2 - z_1}{z_2 + z_1} \Gamma_L e^{-j2\beta l}$$

$$\boxed{\Gamma_{IN} = \frac{\Gamma_{21} + \Gamma_L e^{-j2\beta l}}{1 + \Gamma_{21}\Gamma_L e^{-j2\beta l}}}$$

if $z_2 = z_1$
 $\Rightarrow \Gamma_{21} = 0$
 $\Rightarrow \Gamma_{IN} = \Gamma_L e^{-j2\beta l}$


now in order to ignore second order reflections, we assume $z_2 = z_1$
close to zero $\Rightarrow \Gamma_{21} \rightarrow 0$

$$\Rightarrow \boxed{\Gamma_{IN} \approx \Gamma_{21} + \Gamma_L e^{-j2\beta l}}$$

Theory of small reflection

20/8/19 Lecture 7

to extend same theory to n no.

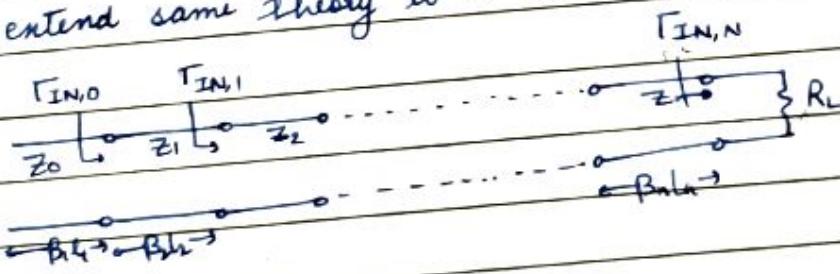

Let assume
 $B_i l_i = B_j l_j \quad \forall i, j \in \{1, 2, \dots, N\}$
 $= \theta$

$$\Gamma_{IN,0} = \Gamma_{IN,1} e^{-j2\beta l} + \Gamma_{10}$$

$$\Gamma_{IN,0}(\theta) = \Gamma_{IN,1} e^{-j2\theta} + \Gamma_{10}$$

$$, \quad \Gamma_{10} = \frac{z_1 - z_0}{z_1 + z_0} \quad \begin{matrix} \text{(measure of mismatch)} \\ \text{btw. } z_1 \text{ & } z_0 \end{matrix}$$

$$\Gamma_{IN,0}(\theta) = \Gamma_{10} + (\Gamma_{21} + \Gamma_{IN,2} e^{-j2\theta}) e^{-j2\theta}$$

$$= \Gamma_{10} + \Gamma_{21} e^{-j2\theta} + \Gamma_{IN,2} e^{-j4\theta}$$

$$\Rightarrow \Gamma_{IN,0}(\theta) = \Gamma_{10} + \Gamma_{21} e^{-j2\theta} + \Gamma_{32} e^{-j4\theta} + \dots + \Gamma_{N,N-1} e^{-j2(N-1)\theta} + \Gamma_L e^{-j2N\theta}$$

where, $\boxed{\Gamma_L = \frac{R_L - Z_N}{R_L + Z_N}}$

terminology changed, $\Gamma_{k+1, k} = \Gamma_k$

$$\Gamma_{IN,0}(\theta) = T_0 + T_1 e^{-j2\theta} + T_2 e^{-j4\theta} + \dots + T_{N-1} e^{-j2(N-1)\theta} + T_N e^{-j2N\theta}$$

$$\Gamma_{IN,0}(\theta) = \sum_{k=0}^N \Gamma_k e^{-j2k\theta}$$

(self constrained solution)

$$\Gamma_{IN,0}(\theta=0) = \sum_{k=0}^N \Gamma_k \quad \left. \right\} \text{from eqn}$$

$$\Gamma_{IN,0}(\theta=0) = \frac{R_L - Z_0}{R_L + Z_0} \quad \left. \right\} \text{from intuition, } \because \text{zero electrical length.}$$

$$\sum_{k=0}^N \Gamma_k - \sum_{k=0}^N \frac{Z_{k+1} - Z_k}{Z_{k+1} + Z_k} = \frac{Z_1 - Z_0 + \dots + \frac{R_L - Z_N}{R_L + Z_N}}{Z_1 + Z_0}$$

(✓) intuition \neq equation (we used single reflection approximation in eqn)

$$\Gamma_k = \frac{Z_{k+1} - Z_k}{Z_{k+1} + Z_k} \approx \frac{Z_{k+1} - Z_k}{2Z_k} \approx \frac{1}{2} \ln \left(1 + \frac{Z_{k+1} - Z_k}{Z_k} \right) = \frac{1}{2} \ln \left(\frac{Z_{k+1}}{Z_k} \right)$$

$$\Gamma_k \approx \frac{1}{2} \ln \left(\frac{Z_{k+1}}{Z_k} \right) \quad \therefore \left. \right\} \ln(1+x) = \underline{x} - \frac{x^2}{2} + \dots$$

$$\Gamma_{IN,0}(\theta) = \sum_{k=0}^N \Gamma_k e^{-j2k\theta}, \text{ at } \theta=0 \Rightarrow \Gamma_{IN,0}(0) = \sum_{k=0}^N \Gamma_k$$

$$\Gamma_{IN,0}(0) = \frac{1}{2} \ln \left(\frac{Z_1}{Z_0} \cdot \frac{Z_2}{Z_1} \cdot \frac{Z_3}{Z_2} \cdots \frac{R_L}{Z_N} \right) = \frac{1}{2} \ln \left(\frac{R_L}{Z_0} \right)$$

$$\boxed{\Gamma_{IN,0}(0) = \frac{1}{2} \ln \left(\frac{R_L}{Z_0} \right)} \quad \left. \right\} \text{multisection transform}$$


DNE PROBLEM in MIDSEM from SYNTHESIS

SYNTHESIS:

Prototype functions: functions that provide a template for how response should be.

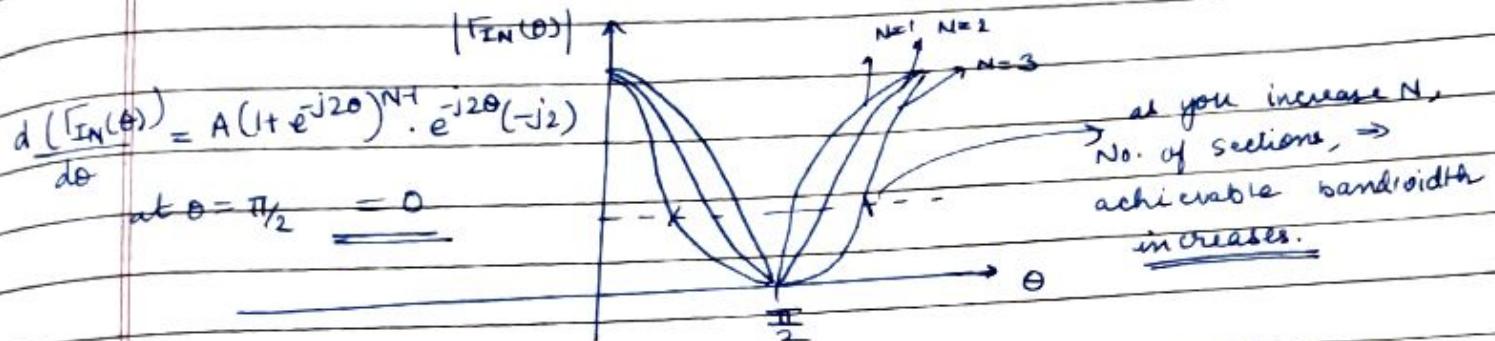1. Binomial function: (maximally flat)

$$\Gamma_{IN}(\theta) = A(1 + e^{-j2\theta})^N$$



$\frac{d^k \Gamma_{IN}(\theta)}{d\theta^k} = 0$ at $\theta = \frac{\pi}{2}$ (maximally flat; not only fn zero but its derivatives too zero.)

eg:



$$\text{at } \theta = 0, \Gamma_{IN}(0) = \frac{R_L - Z_0}{R_L + Z_0} = \Gamma_L$$

$$\text{and } \Gamma_{IN}(\theta=0) = A(2)^N$$

$$\Rightarrow A = \frac{\Gamma_L}{2^N}$$

$$\Gamma_{IN}(\theta) = \frac{1}{2^N} \Gamma_L (1 + e^{-j2\theta})^N$$

$$\Rightarrow |\Gamma_{IN}(\theta)| = \frac{1}{2} |\Gamma_L| \left| e^{-j\theta N} \right| \cdot \left| e^{j\theta} + e^{-j\theta} \right|^N = \frac{1}{2} |\Gamma_L| |2 \cos \theta|^N$$

$$= |\Gamma_L| |\cos \theta|^N$$

$$\text{at } \theta = \theta_m = |\Gamma_{IN}(\theta)| = \Gamma_m, \quad \left| \Gamma_m = |\Gamma_L| (\cos \theta_m)^N \right| \quad \left\{ \begin{array}{l} \therefore \theta_m < \frac{\pi}{2} \\ |\cos \theta_m| = \cos \theta_m \end{array} \right\}$$

$\rightarrow \theta_m \text{ found}$

$$\frac{\Delta f}{f} = 2 - \frac{4\theta_m}{\pi} \quad \left\{ \begin{array}{l} \text{fractional} \\ \text{BW can be} \\ \text{found.} \end{array} \right.$$

This will give us N, i.e. no. of sections used from graph above, now we need to synthesize.

$$\Gamma_{IN}(s) = \sum_{k=0}^N \Gamma_k e^{-j2k\theta}$$

$$\Gamma_{IN}(s) = 2^{-N} \Gamma_L (1 + e^{-j2\theta})^N = 2^{-N} \Gamma_L \sum_{k=0}^N \binom{N}{k} e^{-j2k\theta}$$

$\Rightarrow \boxed{\Gamma_k = 2^{-N} \Gamma_L \binom{N}{k}}$ got this using used prototype fn.
diff. Prototype fn. gives diff. values.


e.g. say, $N=3$, $\Gamma_1 = 2^3 \Gamma_L \binom{3}{1}$, $\Gamma_2 = 2^3 \Gamma_L \binom{3}{2}$

Properties:

Symmetry: $\Gamma_1 = \Gamma_{N-1}$, $\Gamma_0 = \Gamma_N$

All Γ_k 's either all +ve or all -ve. , $\Gamma_k = \frac{Z_{k+1} - Z_k}{Z_{k+1} + Z_k}$

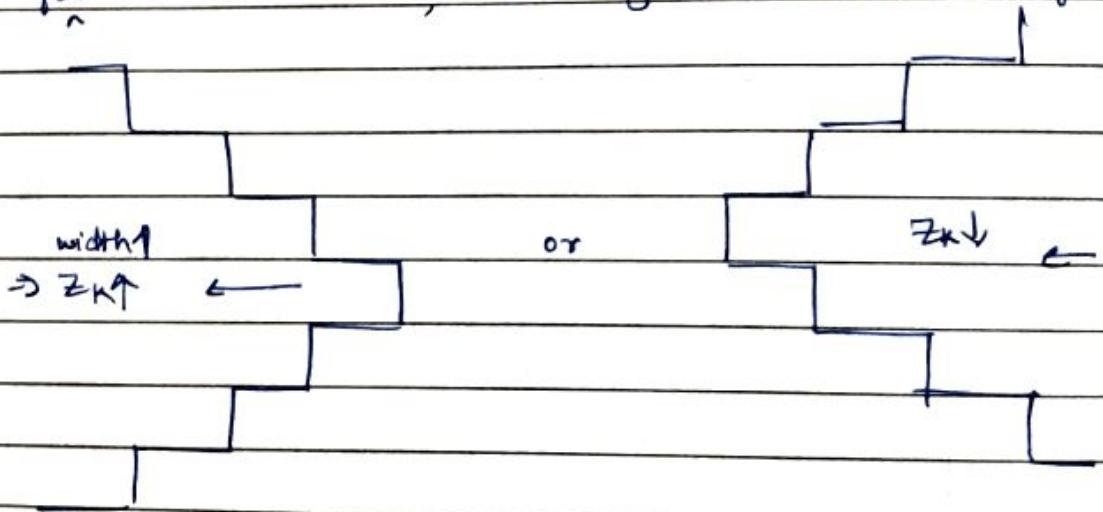now for $\underset{\text{all}}{+ve}$ or $-ve$, matching network either of two,



* $\Gamma_k = 2^{-N} \binom{N}{k} \Gamma_L$, $\Gamma_k = \frac{1}{2} \ln \left(\frac{Z_{k+1}}{Z_k} \right)$ for $N=2$

$$\Gamma_L = \frac{1}{2} \ln \left(\frac{R_L}{Z_0} \right)$$

$$\Rightarrow \ln \left(\frac{Z_{k+1}}{Z_k} \right) = 2^{-N} \binom{N}{k} \ln \left(\frac{R_L}{Z_0} \right)$$

Z_k found

*Date _____
Page _____*

$k=0$,

$$\ln\left(\frac{z_1}{z_0}\right) = \ln\left(\frac{R_L}{z_0}\right)^{\frac{1}{4}}$$

$k=1$,

$$\ln\left(\frac{z_2}{z_1}\right) = \ln\left(\frac{R_L}{z_0}\right)^{\frac{1}{2}}$$

$$z_1 = z_0 \left(\frac{R_L}{z_0}\right)^{\frac{1}{4}},$$

$$\boxed{z_1 = z_0 + R_L^{\frac{1}{4}}}$$

$$z_2 = z_1 \left(\frac{R_L}{z_0}\right)^{\frac{1}{2}}$$

$$z_2 = z_0^{\frac{3}{4}} R_L^{\frac{1}{4}} \times R_L^{\frac{1}{2}} z_0^{-\frac{1}{2}}$$

$$\boxed{z_2 = z_0^{\frac{1}{4}} R_L^{\frac{3}{4}}}$$

2. Chebyshev prototype function:


$$|\Gamma_{IN(\theta)}|$$

→ passband ripples allowed

as long as they are less than Γ_m

→ for even N there is a magnitude of Γ_m at $\theta = \frac{\pi}{2}$, for odd there is a null.

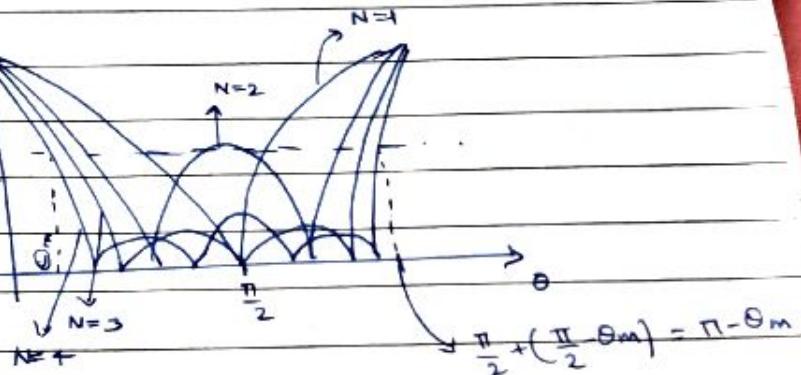→ for a given N , all ripples of the same height



$$B-\omega \Rightarrow (\theta_m, \pi - \theta_m)$$

Chebyshev functions:

$$T_N(x) = \cosh(N \cosh^{-1} x)$$

$$T_1(x) = x$$

$$T_2(x) = 2x^2 - 1$$

$$T_3(x) = 4x^3 - 3x$$

$$T_n(x) = 2x T_{n-1}(x) - T_{n-2}(x)$$

* $T(n\theta) = \cos(n\theta)$

for, $\theta \rightarrow (\theta_m, \pi - \theta_m)$

say $x = \frac{\cos \theta}{\cos \theta_m} = \cos \theta \sec \theta_m$

Why this divide

⇒ Chebyshev prototype fn:

$$\Gamma_n(\theta) = \frac{A e^{j n \theta}}{T_N(\sec \theta_m \cos \theta)} T_N(\sec \theta_m \cos \theta)$$


phase flexibility
magnitude flexibility.

for any transformation
we want to find $A(\text{mag}) \& N(\text{order/no. of secants})$

23/8/19

Lecture 8

Multi section X-mes

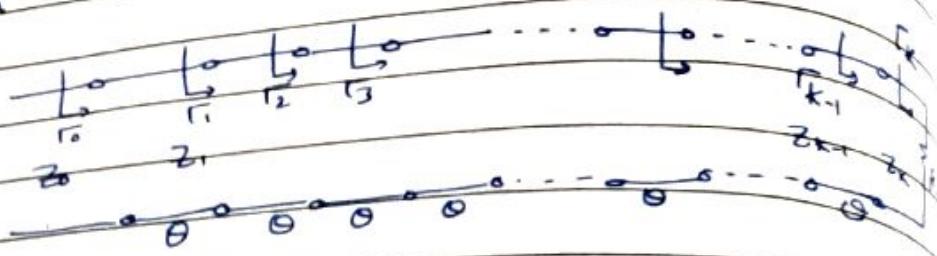

$$\Gamma_{IN}(\theta) = A e^{-jN\theta} T_N(\sec \theta_m \cos \theta)$$

$$\text{when } \theta=0, \Gamma_{IN}(\theta=0) = A T_N(\sec \theta_m)$$

$$\Gamma_{IN}(\theta=0) = \frac{R_L - Z_0}{R_L + Z_0} = \Gamma_L$$

$$\Rightarrow A = \frac{\Gamma_L}{T_N(\sec \theta_m)} \quad \text{--- (1)}$$

(poly. always real, Γ_L either +ve or -ve
So A always real)

$$\Gamma_{IN}(\theta=\theta_m) = A e^{-jN\theta}$$

$$|\Gamma_{IN}(\theta=\theta_m)| = \Gamma_m = |A| \quad \text{--- (2)} \quad (\Gamma_m \text{ always +ve})$$

$$T_N(x) = \cosh(N \cosh^{-1}(x))$$

$$\Gamma_m = |A| = \frac{|\Gamma_L|}{|T_N(\sec \theta_m)|} = \frac{|\Gamma_L|}{T_N(\sec \theta_m)}$$

$$T_N(\sec \theta_m) = \frac{|\Gamma_L|}{\Gamma_m}$$

$$\cosh(N \cosh^{-1}(\sec \theta_m)) = \frac{|\Gamma_L|}{\Gamma_m}$$

$$\Rightarrow \sec \theta_m = \cosh \left[\frac{1}{N} \cosh^{-1} \left(\frac{|\Gamma_L|}{\Gamma_m} \right) \right]$$

{ θ_m ✓ found
 $\frac{\Delta f}{f} = 2 \frac{4\theta_m}{\pi}$ can be found }

if N comes out to be 3/2
we take it as 4.

{ for you know B-W (from requirement)
You calculate θ_m
& then you calculate

Example

$N=3$

$\Gamma_{IN}(\theta) = \sum_{k=0}^3 \Gamma_k e^{-jk\theta}$ (from derivation)

$\Gamma_{IN}(\theta) = Ae^{-jN\theta} T_3 (\sec \theta \cos \theta) \quad \text{(from chebyshev)} \quad \textcircled{1}$

$T_3 (\sec \theta \cos \theta) = 8 \sec^3 \theta (\cos 3\theta + 3 \cos \theta) - 3 \sec \theta \cos \theta \quad \textcircled{2}$

put eqn \textcircled{2} in \textcircled{1} for, $\Gamma_{IN}(\theta) = Ae^{-jN\theta} [8 \sec^3 \theta \cos 3\theta + \cos \theta (3 \sec \theta - 3 \sec^3 \theta)] \quad \textcircled{3}$

also $\Gamma_{IN}(\theta) = \Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta} + \Gamma_3 e^{-j6\theta}$

suppose symmetric $\Rightarrow \Gamma_0 = \Gamma_3$
 $\Gamma_1 = \Gamma_2$

$\Gamma_{IN}(\theta) = \Gamma_0 (1 + e^{-j6\theta}) + \Gamma_1 (e^{-j2\theta} + e^{-j4\theta})$

$= \Gamma_0 e^{-j3\theta} (e^{j3\theta} + e^{-j3\theta}) + \Gamma_1 e^{-j3\theta} (e^{j\theta} + e^{-j\theta})$

$= \Gamma_0 e^{-j3\theta} (2 \cos 3\theta) + \Gamma_1 e^{-j3\theta} (2 \cos \theta)$

$= 2e^{-j3\theta} [\Gamma_0 \cos 3\theta + \Gamma_1 \cos \theta] \quad \textcircled{4}$

from \textcircled{3} & \textcircled{4}

$\Gamma_0 = \frac{A \sec^2 \theta}{2},$

$\Gamma_1 = \frac{3A}{2} [\sec^3 \theta - \sec \theta], \text{ now you know } \Gamma_0, \Gamma_1, \Gamma_2, \Gamma_3$

now you calculate Z_l once Γ_l is found for $l \in \{0, 1\}$

$\Gamma_0 = \frac{1}{2} \ln \left[\frac{Z_1}{Z_0} \right]$


$\Gamma_1 = \frac{1}{2} \ln \left[\frac{Z_2}{Z_1} \right]$

$\Gamma_2 = \frac{1}{2} \ln \left[\frac{Z_3}{Z_2} \right]$

$\Gamma_3 = \frac{1}{2} \ln \left[\frac{Z_L}{Z_3} \right] \xrightarrow{R_L}$

Japan Structure with infinite no. of multisections.

y:

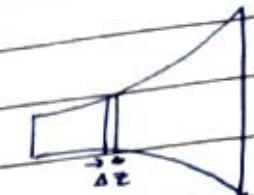elect length $\beta l \rightarrow \beta(k\Delta z)$

instead of Γ_k we can now take $d\Gamma$

$$\frac{Z(KA_2) - Z(L)}{Z(K+1) + Z(K)}$$

$$\frac{Z(S) + dZ - Z(Z)}{Z(Z) + dZ + Z(Z)}$$

$$d\Gamma \approx \frac{dZ(Z)}{2Z(Z)} = \frac{1}{2} \frac{d}{dz} \left(\ln \left(\frac{Z}{Z_0} \right) \right) dz \quad \text{--- ①}$$

$$\text{so, } \Gamma_{IN}(\beta l) = \sum_{k=0}^N \left(\Gamma_k \right) e^{-2\beta(KA_2)}$$

$$K_0 \rightarrow K(\beta A_2) \quad \begin{cases} S_0 \rightarrow B_1 \\ \beta A_3 \end{cases}$$

$$\Gamma_{IN}(\beta l) = \sum_{k=0}^N \Delta \Gamma(KA_2) e^{-2\beta(KA_2)}$$

$$\text{for } \Delta z \rightarrow 0, \Gamma_{IN}(l) = \int_{z=0}^L d\Gamma e^{-j2\beta z}$$

from:

$$\boxed{\Gamma_{IN}(l) = \frac{1}{2} \int_{z=0}^L e^{-j2\beta z} \left[\frac{d}{dz} \ln \left(\frac{Z(z)}{Z_0} \right) \right] dz} \quad \text{--- ②}$$

Total input
reflection coeff.
for Tapered

→ Prototype functions for tapered

Page No.

Date _____
Page _____

1. Exponential tapered:

$$Z(z) = Z_0 e^{az}$$

$$\frac{Z(z)}{Z_0} = e^{az}$$

$$\ln\left(\frac{Z(z)}{Z_0}\right) = az$$

$$\frac{d}{dz} \left[\ln\left(\frac{Z(z)}{Z_0}\right) \right] = a$$

$$\Rightarrow I_{IN}(L) = \frac{a}{2} \int_{z=0}^L e^{-2jBL} dz$$

$$= \frac{a}{2} \left[\frac{e^{-2jBL}}{-2jB} \right]_{z=0}^L$$

$$I_{IN}(L) = \frac{a e^{-jBL}}{-j4B} [-2 \sin(BL)] = \frac{a e^{-jBL}}{2jB} \sin(BL)$$

$$Z(z=0) = Z_0$$

$$Z(z=L) = Z_0 e^{aL} = R_L$$

$$a = \frac{1}{L} \ln\left(\frac{R_L}{Z_0}\right)$$

$$\Rightarrow I_{IN}(L) = \frac{1}{L} \ln\left(\frac{R_L}{Z_0}\right) e^{-jBL} \frac{\sin(BL)}{\frac{2j}{B}}$$

$$= \ln\left(\frac{R_L}{Z_0}\right) \frac{e^{-jBL}}{2j} \text{sinc}(BL)$$

2. Triangular Taper:

$$Z(z) = \begin{cases} Z_0 e^{2\left(\frac{z}{L}\right)^2 \ln\left(\frac{Z_L}{Z_0}\right)} & 0 \leq z \leq \frac{L}{2} \\ Z_0 e^{\left(\frac{4z}{L} - \frac{2z^2}{L^2} - 1\right) \ln\left(\frac{Z_L}{Z_0}\right)} & \frac{L}{2} \leq z \leq L \end{cases}$$


$$\ln\left(\frac{Z_L}{Z_0}\right) = \begin{cases} 2\left(\frac{z}{L}\right)^2 \ln\left(\frac{Z_L}{Z_0}\right) & 0 \leq z \leq \frac{L}{2} \\ \left(\frac{4z}{L} - \frac{2z^2}{L^2} - 1\right) \ln\left(\frac{Z_L}{Z_0}\right) & \frac{L}{2} \leq z \leq L \end{cases}$$

Putting in eq ④ we get

$$I_{IN}(L) = \frac{e^{-jBL}}{2} \ln\left(\frac{R_L}{Z_0}\right) \text{sinc}^2\left(\frac{BL}{2}\right) \quad \left\{ \text{divide it once} \right\}$$

→ instead of sinc, there is a sinc² function. Frequency of 1 to the zero is halved as compared to previous taper.

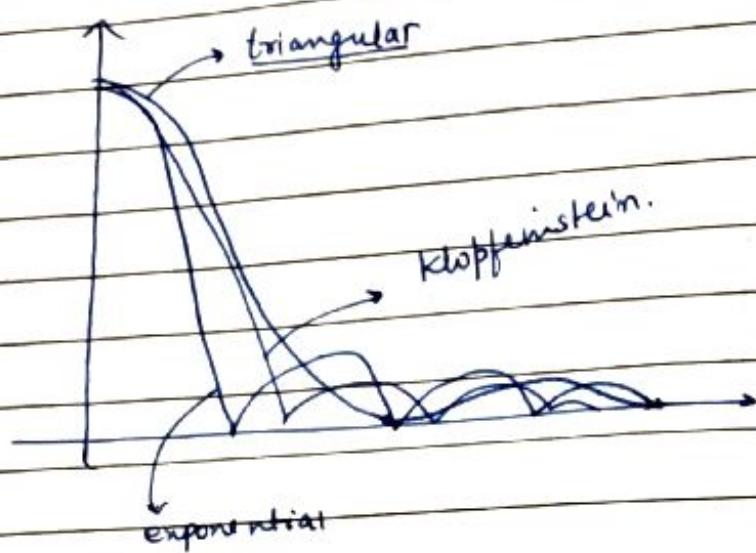→ considered optimum taper
 * Kloffinston taper








Quiz till chebyshov:

30/8/19


friday

Bode - Fahey Criteria:

consists of 4
combinations

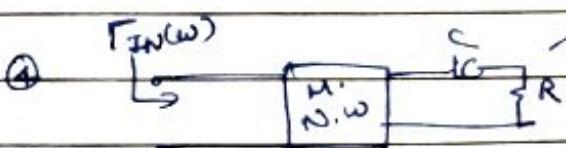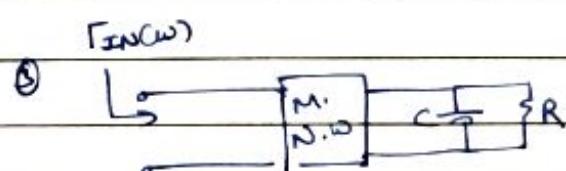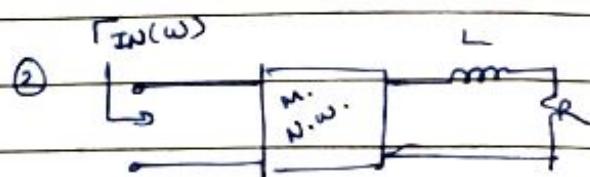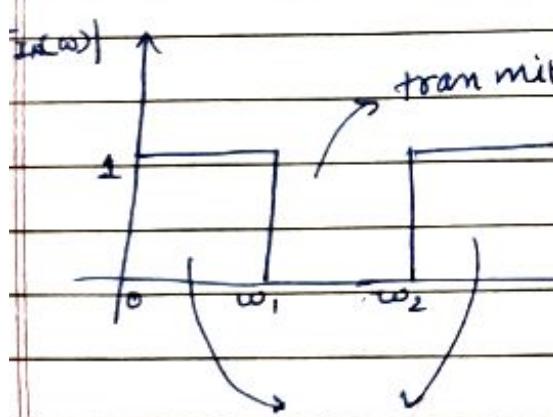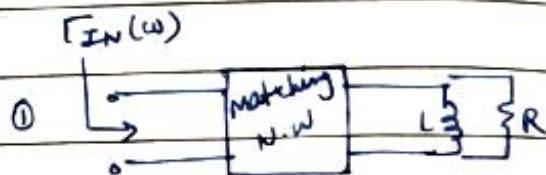

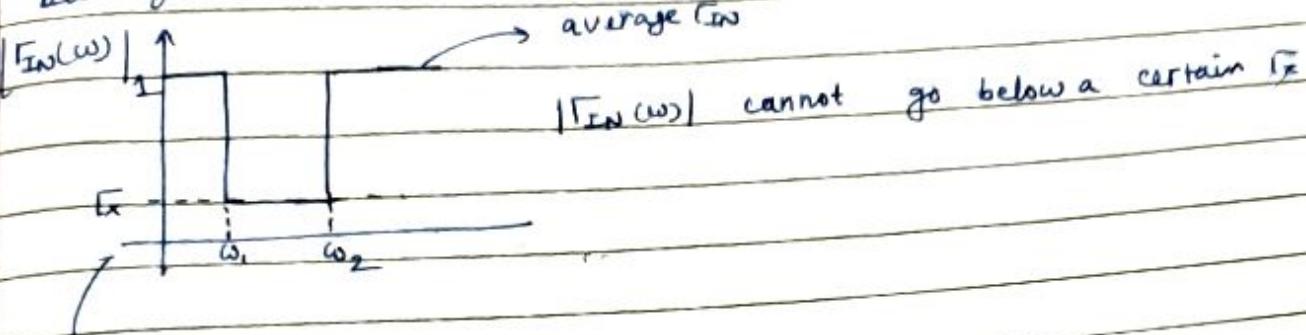Bode Fanno criteria says you can't achieve as last figure.
but you can achieve,



$|\Gamma_{IN}(\omega)|$ cannot go below a certain Γ_x

e.g.: & say case 4 is the combination.

$$\therefore (\Gamma_{IN} = 0)$$

$$\int_{\omega_1}^{\omega_2} \frac{1}{\omega_2} \ln \left| \frac{1}{\Gamma_{IN}} \right| d\omega < \pi R_C \Rightarrow \ln \left| \frac{1}{\Gamma_x} \right| \int_{\omega_1}^{\omega_2} \frac{1}{\omega^2} d\omega < \pi R_C$$

$$\Rightarrow \ln \left| \frac{1}{\Gamma_x} \right| \cdot \left| -\frac{1}{\omega} \right|_{\omega_1}^{\omega_2} < \pi R_C$$


$$\ln \left| \frac{1}{\Gamma_x} \right| \cdot \left\{ \frac{1}{\omega_1} - \frac{1}{\omega_2} \right\} < \pi R_C$$

$$\ln \left| \frac{1}{\Gamma_x} \right| < \frac{\pi R_C (\omega_2 - \omega_1)}{\omega_1 \omega_2} \frac{(\omega_2 - \omega_1)(\omega_1, \omega_2)}{(\omega_2 - \omega_1)}$$

Γ_x ✓ found (minimum-average value of $|\Gamma_{IN}|$ over transmit band.)

→ S parameter Matrix:

first about Y, Z parameters

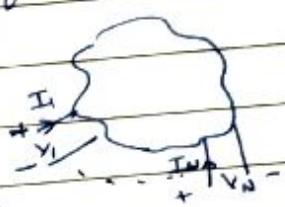

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & & & \vdots \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix}$$

$$Z_{matrix}, Z_{ij} = \frac{Y_i}{Y_j} \quad \begin{cases} I_k = 0 \\ \text{for } k \neq j \end{cases}$$

$$\text{Similarly, } Y_{ij} = \frac{I_i}{V_j} \quad \begin{cases} V_k = 0 \\ \text{for } k \neq j \end{cases}$$

* properties:

① Reciprocity: $Z_{ij}^* = Z_{ji}^*$

② Lossless $N-W$.

$$P_{\text{total}} = \frac{1}{2} V_1 I_1^* + \frac{1}{2} V_2 I_2^* + \dots + \frac{1}{2} V_N I_N^*$$

$$= \frac{1}{2} \sum_{n=1}^N V_n I_n^*$$

where $V_n = \sum_{m=1}^N Z_{nm} I_m$

$$P_{\text{total}} = \frac{1}{2} \sum_{n=1}^N \sum_{m=1}^N \Re(Z_{nm} I_m) I_n^*$$

if Lossless N-W,
 $\Rightarrow \Re(P_{\text{total}}) = 0$

$$\Rightarrow \Re \left[\frac{1}{2} \sum_{n=1}^N \sum_{m=1}^N (Z_{nm} I_m) I_n^* \right] = 0$$

let's make an assumption, $I_i = 0 \forall i, \text{ except } i=n' \Rightarrow I_{n'} \neq 0$

$$\Rightarrow \Re(Z_{nn'} I_{n'} I_{n'}^*) = 0 \Rightarrow \Re(Z_{nn'} |I_{n'}|^2) = 0$$

$$\Rightarrow |I_{n'}|^2 \Re(Z_{nn}) = 0$$

for a lossless only N-W

$$\Rightarrow \Re(Z_{nn'}) = 0 \Rightarrow \text{all diagonal elements would be purely imaginary.}$$

consider another port n'' .

I have now current in n' , n'' .

$$\Rightarrow \Re \left\{ \frac{1}{2} \left(Z_{n'n'} \underbrace{I_{n'} I_{n'}^*}_{|I_{n'}|^2} + Z_{n''n''} \underbrace{I_{n''} I_{n''}^*}_{|I_{n''}|^2} + Z_{n'n''} I_{n'} I_{n''}^* + Z_{n''n'} I_{n''} I_{n'}^* \right) \right\} = 0$$

also, $Z_{n'n''} = Z_{n''n'}$ {reciprocal}

$$\Rightarrow \underbrace{|I_{n'}|^2 \Re(Z_{n'n'})}_{\text{already zero}} + \underbrace{|I_{n''}|^2 \Re(Z_{n''n'})}_{\text{already zero}} + \Re \left[Z_{n'n''} (I_{n'} I_{n''}^* + I_{n''} I_{n'}^*) \right] = 0$$


$$\Rightarrow \Re(Z_{n'n''}) = 0 \quad \text{purely real}$$

\Rightarrow whole matrix has imaginary terms.

classmate

Date _____

2 port N-W

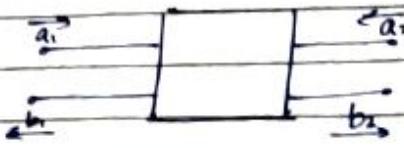

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$$

Data
Page

→ i/p reflection coefficient
→ reverse transmission coeff.

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}$$

→ forward transmission coeff.

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

→ o/p reflection coefficient

$$S_{22} = \frac{b_2}{a_2} \Big|_{a_1=0}$$

* S-parameter matrix is impedance dependent.

$$\begin{bmatrix} [s] \\ [z/y] \end{bmatrix} \xrightarrow[Z_0 = 50\Omega]{Z_0 = 100\Omega}$$

∴ S parameter depends on characteristic impedance
if you want to find $[S]$ at $Z_0 = 100\Omega$
first we need to convert them into $[z]$

∴ they are independent of Z_0 .

Then convert back to $[S]$ at $Z_0 = 100\Omega$

* $[V] = [a] + [b]$

$$\bar{V} = \bar{Z} \bar{I}$$

$$\bar{I} = [a] - [b]$$

$$[a] + [b] = \bar{Z} ([a] - [b])$$

$$[u]([a] + [b]) = \bar{Z} ([a] - [b])$$

$$(\bar{Z} + [u])[b] = (\bar{Z} - [u])[a]$$

$$\Rightarrow [b] = \underbrace{(\bar{Z} + [u])^{-1}}_{S \text{ parameter}} (\bar{Z} - [u])[a]$$

S parameter
matrix, ∴ $[b] = [s][a]$

$$V = [a] + [b]$$

$$\bar{I} = [a] - [b]$$

$$[a] = \frac{\bar{V} + \bar{I}}{2}$$

$$[a] = \frac{1}{2} \{ \bar{Z} + [u] \} \bar{I}$$

$$[b] = \frac{\bar{V} - \bar{I}}{2}$$

$$[b] = \frac{1}{2} \{ \bar{Z} - [u] \} \bar{I}$$


$$[\bar{I}] = 2 \{ \bar{Z} + [u] \}^{-1} [a]$$

~~$$[b] = \{ \bar{Z} - [u] \} \{ \bar{Z} + [u] \}^{-1} [a]$$~~

s

$$[s] = \{ \bar{Z} + [u] \}^{-1} \{ \bar{Z} - [u] \}, s = \{ \bar{Z} - [u] \} \{ \bar{Z} + [u] \}^{-1}$$

now, if $Z_{ij} = Z_{ji}$
 $[Z] = [Z]^t$

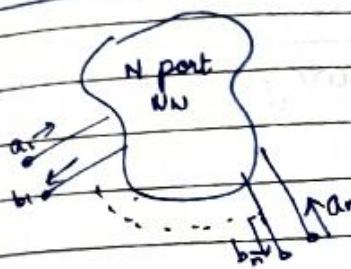

$$P_n = |a_n|^2 - |b_n|^2$$

$$P_{i,n} = \frac{|x_n^+|^2}{z_n}, \quad P_{i,-n} = \frac{|y_n^-|^2}{z_n}$$

$$P_n \text{ (total power entering } n^{\text{th}} \text{ port)} = \frac{|x_n^+|^2}{z_n} - \frac{|y_n^-|^2}{z_n}$$

$$P_{\text{tot}} = \sum_{n=1}^N P_n = \sum_{n=1}^N (|a_n|^2 - |b_n|^2)$$

For lossless N-W,

$$P_{\text{tot}} = 0 \Rightarrow \sum |b_n|^2 = \sum |a_n|^2$$

$$\begin{aligned} [a]^t [a]^* &= [b]^t [b]^* \\ &= [[s][a]]^t [[s][a]]^* \end{aligned}$$

$$[a]^t [a]^* = [a]^t [s]^t [s]^* [a]^*$$


$$\Rightarrow \text{for a lossless N-W, } \boxed{[s]^t [s]^* = [I]} \quad \text{unitary condition}$$

* VNA, Vector network analyzer - used to calibrate devices.



Sophisticated cables (phase stabilized cable)

DUT → design/device under test

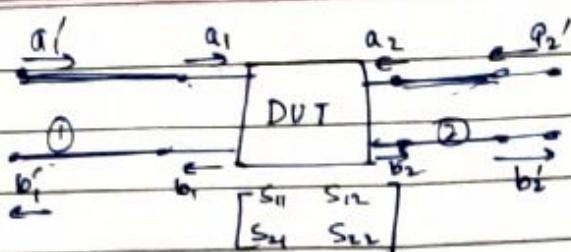

now, $a_1 = a_1' e^{-j\theta_1}$

$a_2 = a_2' e^{-j\theta_2}$

$b_1 = b_1' e^{j\theta_1}$

$b_2 = b_2' e^{j\theta_2}$

$$S_{ki}' = \frac{b_k'}{a_i'} \quad \begin{cases} \text{all other} \\ a_i' = 0 \end{cases} = \frac{b_k e^{-j\theta_k}}{a_i' e^{j\theta_i}} = \frac{b_k}{a_i'} e^{-j(\theta_i + \theta_k)}$$

$\boxed{S_{ki}' = (S_{ki}) e^{-j(\theta_i + \theta_k)}}$

S_{ki} is what we want, but we're measuring shifted version of it.

$$[S'] = \begin{bmatrix} e^{-j\theta_1} & 0 & 0 & \dots \\ 0 & e^{-j\theta_2} & \dots & \dots \\ \vdots & \ddots & \ddots & e^{-j\theta_k} \end{bmatrix} [S] \begin{bmatrix} e^{-j\theta_1} & 0 & \dots \\ 0 & e^{-j\theta_2} & \dots \\ \vdots & \ddots & \ddots & e^{-j\theta_k} \end{bmatrix}$$

VNA takes inverse and all to find $[S]$ from above eqn.

$$[S] = \begin{bmatrix} e^{j\theta_1} & 0 & \dots \\ 0 & e^{j\theta_2} & \dots \\ \vdots & \ddots & e^{j\theta_k} \end{bmatrix} [S'] \begin{bmatrix} e^{j\theta_1} & 0 & \dots \\ 0 & e^{j\theta_2} & \dots \\ \vdots & \ddots & e^{j\theta_k} \end{bmatrix}$$

$$\therefore [S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad \begin{array}{l} \text{if reciprocal} \\ \rightarrow S_{12} = S_{21} \end{array}$$

if lossless

$$[S]^T [S]^* = [I]$$

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} S_{11}^* & S_{12}^* \\ S_{21}^* & S_{22}^* \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$|S_{11}|^2 + |S_{12}|^2 = 1$$

$$|S_{22}|^2 + |S_{21}|^2 = 1$$

$$\Rightarrow |S_{12}| = \sqrt{1 - |S_{11}|^2}$$

$$S_{11} S_{12}^* + S_{12} S_{21}^* = 0$$

$$S_{12} S_{11}^* + S_{22} S_{21}^* = 0$$

$$|S_{22}|^2 + |S_{12}|^2 = 1 \Rightarrow |S_{11}| = |S_{22}|$$

now, $S_{11} = |S_{11}| e^{j\theta_1}$ 5 variables, but $|S_{12}|$ known

$$S_{22} = |S_{22}| e^{j\theta_2}$$

$$S_{12} = S_{21} = |S_{12}| e^{j\theta_{12}}$$

$$S_{11} S_{12}^* + S_{12} S_{11}^* = 0$$

$$|S_{11}| |S_{12}| e^{j(\theta_1 - \theta_{12})} + |S_{12}| |S_{11}| e^{j(\theta_{12} - \theta_2)} = 0$$

$$\Rightarrow e^{j(\theta_1 - \theta_{12})} = e^{j((\theta_{12} - \theta_2) + (2n+1)\pi)}$$


$$\Rightarrow \theta_1 - \theta_{12} = \theta_{12} - \theta_2 + (2n+1)\pi$$

$$\boxed{\theta_{12} = \frac{\theta_1 + \theta_2 - (2n+1)\pi}{2}}$$

$\theta_{12} \checkmark$

3 variables $(|S_{11}|, \theta_1, \theta_2)$

$$S_{11} = \frac{b_1}{a_1} |a_2 = 0$$

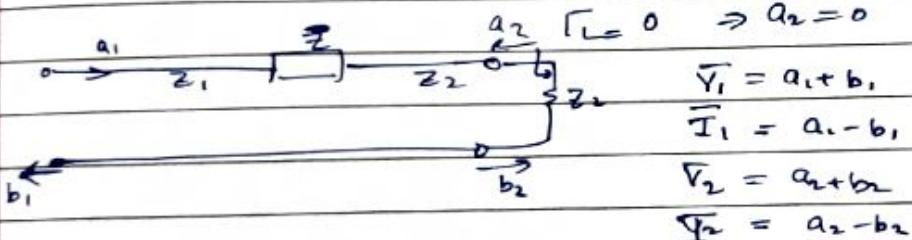

$$I_1 \sqrt{Z_1} = -I_2 \sqrt{Z_2} \cdot \frac{\sqrt{Z_1}}{\sqrt{Z_2}}$$

$$a_1 - b_1 = b_2$$

$$V_2 = V_1 - I_1 Z \star$$

$$a_1 - b_1 = b_2 \frac{\sqrt{Z_1}}{\sqrt{Z_2}}$$

~~$$(a_1 + b_1) \sqrt{Z_1} - (a_1 - b_1) Z$$~~

$$a_1 - b_1 = \sqrt{\frac{Z_1}{Z_2}} \left[(a_1 + b_1) \sqrt{\frac{Z_1}{Z_2}} - \frac{(a_1 - b_1) Z}{\sqrt{Z_1 Z_2}} \right] \quad (a_2 + b_2) \sqrt{Z_2} = (a_1 + b_1) \sqrt{Z_1} - \frac{(a_1 - b_1) Z}{\sqrt{Z_1 Z_2}}$$

$$a_1 - b_1 = \frac{Z_1}{Z_2} (a_1 + b_1) - \frac{Z}{Z_2} (a_1 - b_1) \quad (a_2 + b_2) = (a_1 + b_1) \frac{\sqrt{Z_1}}{\sqrt{Z_2}} - \frac{(a_1 - b_1) Z}{\sqrt{Z_1 Z_2}} \cdot Z$$

$$1 - \frac{b_1}{a_1} = \frac{Z_1}{Z_2} \left(1 + \frac{b_1}{a_1} \right) - \frac{Z}{Z_2} \left(1 - \frac{b_1}{a_1} \right) \quad \therefore a_2 = 0 \Rightarrow \frac{b_2}{a_1} = S_{11}$$

$$\therefore \frac{b_2}{a_1} = \frac{b_2}{a_1} \text{ can also be found.}$$

\therefore reciprocal $n-w$, $S_{12} = S_{21}$
from S_{22} (make $a_1 = 0$)

classmate

Date _____

Page _____

symmetric network $S_{11} = S_{22}$ (like π, T)
only can be used for symmetric Network.