


EEE 313

CMOS ANALOG IC DESIGN.

PROF. RAJESH ZELE

MIDTERM SOLUTIONS


14th SEPT 2017

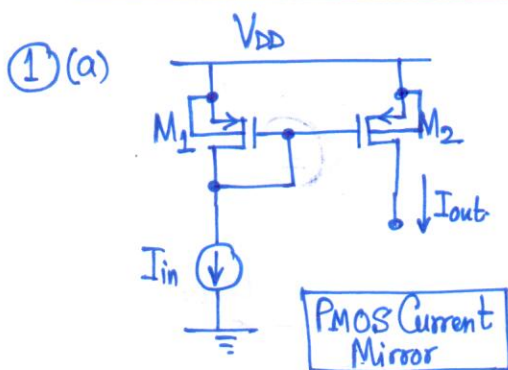

Now, $\frac{I_{out}}{I_{in}} = \frac{(W/L)_2}{(W/L)_1} = 4$
 Keeping 'L's sufficiently large (so that λ becomes smaller) and for better mirroring, $L_1 = L_2$, we get,

$$\boxed{W_2/W_1 = 4}$$

①

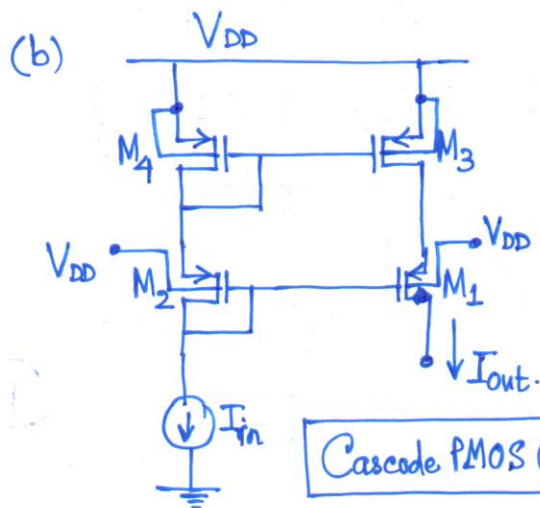

$$L_3 = L_4 \Rightarrow \boxed{W_3/W_4 = 4}$$


$$\boxed{\frac{(W_1/L_1)}{(W_2/L_2)} = 4}$$

Keeping, $L_1 = L_2$,

$$\boxed{W_1/W_2 = 4}$$

(use unit cell design procedure).

①

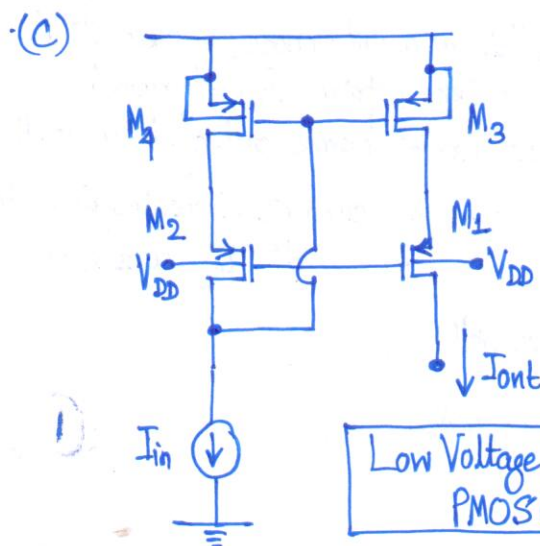


$$\text{Keeping, } L_3 = L_4 \Rightarrow \boxed{W_3/W_4 = 4}$$

$$\boxed{\frac{(W_1/L_1)}{(W_2/L_2)} = 4}$$

Keeping, $L_1 = L_2$,


$$\boxed{W_1/W_2 = 4}$$

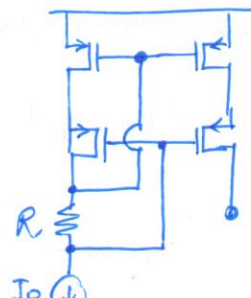

Here, $I_{BR} > V_{DSAT,P}$

②

① (d)

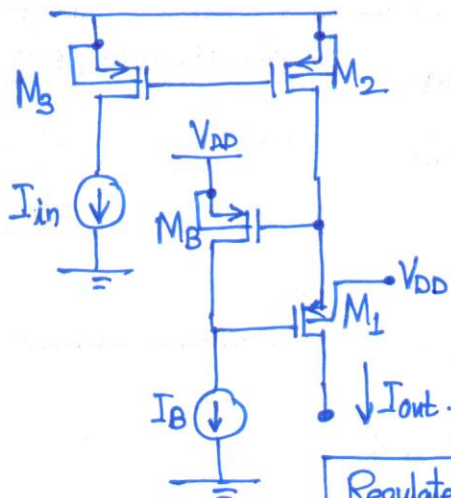


Keeping $L_3 = L_2$,
we have,

$$W_3/W_2 = 1/4 \text{ or } W_2/W_3 = 4$$


Regulated Cascode PMOS
Current Mirror

②

②

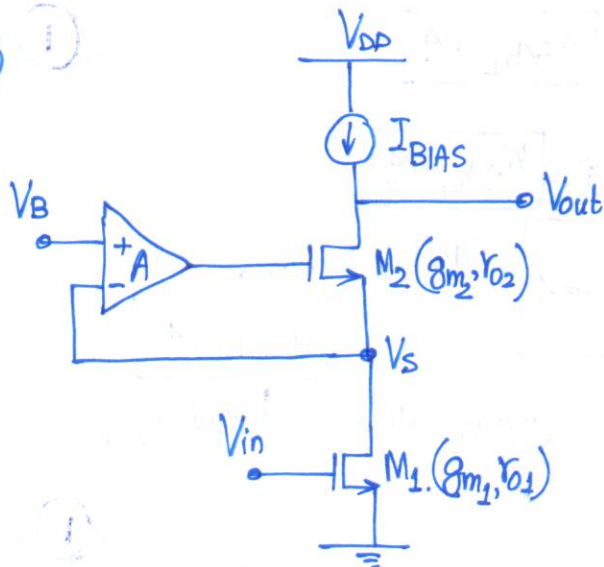

(Ignoring body effect)

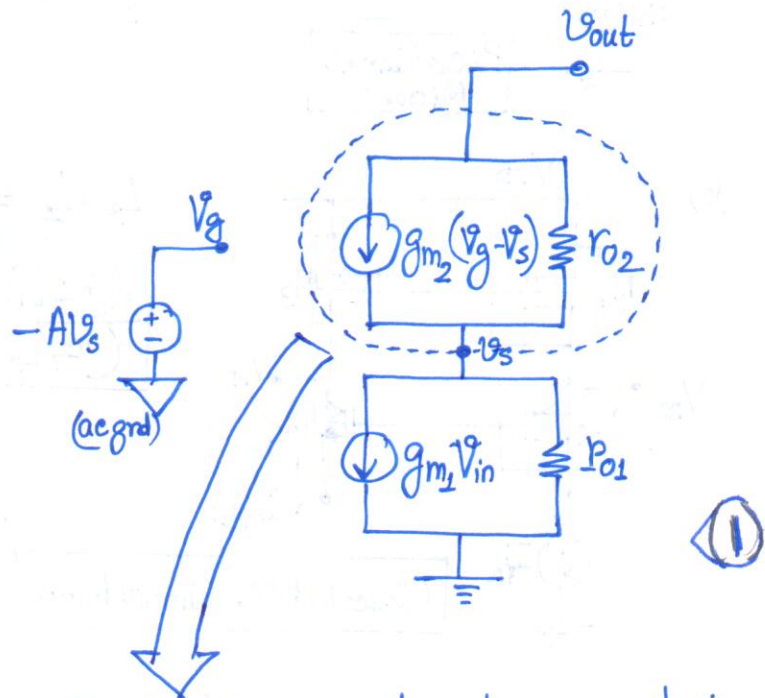

Considering this as a supernode, no current is entering from V_{out} -terminal.

Hence, no current comes out of it as well.

Thus, $g_{m2}(V_g - V_s)$ current circulates in a loop with r_{o2} resistance.

Therefore, same is true for $g_{m1}V_{in}$ and r_{o1} as well.

so, $g_{m1}V_{in} + V_s/r_{o1} = 0$ (KCL @ V_s node)

$$V_s = -(g_{m1}r_{o1})V_{in} \quad \text{--- ①}$$

$$\frac{V_{out} - V_s}{r_{o2}} + g_{m2}(V_s - V_s) = 0 \quad (\text{KCL @ o/p node}) \quad (1)$$

$$\text{so, } \frac{V_{out}}{r_{o2}} + \frac{(g_{m1}r_{o1})}{r_{o2}} V_{in} + g_{m2}(A V_s) - g_{m2}V_s = 0$$

$$\text{i.e., } \frac{V_{out}}{r_{o2}} + \frac{g_{m1}r_{o1}}{r_{o2}} V_{in} - g_{m2}(A+1)V_s = 0$$



$$\text{i.e., } \frac{V_{out}}{r_{o2}} + \frac{g_{m1}r_{o1}}{r_{o2}} V_{in} + (g_{m1}r_{o1})g_{m2}(A+1)V_{in} = 0$$

$$\text{i.e., } V_{out} = - \left[(g_{m1}r_{o1}) + (g_{m1}r_{o1})(g_{m2}r_{o2})(A+1) \right] V_{in}$$

$$\text{i.e., } \frac{V_{out}}{V_{in}} = - (g_{m1}r_{o1}) \left[1 + g_{m2}r_{o2}(A+1) \right] \approx - (g_{m1}r_{o1})(g_{m2}r_{o2})(A+1)$$

$$\boxed{\frac{V_{out}}{V_{in}} \approx - (g_{m1}r_{o1})(g_{m2}r_{o2})(A+1)} \quad (1)$$

(3)

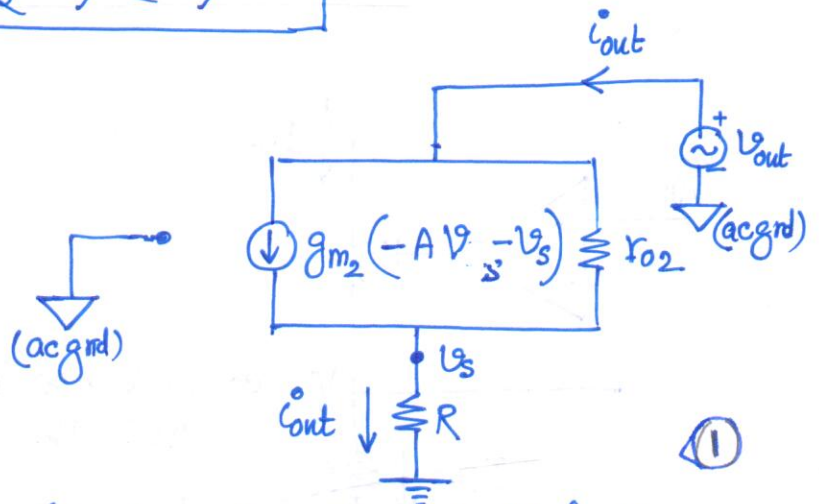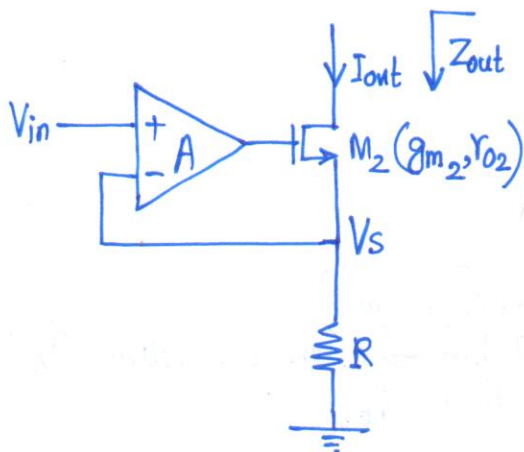

(The above is the small signal setup for Z_{out} characterisation).

$$\text{Now, } V_s = i_{out} R.$$

$$i_{out} = -g_{m2}(A+1)V_s + \frac{V_{out} - V_s}{r_{o2}} \quad (\text{KCL @ o/p node}) \quad (1)$$

$$\text{i.e., } i_{out} = - \left[g_{m2}(A+1) + \frac{1}{r_{o2}} \right] V_s + \frac{V_{out}}{r_{o2}}$$

$$\text{i.e., } \dot{C}_{out} = - \left[g_{m_2}(A+1) + \frac{1}{r_{o_2}} \right] R \dot{C}_{out} + \frac{V_{out}}{r_{o_2}} \quad \left(\text{replacing } V_s = \dot{C}_{out} R \right)$$

$$\text{i.e., } \dot{C}_{out} \left[1 + g_{m_2} R (A+1) + \frac{R}{r_{o_2}} \right] = \frac{V_{out}}{r_{o_2}}$$

$$Z_{out} = \frac{V_{out}}{\dot{C}_{out}} = r_{o_2} + (g_{m_2} r_{o_2})(A+1)R + R \approx (g_{m_2} r_{o_2})(A+1)R$$


(small signal o/p impedance)

if we consider, $A \gg 1$.

$$Z_{out} \approx (A)(g_{m_2} r_{o_2})R$$

Now, let's say, we realise 'A' using a transistor of intrinsic gain $= g_{m_1} r_{o_1}$,
thus,
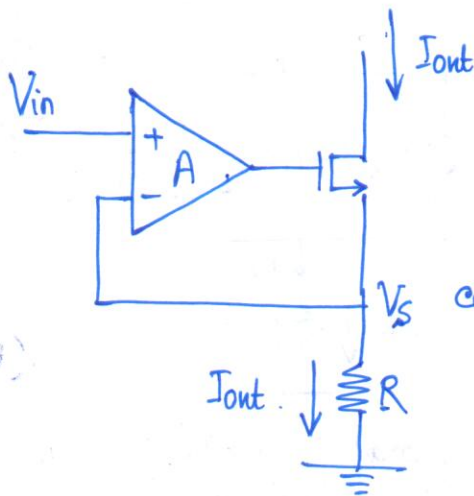
$$Z_{out} \approx (g_{m_1} r_{o_1})(g_{m_2} r_{o_2})R$$




considering $A \gg 1$ (i.e., sufficiently high)
the negative feedback here forces the node voltage (V_s)
to track V_{in} .

$$\text{so, } V_s \approx V_{in}.$$

so, clearly,

$$I_{out} = \frac{V_{in}}{R}$$

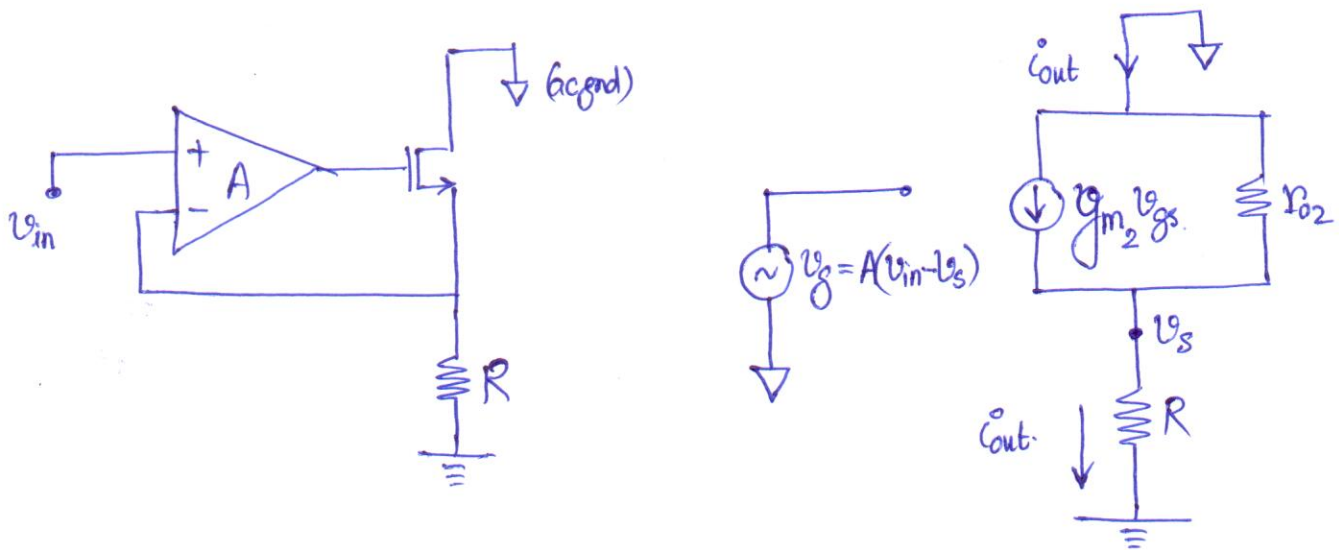Accurate analysis for your enjoyment
 For finding the 'G_m' of the ckt, following small signal structure,



KCL @ o/p node,

$$i_{out} = g_{m2} (A v_{in} - A v_s - v_s) + \frac{0 - v_s}{r_{o2}}$$

$$= g_{m2} A v_{in} - g_{m2} (A+1) v_s - \frac{v_s}{r_{o2}}$$

$$= g_{m2} A v_{in} - \left[g_{m2} (A+1) + \frac{1}{r_{o2}} \right] v_s$$

Replacing, v_s by $i_{out} R$

$$i_{out} = g_{m2} A v_{in} - \left[g_{m2} (A+1) + \frac{1}{r_{o2}} \right] R i_{out}$$

$$i_{out} \left[1 + g_{m2} (A+1) R + \frac{R}{r_{o2}} \right] = g_{m2} A v_{in}$$

$$i_{out} = \left[\frac{(g_{m2} r_{o2}) A}{R + r_{o2} + (g_{m2} r_{o2}) (A+1) R} \right] v_{in} = \left\{ \frac{g_{m2} r_{o2}}{\frac{R + r_{o2}}{A} + (g_{m2} r_{o2}) R \left(1 + \frac{1}{A} \right)} \right\} v_{in}$$

For, $A \gg$ (really high value).

$$i_{out} \approx \frac{g_{m2} r_{o2}}{(g_{m2} r_{o2}) R} v_{in} \Rightarrow \boxed{i_{out} \approx \frac{v_{in}}{R}}$$

LELE@LE


CMOS ANALOG IC DESIGN.

PROF. RAJESH ZELE


MIDTERM SOLUTIONS

14th SEPT 2017

③ Bonus Question :

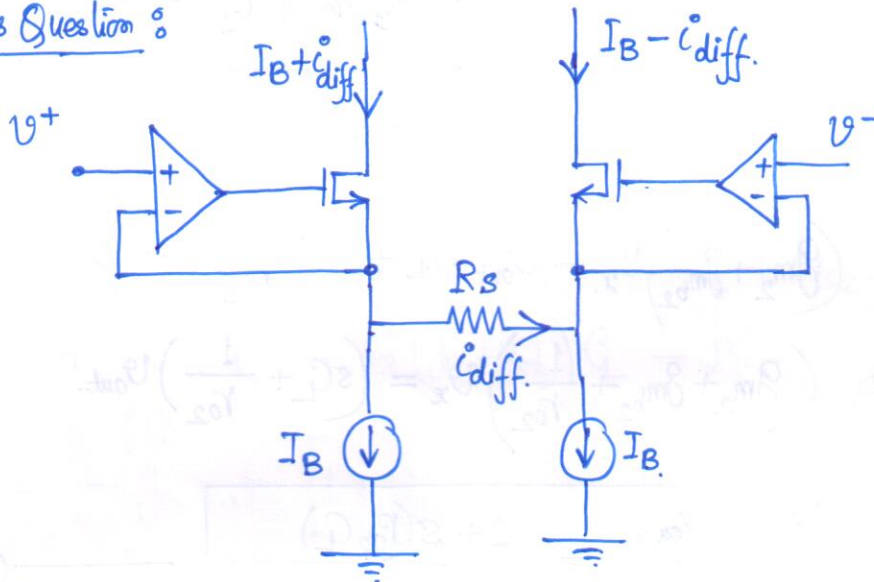



⑤

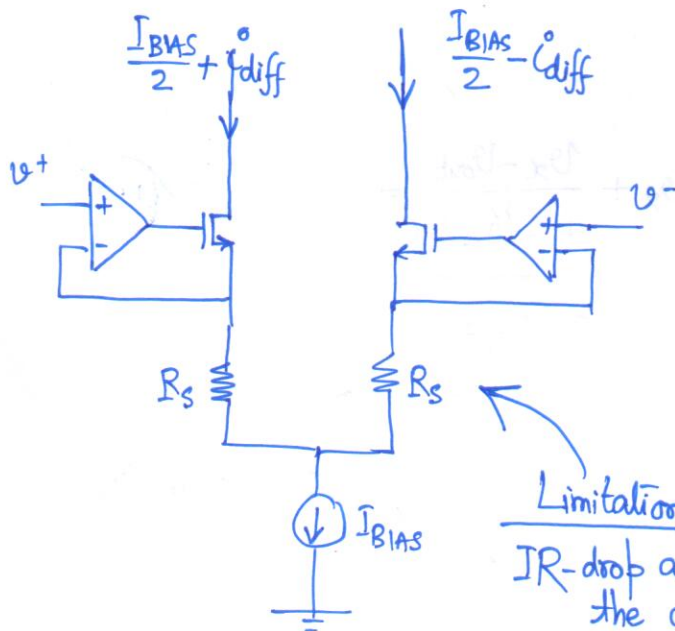

Limitation of this structure :
IR-drop across R_S resistor limits the o/p swing.

Note : Differential architecture means you reject any common mode signal @ the i/p.

4

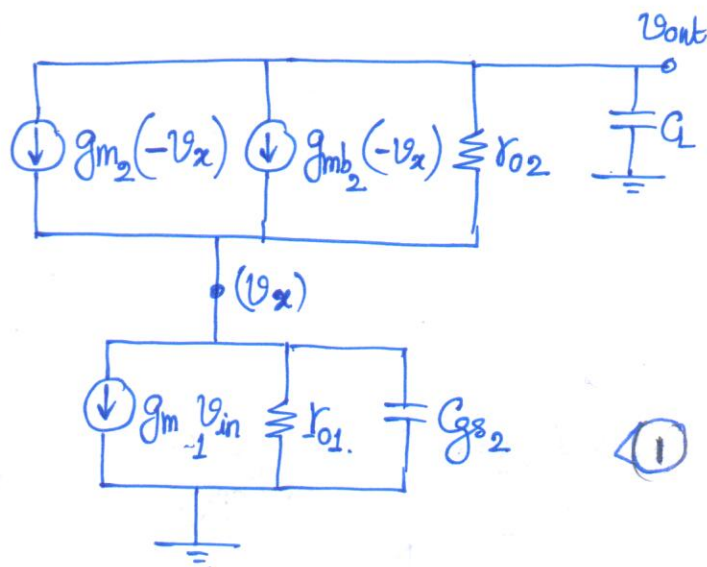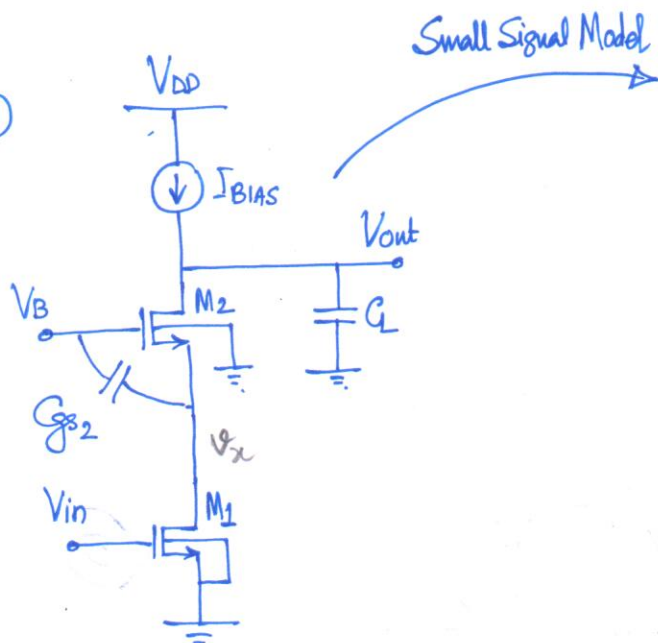

KCL @ o/p node , $(g_{m_2} + g_{m_{b_2}})v_x - v_{out} sC_L + \frac{v_x - v_{out}}{r_{o2}} = 0$

so, $(g_{m_2} + g_{m_{b_2}} + \frac{1}{r_{o2}})v_x = (sC_L + \frac{1}{r_{o2}})v_{out}$

i.e., $\boxed{\frac{v_x}{v_{out}} = \frac{1 + s(r_{o2}C_L)}{1 + (g_{m_2} + g_{m_{b_2}})r_{o2}}}$ ——— ①

KCL @ v_x node ,

$\frac{v_x}{r_{o1}} + v_x sC_{gs2} + g_{m_1}v_{in} + (g_{m_2} + g_{m_{b_2}})v_x + \frac{v_x - v_{out}}{r_{o2}} = 0$

i.e., $v_x \left[\frac{1}{r_{o1}} + sC_{gs2} + g_{m_2} + g_{m_{b_2}} + \frac{1}{r_{o2}} \right] - \frac{v_{out}}{r_{o2}} + g_{m_1}v_{in} = 0$

i.e., $v_{out} \left\{ \left[\frac{1 + s(r_{o2}C_L)}{1 + (g_{m_2} + g_{m_{b_2}})r_{o2}} \right] \left(\frac{1}{r_{o1}} + sC_{gs2} + g_{m_2} + g_{m_{b_2}} + \frac{1}{r_{o2}} \right) - \frac{1}{r_{o2}} \right\} = -g_{m_1}v_{in}$

Multiplying both sides by $(r_{o1} r_{o2})$,

$$V_{out} \left[\frac{1 + s r_{o2} C_L}{1 + (g_{m2} + g_{mb2}) r_{o2}} \right] \left(r_{o2} + s g_{s2} r_{o1} r_{o2} + (g_{m2} + g_{mb2}) r_{o1} r_{o2} + r_{o1} \right) - r_{o1} = -(g_{m1} r_{o1}) r_{o2} V_{in}$$

Multiplying both sides by $[1 + (g_{m2} + g_{mb2}) r_{o2}]$ term,

$$V_{out} \left[(1 + s r_{o2} C_L) \{ r_{o1} + r_{o2} + s g_{s2} r_{o1} r_{o2} + (g_{m2} + g_{mb2}) r_{o1} r_{o2} \} - r_{o1} \{ 1 + (g_{m2} + g_{mb2}) r_{o2} \} \right] \\ = -g_{m1} r_{o1} r_{o2} [1 + (g_{m2} + g_{mb2}) r_{o2}] V_{in}$$

$$V_{out} \left[\cancel{r_{o1} + r_{o2}} + s g_{s2} r_{o1} r_{o2} + \cancel{(g_{m2} + g_{mb2}) r_{o1} r_{o2}} + s r_{o1} r_{o2} C_L + s r_{o2}^2 C_L + s^2 g_{s2} r_{o1} r_{o2}^2 C_L \right. \\ \left. + (s r_{o1} r_{o2}^2 (g_{m2} + g_{mb2}) C_L - \cancel{r_{o1}} - \cancel{(g_{m2} + g_{mb2}) r_{o1} r_{o2}}) \right] \\ = -g_{m1} r_{o1} r_{o2} [1 + (g_{m2} + g_{mb2}) r_{o2}] V_{in}$$

$$V_{out} \cancel{r_{o2}} \left[1 + s g_{s2} r_{o1} + s r_{o1} C_L + s r_{o2} C_L + s^2 r_{o1} r_{o2} g_{s2} C_L + s r_{o1} r_{o2} (g_{m2} + g_{mb2}) C_L \right] \\ = -(g_{m1} r_{o1}) \cancel{r_{o2}} [1 + (g_{m2} + g_{mb2}) r_{o2}] V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1} r_{o1} [1 + (g_{m2} + g_{mb2}) r_{o2}]}{s^2 (r_{o1} r_{o2} g_{s2} C_L) + s [r_{o1} + r_{o2} + r_{o1} r_{o2} (g_{m2} + g_{mb2}) C_L + g_{s2} r_{o1}] + 1}$$

$$\frac{V_o}{V_{in}} \approx \frac{-(g_{m1} r_{o1}) [(g_{m2} + g_{mb2}) r_{o2}]}{s^2 (r_{o1} r_{o2} g_{s2} C_L) + s [r_{o1} r_{o2} (g_{m2} + g_{mb2}) C_L] + 1}$$

Now, Transfer Funcⁿ for a 2nd order system = $\frac{1}{\omega_{p1}\omega_{p2} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1}$

Assuming, $\omega_{p2} \gg \omega_{p1}$
(Dominant Pole approxⁿ)

$$T.F \approx \frac{1}{\omega_{p1}\omega_{p2} + \frac{s}{\omega_{p1}} + 1}$$

Thus, comparing above with previous expression, we get, $-\left(\frac{g_{m2} + g_{mb2}}{C_{gs2}}\right)$ $-\left(\frac{1}{(g_{m2} + g_{mb2})r_{o2}r_{o1}C_L}\right)$


$$\omega_{p1} \approx \frac{1}{(g_{m2} + g_{mb2})r_{o1}r_{o2}C_L}$$

$$\omega_{p1}\omega_{p2} = \frac{1}{r_{o1}r_{o2}C_{gs2}C_L}$$

$$\omega_{p2} \approx \frac{(g_{m2} + g_{mb2})}{C_{gs2}}$$

(1)

(1)

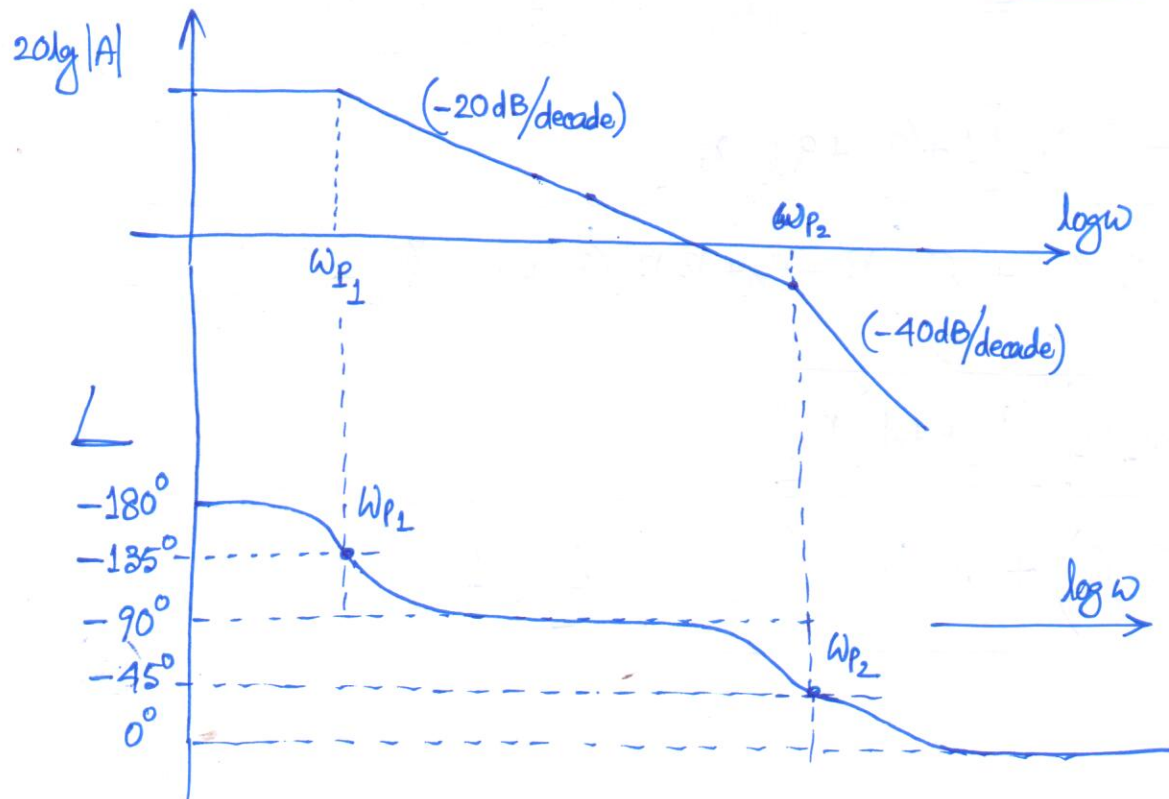

(1.5)

(1.5)

EE631G




CMOS ANALOG IC DESIGN.

PROF. RAJESH ZELE

MIDTERM SOLUTIONS

14th SEPT 2017

⑤

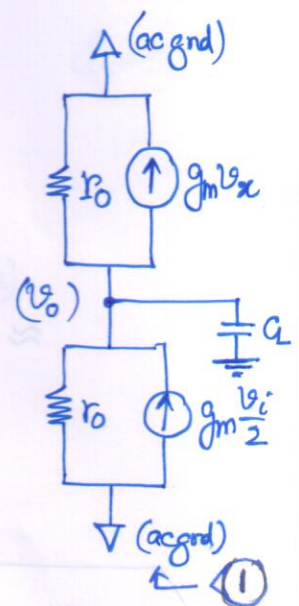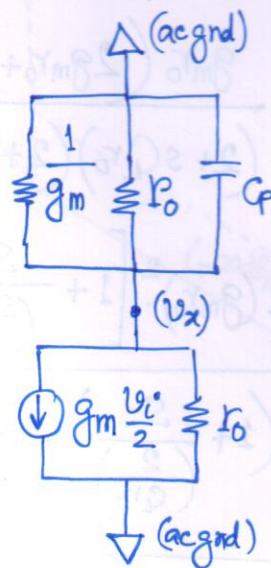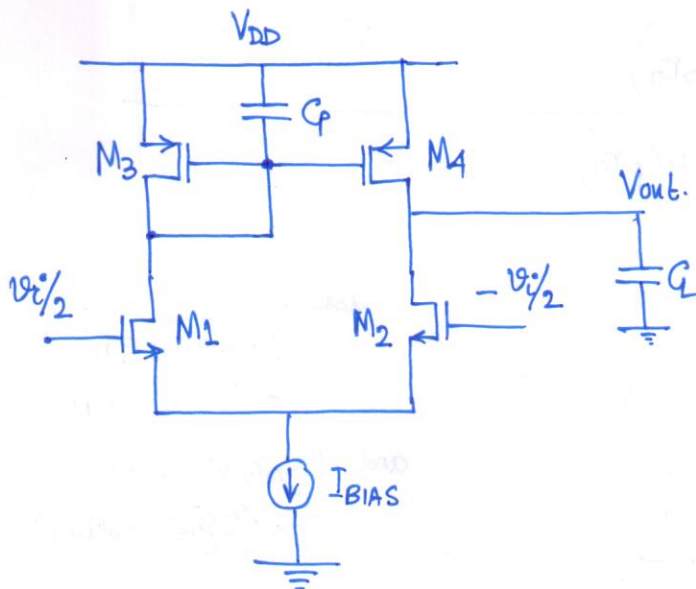

KCL @ node \$v_x\$, $v_x \left(\frac{2}{r_o} + g_m \right) + v_x s C_F + g_m \frac{v_i}{2} = 0$ (0.5)

so, $v_x \left(\frac{2}{r_o} + g_m + s C_F \right) = - \frac{g_m}{2} v_i \Rightarrow v_x = - \left(\frac{\frac{g_m}{2}}{\frac{2}{r_o} + s C_F + g_m} \right) v_i$

KCL @ node \$v_o\$, $v_o \left(\frac{2}{r_o} + s C_L \right) + g_m v_x - g_m \frac{v_i}{2} = 0$ (0.5)

i.e, $v_o \left(2 + s C_L r_o \right) + (g_m r_o) v_x - (g_m r_o) \frac{v_i}{2} = 0$

i.e, $v_o \left(2 + s C_L r_o \right) - \frac{\frac{g_m^2 r_o}{2}}{\frac{2}{r_o} + s C_F + g_m} v_i - (g_m r_o) \frac{v_i}{2} = 0$

i.e, $v_o \left(2 + s C_L r_o \right) - \frac{(g_m r_o)^2}{2 + s C_F r_o + g_m r_o} \cdot \left(\frac{v_i}{2} \right) - g_m r_o \cdot \left(\frac{v_i}{2} \right) = 0$

i.e, $2 v_o \left(2 + s C_L r_o \right) = \left\{ \frac{g_m^2 r_o^2}{2 + g_m r_o + s C_F r_o} + g_m r_o \right\} v_i$

$$2V_o(2+sC_Lr_o) = \frac{(g_m^2r_o^2 + 2g_mr_o + g_m^2r_o^2 + sC_pg_mr_o^2)}{(2+g_mr_o+sC_pr_o)} V_o$$

$$\frac{V_o}{V_i} = \frac{2g_m^2r_o^2 + 2g_mr_o + sC_pg_mr_o^2}{2(2+sC_Lr_o)(2+g_mr_o+sC_pr_o)}$$

$$= \frac{g_mr_o(2g_mr_o+2+sC_pr_o)}{2(2+sC_Lr_o)(2+g_mr_o+sC_pr_o)}$$

$$\approx \frac{2(g_mr_o)^2 \left[1 + \frac{s}{\left(\frac{2g_m}{C_p}\right)} \right]}{4 \left(1 + \frac{s}{\left(\frac{2}{C_Lr_o}\right)} \right) \cdot g_mr_o \cdot \left(1 + \frac{s}{\left(\frac{g_m}{C_p}\right)} \right)}$$

assuming,

$$(g_mr_o+2+sC_pr_o) \approx (g_mr_o+sC_pr_o)$$

$$\text{and, } (2g_mr_o+2+sC_pr_o) \approx (2g_mr_o+sC_pr_o)$$


$$\frac{V_o}{V_i}(s) \approx \frac{\frac{g_mr_o}{2} \left[1 + \frac{s}{\left(\frac{2g_m}{C_p}\right)} \right]}{\left[1 + \frac{s}{\left(\frac{2}{C_Lr_o}\right)} \right] \left[1 + \frac{s}{\left(\frac{g_m}{C_p}\right)} \right]}$$

← TRANSFER FUNCTION


①

$$\text{so, } \boxed{\omega_{p_1} = -\frac{2}{C_Lr_o} ; \omega_{p_2} = -\frac{g_m}{C_p} ; \omega_z = -\frac{2g_m}{C_p}}$$

①

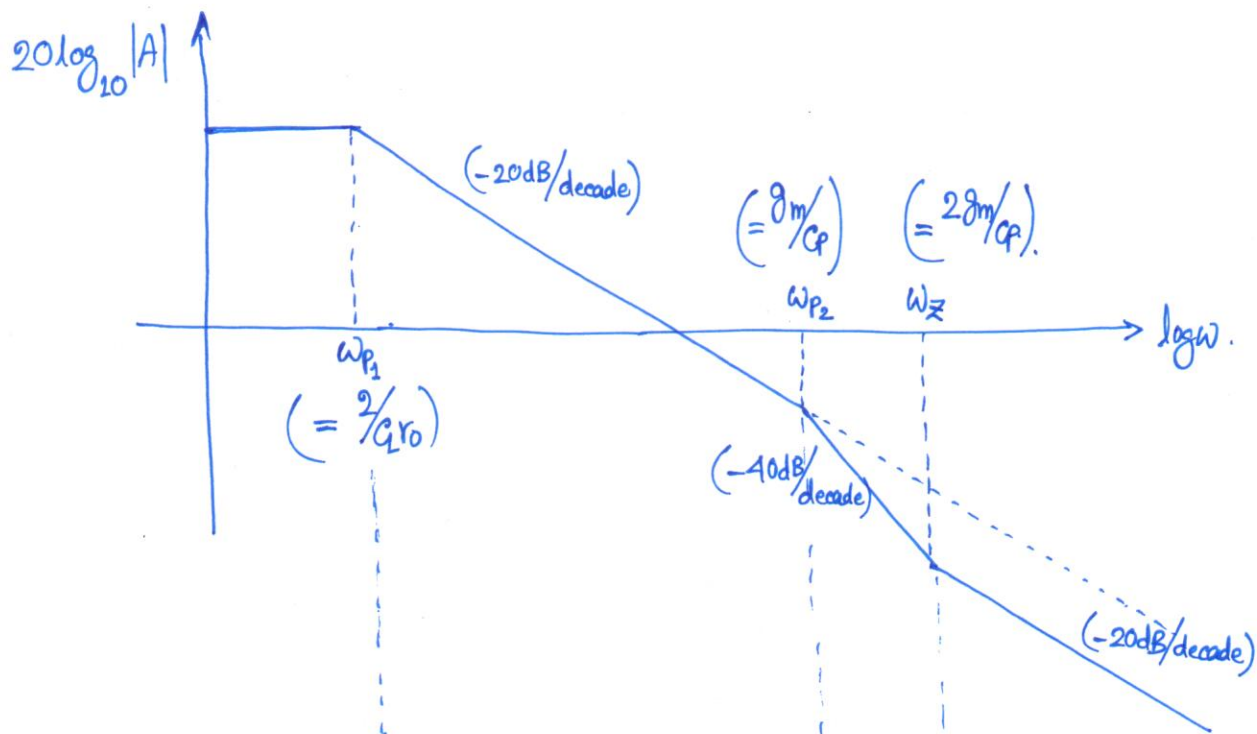


(1.5)

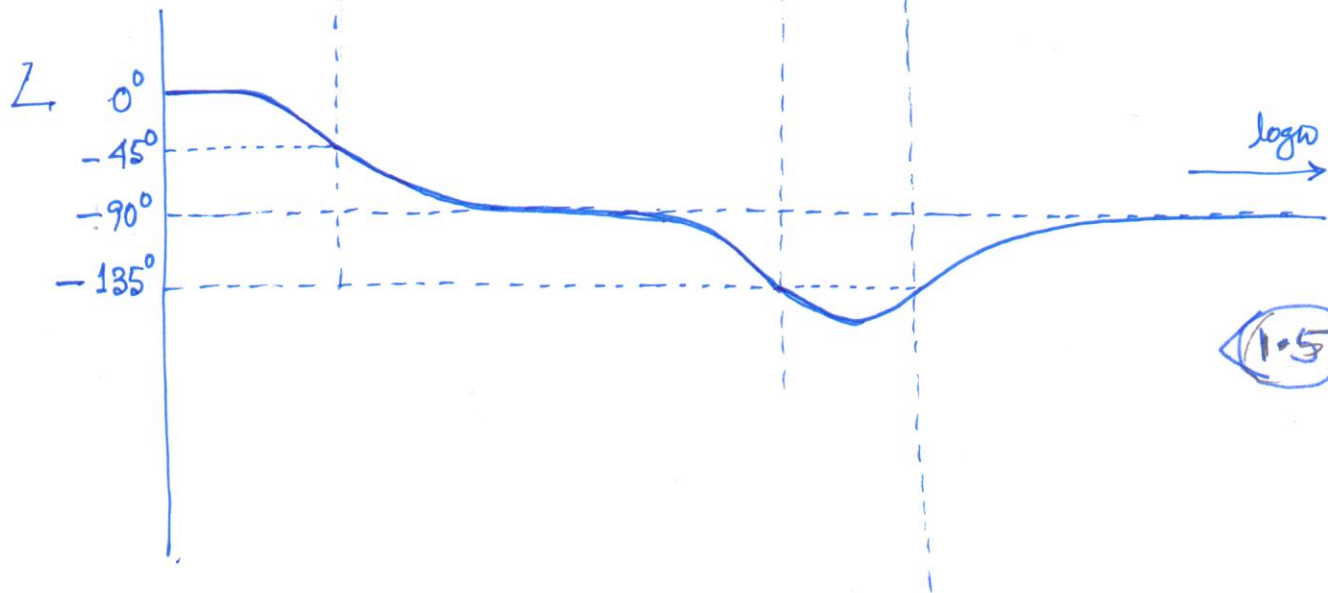

(1.5)

6

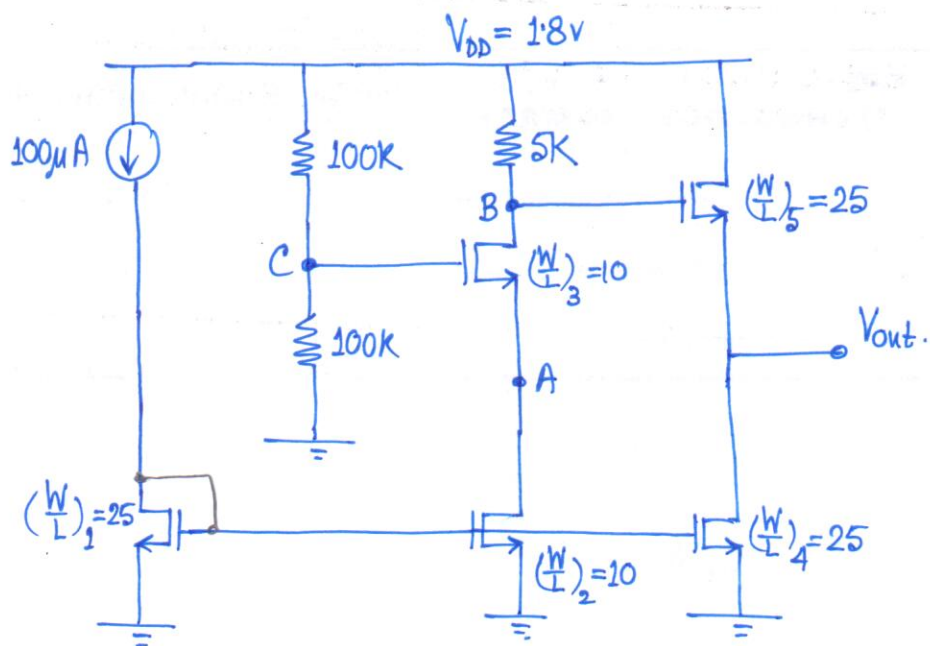

DC biasing structure looks like this.

$$I_{M_2} = I_{M_3} = \left(\frac{10}{25} \times 100 \right) = 40 \mu A.$$

$$I_{M_4} = I_{M_5} = \left(\frac{25}{25} \times 100 \right) = 100 \mu A$$

Current mirroring.

$$V_C = \frac{1.8}{2} = 0.9 \text{ V}$$

$$V_{GS_2} = V_{GS_3} = V_t + \sqrt{\frac{2 \times I_{D_{2,3}}}{\mu_n C_{ox} (W/L)_{2,3}}} = 0.4 + \sqrt{\frac{2 \times 40}{200 \times 10}} = 0.6 \text{ V}$$

$$\text{Now, } V_{GS_3} = V_C - V_A = 0.9 - V_A = 0.6$$

$$\text{so, } V_A = 0.3 \text{ V}$$

$$V_B = 1.8 - (5 \times 10^3) (40 \times 10^{-6}) = 1.6 \text{ V}$$

$$V_{GS_4} = V_{GS_2} = 0.6 = V_{GS_5}$$

$$\text{so, } V_{GS_5} = V_B - V_{out} = 0.6 = 1.6 - V_{out}$$

$$V_{out} = 1 \text{ V}$$

Note, M_5 acts as a source follower. Therefore, $V_B = V_{out}$ (Note, here we're talking about small signal ac signal NOT the DC Bias)

M_3 acts as CS amplifier.

Node 'A' is ac gnd due to the presence of C_{dep} .

$$\begin{aligned} \text{so, gain } A_v &= -(g_{m3}) \times (5k\Omega) \\ &= -\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_3 I_{D3}} \times 5 \times 10^3 \\ &= -\sqrt{2 \times 200 \times 10^{-6} \times 40 \times 10^{-6} \times 10 \times 5 \times 10^3} \\ &= -2. \end{aligned} \quad \text{--- } \textcircled{1}$$

$$\text{so, } \boxed{\text{Inband gain } \frac{V_{out}}{V_{in}} = -2.} \quad \text{--- } \textcircled{1}$$