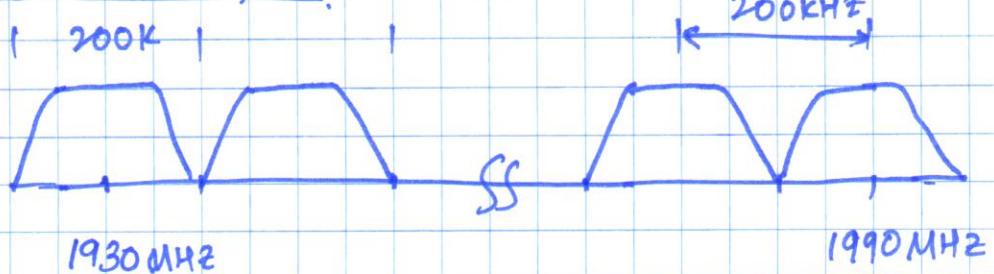


15 OCT 2019

CONTINUOUS TIME FILTERS

GSM Example.



AM , FM Radios — Common Medium Shared between multiple users.

Filters are used to provide frequency selectivity.

- Keep desired spectrum (channel)
- Attenuate undesired channels.

→ Wireline Communication Example


Filters used to compensate for Channel loss (frequency dependent)

→ Equalization & pulse shaping.

- Antialiasing filters for ADC
- Smoothing filters for DAC

Filter Specifications

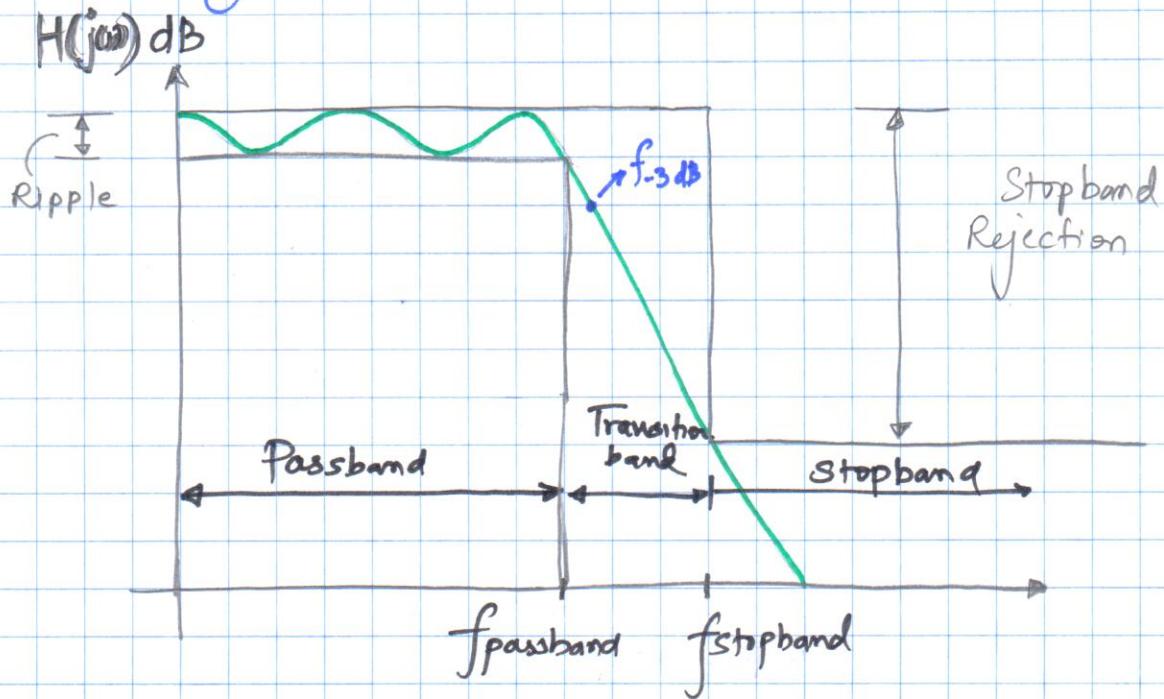Study Low Pass filters first - Then Xform to diff types.



Filter with transfer function $H(s)$

$$H(j\omega) = |H(j\omega)| e^{j\theta(\omega)}$$

$$\text{Phase Delay} = \tau_{PD} = -\frac{\theta(\omega)}{\omega} \text{ (time units)}$$

$$\text{Group Delay} = \tau_{GR} = -\frac{d\theta(\omega)}{d\omega} \text{ (time units)}$$

$$\theta(\omega) = K\omega$$

↑ Constant


$$\tau_{PD} = \tau_{GR} = -K$$

Constant group delay.

→ This property is important for pulse-shaping in Wireline applications

Filter Approximations

(ideal Brickwall)

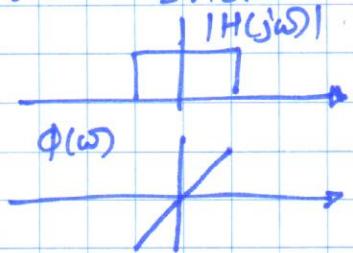


1. Butterworth Approximation

$$|H(j\omega)|^2 = \frac{1}{1 + \omega^{2n}}$$

$$|H(j0)|^2 = 1 ; H(j\omega_0) =$$

$$|H(j1)|^2 = 0.5$$


$$|H(j\infty)|^2 = 0$$

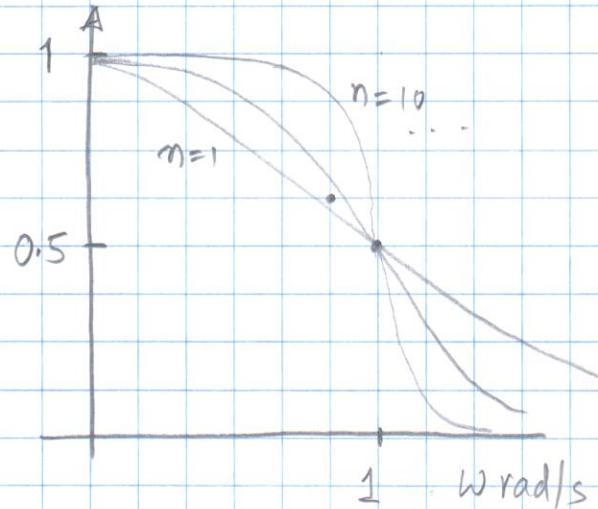

- * Maximally flat passband @ $\omega=0$.


- * Moderate phase distortion. (group delay)

- * Poles located on unit circle

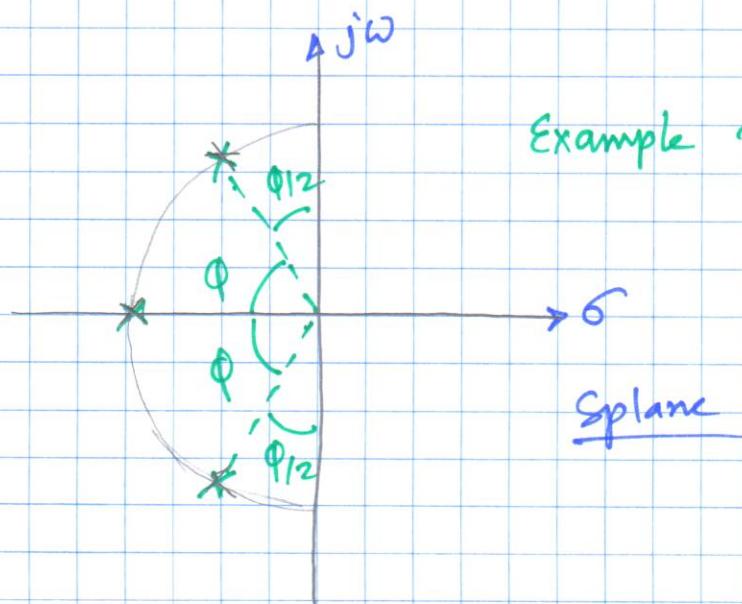

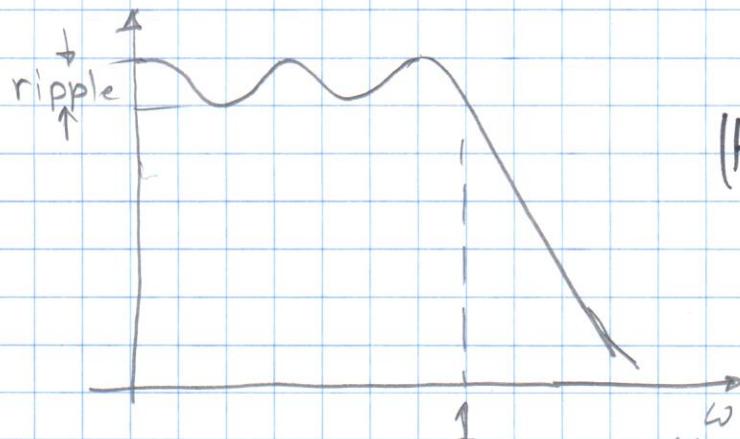2. Chebyshev Approximation

- Keep attenuation in passband minimal
- within Ripple spec.
- Sharper transition band (compared to Butterw)
- Poorer group delay distortion.
- All poles located on Ellipse.




$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega)}$$

$$T_n(\omega) = \cos(n \cos^{-1} \omega)$$


ϵ - sets ripple amplitude

Chebyshev polynomial
(n-th order)

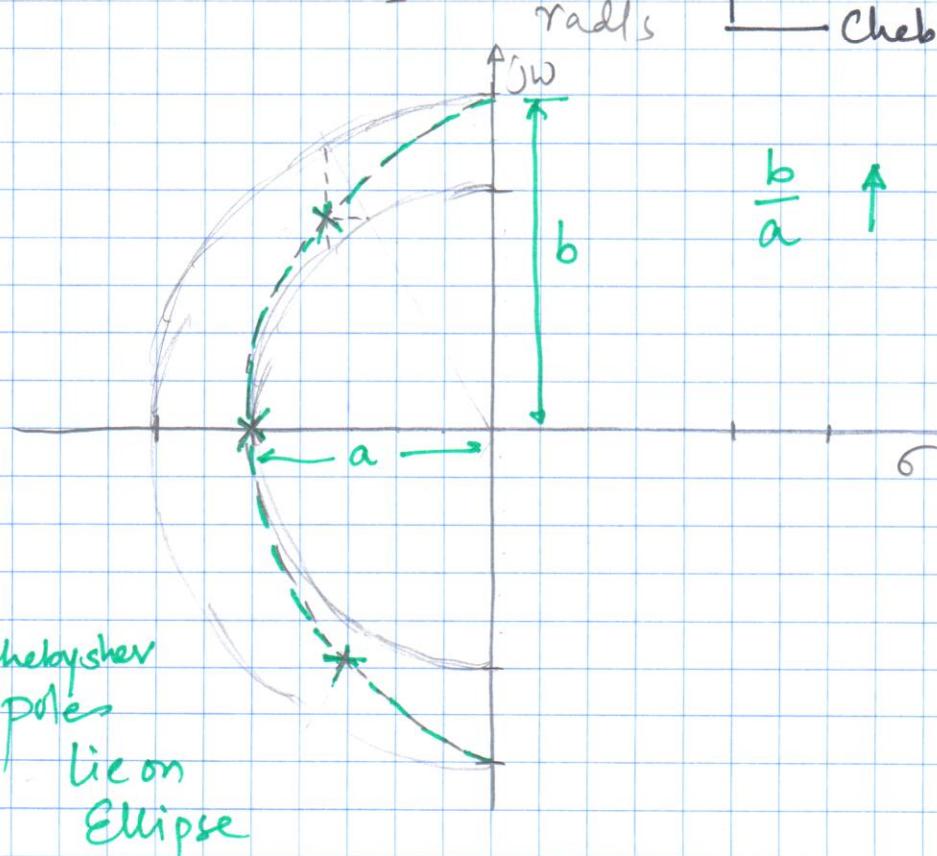

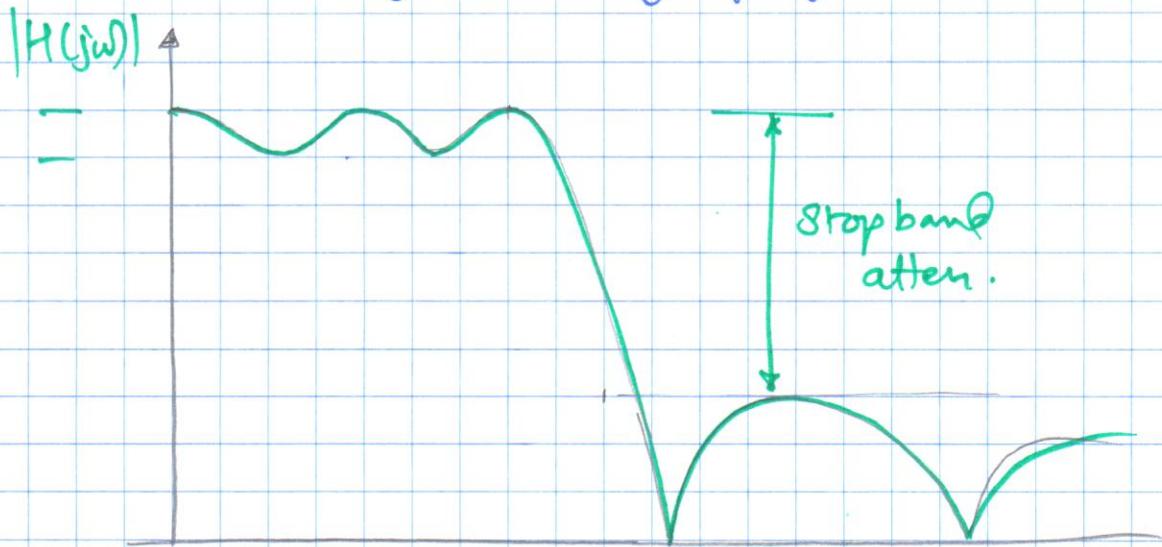
3. Elliptic filters (Cauer filters)

- Zeros in stopband, create nulls.
- Very sharp transition band - highest attenu with lowest order
- poorest group delay performance.




④ Bessel Approximation

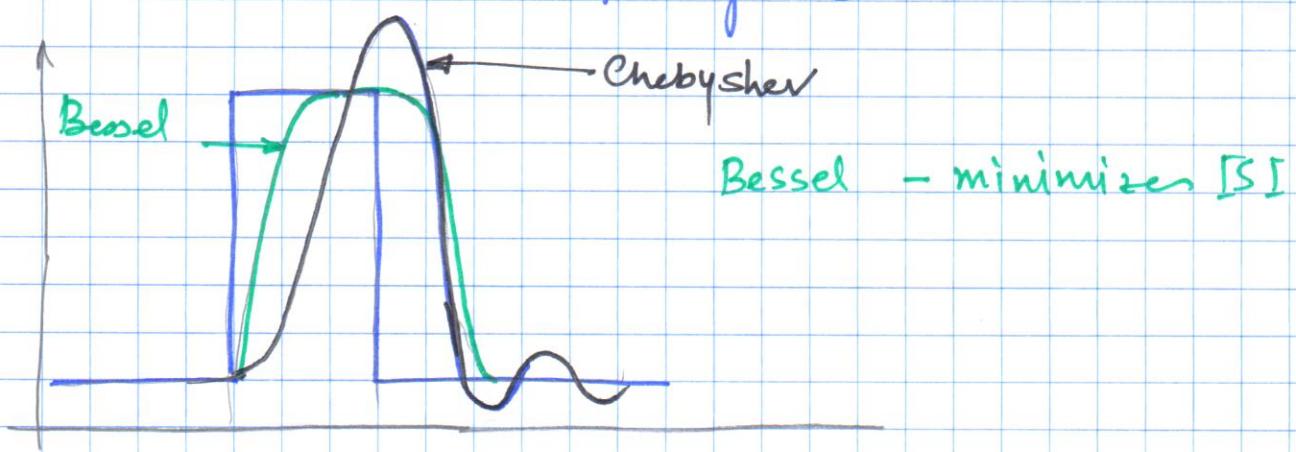- Poles ~~are~~ outside unit circle (low Q)
- Maximally flat group delay
- attenuation \sim Not great.



RC filter - 1st order Example

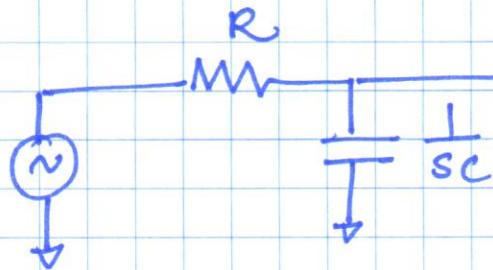


$$V_{out} = \frac{1/sC}{R + 1/sC} = \frac{1}{(1 + s/Rs)}$$

pole @ $-\omega_0 = -\frac{1}{Rs}$


$$@ s = j\omega_0 \quad |H(j\omega)| = \frac{1}{\sqrt{2}}$$

→ 3dB frequency

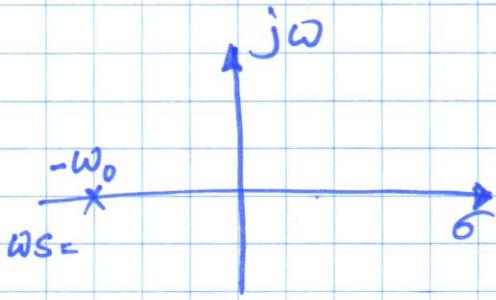

Note: parasitics across R will limit high freq. atten.

Noise Analysis

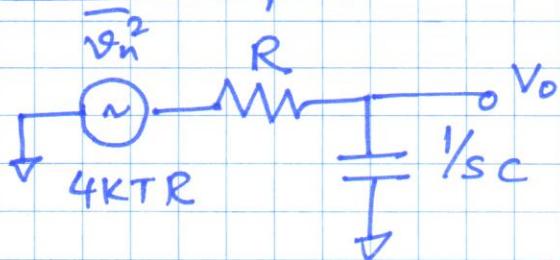

$$S_{out}(f) = 4KTR \cdot \frac{1}{4\pi^2 R^2 C^2 f^2 + 1}$$

Total integrated O/p noise

$$= \int_0^\infty \frac{4KTR}{4\pi^2 R^2 C^2 f^2 + 1} df$$

$$= \frac{KT}{C} \quad \text{indep of } R$$

Example 1 pF cap → 64 μVrms @ 300°K

for complex filter (higher order)

$$\text{O/p noise} = \propto \frac{kT}{C}$$

depends on order

Also - assumption - active circuits - lower noise.

Filter

Dynamic

Range

Max Voltage Swing

Min. discernible signal

V_{DD} , Linearity

Noise

$$\text{Max Voltage Swing} = \frac{1}{\sqrt{2}} \frac{V_{DD}}{2} \quad (\text{Rms Voltage})$$

$$\text{Min. Voltage Swing} = \sqrt{\propto \frac{kT}{C}} \quad (\text{Rms Noise})$$

$$DR = \frac{V_{DD}/2\sqrt{2}}{\sqrt{\propto \frac{kT}{C}}} = V_{DD} \sqrt{\frac{C}{8\propto kT}}$$

$$DR_{dB} = 20 \log_{10} \left(V_{DD} \sqrt{\frac{C}{8\propto kT}} \right)$$

$$= 20 \log_{10} \left(V_{DD} \sqrt{\frac{C}{\propto}} \right) + 75 \text{ dB}$$

(C in pF)

$$\text{For } V_{DD} = 1 \text{ V} \quad C = 1 \text{ pF} \quad \propto = 1$$

$$DR_{dB} = 75 \text{ dB} = (1.76 + 6.02N)$$

3 bits

$$N = 12 \text{ bits}$$

Best possible

Reference - Haideh Khorramabadi
classnotes.


FILTER DESIGN EXAMPLE

Design a Chebyshov filter to meet following req.

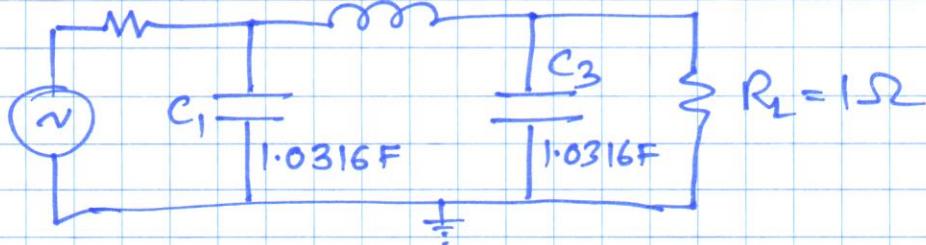- * 0.1 dB ripple
 - * 10MHz ripple BW.
 - * Stopband atten 40dB
 - * Stopband 60MHz
- Ripple BW/Stopband = 1/6
- From 0.1dB ripple Chebyshov Attenuation chara.
(Fig 8.15) for $n=3$ atten@ 6 rad/s = 42dB.
- 3rd order filter.

From Table 8.2

$$R_s = 1\Omega \quad L_2 = 1.1474 \text{ H}$$




$$\omega_{\text{ripple BW}} = 1 \text{ rad/s}$$

$$\begin{aligned} \text{Desired } \omega_{\text{ripple BW}} &= 2\pi \times 10 \text{ MHz} \\ &= 62.8 \text{ M rad/s} \end{aligned}$$

$$C_1 = C_3 = \frac{1.0316 \text{ F}}{62.8 \text{ M}} = 16.4 \text{ nF}$$
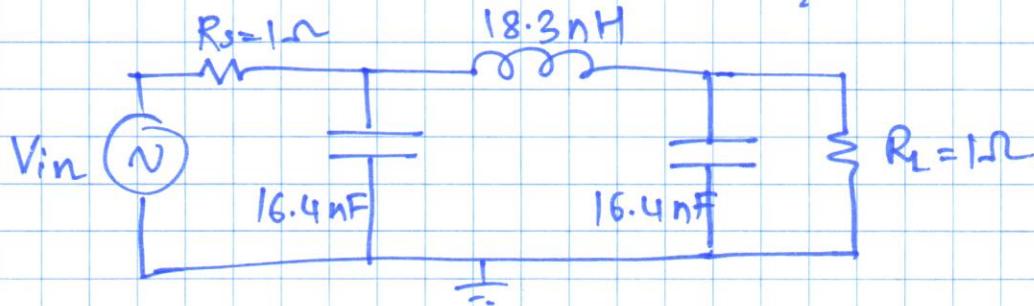
$$L_2 = \frac{1.1474 \text{ H}}{62.8 \text{ M}} = 18.3 \text{ nH}$$



Impractical
for IC
implementation

ANALOG AND DIGITAL FILTERS: DESIGN AND REALIZATION

HARRY Y-F. LAM

Bell Telephone Laboratories, Inc.

Formerly with University of California, Berkeley


100680 Lam, Harry Y-F




Analog and digital filters : design

100680

100680

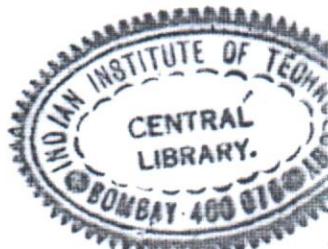

BUTTERWORTH FILTER

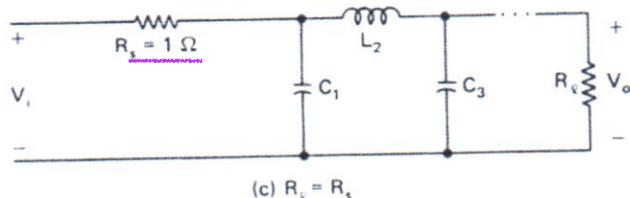


(c) $R_s = R_2$

Fig. 8-9 Circuit structures of low-pass Butterworth filters.

FILTER ORDER

TABLE 8-1 Element Values for the Circuit in Fig. 8-9(c)

n	C ₁	L ₂	C ₃	L ₄	C ₅	L ₆	C ₇	L ₈	C ₉
1	2.0000								
2	1.4142	1.4142							
3	1.0000	2.0000	1.0000						
4	0.7654	1.8478	1.8478	0.7654					
5	0.6180	1.6180	2.0000	1.6180	0.6180				
6	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176			
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450		
8	0.3902	1.1111	1.6629	1.9616	1.9616	1.6629	1.1111	0.3902	
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473

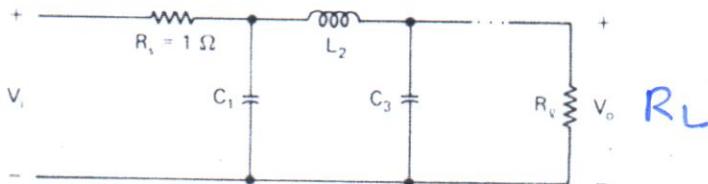

Chebyshev
Filter

Fig. 8-17 Circuit structure of low-pass Chebyshev filters.

R_L
TABLE 8-2 Values of Circuit Elements in Chebyshev Filters
when $A_{\max} = 0.1 \text{ dB}$

n	R_t	C_1	L_2	C_3	L_4	C_5	L_6	C_7	L_8	C_9
1	1.0	0.3052								
2	0.5	1.5715	0.2880							
3	1.0	1.0316	1.1474	1.0316						
4	0.5	2.3545	0.7973	2.6600	0.3626					
5	1.0	1.1468	1.3712	1.9750	1.3712	1.1468				
6	0.5	2.5561	0.8962	3.3962	0.8761	2.8071	0.3785			
7	1.0	1.1812	1.4228	2.0967	1.5734	2.0967	1.4228	1.1812		
8	0.5	2.6324	0.9285	3.5762	0.9619	3.5095	0.8950	2.8547	0.3843	
9	1.0	1.1957	1.4426	2.1346	1.6167	2.2054	1.6167	2.1346	1.4426	1.1957

Ripple 0.1dB

R_L
TABLE 8-3 Values of Circuit Elements in Chebyshev Filters
when $A_{\max} = 1 \text{ dB}$

n	R_t	C_1	L_2	C_3	L_4	C_5	L_6	C_7	L_8	C_9
1	1.00	1.0177								
2	0.25	3.7779	0.3001							
3	1.00	2.0236	0.9941	2.0236						
4	0.25	4.5699	0.5428	5.3680	0.3406					
5	1.00	2.1349	1.0911	3.0009	1.0911	2.1349				
6	0.25	4.7366	0.5716	6.0240	0.5764	5.5353	0.3486			
7	1.00	2.1666	1.1115	3.0936	1.1735	3.0936	1.1115	2.1666		
8	0.25	4.7966	0.5803	6.1592	0.6005	6.1501	0.5836	5.5869	0.3515	
9	1.00	2.1797	1.1192	3.1214	1.1897	3.1746	1.1897	3.1214	1.1192	2.1797

Ripple 1dB

Bessel
Filter

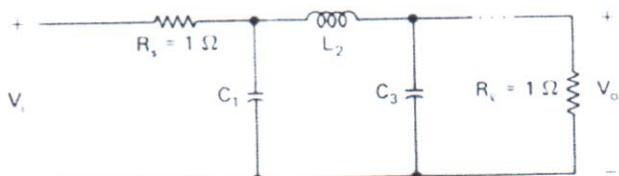


Fig. 8-23 A basic circuit structure for low-pass Bessel filters.

Filter order















TABLE 8-4 Values of Circuit Elements in Bessel Filters

n	C_1	L_2	C_3	L_4	C_5	L_6	C_7	L_8	C_9
1	2.0000								
2	1.5774	0.4226							
3	1.2550	0.5528	0.1922						
4	1.0598	0.5116	0.3181	0.1104					
5	0.9303	0.4577	0.3312	0.2090	0.0718				
6	0.8377	0.4116	0.3158	0.2364	0.1480	0.0505			
7	0.7677	0.3744	0.2944	0.2378	0.1778	0.1104	0.0375		
8	0.7125	0.3446	0.2735	0.2297	0.1867	0.1387	0.0855	0.0289	
9	0.6678	0.3203	0.2547	0.2184	0.1859	0.1506	0.1111	0.0682	0.0230

FILTER TRANSFORMATIONS

TABLE 8-5 Frequency and Element Transformations

264

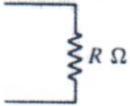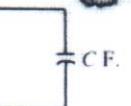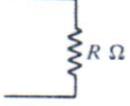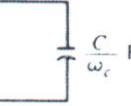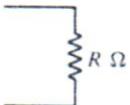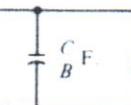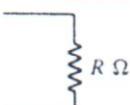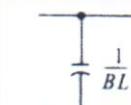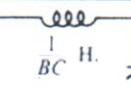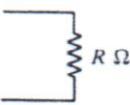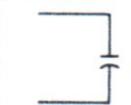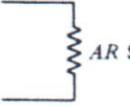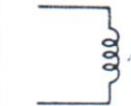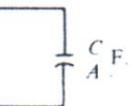From Normalized Low-pass Filter to:	Frequency Transformations			
A low-pass filter with cutoff frequency ω_c	$s \longleftrightarrow \frac{s}{\omega_c}$			
A bandpass filter with center frequency ω_0 and bandwidth B	$s \longleftrightarrow \frac{s^2 + \omega_0^2}{Bs}$			
A band-reject filter with center frequency ω_0 and rejection bandwidth B	$s \longleftrightarrow \frac{Bs}{s^2 + \omega_0^2}$			
A high-pass filter with cutoff frequency ω_c	$s \longleftrightarrow \frac{\omega_c}{s}$			
Impedance scaling by A	No change			

Selected Plots from

ANALOG AND DIGITAL FILTERS: DESIGN AND REALIZATION -- Harry Y.-F. LAM

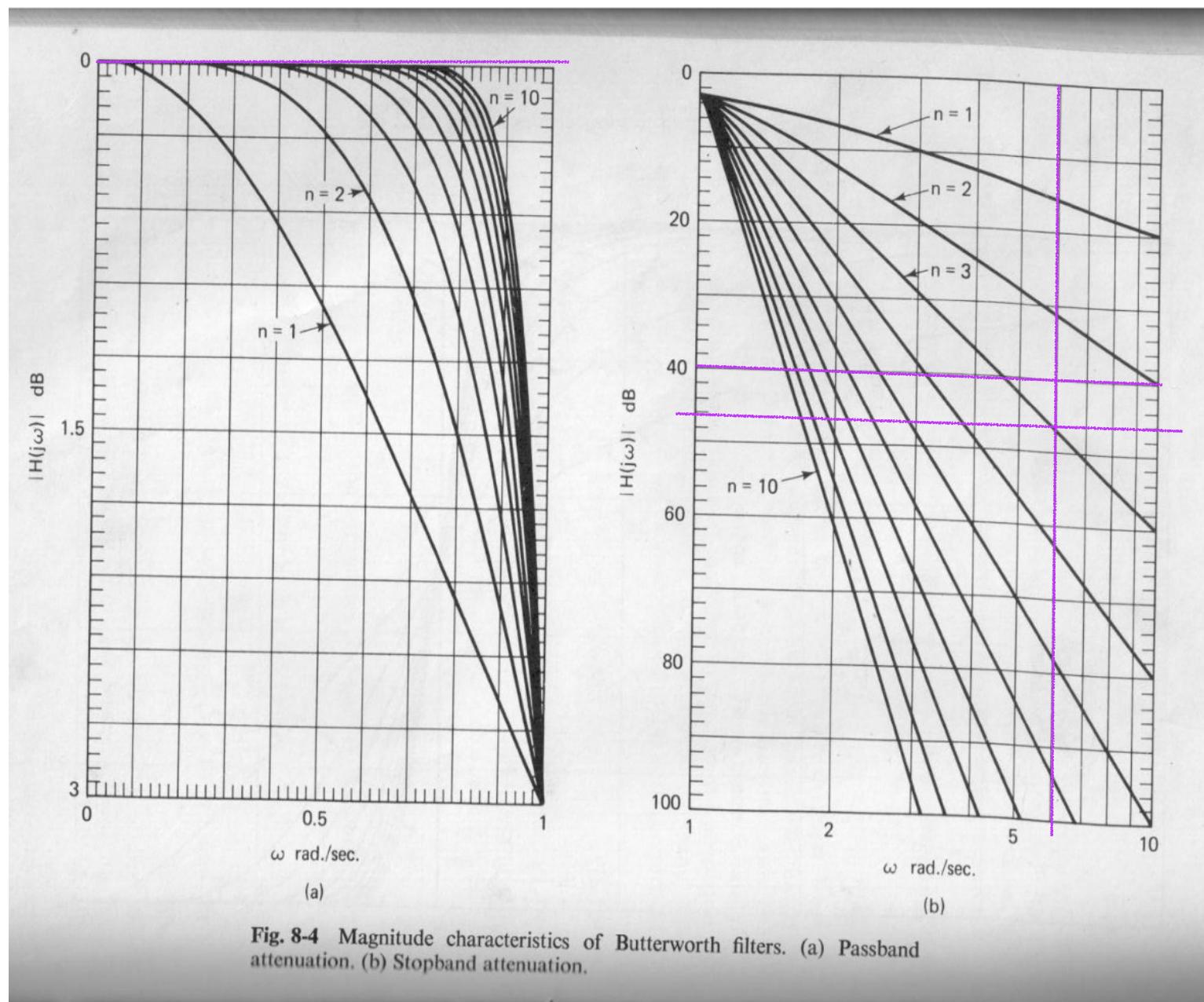


Fig. 8-4 Magnitude characteristics of Butterworth filters. (a) Passband attenuation, (b) Stopband attenuation.



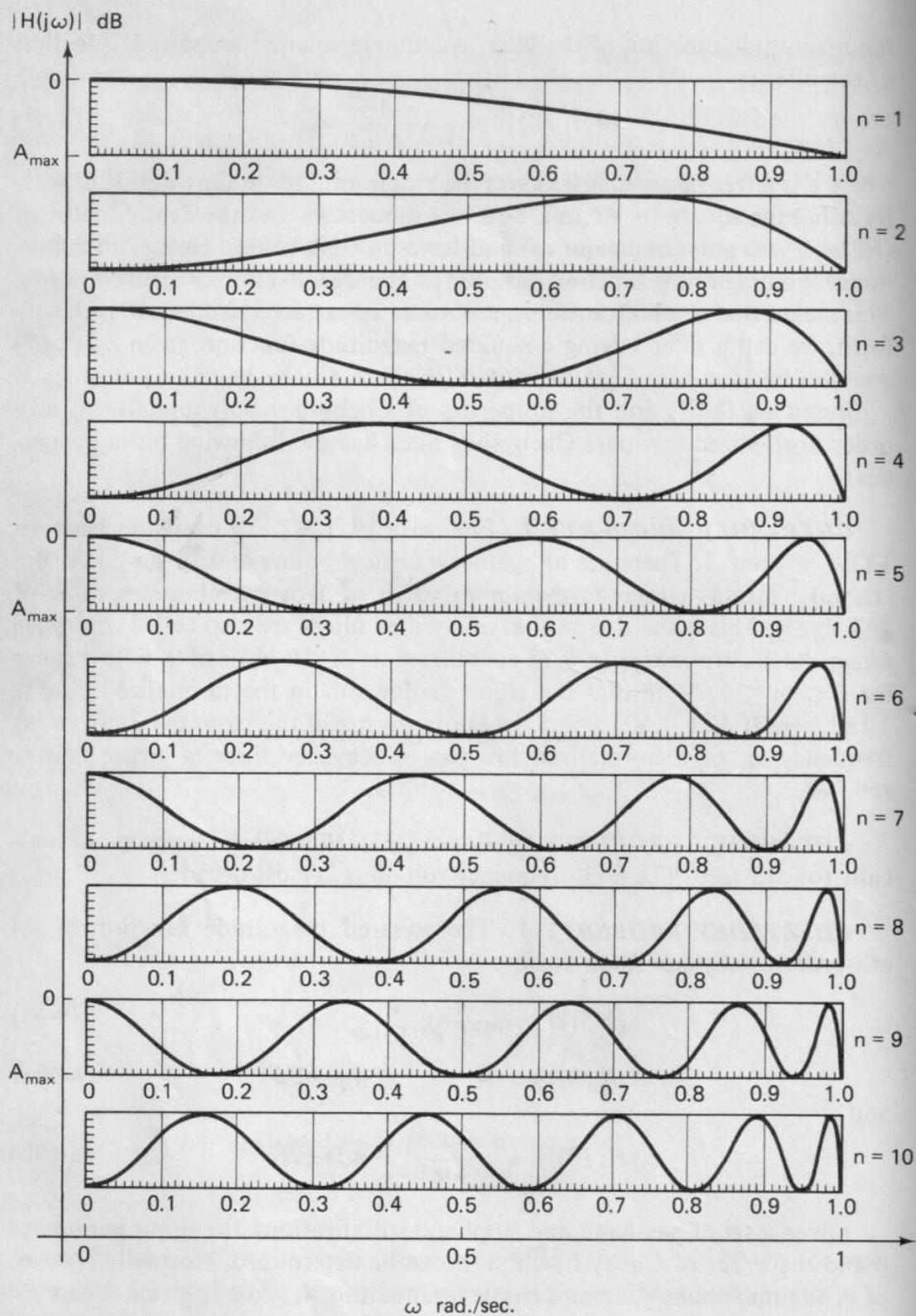


Fig. 8-14 Chebyshev passband ripples.

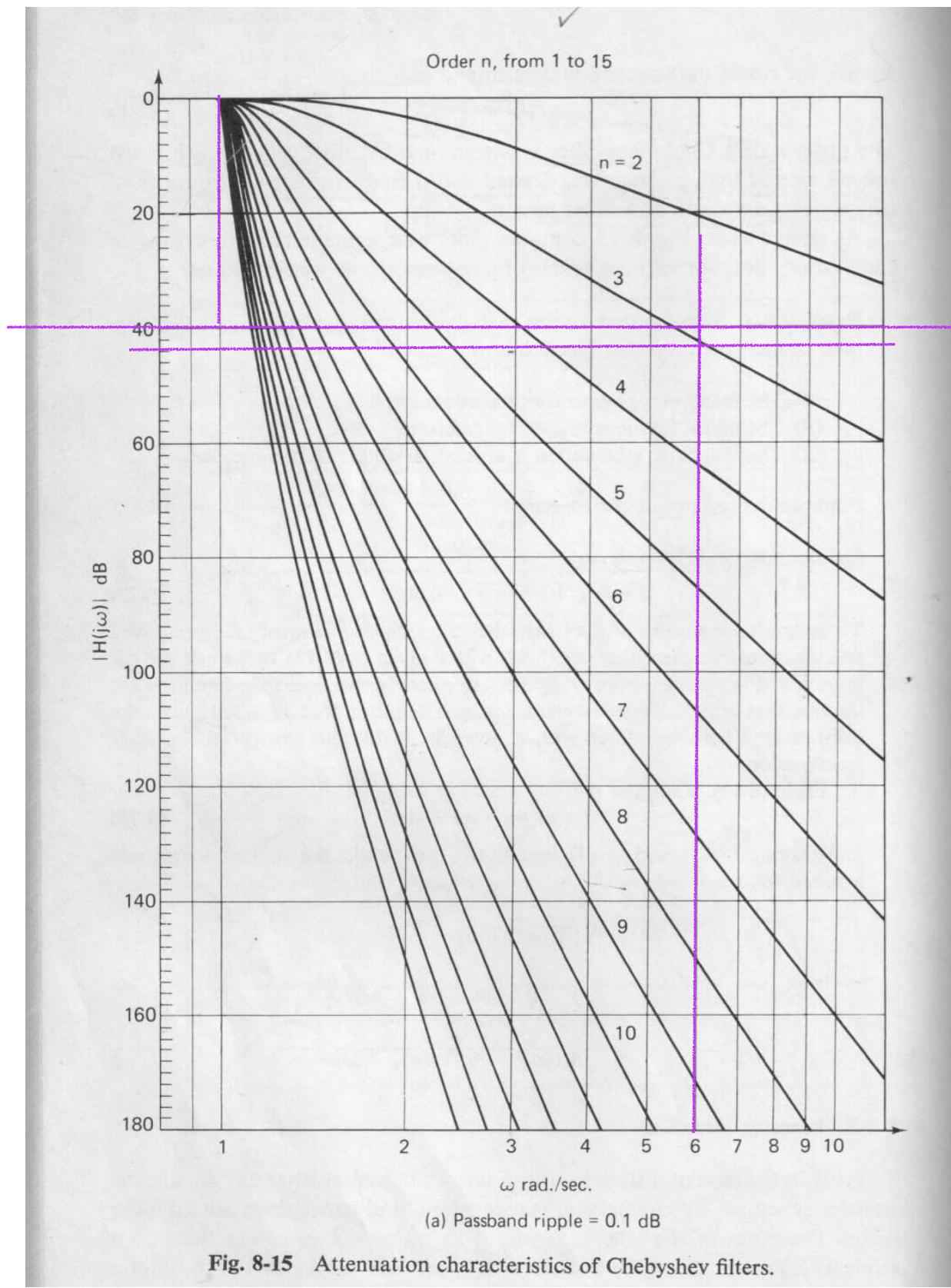

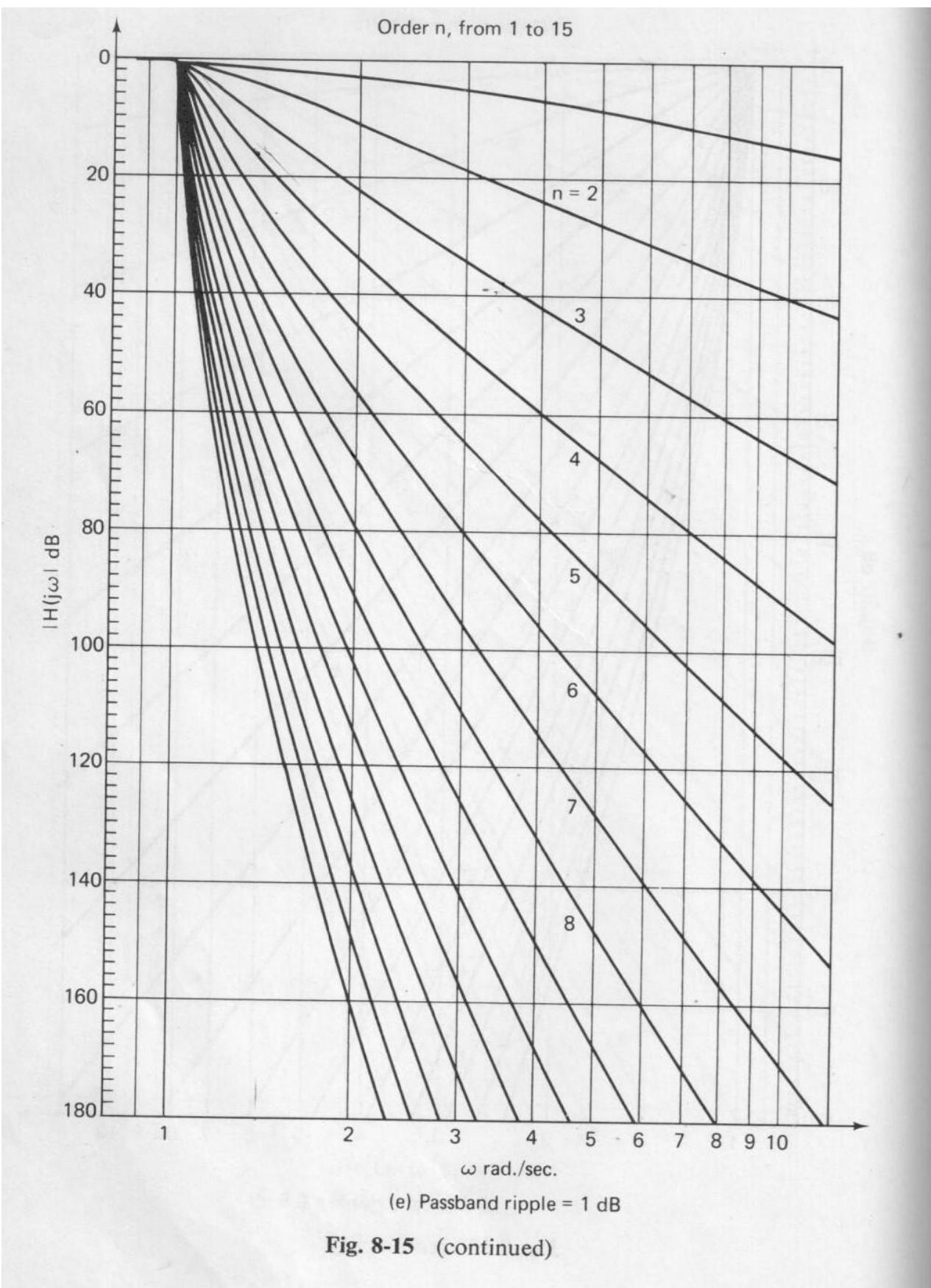

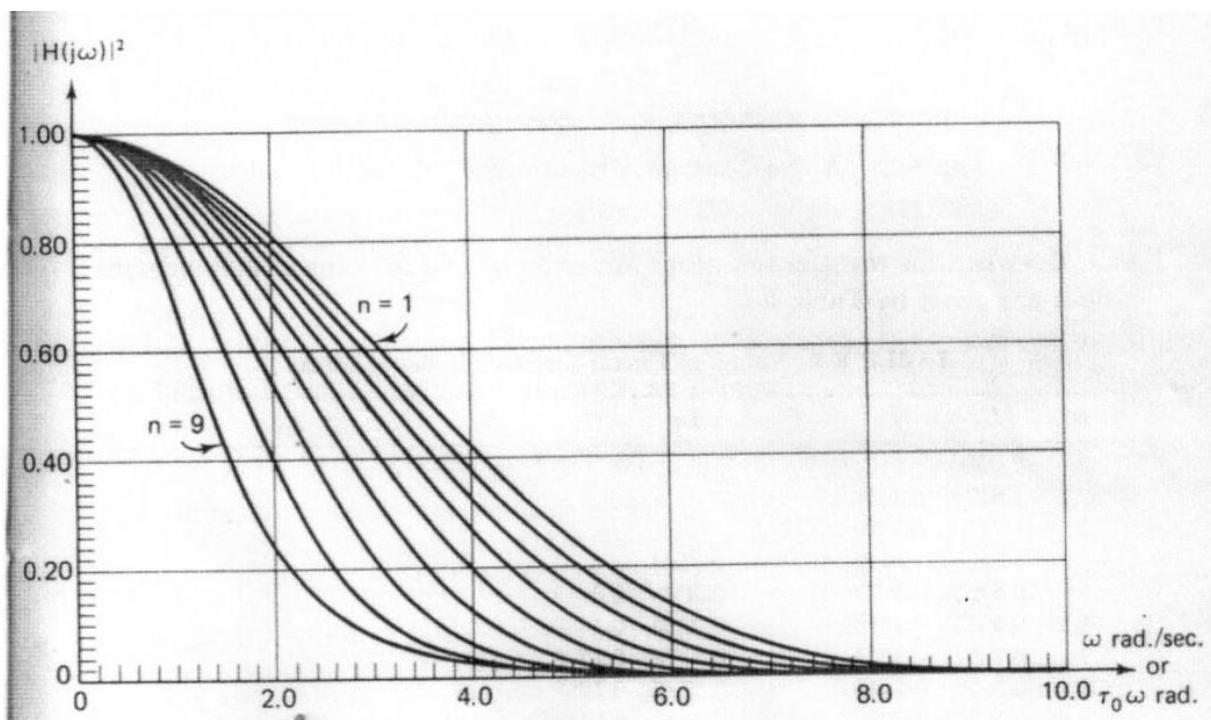


Fig. 8-22 Magnitude characteristics of Bessel filters.

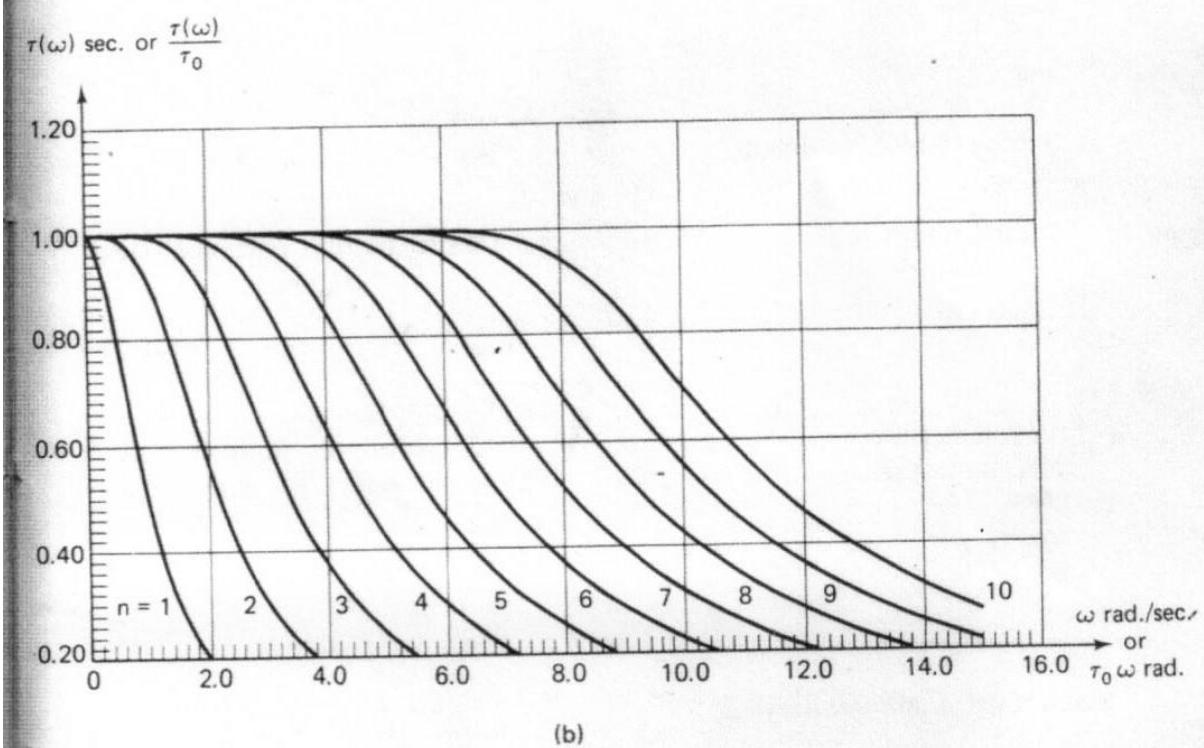
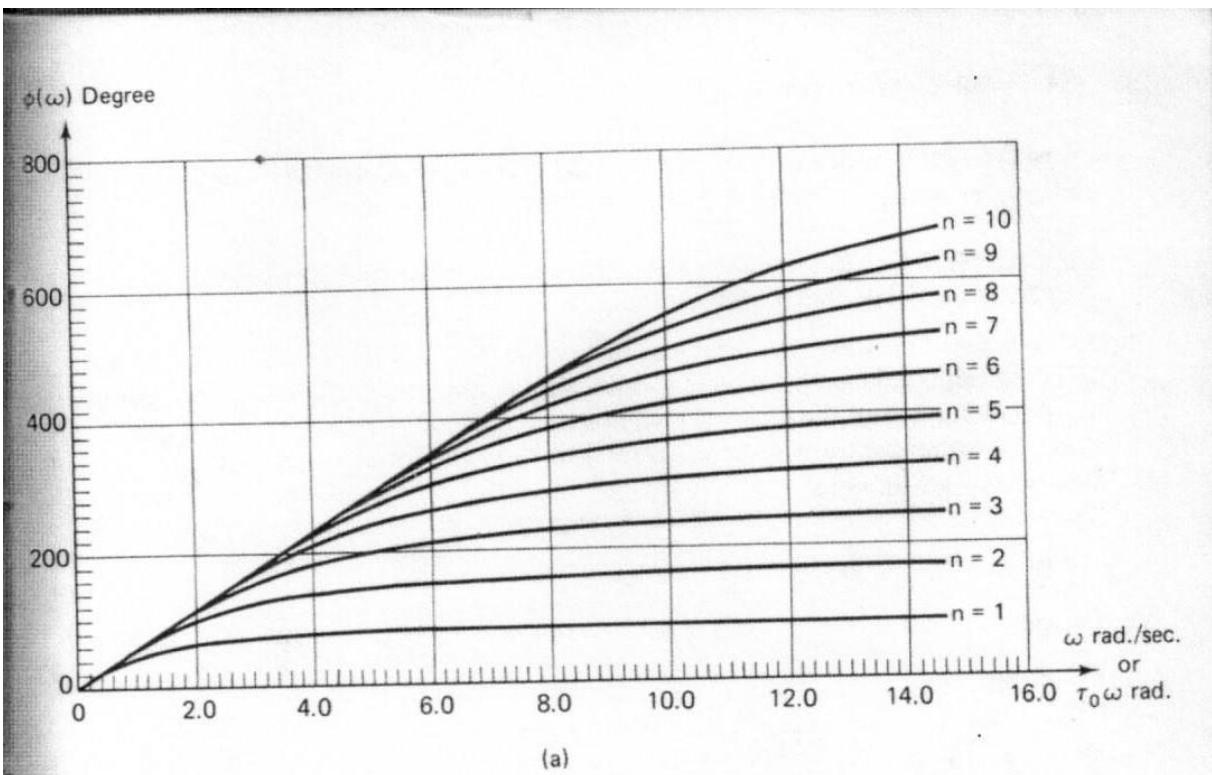


Fig. 8-21 (a) Phase characteristics of Bessel filters. (b) Group delay characteristics of Bessel filters.