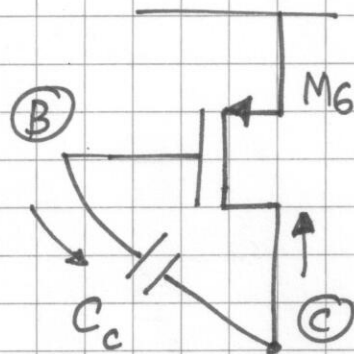



Cause of RHP Zero

C_c around inverting stage
 $\rightarrow \omega_z C_c V_B = g_{m6} V_B$ @ zero freq.

$$s \Rightarrow \omega_z = \frac{g_{m6}}{C_c}$$

\rightarrow Due to feedforward path.


Solⁿ Remove feedforward path.

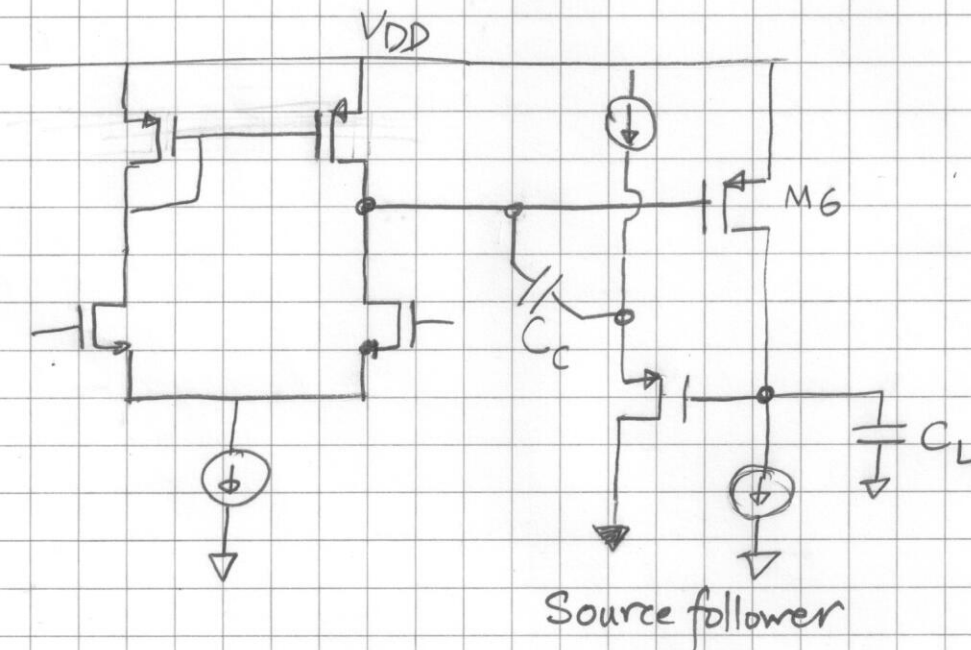

$\rightarrow P_D$ & P_{ND} remain same as before.

⊕ Power dissipation of SF.

⊖ SF frequency response. (must make sure that it doesn't deteriorate PM).

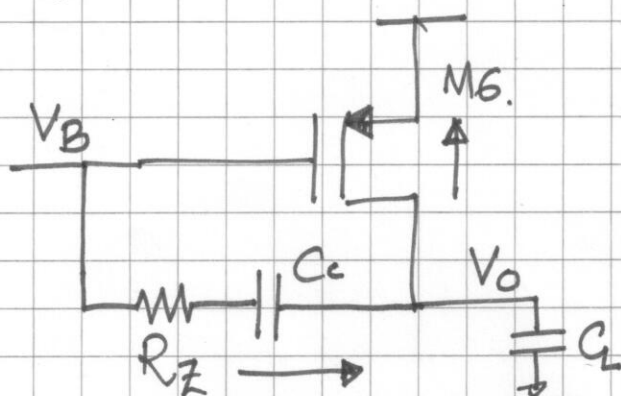Another idea

Location of zero.

At zero freq. ω_z

$$\frac{V_B}{\left(R_Z + \frac{1}{\omega_z C_C}\right)} = V_B g_{m6}$$

$$g_{m6} \left(R_Z + \frac{1}{\omega_z C_C}\right) = 1$$

$$\omega_z \frac{g_{m6}}{C_C} = (1 - g_{m6} R_Z) \Rightarrow \omega_z = \frac{g_{m6} / C_C}{(1 - g_{m6} R_Z)}$$

When $g_{m6} R_Z = 1 \Rightarrow R_Z = \frac{1}{g_{m6}}$

Zero moves to ∞ .

Better yet. When $g_m R_Z > 1$ $\omega_z \rightarrow$ LHP zero.


→ cancel out Non-dominant pole..

$$\omega_z = \frac{g_{m6} / C_C}{(1 - g_{m6} R_Z)} = - \frac{g_{m6}}{C_L} \quad \begin{matrix} \nearrow (-ve) \\ \text{(LHP Pole)} \\ \text{-ve sign.} \end{matrix}$$

$$\frac{C_L}{C_C} = g_m R_Z - 1 \Rightarrow R_Z = \frac{1}{g_{m6}} \left(1 + \frac{C_L}{C_C}\right)$$

Really Cool idea!!How do you achieve this. over PVT? R_Z - resistor. - to track $\frac{1}{g_m}$.

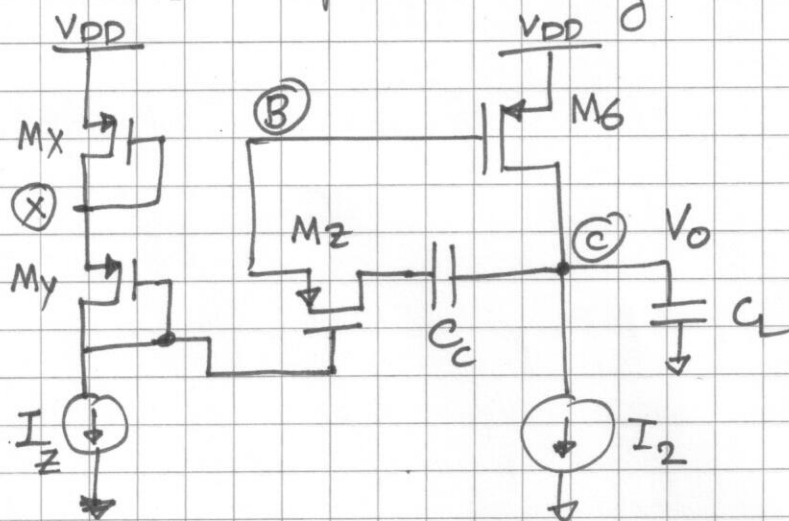$R_z \rightarrow$ implement using triode MOSFET.



TRACKING
BIAS.

M_z - Non Sat.

$$I = \left[(V_{SG} - |V_{TP}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right] \mu_p C_{ox} \left(\frac{W}{L} \right)_z$$

$$R_z^{\#} = \left. \frac{1}{\frac{\partial I}{\partial V_{SD}}} \right|_{V_{SD}=0} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_z (V_{SG} - |V_{TP}|)_z}$$

Looks like
 g_m form.

By design (X) tracks (B) (DC bias)

$$\Rightarrow V_{SG_x} = V_{SG_6} \rightarrow \text{choose } I_z \text{ \& } \left(\frac{W}{L} \right)_x$$

$$R_z = \frac{1}{g_{m_6}} \left(1 + \frac{C_L}{C_c} \right) = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_z (V_{SG} - |V_{TP}|)_z}$$

$$\frac{(1 + \frac{C_L}{C_c})}{\mu_p C_{ox} \left(\frac{W}{L} \right)_6 (V_{SG} - |V_{TP}|)_6} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_z (V_{SG} - |V_{TP}|)_z}$$

$$\left(\frac{W}{L} \right)_z = \left(\frac{W}{L} \right)_6 \cdot \frac{(V_{SG} - |V_{TP}|)_6}{(V_{SG} - |V_{TP}|)_y} \cdot \left(\frac{C_c}{C_c + C_L} \right)$$


$$\left(\frac{W}{L}\right)_Z = \left(\frac{W}{L}\right)_G \sqrt{\frac{2I_G}{\left(\frac{W}{L}\right)_G \mu_p C_{ox}}} \times \sqrt{\frac{\left(\frac{W}{L}\right)_Y \mu_p C_{ox}}{2I_Z}} \cdot \left(\frac{C_c}{C_c + C_L}\right)$$

$$= \sqrt{\frac{I_G}{I_Z}} \cdot \sqrt{\left(\frac{W}{L}\right)_G \cdot \left(\frac{W}{L}\right)_Y} \cdot \left(\frac{C_c}{C_c + C_L}\right)$$

→ All dependent on ratios — Not abs values


→ Tracking compensation.

* Black, Allstot, Reed. — JSSC Dec 83

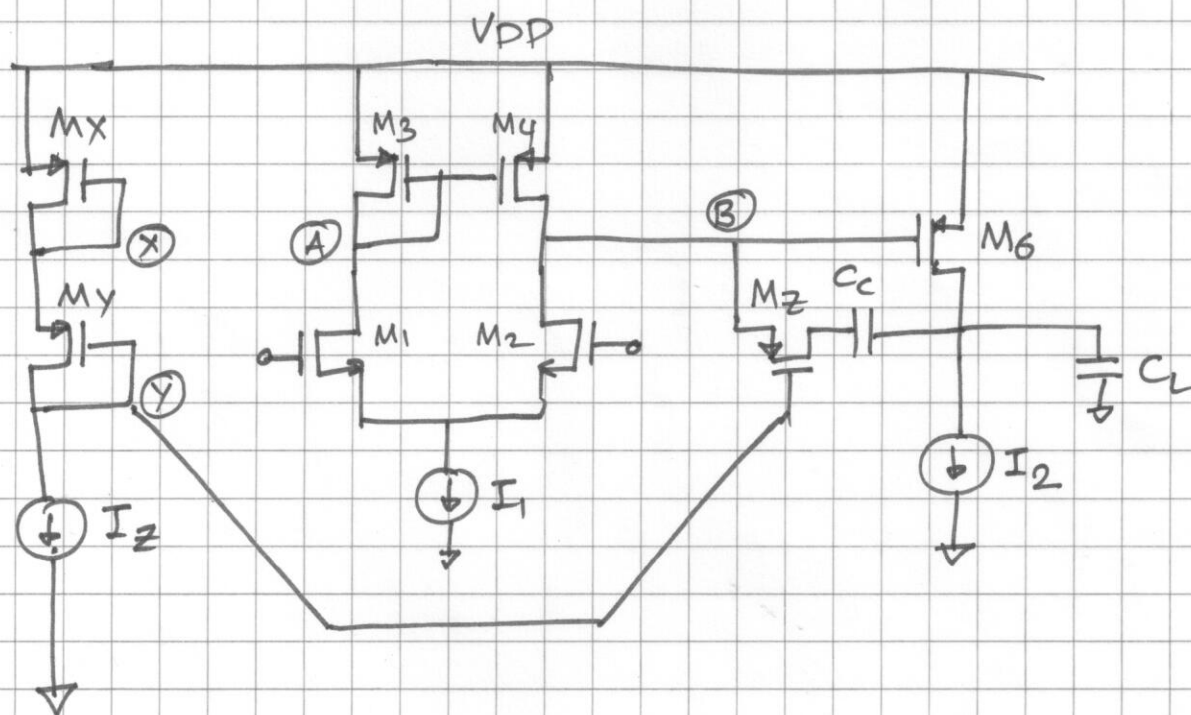

OPAMP ARCHITECTURES

Telescopic CASCODE OPAMP.

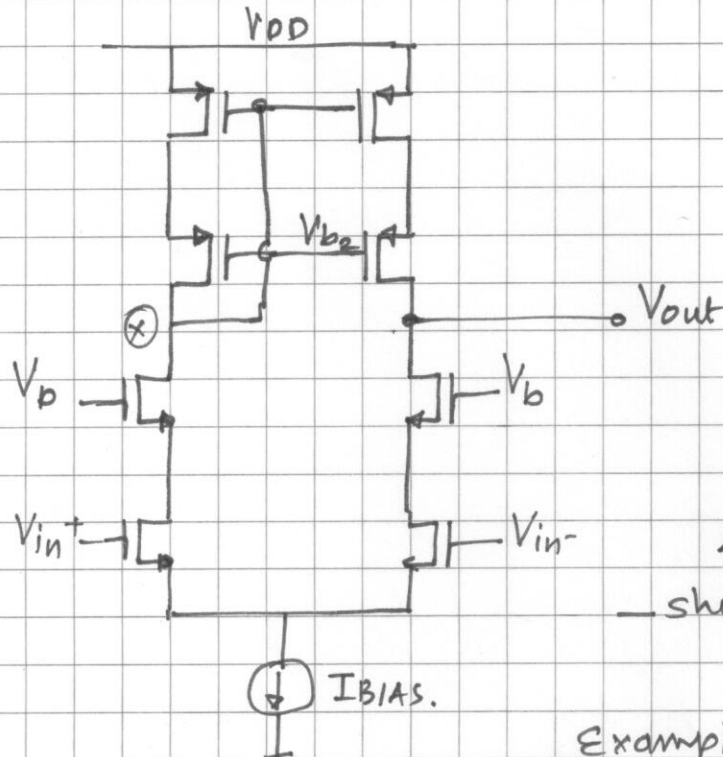



* Single Stage.
Low power - current reuse

* Limited output swing.

$$(V_{DD} - 2V_{dsat_n} - 2|V_{dsat_p}| - V_{IBIAS})$$

* unity gain buffer difficult
— shunting -ve i/p to o/p.


Example

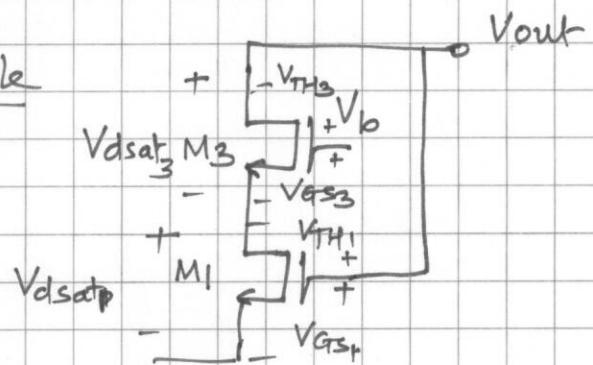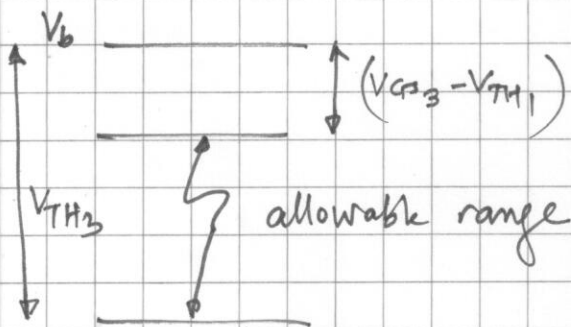

$$Gain = g_{mN} [g_{mN} r_{oN}^2 || g_{mP} r_{oP}^2]$$

* Mirror pole @ x

OPAMP using current mirrors

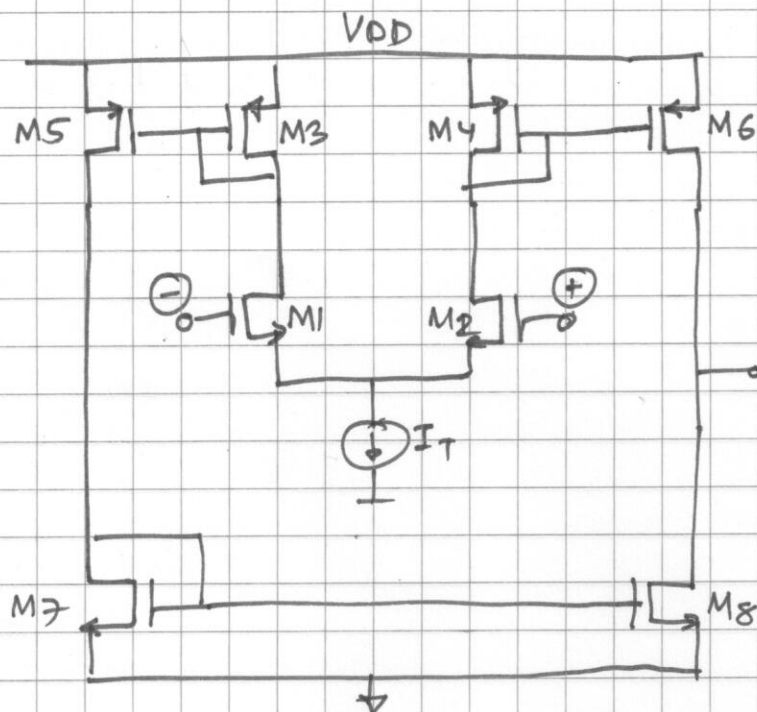

Output pole
dominant-


unloaded
may become
unstable.

Slew rate. $= \frac{I_T}{C_L}$ (if all mirrors are unity gain)

$= M \frac{I_T}{C_L}$ (Mirror gain = M)




Low gain $\frac{g_m r_o}{2}$

Gain Improvement using cascodes

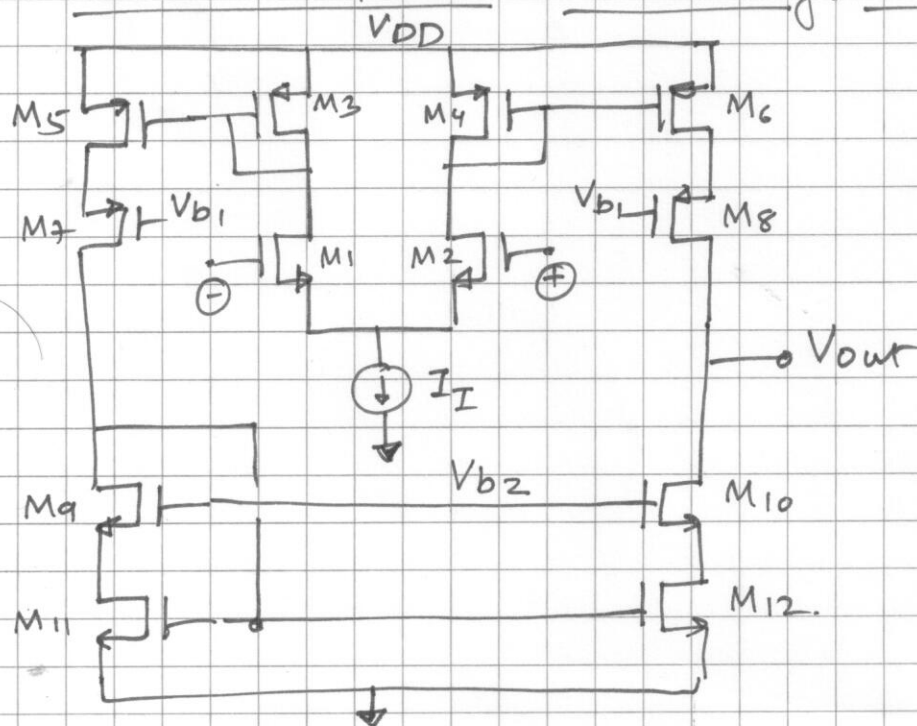

Gain $\frac{(g_m r_o)^2}{2}$


Consider PMOS mirror

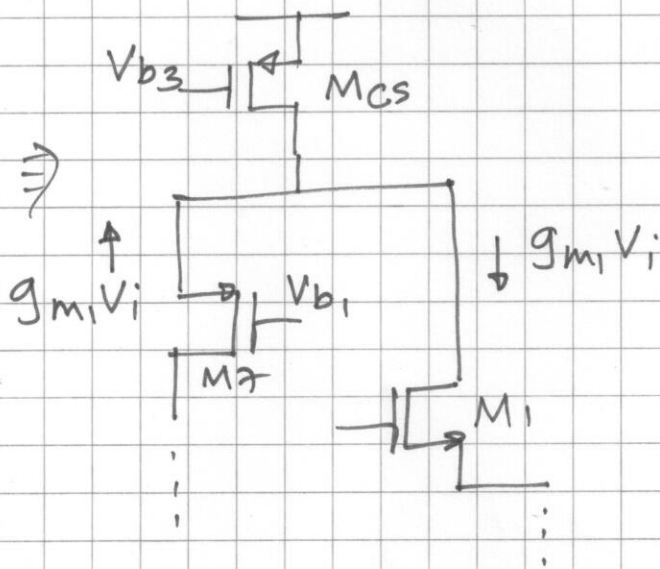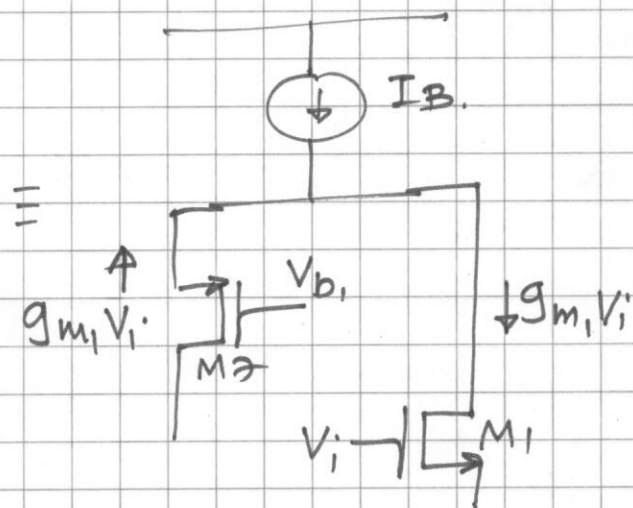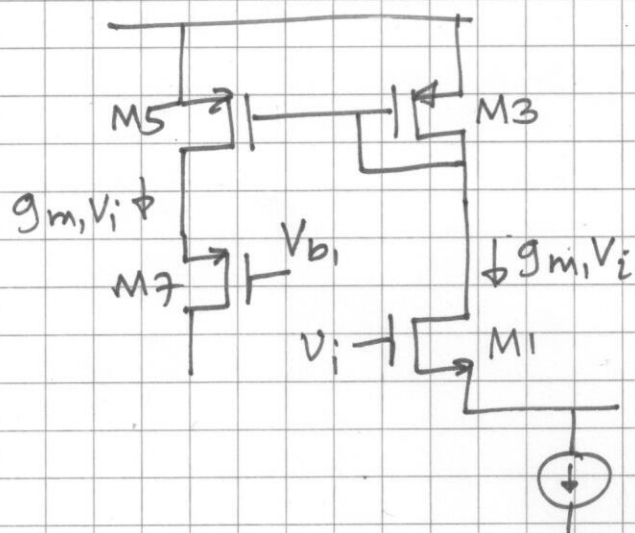


Signal Current flows to o/p.
only sign change

Key Concept of folded Cascode opamp
Avoid Mirror pole. M3/M5 & M4/M6

Folded Cascode OPAMP

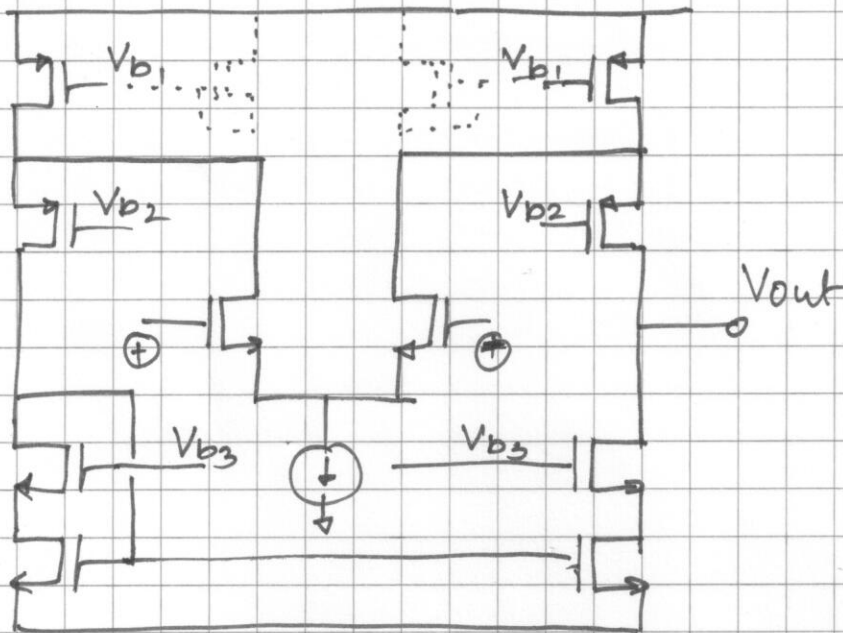

Redrawing

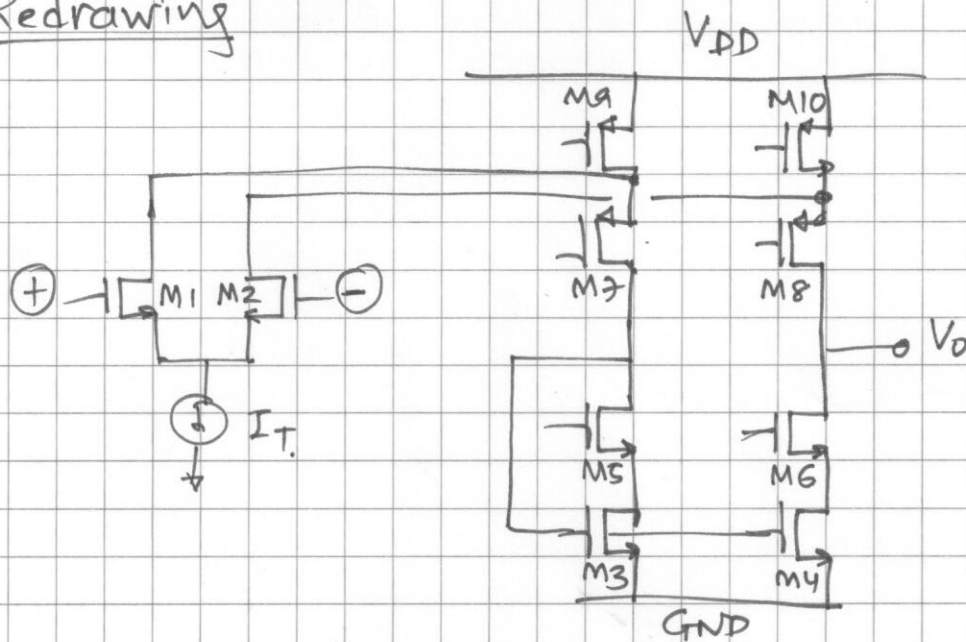


Advantage - No stacking of cascode on top of i/p devices.

Large o/p swing ($V_{DD} - 4V_{dsat}$)

Calculate gain How?

Short o/p to DC $\Rightarrow G_m = g_{m1}$

Output impedance R_{out} .

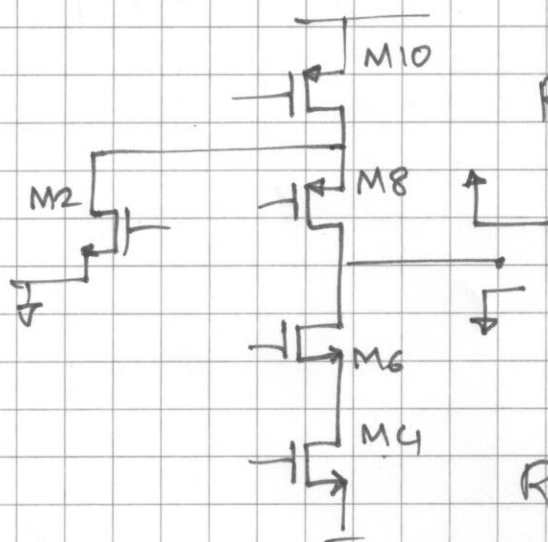

$$R_{out\uparrow} = g_{m8} r_{o8} [r_{o10} \parallel r_{o2}]$$

$$R_{out\downarrow} = (g_{m6} \cdot r_{o6}) r_{o4}$$

$$R_{out} = R_{out\uparrow} \parallel R_{out\downarrow}$$

// impedances lets use g .

$$g_{out\uparrow} = \frac{(g_{ds2} + g_{ds10})}{g_{m8} \cdot r_{o8}}$$

$$g_{out\downarrow} = \frac{g_{ds4}}{g_{m6} \cdot r_{o6}}$$

diff pair

$$\text{Gain} = \frac{G_m}{g_{out}} = \frac{g_{m1} \cdot \cancel{g_{m2}}}{\frac{(g_{ds2} + g_{ds10}) + g_{ds4}}{g_{m8} r_{o8} \quad g_{m6} r_{o6}}}$$

Extreme simplification all g_m s equal. all g_{ds} equal.

$$\begin{aligned} \text{Gain} &= \frac{g_m}{\frac{2g_{ds}}{g_m r_o} + \frac{g_{ds}}{g_m r_o}} = \frac{g_m}{\frac{3g_{ds}}{g_m r_o}} \cdot g_m r_o \\ &= \frac{1}{3} (g_m r_o)^2 \end{aligned}$$