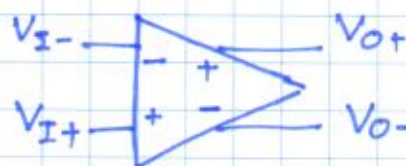


1 OCT 2019

Standard Differential Amplifier (Lecture 7)



- Differential i/p
- Common-mode (i/p) is rejected by diff pair with current source
- Single-Ended Output (DE to SE conversion) using mirrors.



Std. Diff. AmplifierFully Differential AmplifierFully Differential Amplifier

- Differential i/p, Differential o/p.
- i/p common-mode is rejected by i/p diff pair
- O/p common-mode set independently

Why?


- ✱ Increased (double) o/p swing.
- ✱ Excellent Power Supply rejection
- ✱ Immune to noise coupling from any external sources.

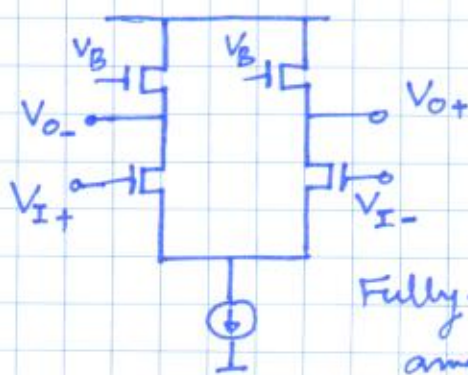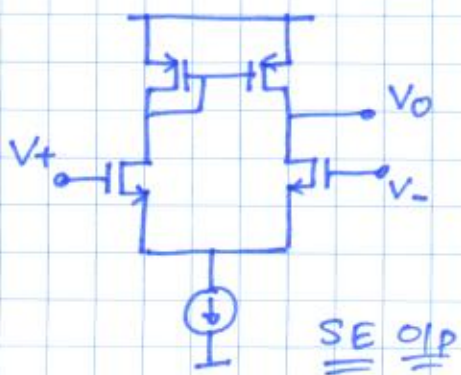Simplest Example✱ Improved freq. response NO DE2SE ConversionFully Diff. amplifier

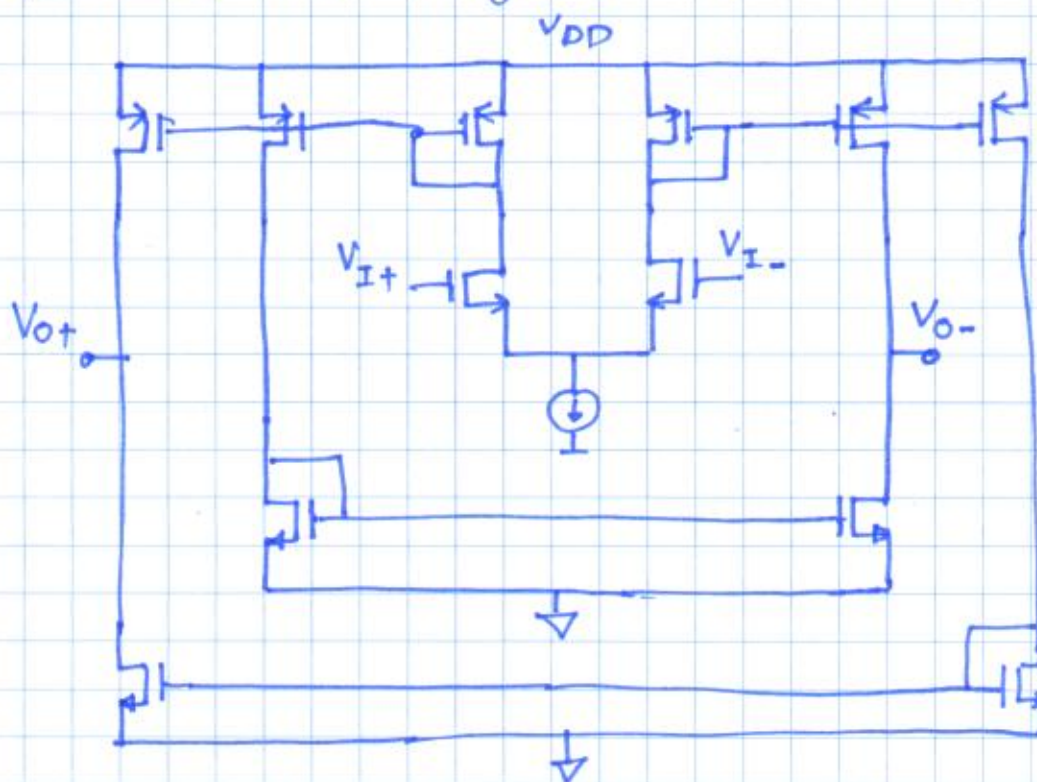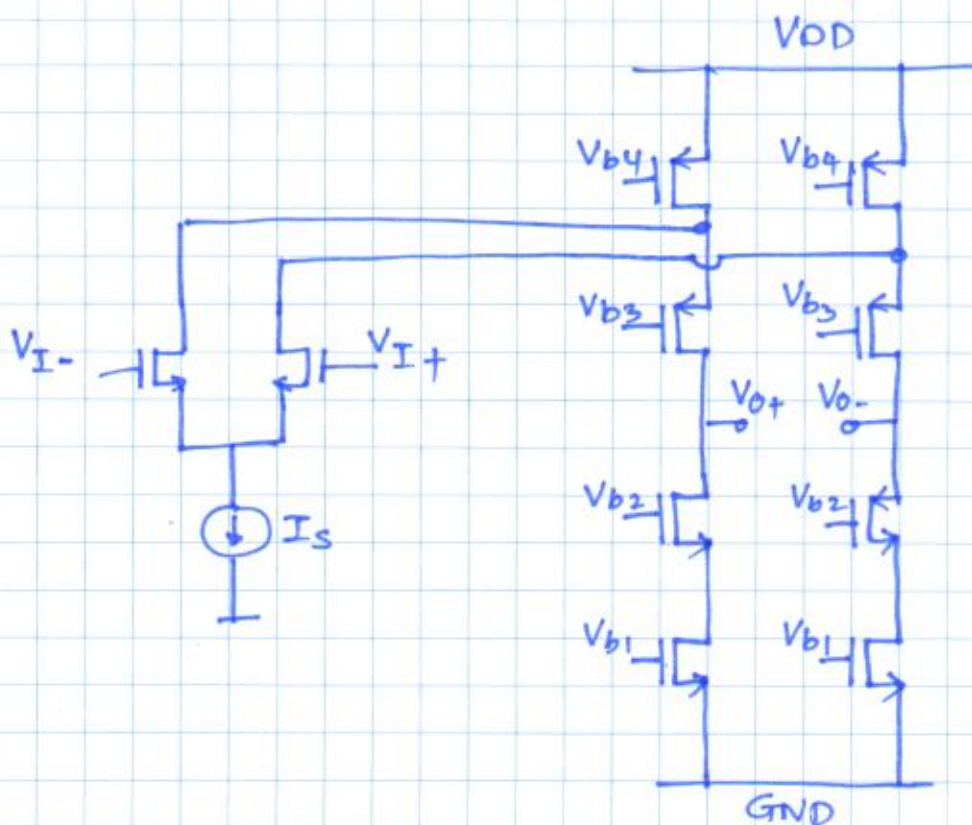
Examples of fully differential AmplifiersFully Diff Folded Cascode Opamp




## Fully-Differential Two Stage Opamp

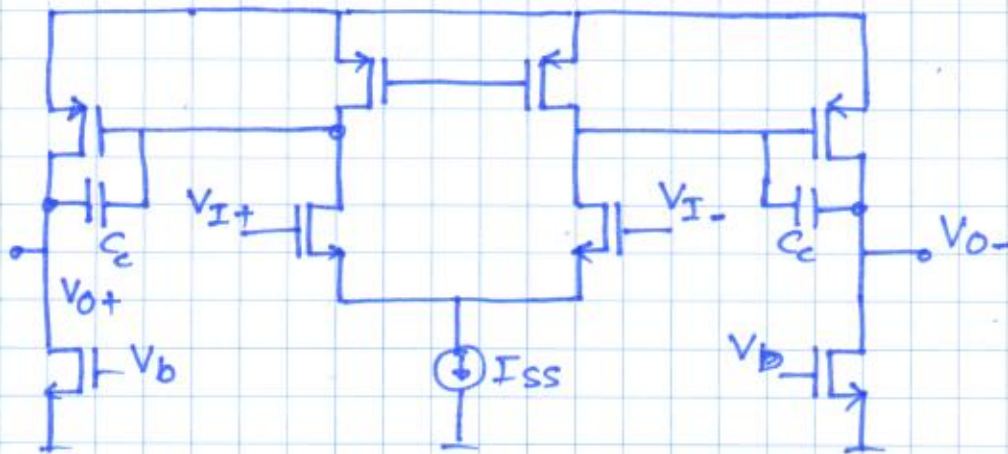

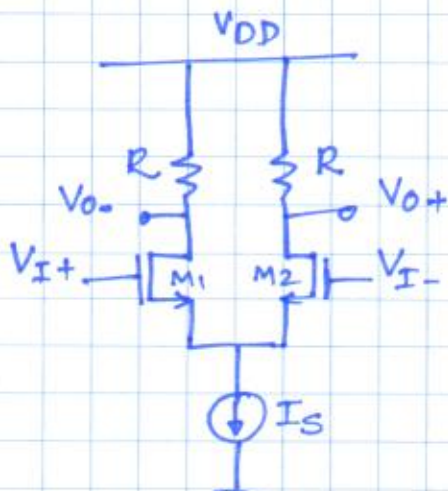Consider Simple diff pair with  $R_{load}$ . (fully diff)



$\Rightarrow$

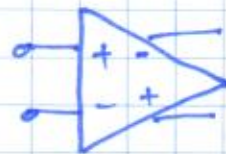


Assume:  $V_{I+} = V_{I-} = V_{ICM}$ .

$M_1, M_2$  sat.

$$V_{OCM} = V_{DD} - \frac{I_S R}{2} \leftarrow \text{very well defined.}$$


Current Source loading

High Gain

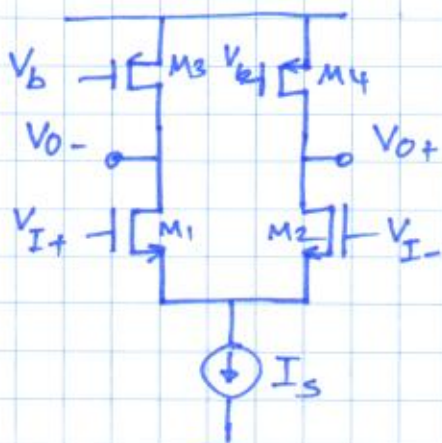

For common mode i/p  $V_{ICM}$ .

Assume all Transistor in Sat.

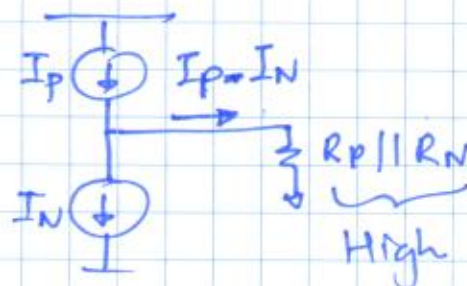


$V_{OCM}$  undefined.



- $I_p$ ;  $I_N$  are defined by process, temp, voltage  
 → will change.  
 → Even mismatches will impact  $V_{ocm}$ .  
 → Tweaking  $I_p$ ,  $I_N$  to get  $V_{ocm} = V_{DD}/2$   
 → DOES NOT work. -  $V_{ocm}$  will keep changing with PVT & mismatches.  
 → Need Feedback at Op to stabilize output common-mode voltage.  
 → Note: Differential feedback does not correct common-mode.

### Example

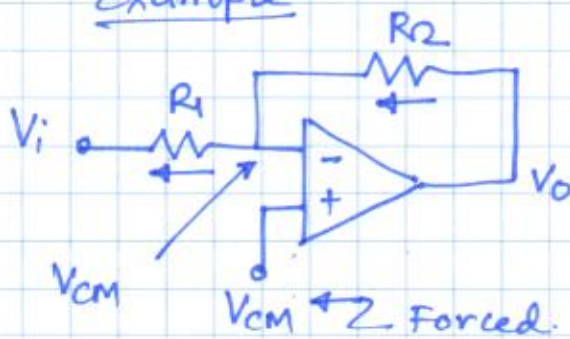


$$\frac{V_o - V_{cm}}{R_2} = \frac{V_{cm} - V_i}{R_1}$$

$$V_o = \frac{R_2}{R_1} (V_{cm} - V_i) + V_{cm}$$

$$= -\frac{R_2}{R_1} V_i + \left(1 + \frac{R_2}{R_1}\right) V_{cm}$$

Op DC (Common Mode) very well defined.

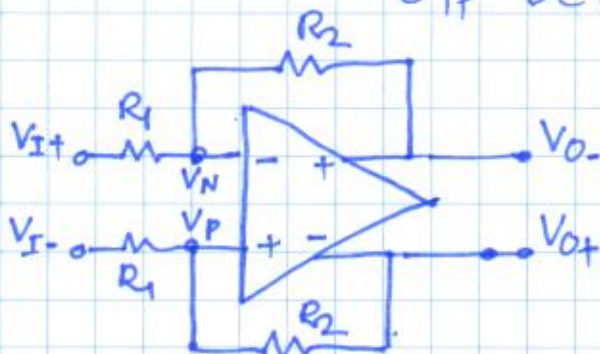


Lets assume  $(V_{I+}, V_{I-})_{cm} = V_{icm} = 1.5V$

$$R_1 = R_2 = R$$

$V_p, V_n$  can take any values


$V_{op}, V_{om}$  can take any values

Op CM poorly defined

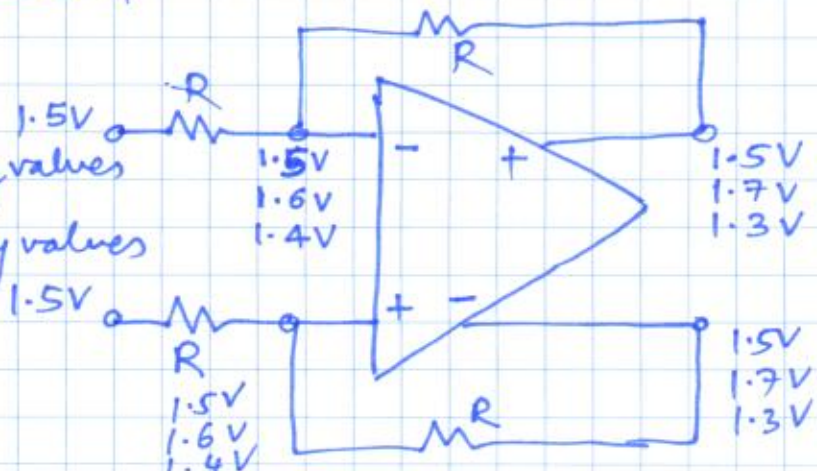

Need CMFB Common-Mode Feedback circuit  
 → Required for high gain fully differential ckt.

### Simple Example

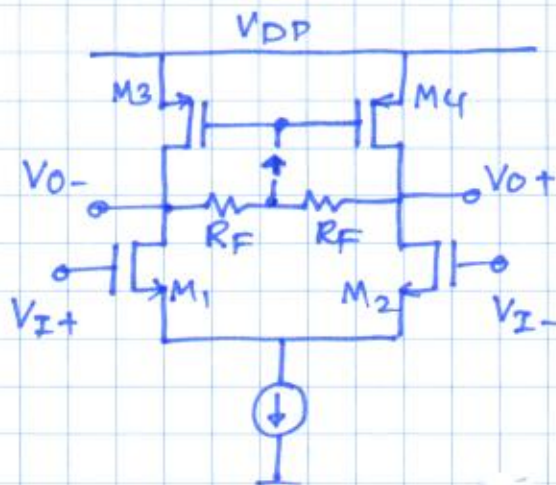


Diff gain  $g_m (r_{o1} \parallel r_{o3} \parallel R_F)$   
 $R_F \rightarrow \text{large}$

O/p Common-mode

$$V_{OCM} = V_{DD} - |V_{GS3}|$$

$$V_{DD \min} = 2V_{dsat} + |V_{GS3}| \\ = 3V_{dsat} + |V_{Tp}|$$

### Generic CMFB Strategy

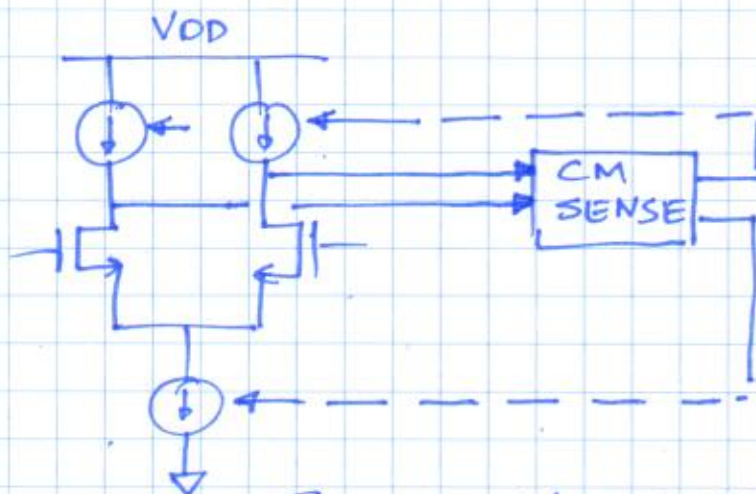


Sense o/p common-mode voltage  
 & adjust one of current sources.





# CMFB using MOSFETS in triode region.

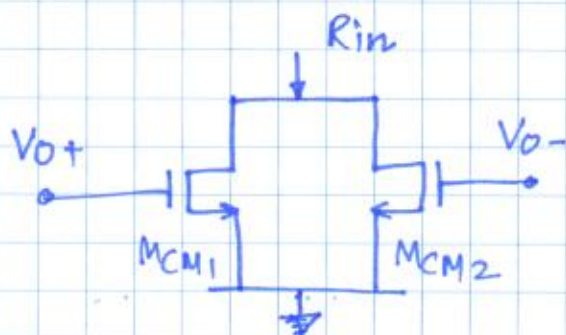

$$R_{in} = R_{CM1} \parallel R_{CM2}$$

Triode region Resistance

$$R_{in} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{O+} - V_{TH})} \parallel \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{O-} - V_{TH})}$$



$$= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{O+} + V_{O-} - 2V_{TH})}$$

$$\propto \frac{1}{V_{CM}}$$

← Independent of  
( $V_{O+} - V_{O-}$ )  
(diff o/p voltage)



# CMFB using triode region transistors

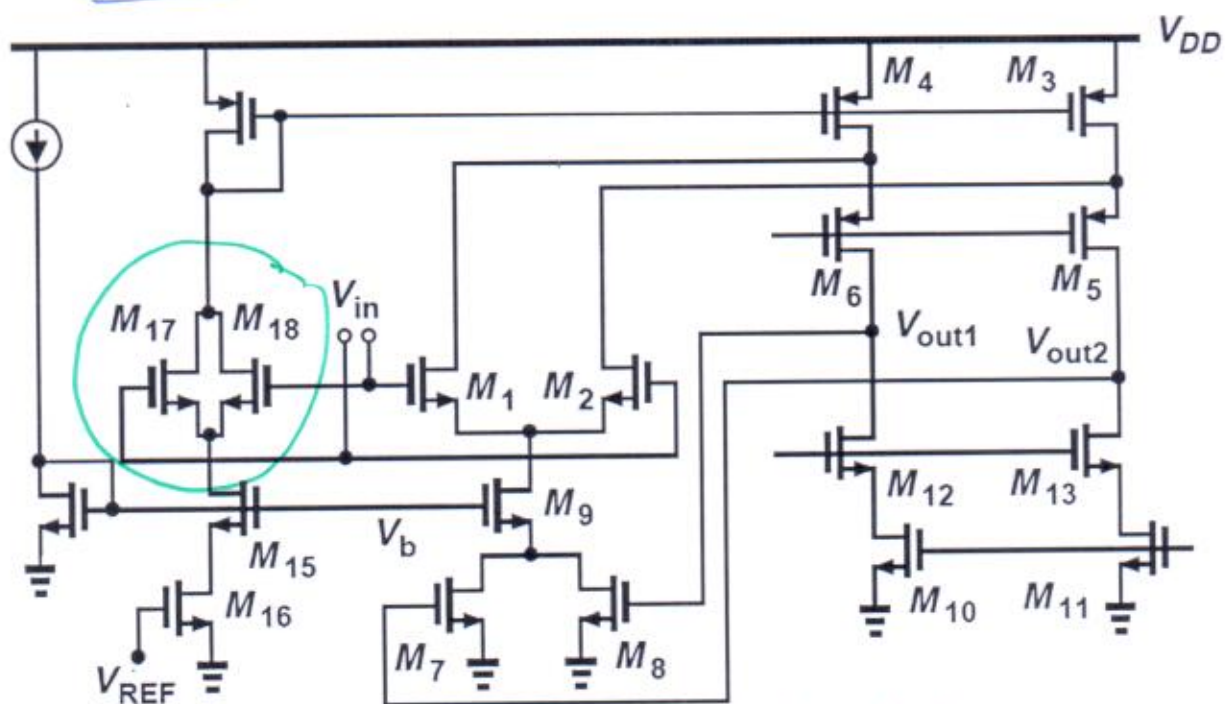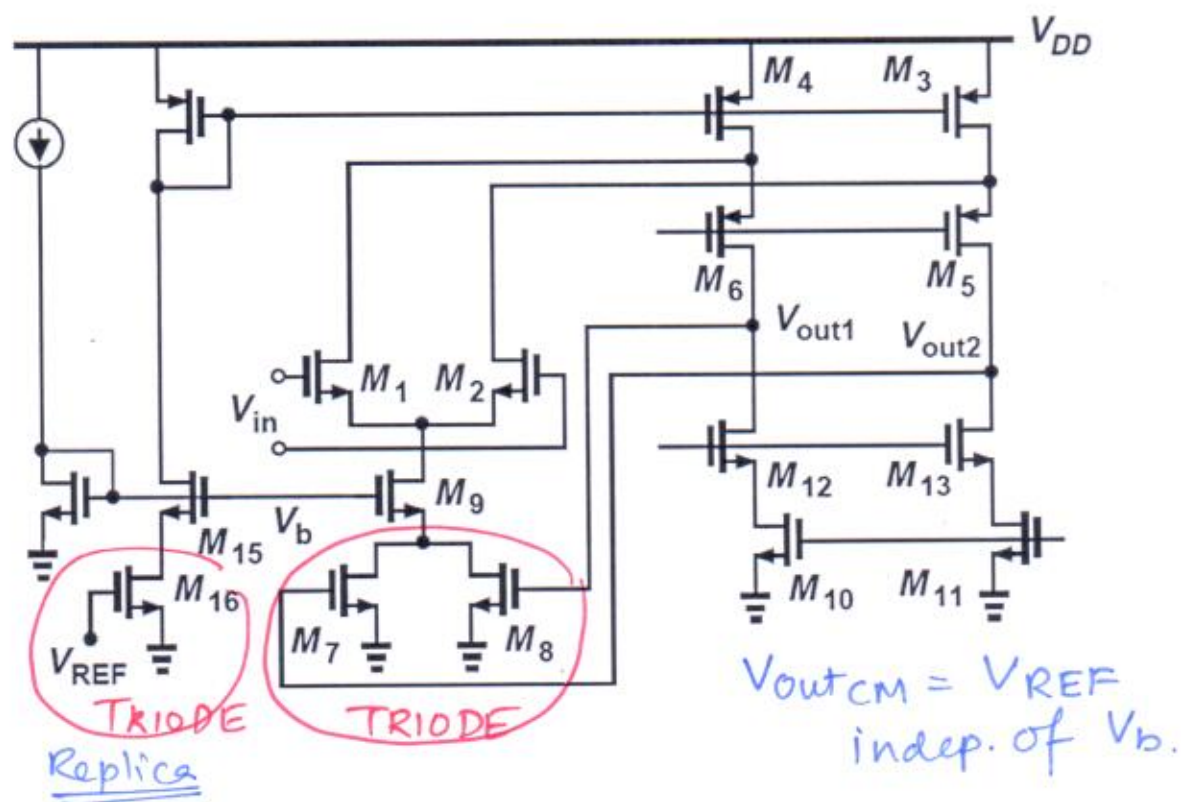

M17 & M18 - Replica of diff pair  
 → Make sure  $V_{DS15} = V_{DS9}$   
 Indep. of Ch. length Mod?