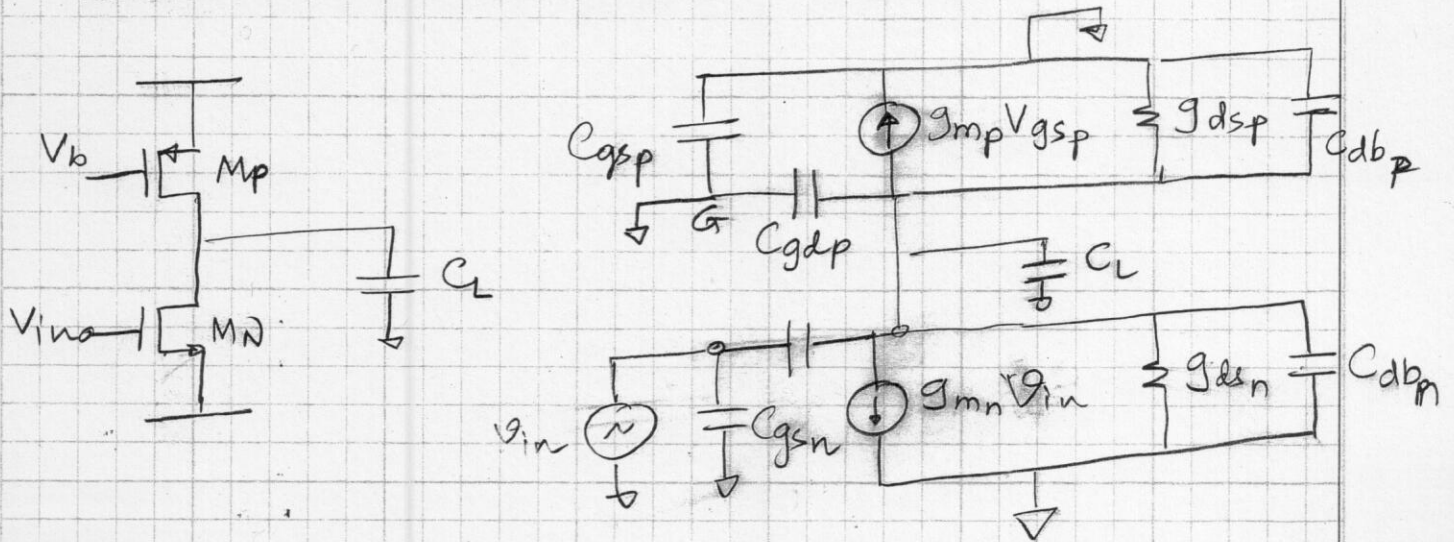


13 AUG 2018


C-S Amplifier with Current source load. FREQUENCY RESPONSE - Detailed



Neglect g_{mp} , g_{mbsn} , g_{mbsp} - No sig.

Neglect C_{gsn} , C_{gsp} - driven by v_{in}

Simplify

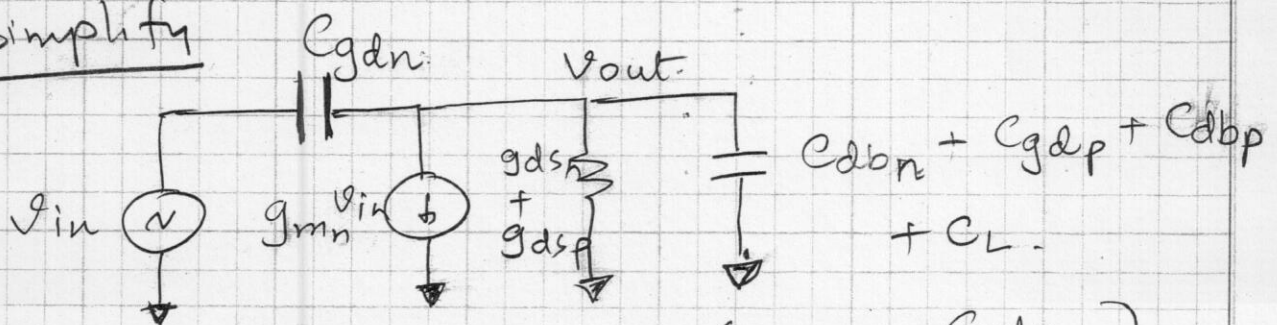

$$A_v = \frac{V_{out}}{V_{in}} = \frac{-g_{mn}}{g_{dsn} + g_{dsp}} \frac{\left(1 - s \frac{C_{gdn}}{g_{mn}}\right)}{\left(1 + s \frac{C_{gdn} + C_{gdp} + C_{dbn} + C_{dbp}}{g_{dsn} + g_{dsp}}\right)}$$


RHP zero

$$\omega_z = + \frac{g_{mn}}{C_{gdn}}$$

LHP pole

$$\omega_p = - \frac{g_{out}}{C_{out}} = - \frac{g_{dsn} + g_{dsp}}{C_{gdn} + C_{gdp} + C_{dbn} + C_{dbp} + C_L}$$


Bode Plots

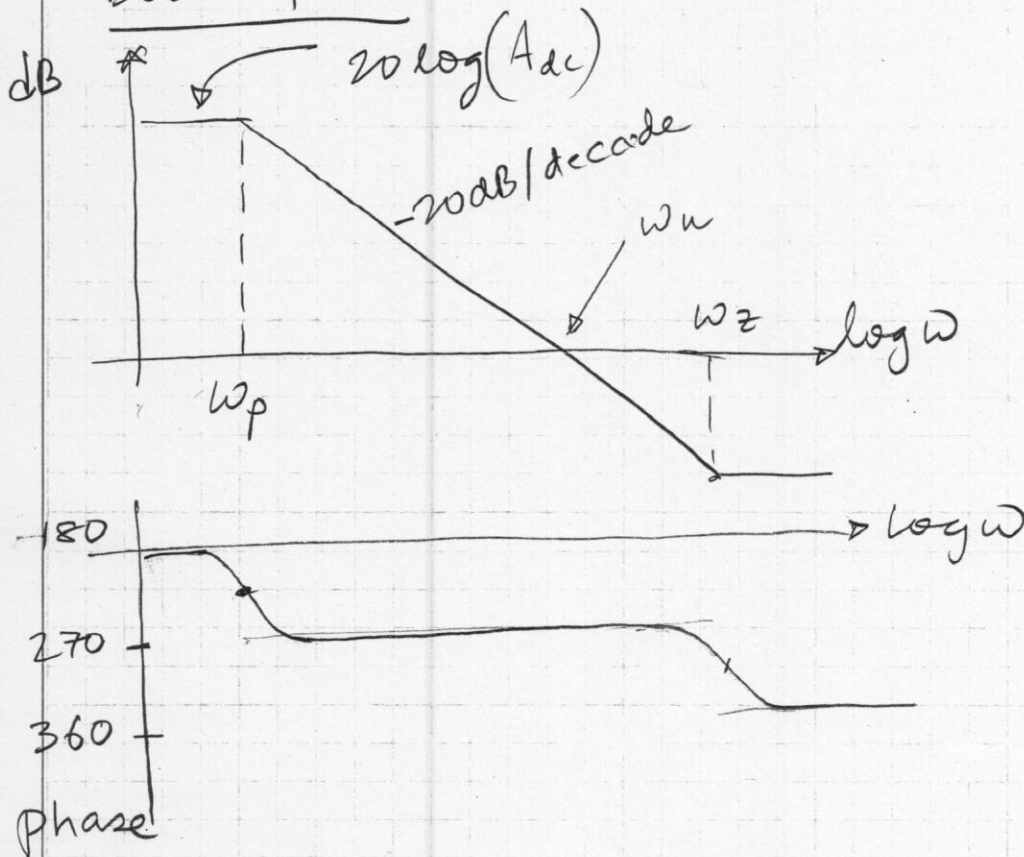

In Closed-loop feedback system (study Later)

RHP zero

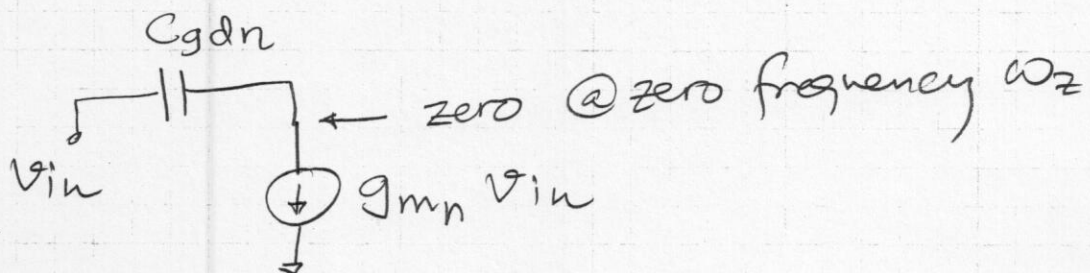- keeps gain high @ high freq.
- phase shift degrades @ high freq.





$$s_z C_{gdn} \cdot V_{in} = g_{mn} V_{in}$$

$$s_z = \frac{g_{mn}}{C_{gdn}} \leftarrow \text{Real \& +ve RHP.}$$

Quick way to analyse.

cap across inverting stage
RHP zero
cap across non inverting stage

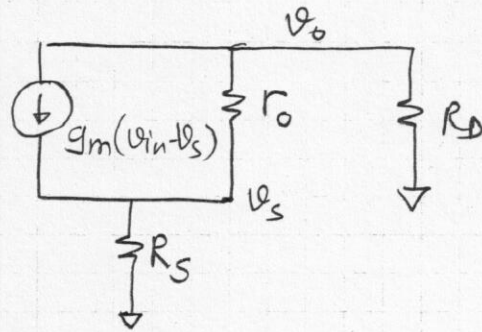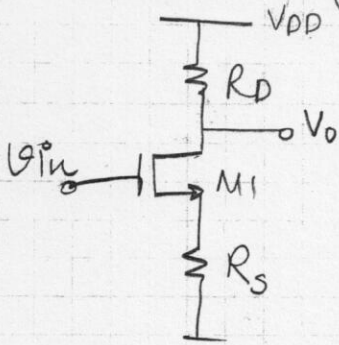Source degeneration


$$g_m(v_{in} - v_s) + \frac{v_o - v_s}{r_o} = \frac{v_s}{R_s} \quad \Bigg| \quad \text{Also} \quad \frac{v_s}{R_s} = -\frac{v_o}{R_D} \Rightarrow \underline{\underline{v_s = -\frac{R_s}{R_D} v_o}}$$

$$g_m v_{in} - \left[g_m + \frac{1}{r_o} + \frac{1}{R_s} \right] v_s + \frac{v_o}{r_o} = 0$$

$$g_m v_{in} + \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right) \frac{R_s}{R_D} v_o + \frac{v_o}{r_o} = 0$$

$$g_m r_o R_D v_{in} + \left[(g_m r_o + 1 + \frac{r_o}{R_s}) R_s + R_D \right] v_o = 0$$
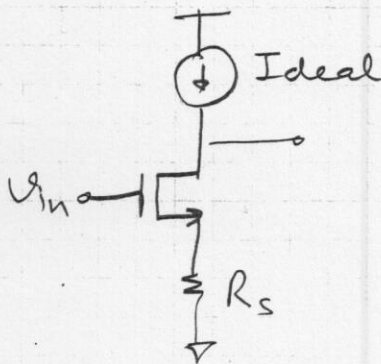
$$\boxed{\frac{v_{out}}{v_{in}} = \frac{-g_m r_o R_D}{R_D + r_o + R_s(g_m r_o + 1)}}$$



$$\frac{v_{out}}{v_{in}} = -g_m r_o$$

$$\left\{ R_D = \infty \right.$$

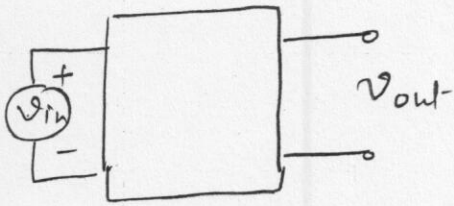
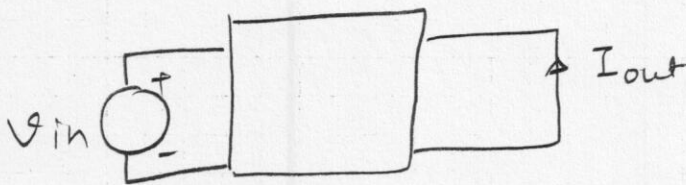
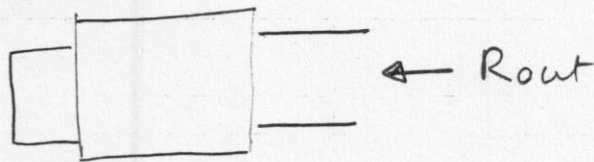
Theorem

Figure out voltage gain

$$\frac{v_{out}}{v_{in}}$$



① Short ckt G_m 

$$G_m = \frac{I_{out}}{v_{in}}$$

② R_{out} calculation

Voltage Gain $\frac{v_{out}}{v_{in}} = -G_m R_{out}$

Source degen Example

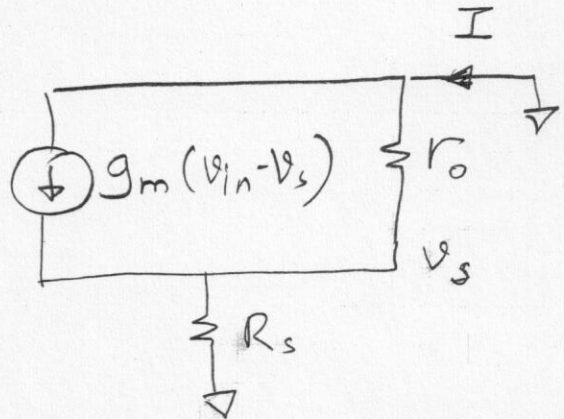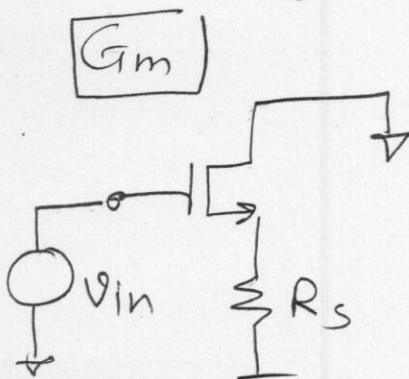

$$g_m(v_{in} - v_s) - \frac{v_s}{r_o} - \frac{v_s}{R_s} = 0$$

$$g_m v_{in} = \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right) v_s$$

$$I = \frac{v_s}{R_s} = \frac{g_m v_{in}}{R_s \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)}$$


$$G_m = \frac{I}{v_{in}} = \frac{g_m}{g_m R_s + 1 + \frac{R_s}{r_o}}$$

\Rightarrow if r_o is large

$$G_m \approx \frac{g_m}{g_m R_s + 1}$$

$$G_m = \frac{g_m r_o}{(g_m r_o + 1) R_s + r_o}$$

ROUT Calculation

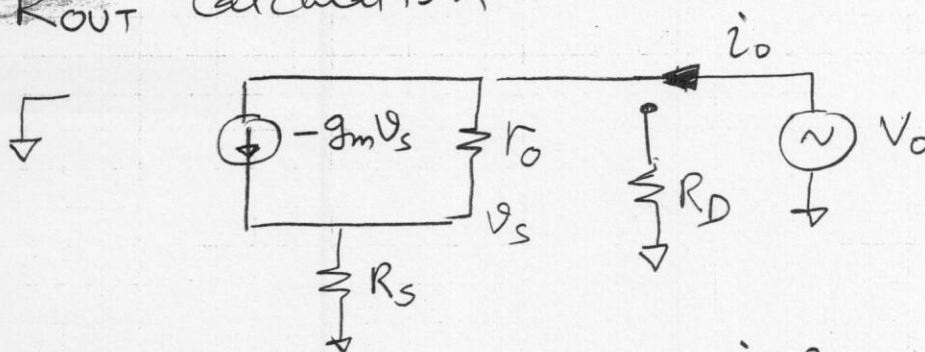

① W/o R_D

$$v_s = i_o R_s$$

$$g_m v_s + i_o = \frac{v_o - v_s}{r_o}$$

$$(g_m i_o R_s + i_o) r_o = v_o - i_o R_s$$

$$\frac{v_o}{i_o} = [(1 + g_m r_o) R_s + r_o]$$

$$\approx g_m r_o R_s + r_o$$

including $\parallel R_D$

$$R_{out} = \frac{[(1 + g_m r_o) R_s + r_o] R_D}{R_D + r_o + (1 + g_m r_o) R_s}$$

$$\frac{V_{out}}{V_{in}} = -G_m R_{out}$$

$$= - \frac{g_m r_o}{\cancel{(g_m r_o + 1) R_s + r_o}} \times \frac{\cancel{[(g_m r_o + 1) R_s + r_o] R_D}}{R_D + r_o + (1 + g_m r_o) R_s}$$

$$= - \frac{g_m r_o R_D}{R_D + r_o + (1 + g_m r_o) R_s} \leftarrow$$

Same as what we directly derived !!!


If we ignore r_o

$$G_m = \frac{g_m}{1 + g_m R_s} ; R_{out} = R_D$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_m R_D}{1 + g_m R_s}$$

{(Quick Calculation)}

Common Gate amplifier

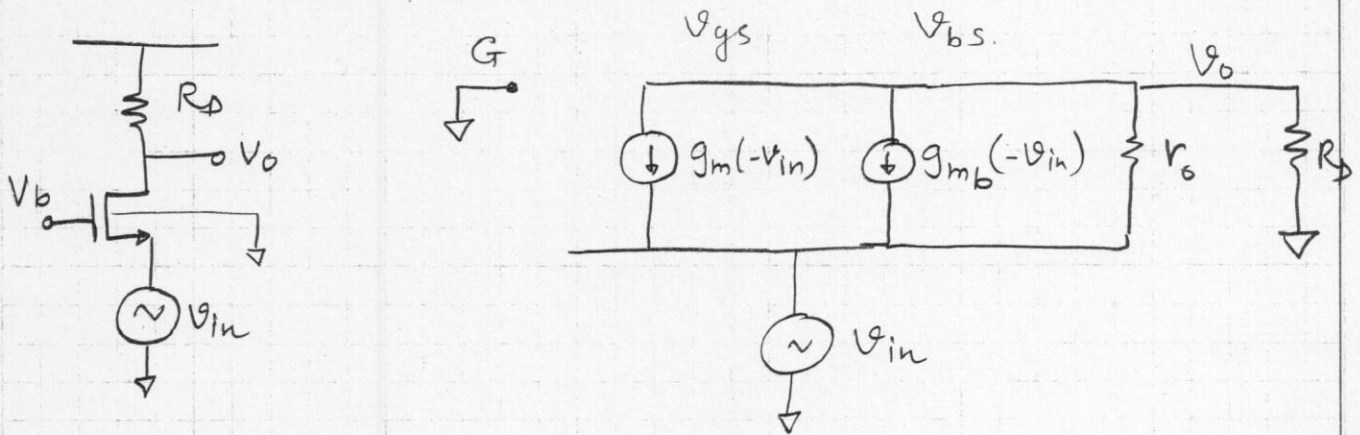

$$\frac{V_o}{R_D} = g_m V_{in} + g_{mb} V_{in} + \frac{V_{in} - V_o}{r_o}$$

$$\frac{V_o}{R_D} \left(\frac{1}{R_D} + \frac{1}{r_o} \right) = (g_m + g_{mb}) V_{in} + \frac{V_{in}}{r_o}$$

$$\frac{V_o}{V_{in}} = \frac{((g_m + g_{mb}) r_o + 1) R_D}{(r_o + R_D)}$$

If we ignore body effect

$$\frac{V_o}{V_{in}} = \frac{g_m r_o + 1}{(r_o + R_D)} R_D \longrightarrow \star$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{V_o / R_D} = \frac{R_D \cdot (r_o + R_D)}{(g_m r_o + 1) R_D}$$

$$Z_{in} = \frac{r_o + R_D}{(g_m r_o + 1)} \approx \frac{r_o + R_D}{g_m r_o}$$


Drain impedance div by $(g_m r_o)$ ↓



ONLY WHEN $R_D \ll r_o$

$$Z_{in} \approx r_o / (g_m r_o) = 1/g_m \text{ (low impedance)}$$

In case of source degeneration

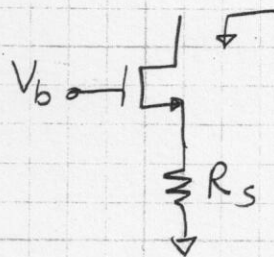

$$R_{out} \approx (g_m r_o) R_s + r_o$$

$R_{out} \uparrow$ by $(g_m r_o)$




Cascode from Vacuum tubes
1939 - Frederick HUNT
Cascode of two triodes instead of pentode
I guitar amp

Cascode CS Amplifier

Figure out G_m & R_{out}

$$A_v = -G_m R_{out}$$

G_m calculation

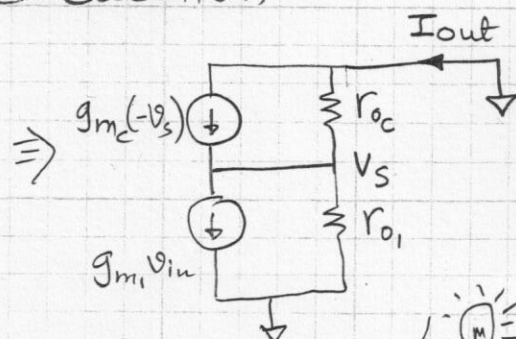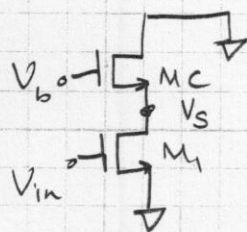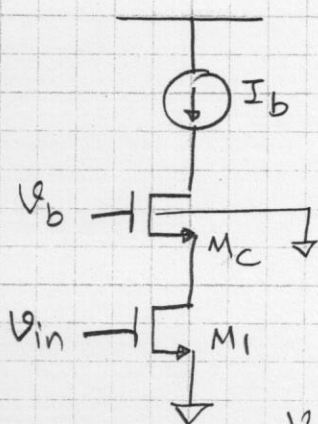

$$g_{m_i} v_{in} + \frac{v_s}{r_{o_i}} + g_{m_c} v_s + \frac{v_s}{r_{o_c}} = 0$$

$$g_{m_i} v_{in} + v_s \left(\frac{1}{r_{o_i}} + \frac{1}{r_{o_c}} + g_{m_c} \right) = 0$$

$g_{ds_i} \quad g_{ds_c}$

$$v_s = \frac{-g_{m_i} v_{in}}{(g_{ds_i} + g_{ds_c} + g_{m_c})}$$


$$i_{out} = g_{m_i} v_{in} + v_s g_{ds_i} = g_{m_i} v_{in} - \frac{g_{m_i} v_{in} g_{ds_i}}{(g_{ds_i} + g_{ds_c} + g_{m_c})}$$

Use g_{ds} & r_o interchange for convenience

$$\frac{i_{out}}{v_{in}} = \frac{g_{m1} (g_{ds1} + g_{dsc} + g_{mc} - g_{ds1})}{(g_{ds1} + g_{dsc} + g_{mc})}$$

$$G_m \approx g_{m1}$$

Rout Calculation

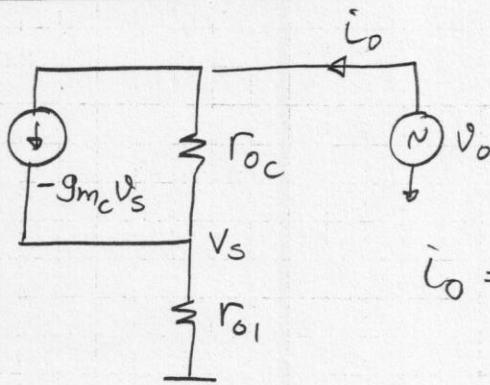

$$v_s = i_o r_{o1}$$

$$i_o = -g_{m_c} v_s + \frac{(v_o - v_s)}{r_{oc}}$$

$$i_o = -g_{m_c} i_o r_{o1} + \frac{(v_o - i_o r_{o1})}{r_{oc}}$$

$$i_o r_{oc} = -g_{m_c} i_o r_{o1} r_{oc} + v_o - i_o r_{o1}$$

$$R_{out} = \frac{v_o}{i_o} = \underbrace{(g_{m_c} r_{oc} r_{o1})}_{\text{large}} + \underbrace{(r_{o1} + r_{oc})}_{\text{small}}$$

$$R_{out} \approx (g_{m_c} r_{oc}) r_{o1}$$

Cascode self gain multiplier effect

$$A_v = (g_{m1} r_{o1}) (g_{m_c} r_{oc}) \approx (g_m r_o)^2$$

Benefits of cascoding

- (+) $R_{out} \rightarrow$ self gain of cascode multiplication
 - (+) gain \uparrow squared
 - (-) Headroom Reduced to keep two transistors in saturation
- Can be used for high o/p impedance current source

$$V_{out_{min}} = V_{dsat1} + V_{dsatc}$$