
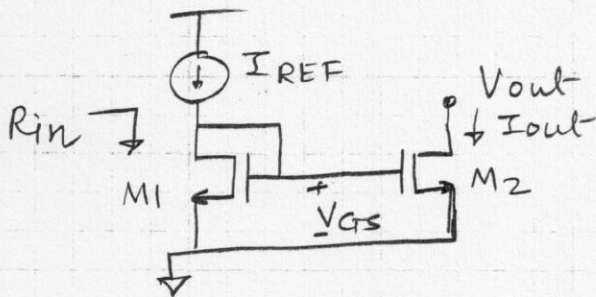


20 AUG 2019

Simple Current mirror
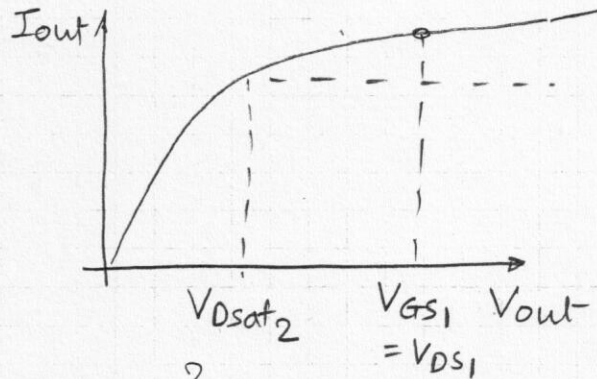
$$R_{in} = \frac{1}{g_{m1} + g_{ds1}} \approx \frac{1}{g_{m1}}$$



$$I_{REF} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{T1})^2 (1 + \lambda_1 V_{GS1})$$

$$I_{OUT} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_2 (V_{GS} - V_{T2})^2 (1 + \lambda_2 V_{out})$$

Assume $V_{T1} = V_{T2}$

$$\frac{I_{OUT}}{I_{REF}} = \frac{(W/L)_2 (1 + \lambda_2 V_{out})}{(W/L)_1 (1 + \lambda_1 V_{GS})}$$

For accurate mirroring, Small keep L same $\Rightarrow \lambda_1 = \lambda_2$

$$\frac{I_{OUT}}{I_{REF}} = \frac{W_2}{W_1} (1 + \lambda (V_{out} - V_{GS}))$$


To keep λ small \rightarrow use long channel device
 L large $\gg L_{min}$

$$I_{OUT} = \frac{W_2}{W_1} I_{REF}$$




For accurate mirroring $W_2 = \underset{\substack{\uparrow \\ \text{Integer}}}{N} W_1$
 DO NOT SCALE THE TRANSISTOR SIZE

Example

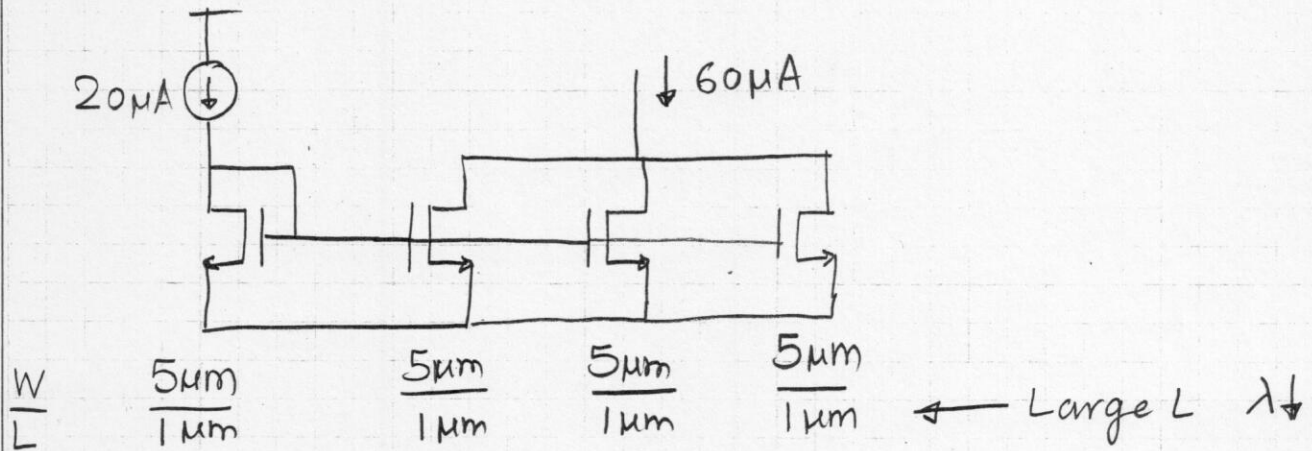

$$V_{outmin} = V_{dsat2}$$

$$R_{out} = \frac{1}{g_{ds2}}$$

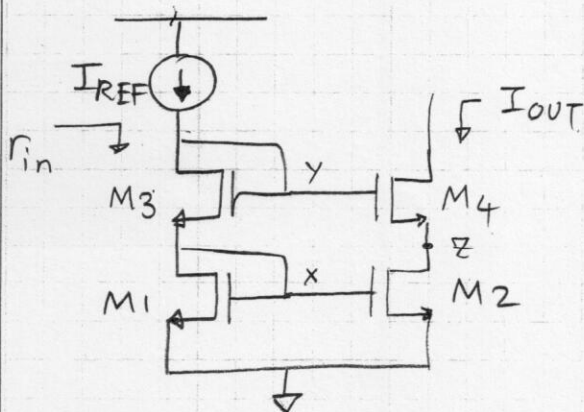CASCODE CURRENT MIRROR

$$r_{in} = \frac{2}{g_m}$$

$$r_{out} \approx (g_{m4} r_{o4}) r_{o2}$$

$$V_y = V_{GS3} + V_{GS1}$$


$$V_z = V_{GS2} + V_{GS1} - V_{GS4} = V_{GS1}$$

$$V_{outmin} = V_z + V_{dsat4}$$


$$= V_{GS1} + V_{dsat4}$$

$$\approx V_T + 2V_{dsat}$$

$$0.5V + 0.4V = 0.9V$$

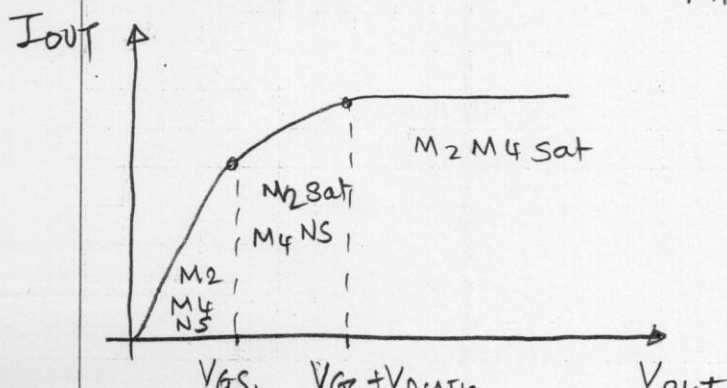NOT SUITABLE
for low voltage.

High Swing Cascode CM

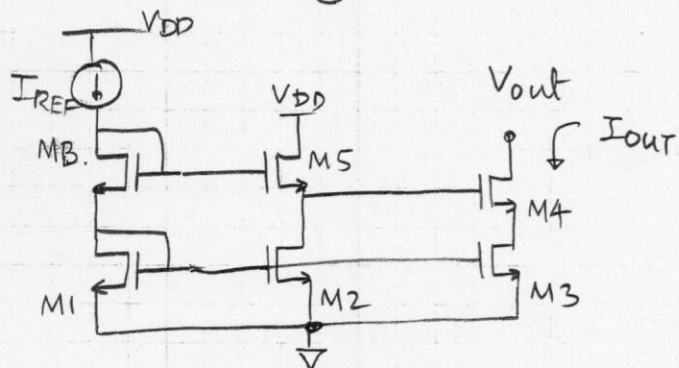

DC imbalance $M1 \leftrightarrow M3$
different V_{DS} .


$M1 - M5$ identical.

$$\left(\frac{W}{L}\right)_B = \frac{1}{4} \left(\frac{W}{L}\right)_{1-5}$$

$$\Rightarrow V_{GSB} = V_T + 2V_{DSat}$$

$$V_{OUT\min} = 2V_{DSat}$$

Low-voltage High Swing Cascode CM

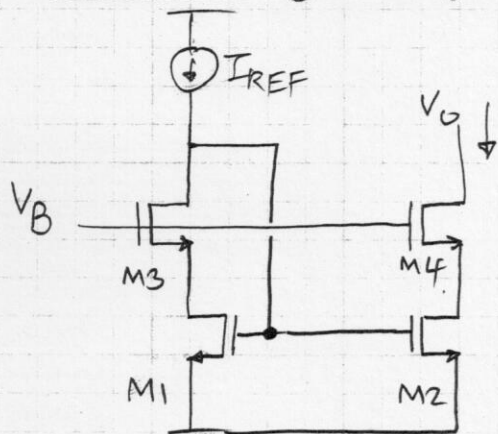


DC balance ✓


$$V_{DS1} = V_{DS2} = V_{DSat}$$

$$V_B = V_T + 2V_{DSat}$$

$$V_{O\min} = 2V_{DSat}$$

Smart Biasing

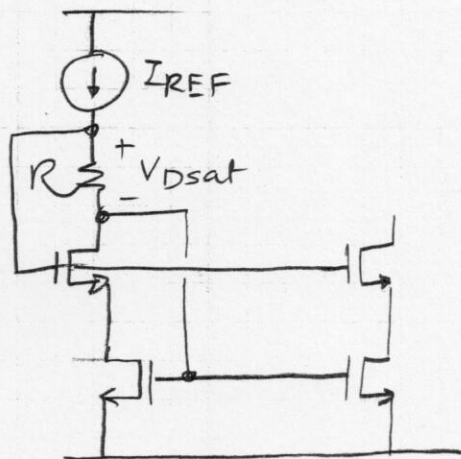

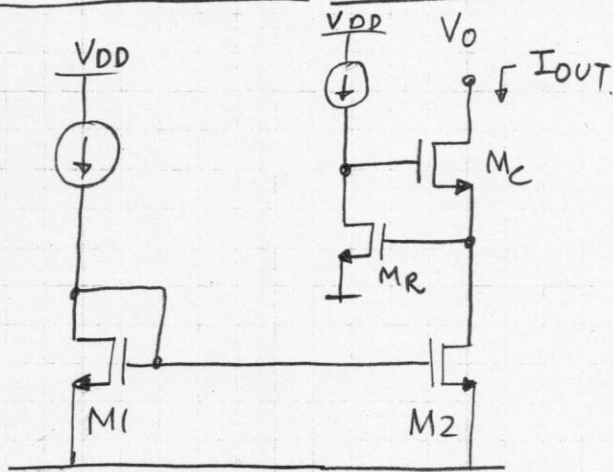REGULATED CASCODE CMYANG - ALLSTOT1990 - CAS
TranSeries feedback

$$V_{Omin} = V_{GS_R} + V_{DSAT_C}$$

$$= V_T + 2V_{DSAT}$$

Feedback loop $M_R - M_C$ - loop gain = $(g_{m_R} r_{o_R}) \times 1$

$$r_{out} \text{ (without feedback)} = r_{o_2} \cdot (g_{m_C} r_{o_C})$$


$$r_{out} \text{ (with feedback)} = r_{o_2} (g_{m_C} r_{o_C}) \cdot (g_{m_R} r_{o_R})$$

$$= \underline{\underline{(g_m r_o)^2 r_o}}$$

$$= (25)^2 \times 10K \approx \underline{\underline{6.25 M\Omega}}$$

Really large

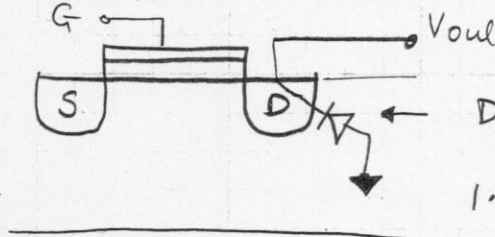
→ In reality r_{out} limited by leakage current due to Drain-Bulk diode of M_C .



Diode leakage at high temperature

$$1.5V \quad 500nA \rightarrow \underline{\underline{3 M\Omega}}$$

MATCHING CONSIDERATIONS

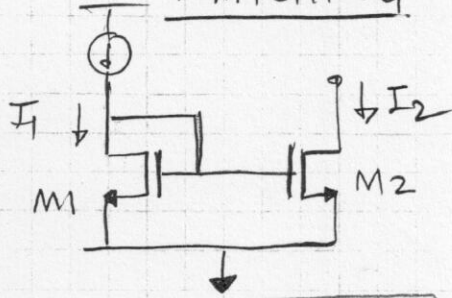

Variaⁿ $\boxed{\mu_n, C_{ox}, W, L, V_T}$

$$\frac{I_2}{I_1} = \frac{\beta_2}{\beta_1}$$

(assume all else equal)

$$\beta = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)$$

$$I_1 = \beta_1 (V_{GS} - V_{T1})^2 (1 + \lambda V_{DS1})$$

$$I_2 = \beta_2 (V_{GS} - V_{T2})^2 (1 + \lambda V_{DS2})$$

Incremental analysis

$$\Delta \beta = \beta_2 - \beta_1 \quad \left. \begin{array}{l} \beta_1 = \beta - \frac{\Delta \beta}{2} \\ \beta_2 = \beta + \frac{\Delta \beta}{2} \end{array} \right\}$$

$$\beta = \frac{\beta_1 + \beta_2}{2}$$

$$I_2 = \frac{\left(\beta + \frac{\Delta \beta}{2} \right)}{\left(\beta - \frac{\Delta \beta}{2} \right)} I_1 = \frac{\left(1 + \frac{\Delta \beta}{2\beta} \right)}{\left(1 - \frac{\Delta \beta}{2\beta} \right)} I_1 \approx \left(1 + \frac{\Delta \beta}{\beta} \right) I_1$$

Large $\beta \rightarrow$ large $\frac{W}{L} \rightarrow$ smaller mismatch

V_T variations

$$V_{T1} = V_T \left(1 + \frac{\Delta V_T}{2V_T} \right); \quad V_{T2} = V_T \left(1 - \frac{\Delta V_T}{2V_T} \right)$$

$$\frac{I_2}{I_1} = \frac{(V_{GS} - V_{T2})^2}{(V_{GS} - V_{T1})^2} = \frac{\left(V_{GS} - V_T + \frac{\Delta V_T}{2} \right)^2}{\left(V_{GS} - V_T - \frac{\Delta V_T}{2} \right)^2}$$

$$= \frac{\left(1 + \frac{\Delta V_T}{2(V_{GS} - V_T)} \right)^2}{\left(1 - \frac{\Delta V_T}{2(V_{GS} - V_T)} \right)^2} = \left(1 + \frac{\Delta V_T}{(V_{GS} - V_T)} \right) \left(1 + \frac{\Delta V_T}{(V_{GS} - V_T)} \right)$$

$$= \left[1 + \frac{2\Delta V_T}{(V_{GS} - V_T)} \right]$$

To reduce mismatches
increase $(V_{GS} - V_T)$ or V_{dsat}

Tradeoff with o/p swing

NEW TOPIC DIFFERENTIAL AMPLIFIERS

Why differential amplifier?


— Example — ECG

— Detecting very small signal in presence of very large signal


— Understanding whisper in presence of screaming voice

— Difference Amplifier

Single Ended & Differential Signal

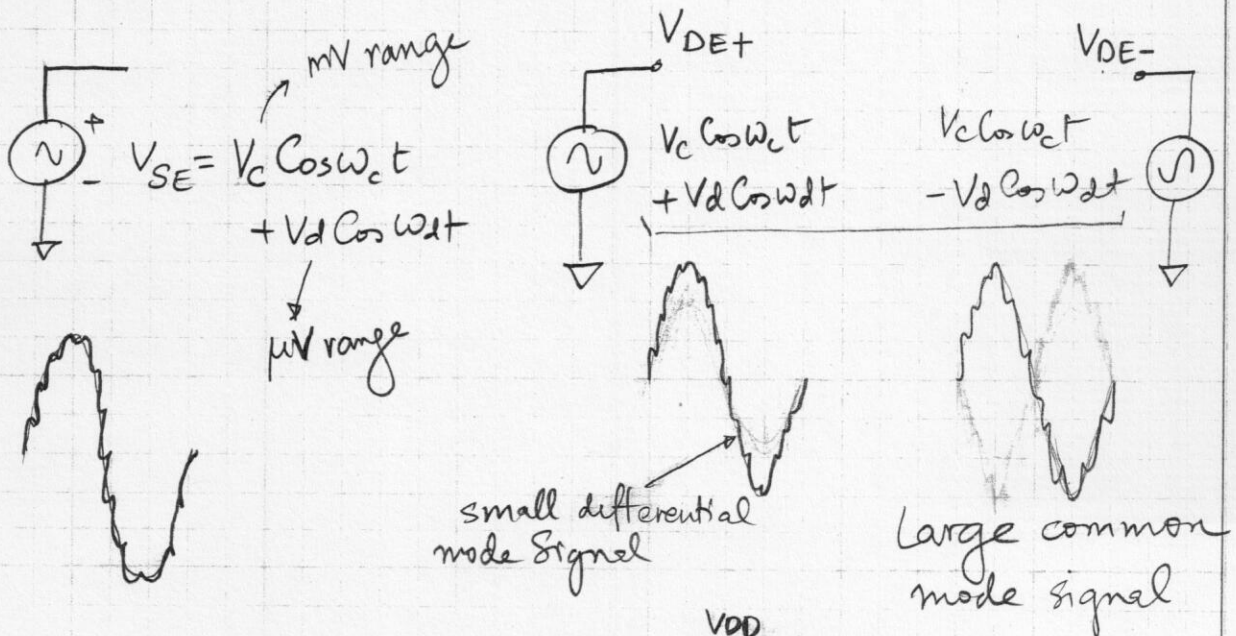

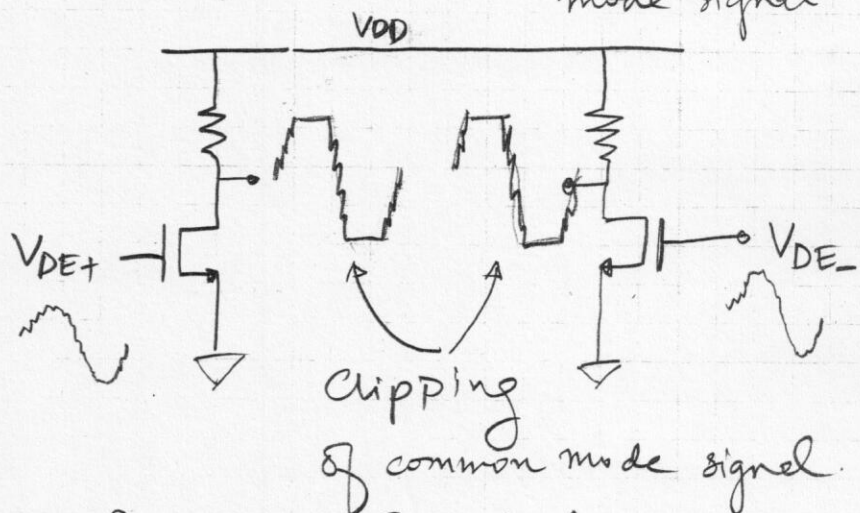Large common mode signal could be 50 Hz supply hum, common mode coupling



V_{DD} - Noise

Pseudo-Differential