

CMOS Analog IC Design [2019 -2020]

OTA Design Example[1]

Tutorial 4

1 SCL180 Process Parameters [Estimated]

$$\boxed{\mu_n = 300 \text{ cm}^2/\text{Vs}; \mu_p = 70 \text{ cm}^2/\text{Vs}}$$

$$t_{ox} = 4 \text{ nm} \implies C_{ox} = \frac{\epsilon_{ox} \cdot \epsilon_0}{t_{ox}} = \frac{3.97 \times 8.85 \times 10^{-12} (\text{F m}^{-1})}{(40 \times 10^{-10}) \text{ m}}$$

$$\implies \boxed{C_{ox} = 8.78 \text{ fF}/\mu\text{m}^2}$$

$$K_n = \mu_n C_{ox} = 300 \text{ cm}^2/\text{Vs} \times 8.78 \text{ fF}/\mu\text{m}^2$$

$$\implies K_n = 263 \mu\text{A}/\text{V}^2$$

$$K_p = \mu_p C_{ox} = 70 \text{ cm}^2/\text{Vs} \times 8.78 \text{ fF}/\mu\text{m}^2$$

$$\implies K_p = 62 \mu\text{A}/\text{V}^2$$

$$\text{For } L = 0.18 \mu\text{m (min L)}, \boxed{\lambda_p = 0.328 \text{ V}^{-1}, \lambda_n = 0.48 \text{ V}^{-1}}$$

$$\boxed{|V_{TP}| = 0.4 \text{ V}; V_{TN} = 0.48 \text{ V}}$$

2 Specifications

Design a 2 stage OTA with the following specifications:

Parameter	Specification
Voltage Gain (A_v)	$\geq 66 \text{ dB}$
Unity Gain Frequency (f_u)	$\geq 100 \text{ MHz}$
V_{DD}	1.8 V
Slew Rate	$\geq 100 \text{ V}/\mu\text{s}$
Output Swing	$\geq 1.3 \text{ V}_{pp}$
I/P Referred White Noise (Thermal only)	$\leq 8 \text{ nV}/\sqrt{\text{Hz}}$
Phase Margin	60°

3 Chosen Architecture

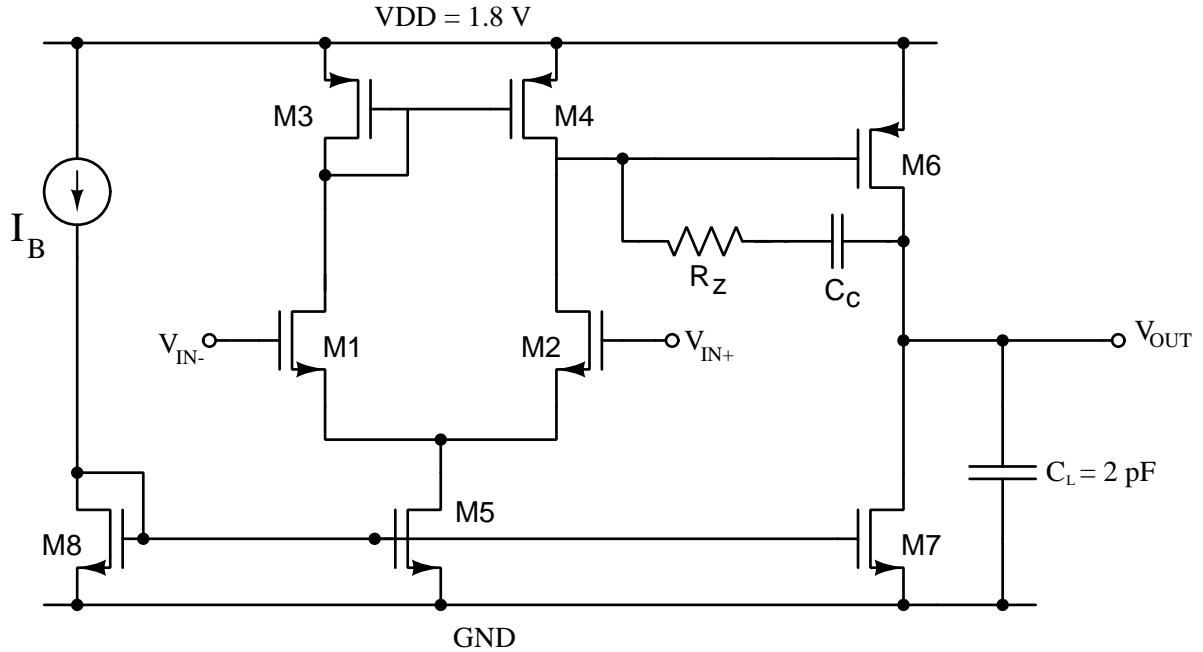


Figure 1: Basic 2-Stage OTA with Frequency Compensation and Zero Nulling

References

- [1] G. Palmisano, G. Palumbo, and S. Pennisi, “Design Procedure for two-stage CMOS Transconductance Operational Amplifiers: A Tutorial,” *Analog Integrated Circuits and Signal Processing*, vol. 27, pp. 179–189, May 2001.

FROM L-15, opamp i/p referred noise

$$\begin{aligned}\bar{V}_{\text{neg}}^2 &= 2 \left[\bar{v}_{n_1}^2 + \bar{v}_{n_3}^2 \left(\frac{g_{m_3}}{g_{m_1}} \right)^2 \right] \quad \text{Thermal Noise only} \\ &= 2 \left[4kT \frac{2}{3} \frac{1}{g_{m_1}} + 4kT \frac{2}{3} \frac{1}{g_{m_3}} \left(\frac{g_{m_3}}{g_{m_1}} \right)^2 \right] \\ &= \frac{16kT}{3} \cdot \frac{1}{g_{m_1}} \left[1 + \frac{g_{m_3}}{g_{m_1}} \right]\end{aligned}$$

Assuming $g_{m_3} \ll g_{m_1}$

$$\bar{V}_{\text{neg}}^2 = \frac{16kT}{3} \cdot \frac{1}{g_{m_1}} = \left(8 \text{nV}/\sqrt{\text{Hz}} \right)^2$$

$$\begin{aligned}g_{m_1} &= \frac{16kT}{3 \cdot \left(8 \text{nV}/\sqrt{\text{Hz}} \right)^2} \\ &= \frac{16 \times 1.38 \times 10^{-23} \times 300}{3 \times 64 \times 10^{-18}} \text{ S} \\ &= 345 \mu\text{S}\end{aligned}$$

From L-11 page(3-4.)

$$UGF = f_{GBW} = DC \text{ gain} \times P_D$$

$$= \frac{g_{m_1}}{g_B} \cdot \frac{g_{m_6}}{g_C} \cdot \frac{g_B/C_C}{(g_{m_6}/g_C)} = \frac{g_{m_1}}{C_C}$$

$$\text{Remember } \omega_u = 2\pi f_u = g_{m_1}/C_C$$

$$C_C = \frac{g_{m1}}{2\pi f_u} = \frac{345 \mu S}{2\pi \times 100 \text{ MHz}} \\ = 0.55 \text{ pF}$$

Slew Rate (L - 13 page 6)

$$\frac{dV_{out}}{dt} = \frac{I_{ss}}{C_C} \quad (\text{i/p diff pair lim Slew rate})$$

$$I_{ss} = C_C \cdot \frac{dV_{out}}{dt} = 0.55 \text{ pF} \times 100 \text{ V/}\mu\text{s}$$

$$I_{ss} = 55 \text{ mA} \Rightarrow I_{ss} \geq 55 \mu\text{A}.$$

$$\begin{aligned} \text{Similarly } I_{oss} &= \left(1 + \frac{C_L}{C_C}\right) I_{ss} \quad \left(\text{o/p Slew Rate limit}\right) \\ &= \left(1 + \frac{2 \text{ pF}}{0.55 \text{ pF}}\right) 55 \mu\text{A} \\ &= 255 \text{ mA} \\ \Rightarrow I_{oss} &\geq 255 \mu\text{A} \end{aligned}$$

Figuring out M₁, M₂ diff pair sizes. —

$$\begin{aligned} g_{m1} &= \sqrt{2 I_1 K_n \left(\frac{W}{L}\right)_1} = \sqrt{2 \frac{I_{ss}}{2} K_n \left(\frac{W}{L}\right)_1} \\ \left(\frac{W}{L}\right)_1 &= \frac{g_{m1}^2}{I_{ss} \cdot K_n} = \frac{(345 \mu\text{s})^2}{(55 \mu\text{A}) \times (263 \text{ mA/V}^2)} \\ \left(\frac{W}{L}\right)_1 &= 8.23 \end{aligned}$$

Assuming two pole (dom & non-dom) response.

$$\text{Phase Margin} = 90 - \tan^{-1} \left(\frac{f_{GBW}}{f_{ND}} \right)$$

(for example if $f_{ND} = f_{GBW}$
 $PM = 45^\circ$)

For $PM = 60^\circ$

$$\Rightarrow f_{ND} = [\tan(90 - 60^\circ)]^{-1} f_{GBW}$$

$$= \frac{100 \text{ MHz}}{\tan(30)} = 173.2 \text{ MHz}$$

$$= \frac{g_{m6}}{C_L} \cdot \frac{1}{2\pi}$$

$$\Rightarrow g_{m6} = 2\pi C_L \times 173.2 \times 10^6$$

$$= 2\pi \times 2 \times 10^{-12} \times 173.2 \times 10^6$$

$$= 2.176 \text{ mS}$$

$$\left(\frac{W}{L}\right)_6 = \frac{g_{m6}^2}{2 K_p I_{oss}} = \frac{(2.176 \times 10^{-3})^2}{2 \times 62 \mu A \times 255 \mu A}$$

$$= \frac{(2.176)^2 \mu A^2 S^2}{2 \times 62 \mu A \times 255 \mu A} = 150$$

From (L-12 p. 2)

If we push zero to infinity, $R_Z = \frac{1}{g_{m6}}$

$$\Rightarrow R_Z = \frac{1}{2.176 \text{ mS}} = 460 \Omega$$

= If we line up RHP zero on non-dom pole

$$R_2 = \frac{1}{g_m 6} \left(1 + \frac{C_L}{C_C} \right) = 460 \left(1 + \frac{2}{0.55} \right)$$

$= 2.132 \text{ k}\Omega \rightarrow$ This choice would improve PM further.

Swing $1.3 \text{ V}_{\text{PP}} \Rightarrow V_{\text{dsat6}} = V_{\text{dsatn}} = 250 \text{ mV}$
(output devices)

$$V_{\text{dsat6}} = \sqrt{\frac{2 I_{\text{loss}}}{K_P \left(\frac{w}{L}\right)_6}} = \sqrt{\frac{2 \times 255 \text{ mA}}{62 \text{ mA/v}^2 \times 150}}$$

$$\approx 234 \text{ mV} \quad \text{OK.}$$

$$V_{\text{dsat7}} = \sqrt{\frac{2 I_{\text{loss}}}{K_n \left(\frac{w}{L}\right)_7}} \Rightarrow \left(\frac{w}{L}\right)_7 = \frac{2 I_{\text{loss}}}{K_n \cdot V_{\text{dsat7}}^2}$$

$$\left(\frac{w}{L}\right)_7 = \frac{2 \times 255 \text{ mA}}{263 \text{ mA/v}^2 \times 0.0625 \text{ v}^2}$$

$$\left(\frac{w}{L}\right)_7 = 31$$

For zero systematic offset.

$$V_{\text{dsat3}} = V_{\text{dsat4}} = V_{\text{dsat6}} = 234 \text{ mV}$$

$$\left(\frac{w}{L}\right)_{3,4} = \frac{I_{\text{ss}}/2}{I_{\text{loss}}} \times \left(\frac{w}{L}\right)_6 = \frac{55/2}{255} \times 150$$

$$= 16.2$$

Gain Spec $A_v = A_{v_1}, A_{v_2}$

$$A_{v_1} = \frac{g_{m_1}}{g_{ds_2} + g_{ds_4}} = \frac{\sqrt{2 K_n (W/L)_1 I_{ss}/2}}{(\lambda_n + \lambda_p) I_{ss}/2}$$

$$= \sqrt{\frac{2 K_n (W/L)_1}{I_{ss}/2}} \cdot \frac{1}{(\lambda_n + \lambda_p)}$$

$$= \sqrt{\frac{2 \times 263 \times 8.23}{55/2}} \cdot \frac{1}{(\lambda_n + \lambda_p)}$$

$$= \frac{12.54}{(\lambda_n + \lambda_p)}$$

$$A_{v_2} = \frac{g_{m_6}}{g_{ds_6} + g_{ds_7}} = \frac{\sqrt{2 K_p (W/L)_6 I_{oss}}}{(\lambda_n + \lambda_p) I_{oss}}$$

$$= \sqrt{\frac{2 K_p (W/L)_6}{I_{oss}}} \cdot \frac{1}{(\lambda_n + \lambda_p)}$$

$$= \sqrt{\frac{2 \times 62 \times 150}{255}} \cdot \frac{1}{(\lambda_n + \lambda_p)} = \frac{8.54}{(\lambda_n + \lambda_p)}$$

$$66 \text{ dB gain} \Rightarrow 2000 = A_v$$

$$2000 = A_{v_1} \cdot A_{v_2} = \frac{12.54}{(\lambda_p + \lambda_n)} \cdot \frac{8.54}{(\lambda_p + \lambda_n)}$$

assume all λ equal

$$2000 = \frac{107.09}{4\lambda^2} \Rightarrow \lambda = \underline{0.1156}$$

Note $A_1 L_1 = A_2 L_2$ ($1, 2$ Not for transistors)

For PMOS $A_1 = 0.328 V^+$ for $L_1 = 0.18 \mu m$

for desired $A_2 = 0.1156$

$$\text{pmos } L_2 = \frac{0.328 \times 0.18}{0.1156} \mu m$$

$$= 0.510 \mu m \quad \text{Roundup to } 0.6 \mu m$$

For NMOS $A_1 = 0.48$ for $L_1 = 0.18 \mu m$

for desired $A_2 = 0.1156$

$$\text{nmos } L_2 = \frac{0.48 \times 0.18}{0.1156} = 0.747 \mu m$$

Roundup to $0.8 \mu m$

Reference

Design Procedure for 2-stage OTA. -

G. Palmisano

- AICSP -27-2001
Kluwer

Complete schematic

