

★ Butler matrix ⇒

→ Array Factor

$$\vec{E}_{array} = \vec{E}_{single\ element} \times AF$$

→ $\psi = 0$ Gives a θ_0 which is the direction of max.



To maximize $\vec{E}_{array} \Rightarrow \max AF \Rightarrow \psi = 0 \Rightarrow$ (some θ_0)

$$\left(\text{as } AF = \frac{\sin\left(\frac{N\psi}{2}\right)}{\frac{\psi}{2}} \right)$$

↓
sin(x)
max at $\psi = 0$

$$\psi = kd \cos \theta + \beta = 0 \Rightarrow \beta = -kd \cos \theta$$

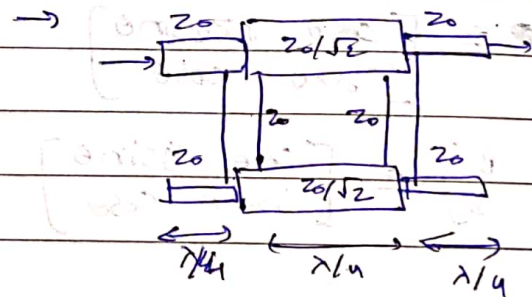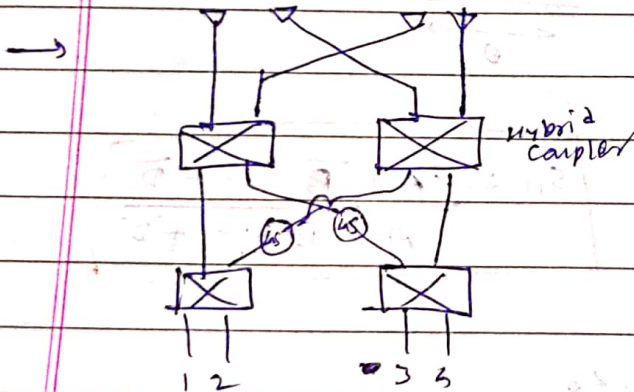For our choice of ~~the~~ direction of max. rad. θ we get a certain β




→ In ADS, for Designing Hybrid Coupler, each TLine has F which ~~must be set~~ is the frequency at which $\ell = \frac{\lambda}{4}$ s.t. $\theta = \beta \ell = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$ which is required in Hybrid coupler


11/10/19
Tue

AM 10:45
STAG


1. Ideal T-Line
2. Real T-lines $MLIN, mSUBS$
3. E Simulations

★ 1 port microwave circuit \Rightarrow

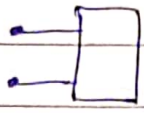$[S_{11}]$ 
 $S^t = S$
 $S^* S^t = [u]$
 $\Rightarrow |S_{11}| = 1$

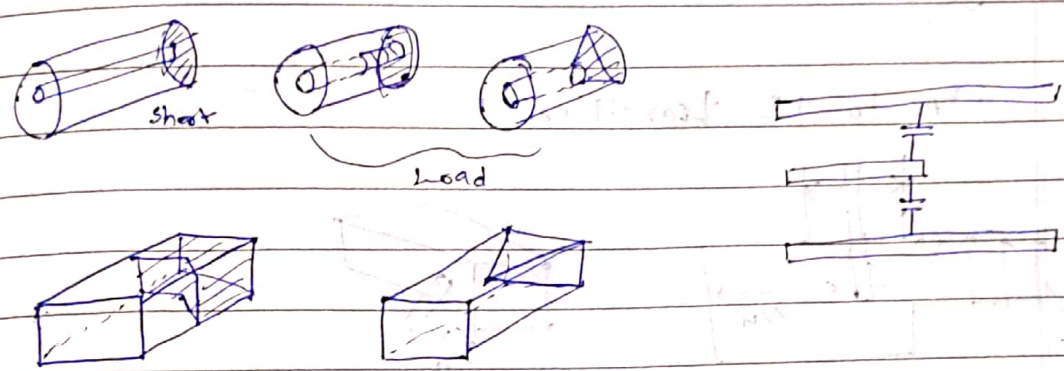


★ 2 port Microwave Circuits \Rightarrow

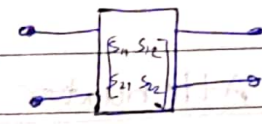


$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$ $|S_{11}| \theta_1 \theta_2$
 Params

1. Transmission line
2. bends
3. discontinuities
4. Transition
5. Attenuation
6. Mode suppressor


• Radial bend:

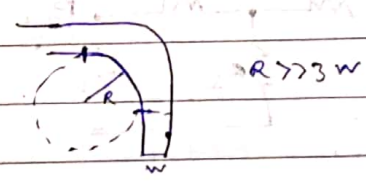


• Mitral Bend:

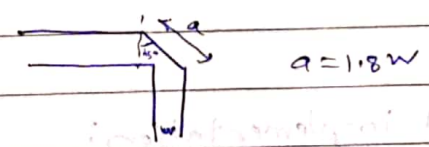


① Discontinuity

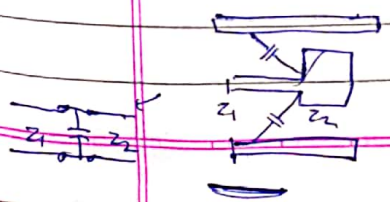


② Gap

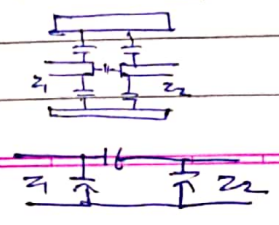

(Discontinuities)

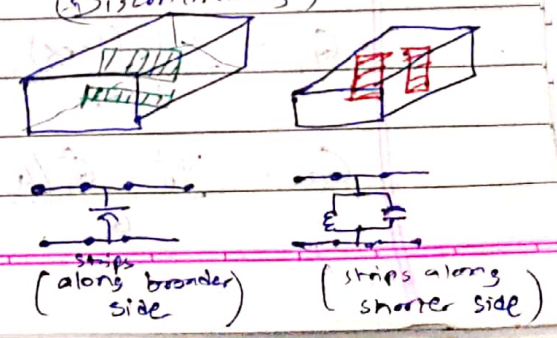


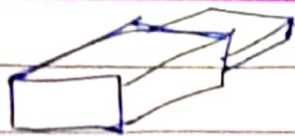



★ SMA Launcher ⇒

- For min. VSWR, $L = Z_0^2 (C_1 + C_2)$


- TEM → TEM

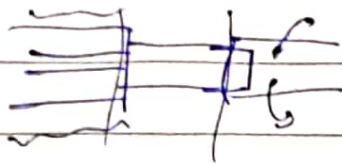

- TEM to TE transition

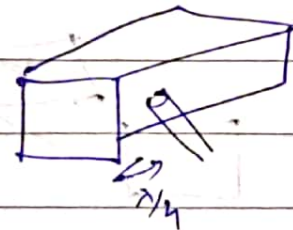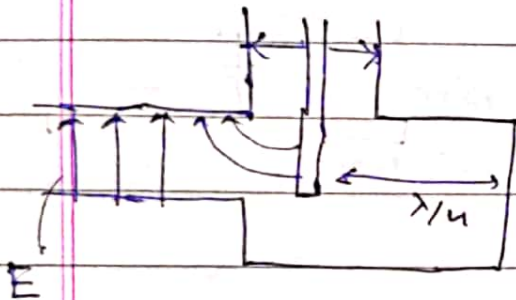

★ Attenuator ⇒

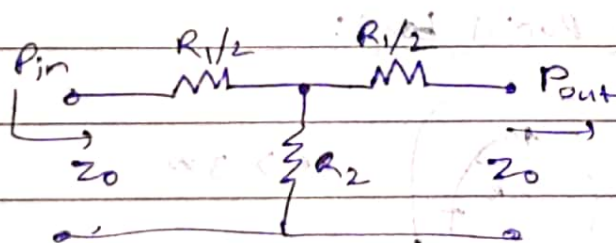


$$\alpha = \frac{P_{out}}{P_{in}} = |S_{21}|^2$$


$$R_1 = \frac{2Z_0(1-\alpha)}{1+\alpha}$$

$$R_2 = Z_0 - R_1^2/4$$

* mode Suppressor \Rightarrow

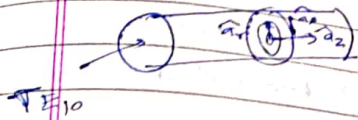

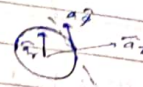a_2 will be nullified
due to metallic part



TM₀₁ Suppressor



* 3 port device \Rightarrow

$$\begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12}^* & 0 & S_{23} \\ S_{13}^* & S_{23}^* & 0 \end{bmatrix}$$

$$S_{12} = S_{21}$$

$$S_{13} = S_{31}$$

$$S_{23} = S_{32}$$

$$S^R S^+ = [U]$$

$$\begin{bmatrix} 0 & S_{12}^* & S_{13}^* \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix} \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12}^* & 0 & S_{23} \\ S_{13}^* & S_{23}^* & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\Rightarrow |S_{12}|^2 + |S_{13}|^2 = 1 \quad S_{13}^* S_{23} = 0$$

$$|S_{12}|^2 + |S_{23}|^2 = 1 \quad S_{12}^* S_{23} = 0$$

$$|S_{13}|^2 + |S_{23}|^2 = 1 \quad S_{23}^* S_{13} = 0$$

Now, it is mathematically impossible to achieve lossless, reciprocal & matched at the same time. At most we can achieve 2 out of 3 properties

	Circulator	Tee	Power Divider
Lossless	✓	✓	
Matched at all ports	✓		✓
Reciprocal		✓	✓



4/10/19

Exi

★ 3 port devices →

1. matched at all ports
 2. Lossless
 3. Reciprocal
- 1, 2 → Circulant
1, 3 → Power divider
2, 3 → tee

★ Tee Configuration in 3 port →

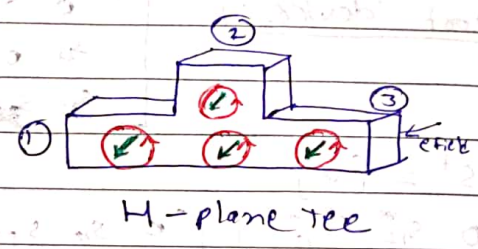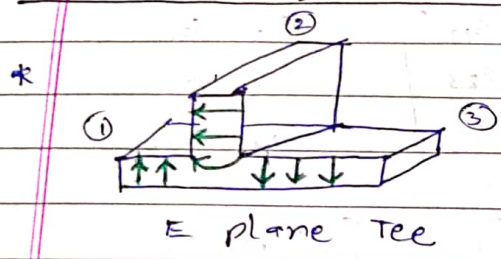

— E field
— H field
E field is along least possible distance

$$\rightarrow \begin{cases} S_{12} = -S_{32} \\ S_{11} = S_{33} \\ S_{22} = 0 \end{cases}$$

$$\begin{cases} S_{12} = S_{32} \\ S_{11} = S_{33} \\ S_{22} = 0 \end{cases}$$

for S_{ij} nature
check by giving input wave at i

★ $S^* S^t = [u]$

E plane Tee

$$\Rightarrow \begin{bmatrix} S_{11}^* & S_{12}^* & S_{13}^* \\ S_{12}^* & 0 & -S_{12}^* \\ S_{13}^* & -S_{12}^* & S_{11}^* \end{bmatrix} \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & 0 & -S_{12} \\ S_{13} & -S_{12} & S_{11} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\Rightarrow |S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1$$

$$|S_{12}|^2 + |S_{12}|^2 = 1 \Rightarrow$$

$$|S_{12}| = \frac{1}{\sqrt{2}}$$

$$S_{11}^* S_{12}^* - S_{12}^* S_{13} = 0$$

$$\Rightarrow S_{12}^* (-S_{11} - S_{13}) = 0$$

$$\Rightarrow S_{11} = S_{13} \quad (\text{as } S_{12} \neq 0)$$

Put this in $S^* S^t = [u] \Rightarrow 2|S_{11}|^2 + \frac{1}{2} = 1 \Rightarrow |S_{11}| = \frac{1}{2}$

$$\therefore [S] = \begin{bmatrix} \frac{1}{2} e^{j\theta_{11}} & \frac{1}{\sqrt{2}} e^{j\theta_{12}} & \frac{1}{2} e^{j\theta_{11}} \\ \frac{1}{\sqrt{2}} e^{j\theta_{12}} & 0 & -\frac{1}{\sqrt{2}} e^{j\theta_{12}} \\ \frac{1}{2} e^{j\theta_{11}} & -\frac{1}{\sqrt{2}} e^{j\theta_{12}} & \frac{1}{2} e^{j\theta_{11}} \end{bmatrix}$$

→ remaining variables θ_{11}, θ_{12}

$$[S] = \begin{bmatrix} \frac{1}{2} & \frac{1}{\sqrt{2}} & \frac{1}{2} \\ \frac{1}{\sqrt{2}} & 0 & -\frac{1}{\sqrt{2}} \\ \frac{1}{2} & -\frac{1}{\sqrt{2}} & \frac{1}{2} \end{bmatrix}$$

$$\theta_{11} = \theta_{12} = 0 \text{ or } 2\pi \text{ why?}$$

By shifting plane 1 & 2

E plane tee




$$[S] = \begin{bmatrix} \frac{1}{2} & \frac{1}{\sqrt{2}} & \frac{1}{2} \\ \frac{1}{\sqrt{2}} & 0 & -\frac{1}{\sqrt{2}} \\ \frac{1}{2} & \frac{1}{\sqrt{2}} & \frac{1}{2} \end{bmatrix}$$



H plane tee

→ just $S_{12} = S_{32}$ instead of $S_{12} = -S_{32}$

*

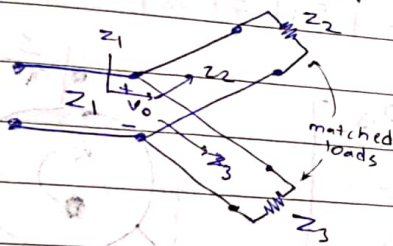

$$Z_1 = Z_2 \parallel Z_3$$

• For $Z_2 = Z_3$, $Z_1 = \frac{Z_2}{2}$

s.t. $Z_2 = Z_3 = 2Z_1$

• From power's perspective

$$P_1 = \frac{V_0^2}{Z_1}, P_2 = \frac{V_0^2}{Z_2}, P_3 = \frac{V_0^2}{Z_3}$$

• Now if Z_1 is also matched

then from Z_2 we see that

$$Z_2 = Z_1 \parallel Z_3$$

$$= Z_1 \parallel 2Z_1 \quad (\text{if } Z_2, Z_3 \text{ are still matched})$$

$$= \frac{2}{3} Z_1$$

Not possible as $Z_2 = 2Z_1$ for Z_2, Z_3 matching

(matching at 2,3)

$$P_1 = P_2 + P_3 = 2P_2$$

$$\frac{V_0^2}{Z_1} = \frac{2V_0^2}{Z_2} \Rightarrow Z_2 = 2Z_1$$

If 3 port network is lossless

all 3 matching cannot hold at same time as for one matching (2,3)

we get $Z_2 = 2Z_1$ for (1,3) matching we get $Z_2 = \frac{2}{3} Z_1$ so

a LOSSLESS network cannot satisfy matching at all

3 ports

* Circulators →

Satisfies
$$\begin{bmatrix} 0 & s_{12} & s_{13} \\ s_{21} & 0 & s_{23} \\ s_{31} & s_{32} & 0 \end{bmatrix}$$

* $s^* s^t = [u]$

$$\begin{bmatrix} 0 & s_{12}^* & s_{13}^* \\ s_{21}^* & 0 & s_{23}^* \\ s_{31}^* & s_{32}^* & 0 \end{bmatrix} \begin{bmatrix} 0 & s_{21} & s_{31} \\ s_{12} & 0 & s_{32} \\ s_{31} & s_{23} & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$


$$|s_{12}|^2 + |s_{13}|^2 = |s_{21}|^2 + |s_{23}|^2 = |s_{31}|^2 + |s_{32}|^2 = 1$$

$$s_{13}^* s_{23} = s_{21}^* s_{31} = s_{32}^* s_{12} = 0$$

Lets take, $s_{23} = s_{31} = s_{12} = 0$

This gives us, $|s_{13}| = |s_{21}| = |s_{32}| = 1$

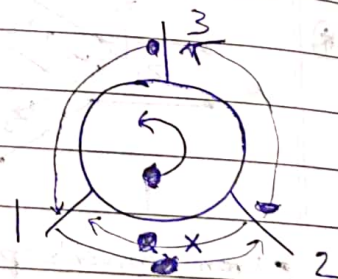* $\Rightarrow [S] = \begin{bmatrix} 0 & 0 & e^{j\theta_{13}} \\ e^{j\theta_{21}} & 0 & 0 \\ 0 & e^{j\theta_{32}} & 0 \end{bmatrix}$



For $\theta_{13} = \theta_{21} = \theta_{32} = 2\pi$

$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

1 to 2 is possible (Non Reciprocal)


2 to 1 is not possible (Reciprocal)

Showing non reciprocity



anticlockwise solⁿ

* If we take $s_{13} = s_{21} = s_{32} = 0$ we get for $\theta_{12} = \theta_{31} = \theta_{23}$
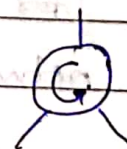
$$[S] = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



Clockwise solⁿ

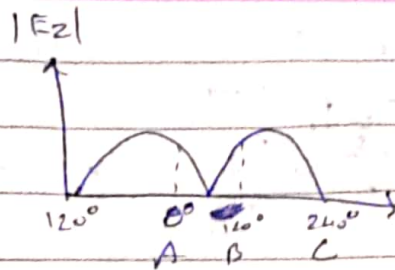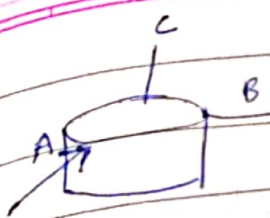


• No power at C
(destructive interference)

• If we introduce power at port A

then port C will have no power

Isolation

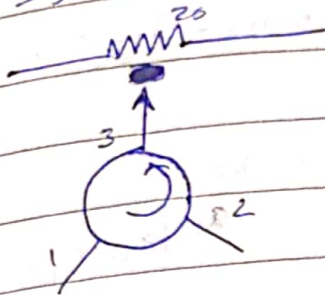


• If we introduce power at port 2

port 3 no longer has absence of power


& port 1 will be isolated

• We are using Circulator as a blocker to isolate.
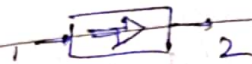
$$\begin{bmatrix} 0 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix}$$



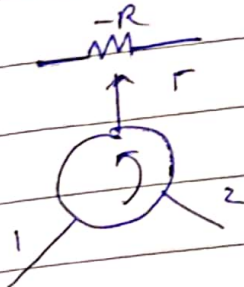For $R < 0$ we can use circulator as an amplifier




$$|\Gamma| > 1$$


$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = \frac{R + jX - Z_0}{R + jX + Z_0} \Rightarrow |\Gamma| = \frac{\sqrt{(R+Z_0)^2 + X^2}}{\sqrt{(R-Z_0)^2 + X^2}}$$

$$\text{For } R < 0, |\Gamma| > 1$$

~~By $R < 0$ in $Z = R + jX$~~
 ~~$|Z| > Z_0$~~

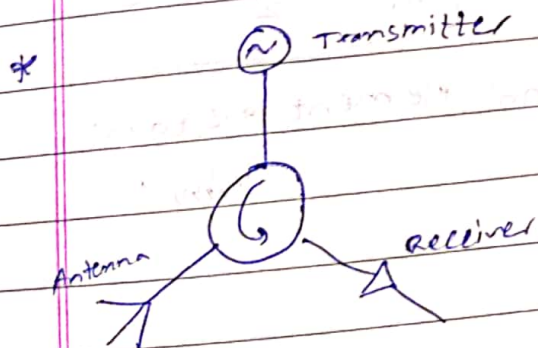

* Power Divider \Rightarrow

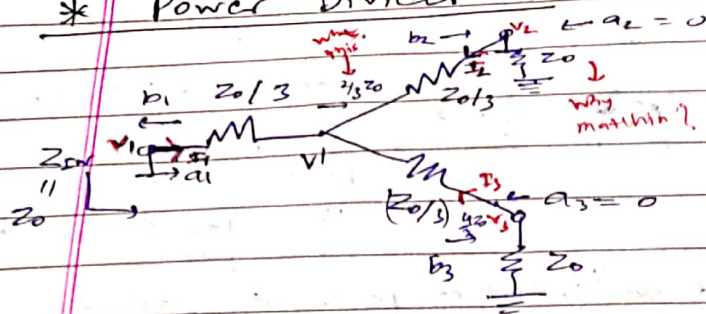

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=a_3=0}$$

$$\Gamma_{\text{in}} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

$$S_{11} = S_{22} = S_{33} = 0$$

$$I_1 = \frac{V_1}{Z_0}$$

$$V' = V_1 - I_1 \frac{Z_0}{3}$$

$$V_2 = V' - \frac{I_1}{2} \cdot \frac{Z_0}{3}$$

$$= V_1 - \frac{I_1 Z_0}{3} - \frac{I_1 Z_0}{6}$$

$$V_2 = \frac{V_1}{2}$$

$$\text{For } S_{21} = \frac{b_2}{a_1} \Big|_{a_2=a_3=0}$$

$$I_2 = -\frac{I_1}{2}$$

$$\frac{a_2 - b_2}{\sqrt{Z_0}} = -\frac{1}{2} \left(\frac{a_1 - b_1}{\sqrt{Z_0}} \right)$$

$$\Rightarrow \frac{a_1 - b_1}{2} = b_2 \quad \text{--- (1)}$$

$$\Rightarrow \frac{a_2 + b_2}{2} = \frac{a_1 + b_1}{2}$$

$$\Rightarrow 2b_2 = a_1 + b_1 \quad \text{--- (2)}$$

from (1) & (2) $a_1 = 2b_2$, $\Rightarrow \frac{b_2}{a_1} = \frac{1}{2} = S_{12}$


from symmetry all off diagonal elements are equal

$$S = \begin{bmatrix} 0 & 1/2 & 1/2 \\ 1/2 & 0 & 1/2 \\ 1/2 & 1/2 & 0 \end{bmatrix}$$

Why?

11/10/12

★ Wilkinson Power Divider \Rightarrow



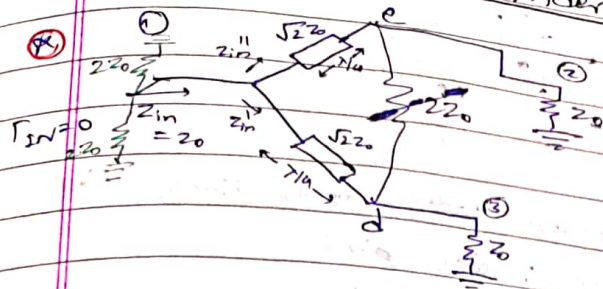


$$Z_{IN}^I = \frac{(\sqrt{2}Z_0)^2}{Z_0}$$

$$= 2Z_0$$

$$Z_{IN}^{II} = 2Z_0$$

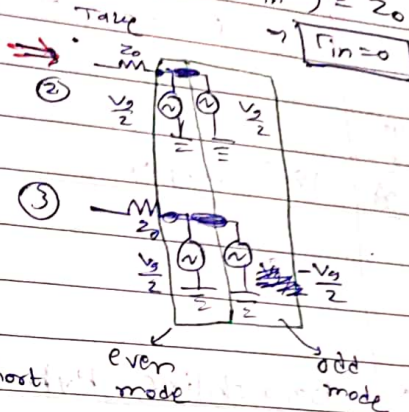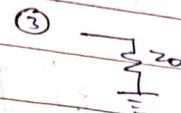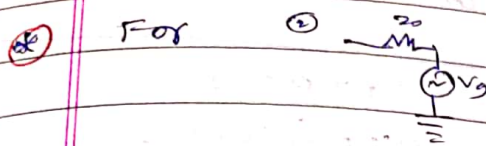
$$\Rightarrow Z_{IN} = (Z_{IN}^I \parallel Z_{IN}^{II}) = Z_0$$




- Due to symmetry of circuit & applying same voltage (2) & (3)

- across $2Z_0$ we have short. i.e. $V_e = V_d$ such that no current flows in $2Z_0$.

Even mode ckt :

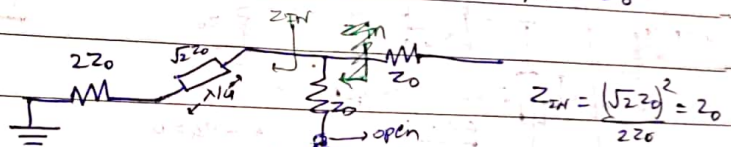

Odd mode ckt :

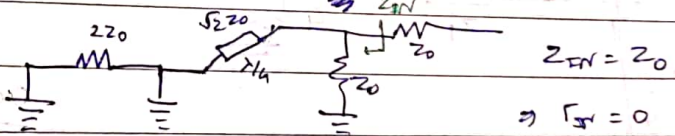

\therefore as $\Gamma_{IN} = 0$ in (2), (3) $\Rightarrow S_{22} = S_{33} = 0$ also $S_{11} = 0$ from return

port (2) & (3) are isolated $\Rightarrow S_{23} = S_{32} = 0$

By symmetry $\Rightarrow S_{21} = S_{12} = S_{31} = S_{13}$ (reciprocity)



$$\therefore [S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix}$$

For equal power distribution, $|S_{12}| = |S_{13}| = \frac{1}{\sqrt{2}}$

★ 4 Port Devices : Couplers ⇒

(destructive interference)
Isolated 2

(constructive interference)
3 coupled

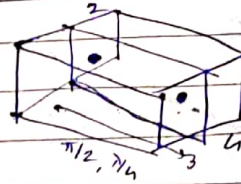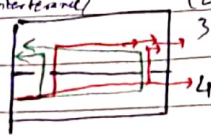


at ② 0 & π phase waves are added destructively C_{opp}

at ③ 0 & π phase waves : des. int

③ π & π phase waves : cons. int

10/10/19
Tare

★ 180° coupler ⇒

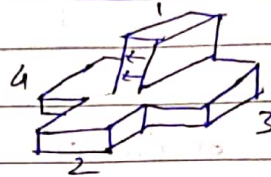

$$S_{12} = 0 = S_{21}$$


$$(S_{ii} = 0) \quad i = 1, 2, 3, 4$$

$$S_{42} = S_{32} = \frac{1}{\sqrt{2}}$$


$$S_{41} = -S_{31} = 1/\sqrt{2}$$

$$S_{34} = S_{43} = 0$$


★ Branchline Hybrid Coupler ⇒

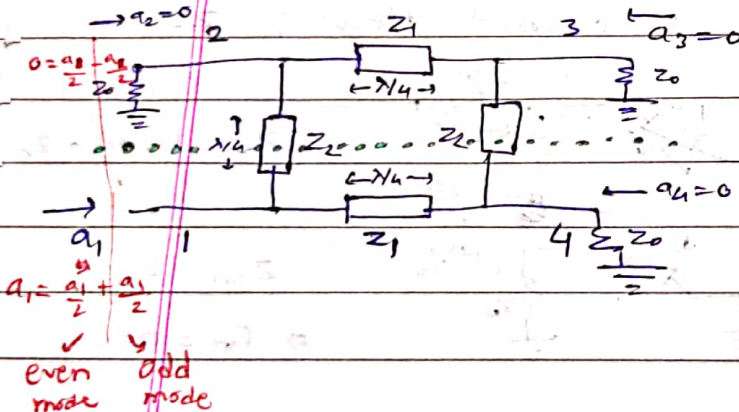

Even mode

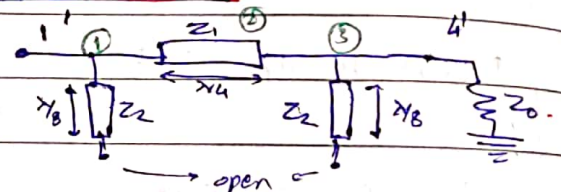

odd mode

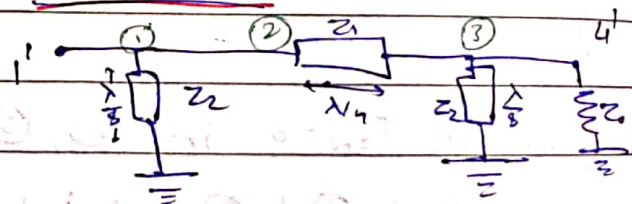

$$\textcircled{*} \quad b_1 = S_{11e} \frac{a_1}{2} + S_{11o} \frac{a_1}{2}$$

$$\Rightarrow S_{11} = \frac{b_1}{a_1} = \frac{S_{11e}}{2} + \frac{S_{11o}}{2}$$

$$\textcircled{*} \quad b_2 = S_{11e} \frac{a_2}{2} + S_{11o} \frac{a_2}{2} \left(-\frac{a_1}{2} \right)$$

→ $S_{22} = S_{11}$ as after dividing network both sides are identical

$$S_{21} = \frac{b_2}{a_1} = \frac{S_{11e}}{2} - \frac{S_{11o}}{2}$$

② $b_4 = S_{41} e^{j\theta} \frac{a_1}{2} + S_{41} e^{j\theta} \left(\frac{a_1}{2} \right)$
 $\Rightarrow S_{41} = \frac{b_4}{a_1} = \frac{S_{41} e^{j\theta}}{2} + \frac{S_{41} e^{j\theta}}{2}$

③ $b_3 = S_{31} e^{j\theta} \frac{a_1}{2} + S_{31} e^{j\theta} \left(-\frac{a_1}{2} \right)$
 $\Rightarrow S_{31} = \frac{b_3}{a_1} = \frac{S_{31} e^{j\theta}}{2} - \frac{S_{31} e^{j\theta}}{2}$

* $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{bmatrix}$ for 1x line

* $\frac{V}{Z} = Z = \begin{cases} -jZ_2 \cot \theta & \text{open (even)} \\ jZ_2 \tan \theta & \text{short (odd)} \end{cases}$
 $\left(\theta = \pi/4 \text{ for } N/8 \text{ in } Z_2 \right)$

* $[m]_{e/o} = \begin{matrix} \textcircled{1} & \textcircled{2} & \textcircled{3} \end{matrix} \begin{bmatrix} 1 & 0 \\ \pm jY_2 & 1 \end{bmatrix} \begin{bmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \pm jY_2 & 1 \end{bmatrix}$ + \rightarrow odd
- \rightarrow even
 $= \begin{bmatrix} 1 - Z_1/Z_2 & jZ_1 \\ jZ_1 \left(\frac{1}{Z_1^2} - \frac{1}{Z_2^2} \right) & 1 - \frac{Z_1}{Z_2} \end{bmatrix}$

* $S_{11} e^{j\theta} = \frac{A_{e/o} + B_{e/o} - C_{e/o} Z_0 - D_{e/o}}{A_{e/o} + B_{e/o} + C_{e/o} Z_0 + D_{e/o}}$
 $= \frac{B_{e/o} - C_{e/o} Z_0}{A_{e/o} + B_{e/o} + C_{e/o} Z_0 + D_{e/o}}$

$S_{41} e^{j\theta} = \frac{2}{A_{e/o} + B_{e/o} + C_{e/o} Z_0 + D_{e/o}}$

for $S_{11} = S_{21}$
 $\Rightarrow S_{11} = S_{110} = 0$
 $\Rightarrow \frac{B_{e/o}}{Z_0} = C_{e/o} Z_0$
 $\Rightarrow Z_2 = \frac{Z_1}{\sqrt{1 - \frac{Z_1^2}{Z_2^2}}}$

$$S_{31} = \frac{1}{2} S_{4110} - \frac{1}{2} S_{4110} = -\sqrt{1 - \frac{Z_1^2}{Z_0^2}}$$


$$S_{41} = \frac{1}{2} S_{4110} + \frac{1}{2} S_{4110} = -j \frac{Z_1}{Z_0}$$

$$|S_{31}| = |S_{41}| \Rightarrow Z_1 = \frac{Z_0}{\sqrt{2}}, Z_2 = Z_0$$

$$[S] = \begin{bmatrix} 0 & 0 & -\sqrt{1 - \frac{Z_1^2}{Z_0^2}} & -j \frac{Z_1}{Z_0} \\ 0 & 0 & -j \frac{Z_1}{Z_0} & -\sqrt{1 - \frac{Z_1^2}{Z_0^2}} \\ -\sqrt{1 - \frac{Z_1^2}{Z_0^2}} & -j \frac{Z_1}{Z_0} & 0 & 0 \\ -j \frac{Z_1}{Z_0} & -\sqrt{1 - \frac{Z_1^2}{Z_0^2}} & 0 & 0 \end{bmatrix}$$

After putting $Z_1 = Z_0/\sqrt{2}$, $Z_2 = Z_0 \Rightarrow [S] = -\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 0 & 1 & j \\ 0 & 0 & j & 1 \\ 1 & j & 0 & 0 \\ j & 1 & 0 & 0 \end{bmatrix}$

RAT - RACE Coupler

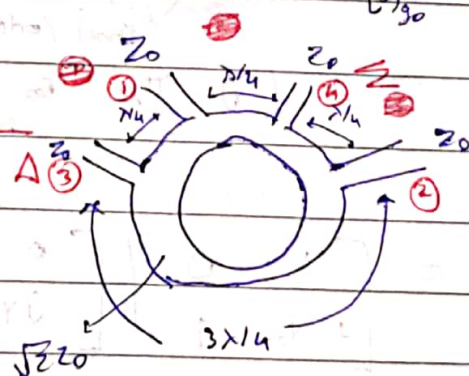

$$[S] = -\frac{j}{\sqrt{2}} \begin{bmatrix} 0 & 0 & 1 & 1 \\ 0 & 0 & -1 & 1 \\ 1 & -1 & 0 & 0 \\ 1 & 1 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = -\frac{j}{\sqrt{2}} \begin{bmatrix} 0 & 0 & 1 & 1 \\ 0 & 0 & -1 & 1 \\ 1 & -1 & 0 & 0 \\ 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{bmatrix}$$

$$b_3 = -j/\sqrt{2} (a_1 - a_2)$$

$$b_4 = -j/\sqrt{2} (a_1 + a_2)$$